

1. (8 points) Design a circuit that tells the number of days in a given month. For example, when input is 1 (for January), your circuit should output 31. You can assume that February always has 28 days.
  - a. (4 points) Draw the truth table for this circuit, assuming both input and output are in binary.
  - b. (4 points) Simplify the output to the format of **sum of product** with minimum number of literals. (You do not have to draw the circuit.)

2. (4 points) A gate or a set of gates is called universal if it can implement all digital system (Boolean function). A standard way to show that a gate or a set of gates is universal is to show that it can implement the standard universal gates {AND, OR, NOT}.

A multiplexer is a circuit that outputs one of many inputs based on selection control. A 2-to-1 multiplexer has two inputs, x and y, and one selection bit, s. Its output z will be x if s=0 and y if s=1.

- a. (1 point) Give a Boolean expression of the above 2-to-1 multiplexer.
  - b. (3 point) Show that the 2-to-1 multiplexer is universal.
3. (8 points) Analyze the following sequential circuit by deriving the output, flip-flop input and next state functions in the **sum of product** form. You don't need to draw the state transition graph/table.

x and y are the inputs, z<sub>1</sub> and z<sub>2</sub> are the outputs. T flip-flop's next state is given by:  $Q(t+1) = T \oplus Q(t)$ , where  $\oplus$  is the logic XOR operator defined as  $x \oplus y = x'y + xy'$

