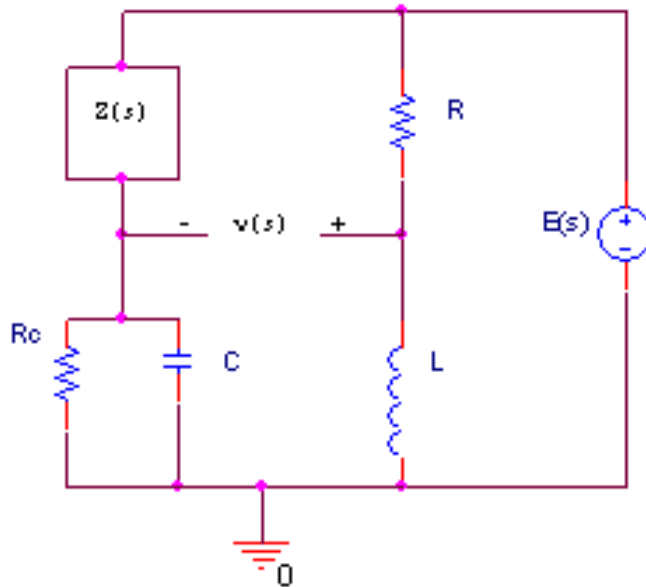


CIRCUITS – Ph.D. Qualifying Exam Spring 2009


(i) (5 pts)



Assume that numerically  $R=R_c=L=1/C$  and give  $v(s)$  for the above bridge circuit in terms of  $R$ ,  $Z(s)$  and  $E(s)$ . Here  $s = \sigma + j\omega$  is complex frequency.

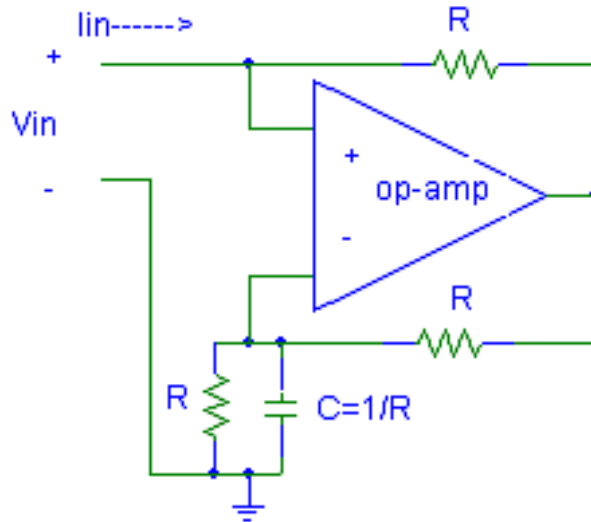(ii) (5 pts).


For the following circuit find the input impedance,  $V_{in}(s)/I_{in}(s)$ . The op-amp is ideal (zero input currents and zero differential input voltage). Numerically  $C=1/R$ .



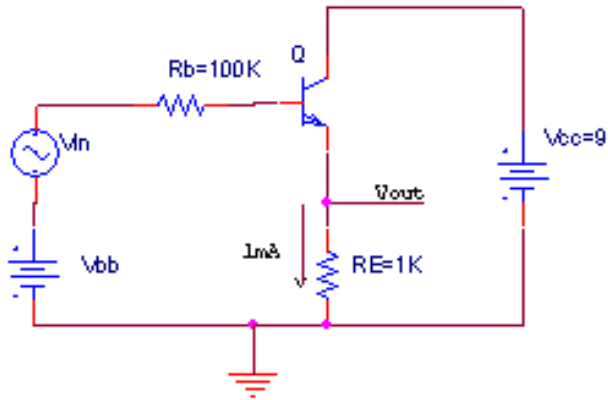(iii) (5 pts)

For the following circuit find  $V_{bb}$  so that the bias current in  $R_E$  is 1 mA.

Assume  $\beta = 99$ ,  $V_T = 0.025$  V = thermal voltage,  $V_{BE} = 0.7$  V and  $V_{in}$  is a small AC signal. Here  $R_b = 100$  K $\Omega$ ,  $R_E = 1$  K $\Omega$ ,  $V_{cc} = 9$  V.



(iv) (5pts)

Find  $W/L$  needed to properly bias the transistor  $M$  in the following circuit.

Assume Threshold voltage =  $V_{TO} = 1.5$  V,  $C_{gs} = 20$  pF,  $C_{gd} = 0$ ,  $k_n = (\mu C_{ox}/2) = 10^{-4}$  A/V<sup>2</sup>,  $I_D = k_n(W/L)(V_{GS} - V_{TO})^2$ . Here the bias current in  $R_S$  is 1 mA,  $V_{gg} = 4.5$  V,  $V_{dd} = 9$  V while  $V_{in}$  is a small AC signal;  $R_g = 100$  Kohm,  $R_S = 1$  Kohm

