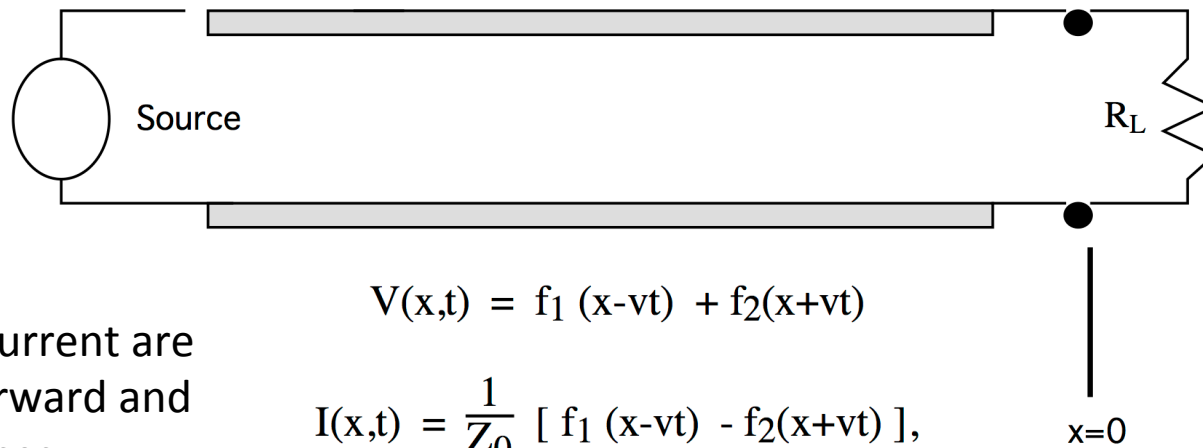


ENEE381

Signals on Transmission Lines

Transmission Line



Voltage and current are the sum of forward and backward pulses

$$V(x,t) = f_1(x-vt) + f_2(x+vt)$$

$$I(x,t) = \frac{1}{Z_0} [f_1(x-vt) - f_2(x+vt)],$$

$$I(0,t) = \frac{1}{Z_0} [f_1(-vt) - f_2(+vt)] = \frac{1}{R_L} [f_1(-vt) + f_2(+vt)] = \frac{V(0,t)}{R_L}$$

$$f_2(+vt) = \rho f_1(-vt),$$

where the reflection coefficient ρ is given by,

$$\rho = \frac{R_L - Z_0}{R_L + Z_0}.$$


Forward Pulse

The incident pulse is chosen to be


$$f_1(x) = \exp[-2x - 4\sqrt{x^2 + .01}]$$

Forward travelling pulse

$$V(x,t) = f_1(x-vt)$$

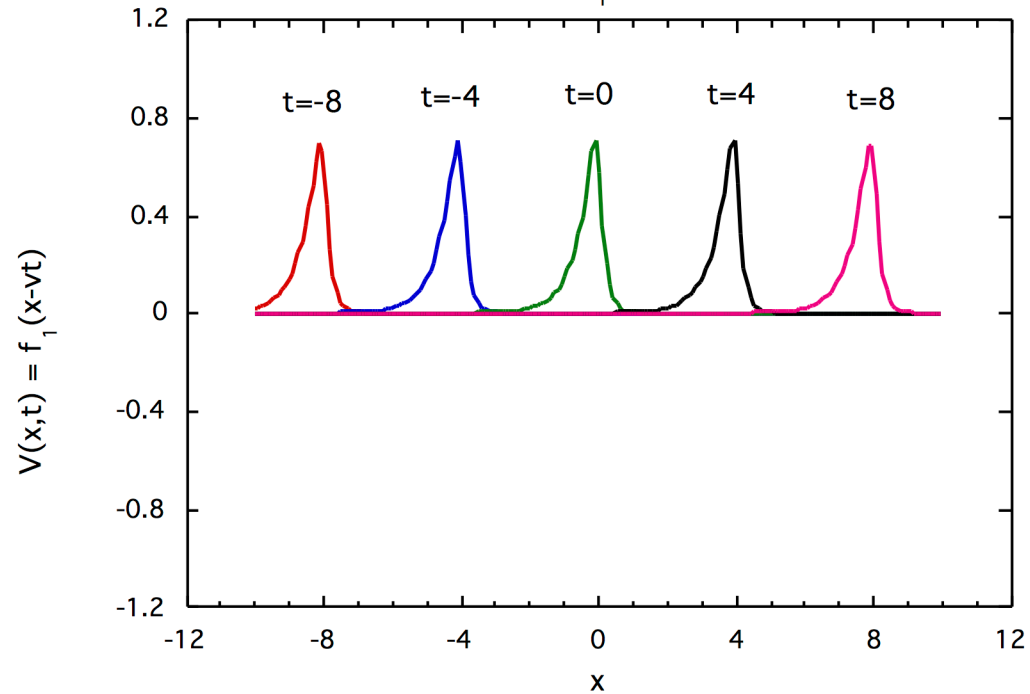

Backward Pulse

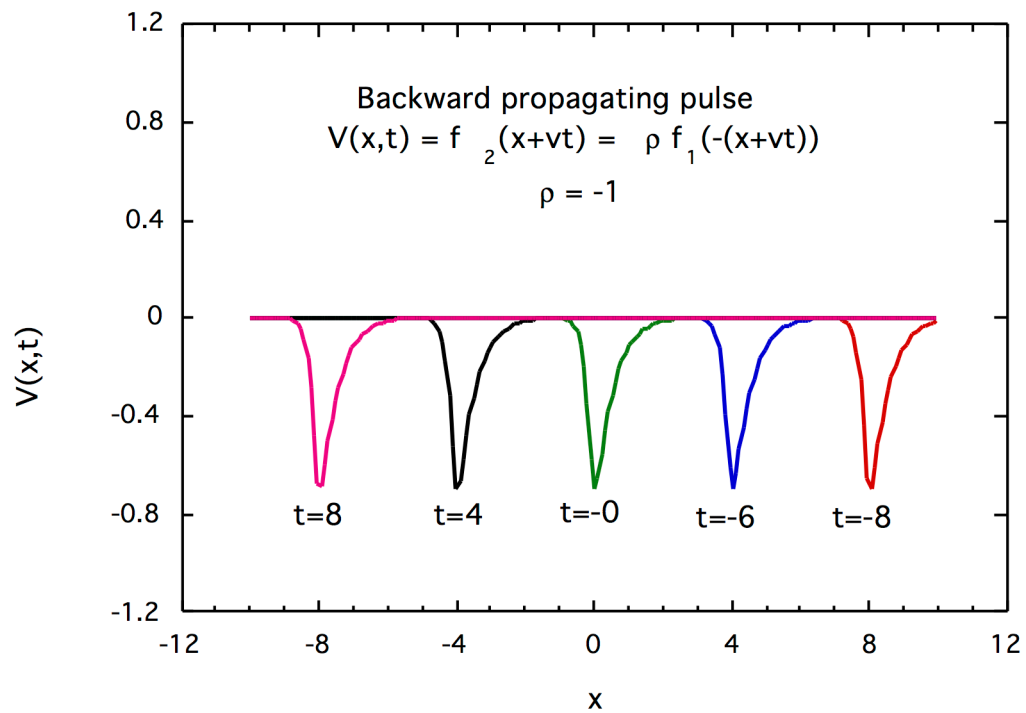


Forward + Backward

Incident and reflected pulses

$$V(x,t) = f_1(x-vt) + \rho f_1(-(x+vt))$$

$$\rho = -1$$

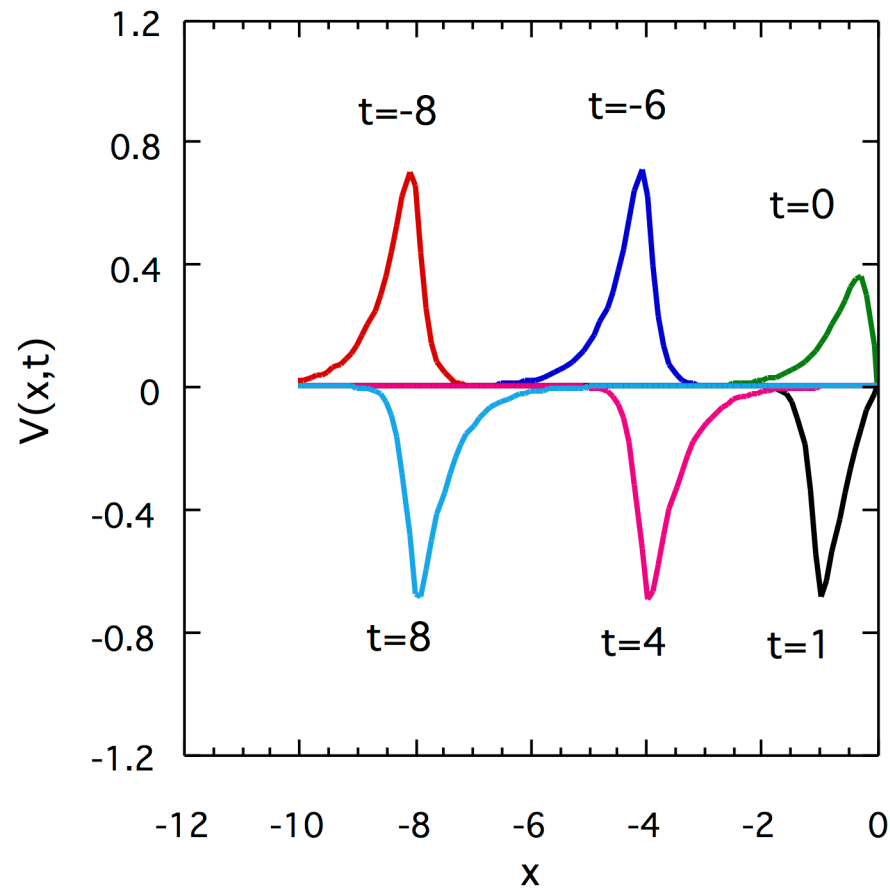

$$\rho = \frac{R_L - Z_0}{R_L + Z_0},$$



$$R_L = 0$$

$$\rho = -1$$

Forward + Backward

Incident pulse $\rho = 1$
 $t \leq 0$

Reflected pulse, $\rho = 1$
 $t \geq 0$

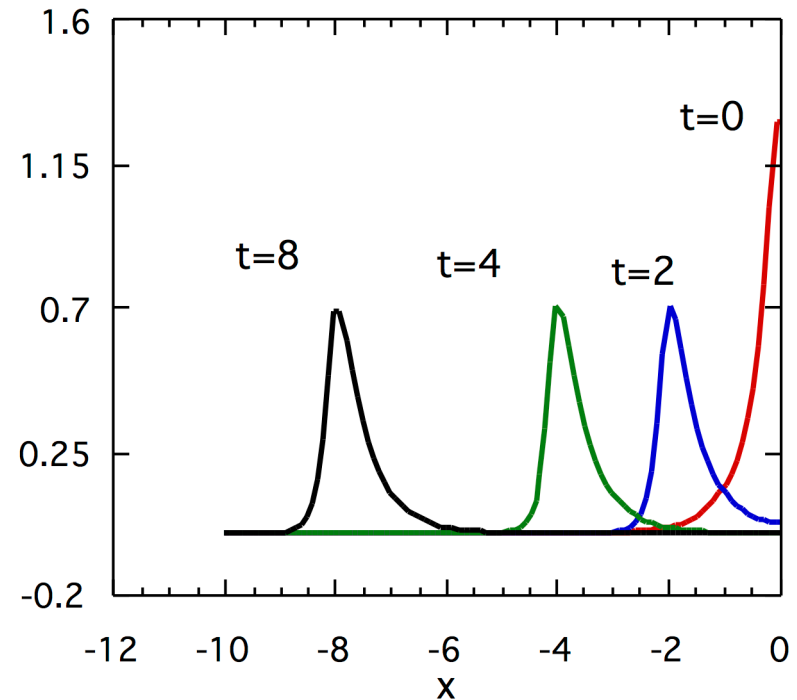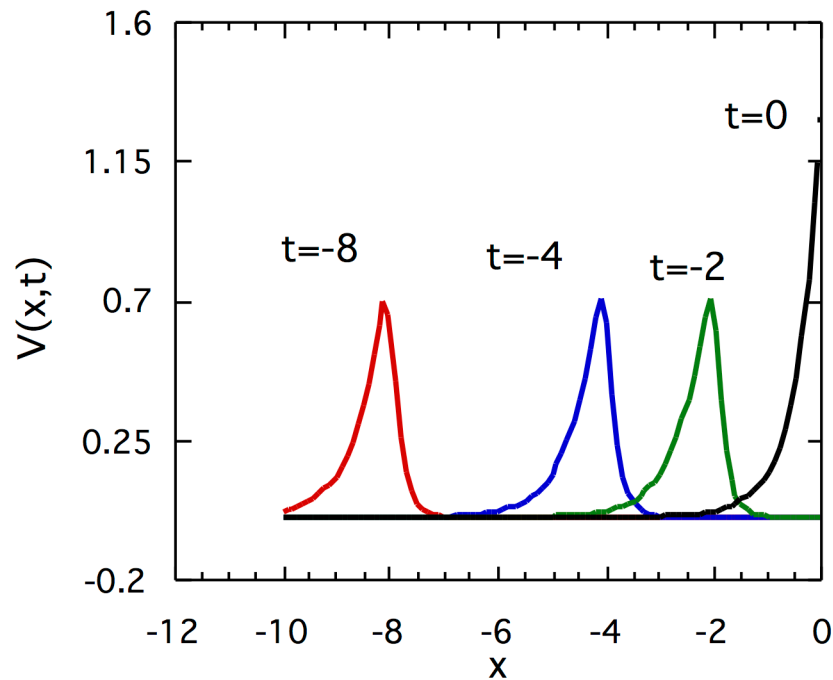


$$\rho = \frac{R_L - Z_0}{R_L + Z_0},$$


$$R_L = \infty$$

$$\rho = 1$$


Pulse Forming Network

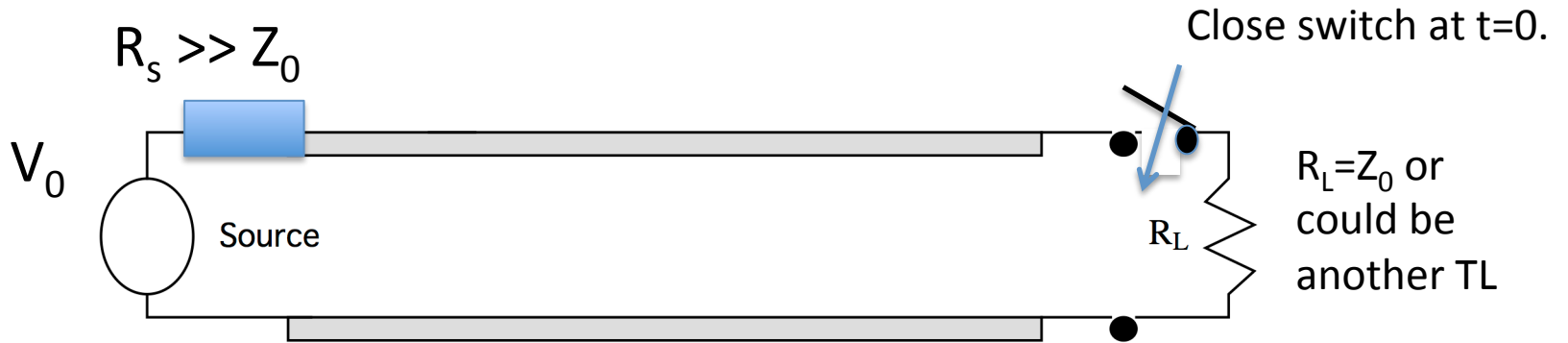

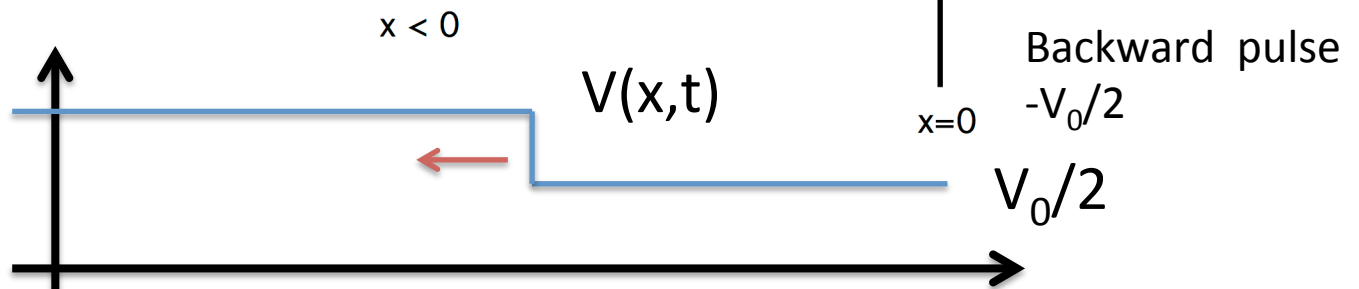
For $t < 0$ line slowly charges to $V = V_0$



Forward pulse $-V_0/2$

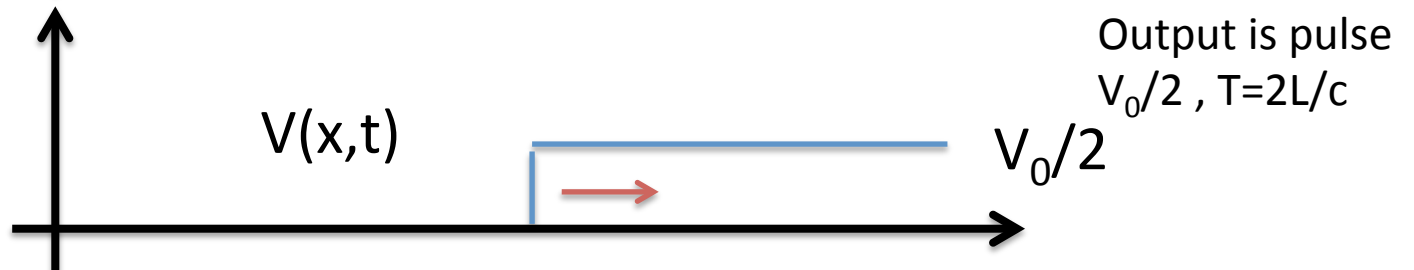

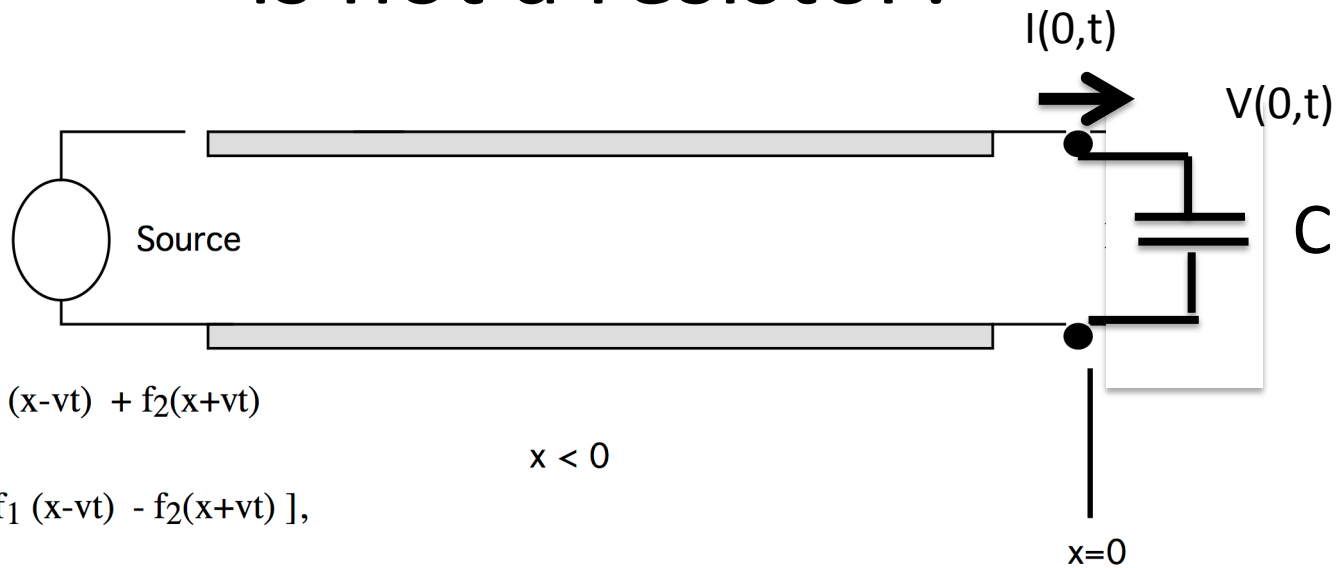What happens when the termination is not a resistor?



$$V(x,t) = f_1(x-vt) + f_2(x+vt)$$

$$I(x,t) = \frac{1}{Z_0} [f_1(x-vt) - f_2(x+vt)],$$




$$x < 0$$

At $x = 0$

$$I(0,t) = C \frac{dV(0,t)}{dt}$$


$$I(0,t) = \frac{1}{Z_0} (f_1 - f_2) = \frac{1}{Z_0} (2f_1 - (f_1 + f_2)) = \frac{1}{Z_0} (2f_1 - V(0,t))$$
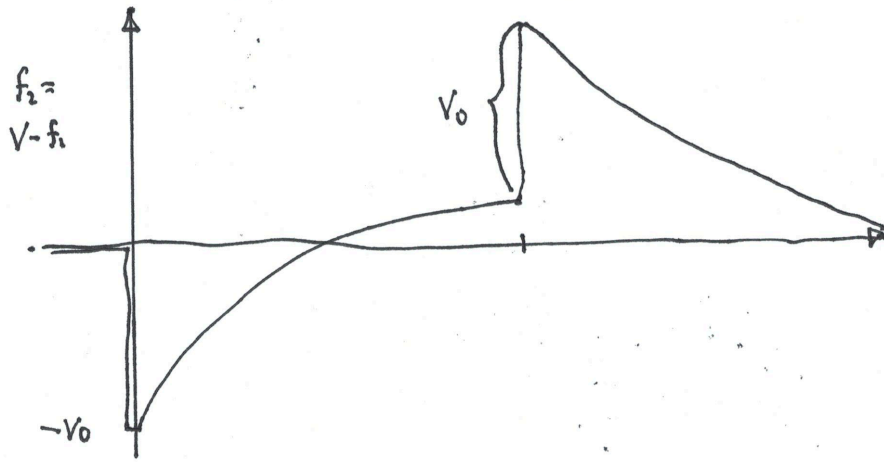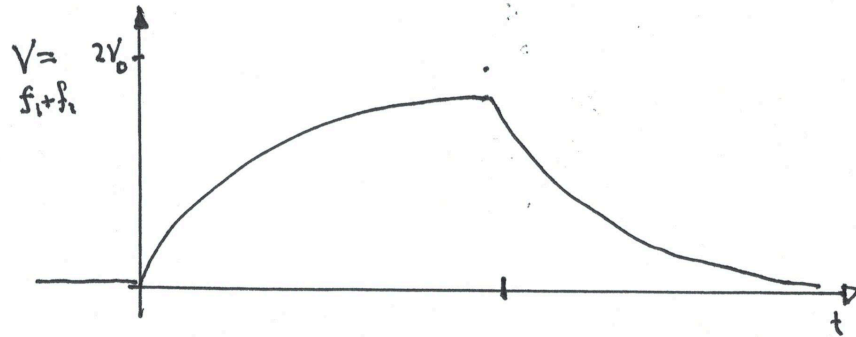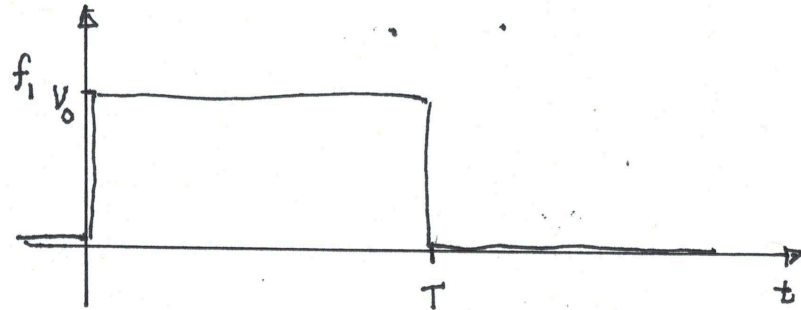
$$2f_1 = V(0,t) + \tau \frac{dV(0,t)}{dt}, \quad \tau = Z_0 C$$




$$2f_1 = V(0,t) + \tau \frac{dV(0,t)}{dt}, \quad \tau = Z_0 C$$

$$f_2 = V(0,t) - f_1$$

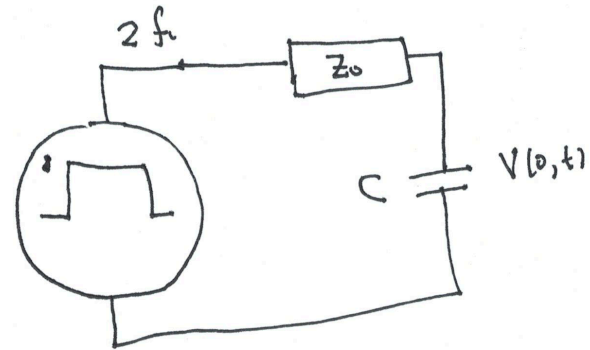

Capacitor initially acts like a short circuit, then transitions to an open circuit

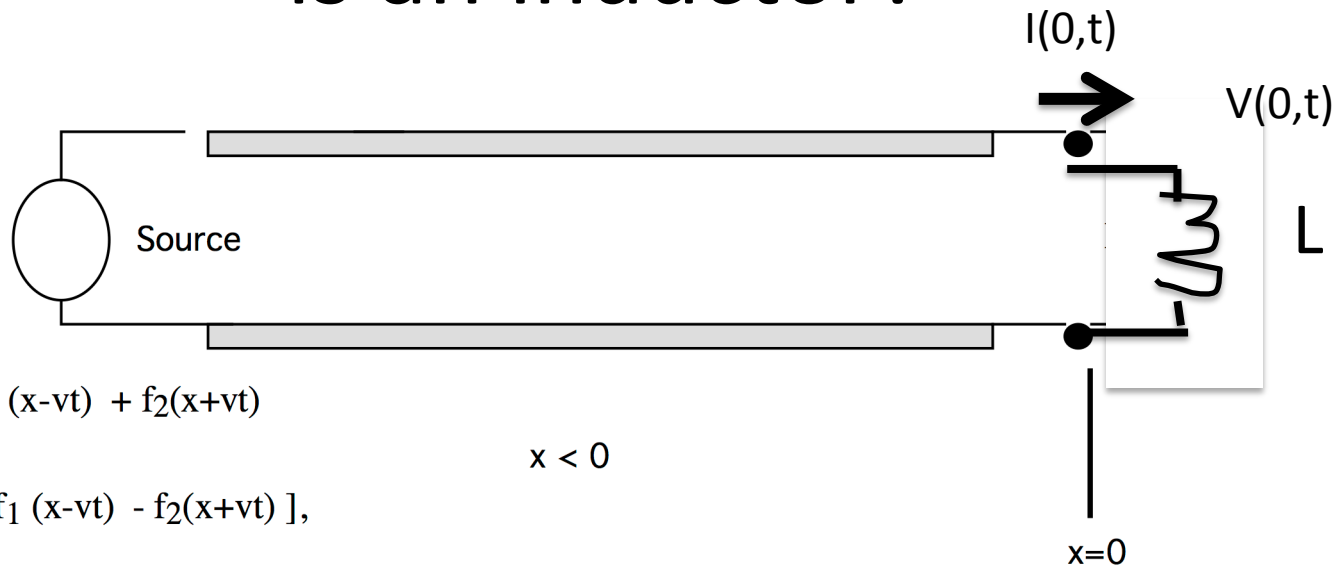What happens when the termination is an inductor?



$$V(x,t) = f_1(x-vt) + f_2(x+vt)$$

$$I(x,t) = \frac{1}{Z_0} [f_1(x-vt) - f_2(x+vt)],$$

$$x < 0$$



At $x = 0$

$$V(0,t) = L \frac{dI(0,t)}{dt}$$

$$V = f_1 + f_2 = 2f_1 - (f_1 - f_2) = 2f_1 - Z_0 I(0,t) = L \frac{dI(0,t)}{dt}$$

$$2f_1 = Z_0 \left(I(0,t) + \tau \frac{dI(0,t)}{dt} \right), \quad \tau = L / Z_0$$

What about AC signals?

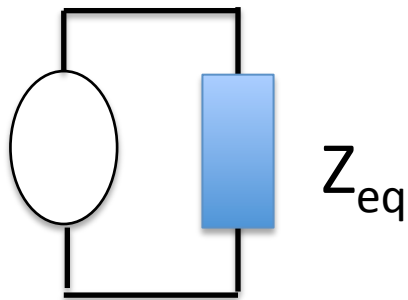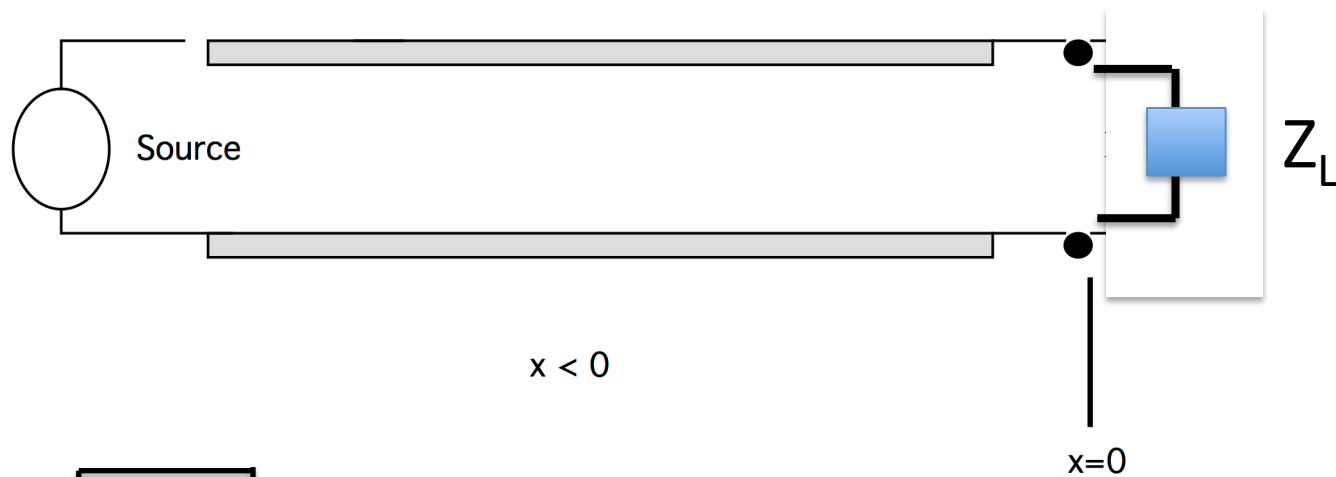

The impedance presented to the source is modified to Z_{eq} , Depends on the load, the length and the characteristic impedance of the line.

Standing Waves

$$V = \text{Re} \left\{ \hat{V}_{inc} \left(e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\}$$

$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left(e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\}$$


$V(z,t)$

$$\rho = -1$$

Nodes are short circuits

Anti nodes are open circuits

Plots of $E_x(z,t)$ at different times

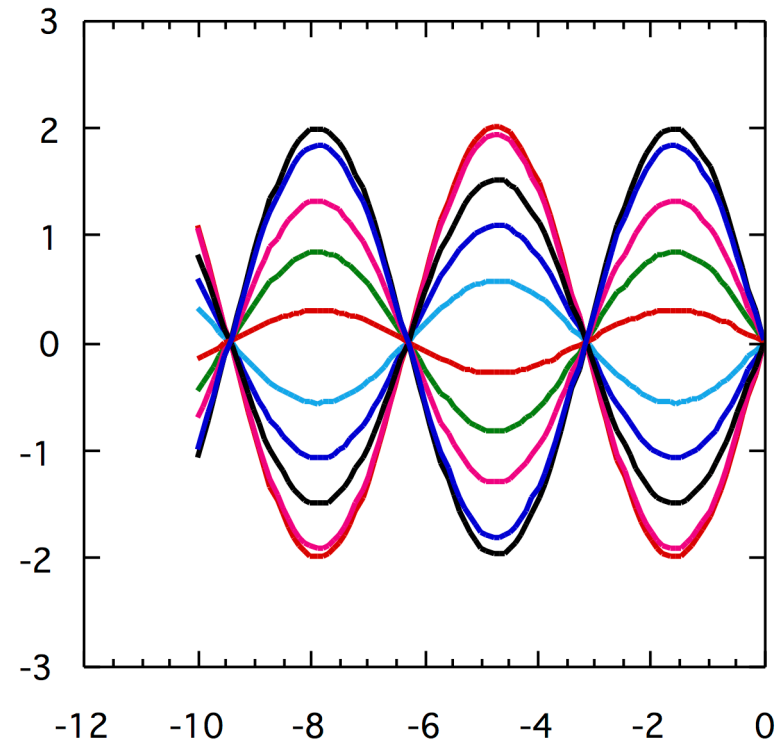

Z [m]

Standing Waves

$$V = \text{Re} \left\{ \hat{V}_{inc} \left(e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\}$$


$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left(e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\}$$

$V(z,t)$


$$\rho = -0.5$$

Impedance is complex and depends on where V/I is measured

Plots of $E_x(z,t)$ at different times

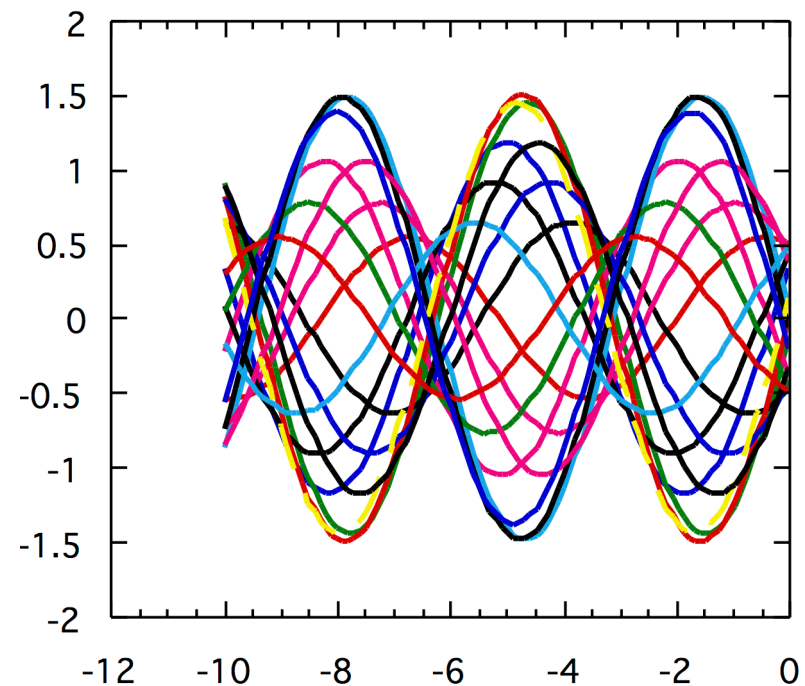

z [m]

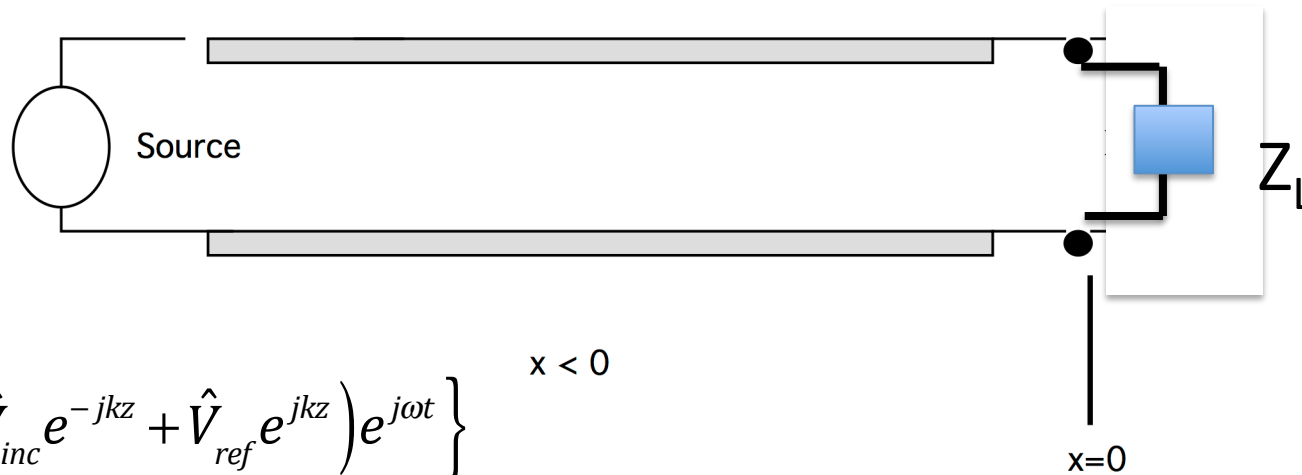

$$V = \text{Re} \left\{ \left(\hat{V}_{inc} e^{-jkz} + \hat{V}_{ref} e^{jkz} \right) e^{j\omega t} \right\} \quad x < 0$$

$$V = \text{Re} \left\{ \hat{V}_{inc} \left(e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{V}(z) e^{j\omega t} \right\} \quad \text{The reflection coefficient at the load}$$

$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left(e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{I}(z) e^{j\omega t} \right\}$$

$$\rho = \frac{Z_L - Z_0}{Z_L + Z_0}$$

At $z = -L$

$$Z_{eq} = \frac{\hat{V}(-L)}{\hat{I}(-L)} = Z_0 \frac{\left(e^{-jkz} + \rho e^{jkz} \right)}{\left(e^{-jkz} - \rho e^{jkz} \right)} \Bigg|_{z=-L} = Z_0 \frac{1 + \rho e^{-2jkL}}{1 - \rho e^{-2jkL}}$$

The reflection coefficient at $z = -L$

$$\rho(L) = \frac{Z_{eq} - Z_0}{Z_{eq} + Z_0} = \rho e^{-2jkL}$$

Equivalent Impedance

$$Z_{eq} = Z_0 \frac{1 + \rho e^{-2jkL}}{1 - \rho e^{-2jkL}}$$

$$Z_{eq} = Z_0 \frac{(Z_L + Z_0)e^{jkL} + (Z_L - Z_0)e^{-jkL}}{(Z_L + Z_0)e^{jkL} - (Z_L - Z_0)e^{-jkL}}$$

$$Z_{eq} = Z_0 \frac{Z_L \cos(kL) + jZ_0 \sin(kL)}{jZ_L \sin(kL) + Z_0 \cos(kL)}$$

If line has losses effect of reflections is diminished

$$k = k' - jk'', \quad e^{-2jkL} = e^{-2k''L} e^{-2jk'L}$$

$$Z_{eq} = Z_0 \frac{1 + (\rho e^{-2k''L}) e^{-2jk'L}}{1 - (\rho e^{-2k''L}) e^{-2jk'L}}$$

If $L \rightarrow 0$, $\sin(kL) \rightarrow 0$, $\cos(kL) \rightarrow 1$, $Z_{eq} \rightarrow Z_L$

If $kL \rightarrow \frac{\pi}{2}$, $\sin(kL) \rightarrow 1$, $\cos(kL) \rightarrow 0$, $Z_{eq} \rightarrow Z_0^2 / Z_L$

Special Cases

$$Z_{eq} = Z_0 \frac{1 + \rho e^{-2jk_1L}}{1 - \rho e^{-2jk_1L}}$$

$$L = n\lambda / 2, \quad 2k_1L = 2\pi n \quad Z_{eq} = Z_0 \frac{1 + \rho}{1 - \rho} = Z_L \quad \text{Remember half-wave window}$$

$$L = \left(n + \frac{1}{2} \right) \lambda / 2, \quad 2k_1L = 2\pi \left(n + \frac{1}{2} \right) \quad Z_{eq} = Z_0 \frac{1 - \rho}{1 + \rho} = Z_0^2 / Z_L$$

Quarter-wave transformer

Admittance vs Impedance

$$I = \text{Re} \left\{ \left(\hat{I}_{inc} e^{-jkz} + \hat{I}_{ref} e^{jkz} \right) e^{j\omega t} \right\}$$

$$V = \text{Re} \left\{ Z_0 \left(\hat{I}_{inc} e^{-jkz} - \hat{I}_{inc} e^{jkz} \right) e^{j\omega t} \right\}$$

Same formulas apply to current amplitudes.


$$I = \text{Re} \left\{ \hat{I}_{inc} \left(e^{-jkz} + \rho_I e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{I}(z) e^{j\omega t} \right\}$$

$$V = \text{Re} \left\{ Z_0 \hat{I}_{inc} \left(e^{-jkz} - \rho_I e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{V}(z) e^{j\omega t} \right\}$$

Current reflection coefficient = - voltage reflection coefficient

$$\rho_I = -\rho \quad \rho_I = -\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_L - Y_0}{Y_L + Y_0}$$


High Q cavity model

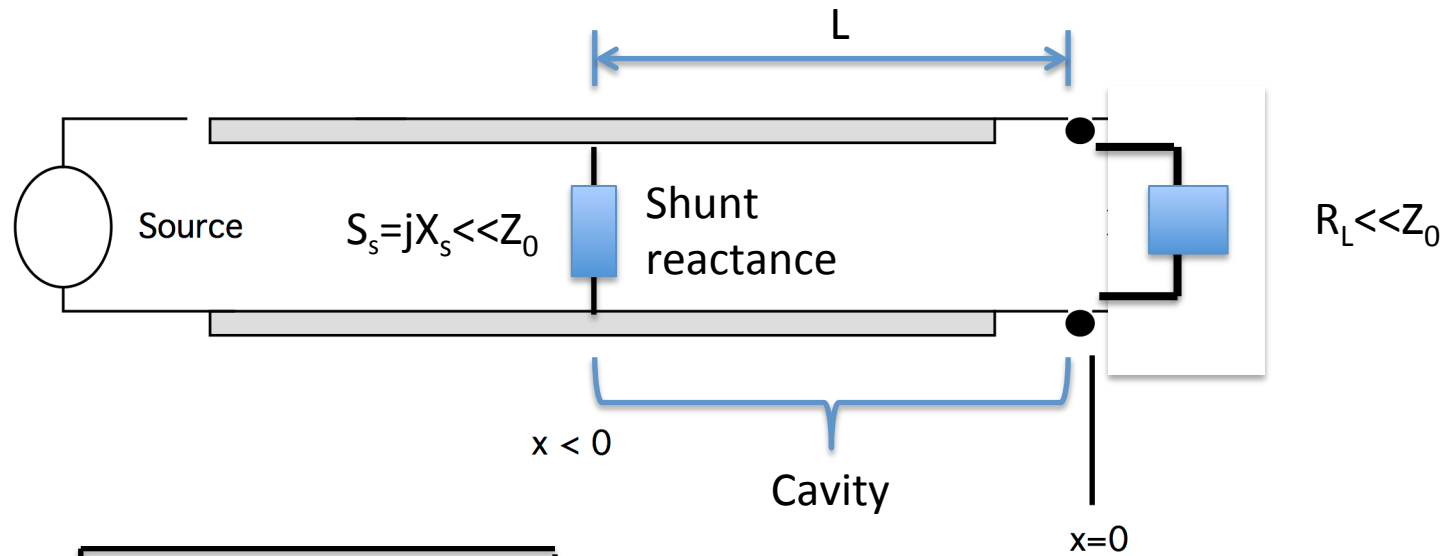


$$Z'_L = Z_{eq} \parallel jX = \frac{Z_{eq} jX}{Z_{eq} + jX}$$

$$\rho = \frac{Z'_{eq} - Z_0}{Z'_{eq} + Z_0}$$

High Q Cavity Model

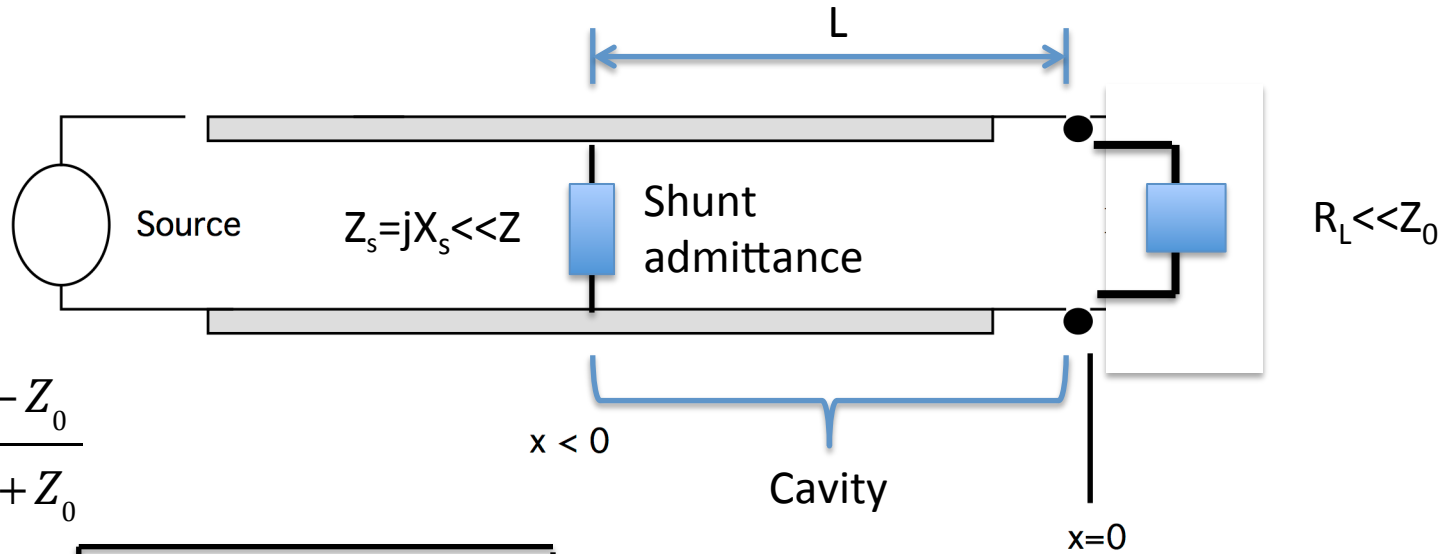
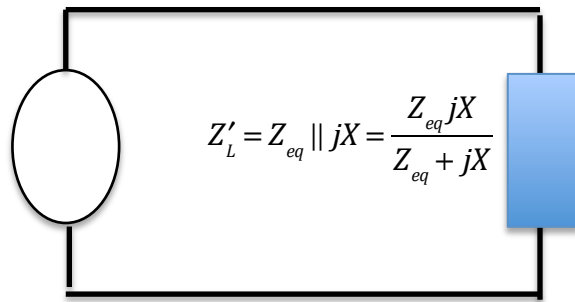
$$\rho_{cav} = \frac{(Z_{eq} \parallel jX_s) - Z_0}{(Z_{eq} \parallel jX_s) + Z_0}$$



$$Z_{eq} = Z_0 \frac{R_L \cos(kL) + jZ_0 \sin(kL)}{jR_L \sin(kL) + Z_0 \cos(kL)} \approx jZ_0 \tan(kL) + R_L$$

$$\rho_{cav} \approx -\frac{j(Z_0 \tan(kL) + X_s) + R_L - X_s^2 / Z_0}{j(Z_0 \tan(kL) + X_s) + R_L + X_s^2 / Z_0} = -\frac{j2(\omega - \omega_c) / \omega_c + Q_{int}^{-1} - Q_{ext}^{-1}}{j2(\omega - \omega_c) / \omega_c + Q_{int}^{-1} + Q_{ext}^{-1}}$$