
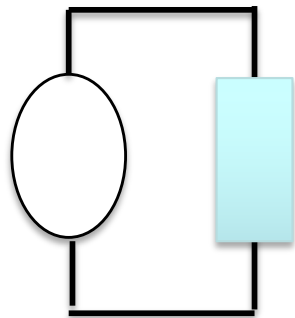


# What about AC signals?

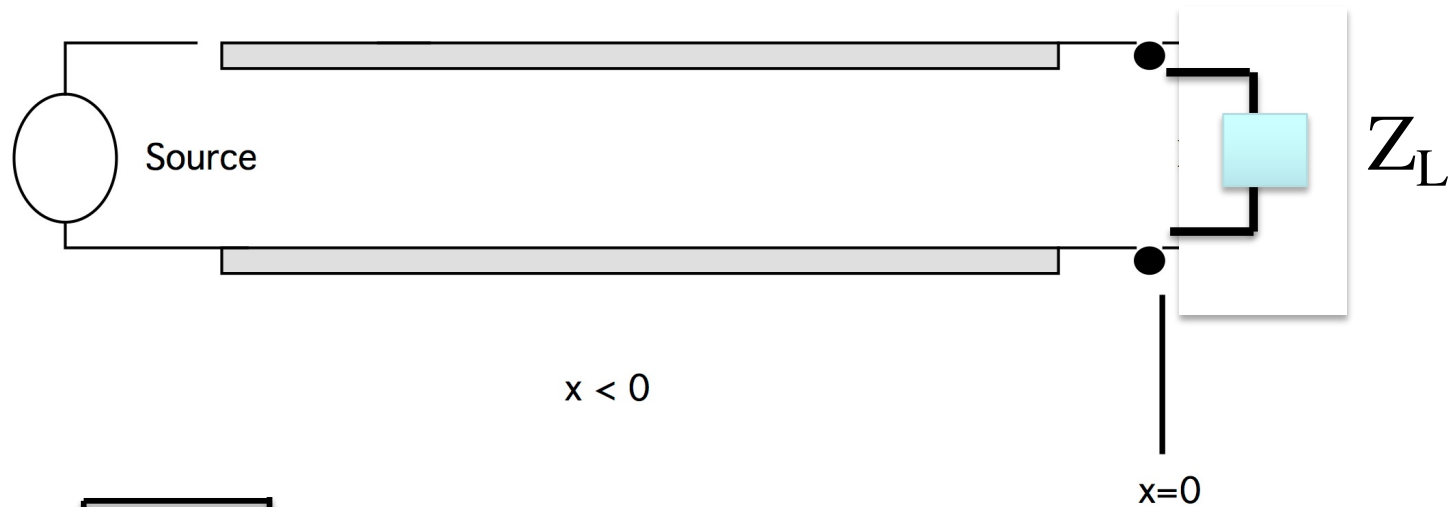

$Z_{eq}$

The impedance presented to the source is modified to  $Z_{eq}$ , Depends on the load, the length and the characteristic impedance of the line.

# Standing Waves

Plots of  $E_x(z,t)$  at different time

$$V = \text{Re} \left\{ \hat{V}_{inc} \left( e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\}$$


$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left( e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\}$$

$V(z,t)$

$$\rho = -1$$

Nodes are short circuits

Anti nodes are open circuits

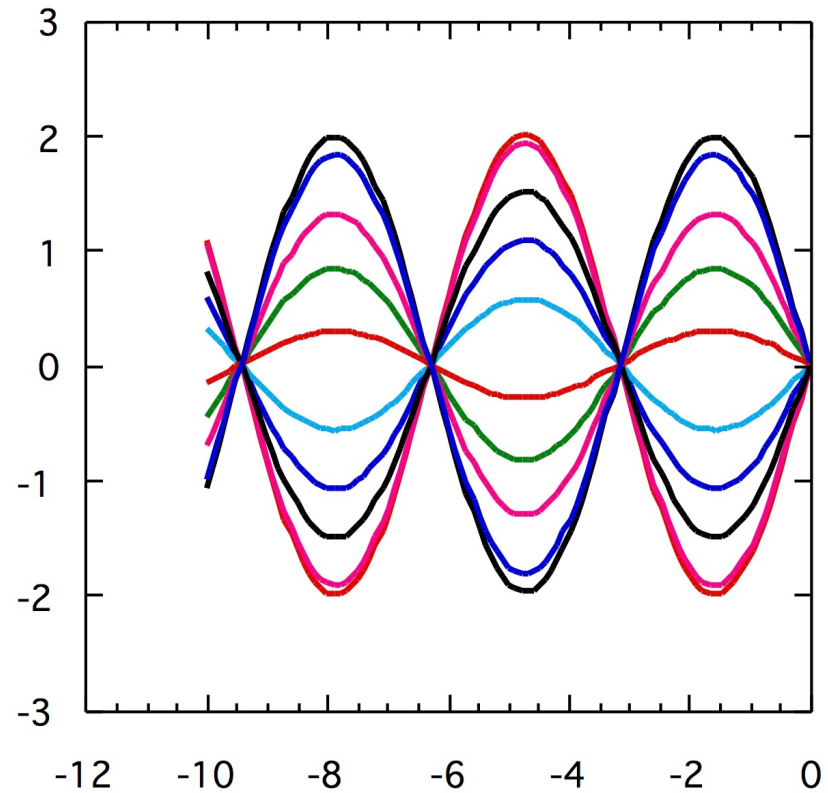

$Z$  [m]

# Standing Waves

Plots of  $E_x(z,t)$  at different time


$$V = \text{Re} \left\{ \hat{V}_{inc} \left( e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\}$$

$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left( e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\}$$


$V(z,t)$

$$\rho = -0.5$$

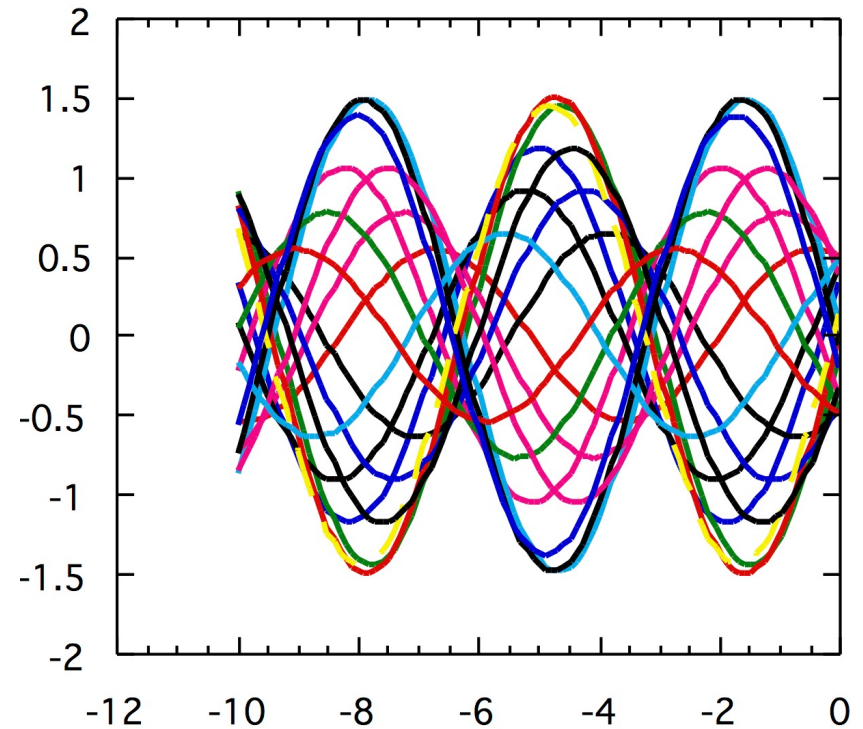Impedance is complex and depends on where  $V/I$  is measured



$Z$  [m]

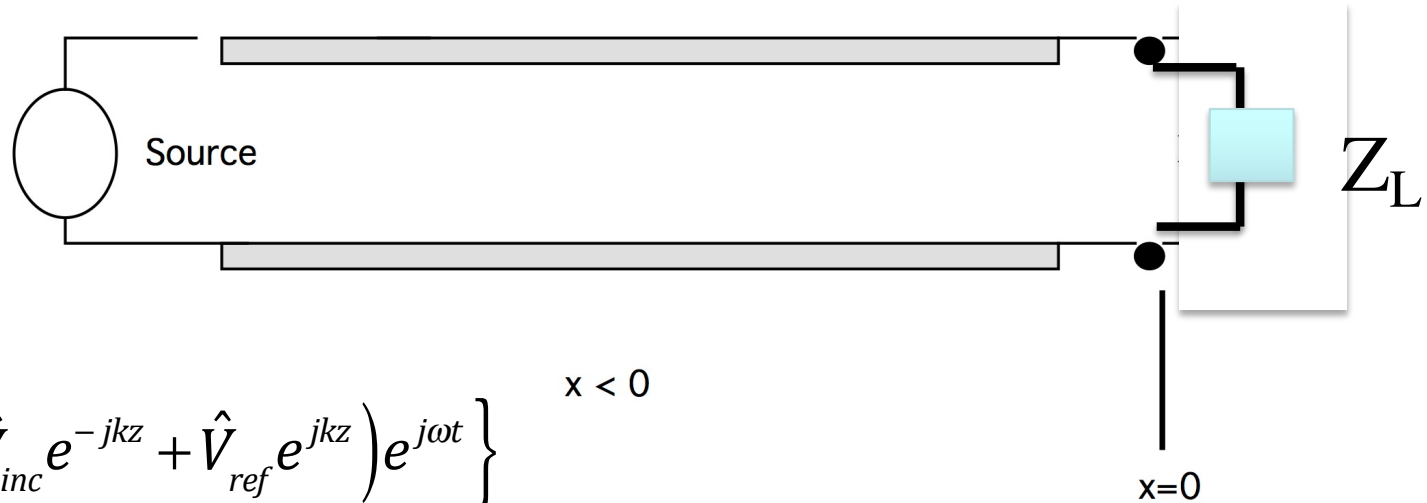

$$V = \text{Re} \left\{ \left( \hat{V}_{inc} e^{-jkz} + \hat{V}_{ref} e^{jkz} \right) e^{j\omega t} \right\} \quad x < 0$$

$$V = \text{Re} \left\{ \hat{V}_{inc} \left( e^{-jkz} + \rho e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{V}(z) e^{j\omega t} \right\} \quad \text{The reflection coefficient at the}$$

$$I = \text{Re} \left\{ \frac{\hat{V}_{inc}}{Z_0} \left( e^{-jkz} - \rho e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{I}(z) e^{j\omega t} \right\}$$

$$\rho = \frac{Z_L - Z_0}{Z_L + Z_0}$$

At  $z = -L$

$$Z_{eq} = \frac{\hat{V}(-L)}{\hat{I}(-L)} = Z_0 \left. \frac{e^{-jkz} + \rho e^{jkz}}{e^{-jkz} - \rho e^{jkz}} \right|_{z=-L} = Z_0 \frac{1 + \rho e^{-2jkL}}{1 - \rho e^{-2jkL}}$$

The reflection coefficient

$$\rho(L) = \frac{Z_{eq} - Z_0}{Z_{eq} + Z_0} = \rho e^{-2jkL}$$

# Equivalent Impedance

$$Z_{eq} = Z_0 \frac{1 + \rho e^{-2jkL}}{1 - \rho e^{-2jkL}}$$

$$Z_{eq} = Z_0 \frac{(Z_L + Z_0)e^{jkL} + (Z_L - Z_0)e^{-jkL}}{(Z_L + Z_0)e^{jkL} - (Z_L - Z_0)e^{-jkL}}$$

$$Z_{eq} = Z_0 \frac{Z_L \cos(kL) + jZ_0 \sin(kL)}{jZ_L \sin(kL) + Z_0 \cos(kL)}$$

If line has losses effect of reflections is diminished

$$k = k' - jk'', \quad e^{-2jkL} = e^{-2k''L} e^{-2jk'L}$$

$$Z_{eq} = Z_0 \frac{1 + (\rho e^{-2k''L})e^{-2jk'L}}{1 - (\rho e^{-2k''L})e^{-2jk'L}}$$

If  $L \rightarrow 0$ ,  $\sin(kL) \rightarrow 0$ ,  $\cos(kL) \rightarrow 1$ ,  $Z_{eq} \rightarrow Z_L$

If  $kL \rightarrow \frac{\pi}{2}$ ,  $\sin(kL) \rightarrow 1$ ,  $\cos(kL) \rightarrow 0$   $Z_{eq} \rightarrow Z_0^2 / Z_L$

# Special Cases

$$Z_{eq} = Z_0 \frac{1 + \rho e^{-2jk_1L}}{1 - \rho e^{-2jk_1L}}$$

$$L = n\lambda / 2, \quad 2k_1L = 2\pi n \quad Z_{eq} = Z_0 \frac{1 + \rho}{1 - \rho} = Z_L \quad \text{Remember half-wave wind}$$

$$L = \left( n + \frac{1}{2} \right) \lambda / 2, \quad 2k_1L = 2\pi \left( n + \frac{1}{2} \right) \quad Z_{eq} = Z_0 \frac{1 - \rho}{1 + \rho} = Z_0^2 / Z_L$$

Quarter-wave transformer

# Admittance vs Impedance

$$I = \text{Re} \left\{ \left( \hat{I}_{inc} e^{-jkz} + \hat{I}_{ref} e^{jkz} \right) e^{j\omega t} \right\}$$

$$V = \text{Re} \left\{ Z_0 \left( \hat{I}_{inc} e^{-jkz} - \hat{I}_{inc} e^{jkz} \right) e^{j\omega t} \right\}$$

Same formulas apply to current amplitudeS.


$$I = \text{Re} \left\{ \hat{I}_{inc} \left( e^{-jkz} + \rho_I e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{I}(z) e^{j\omega t} \right\}$$

$$V = \text{Re} \left\{ Z_0 \hat{I}_{inc} \left( e^{-jkz} - \rho_I e^{jkz} \right) e^{j\omega t} \right\} = \text{Re} \left\{ \hat{V}(z) e^{j\omega t} \right\}$$

Current reflection coefficient = - voltage reflection coefficient

$$\rho_I = -\rho \quad \rho_I = -\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_L - Y_0}{Y_L + Y_0}$$

# High Q cavity model

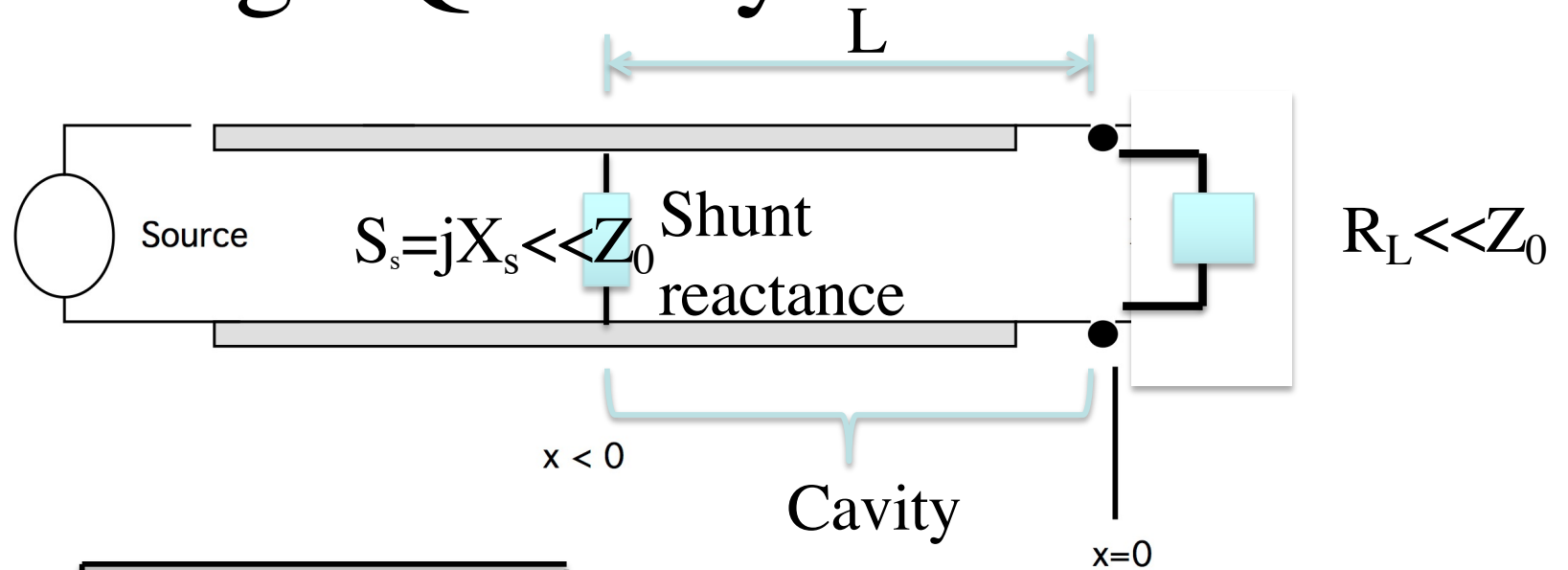


$$Z'_L = Z_{eq} \parallel jX = \frac{Z_{eq} jX}{Z_{eq} + jX}$$


$$\rho = \frac{Z'_{eq} - Z_0}{Z'_{eq} + Z_0}$$



# High Q Cavity Model

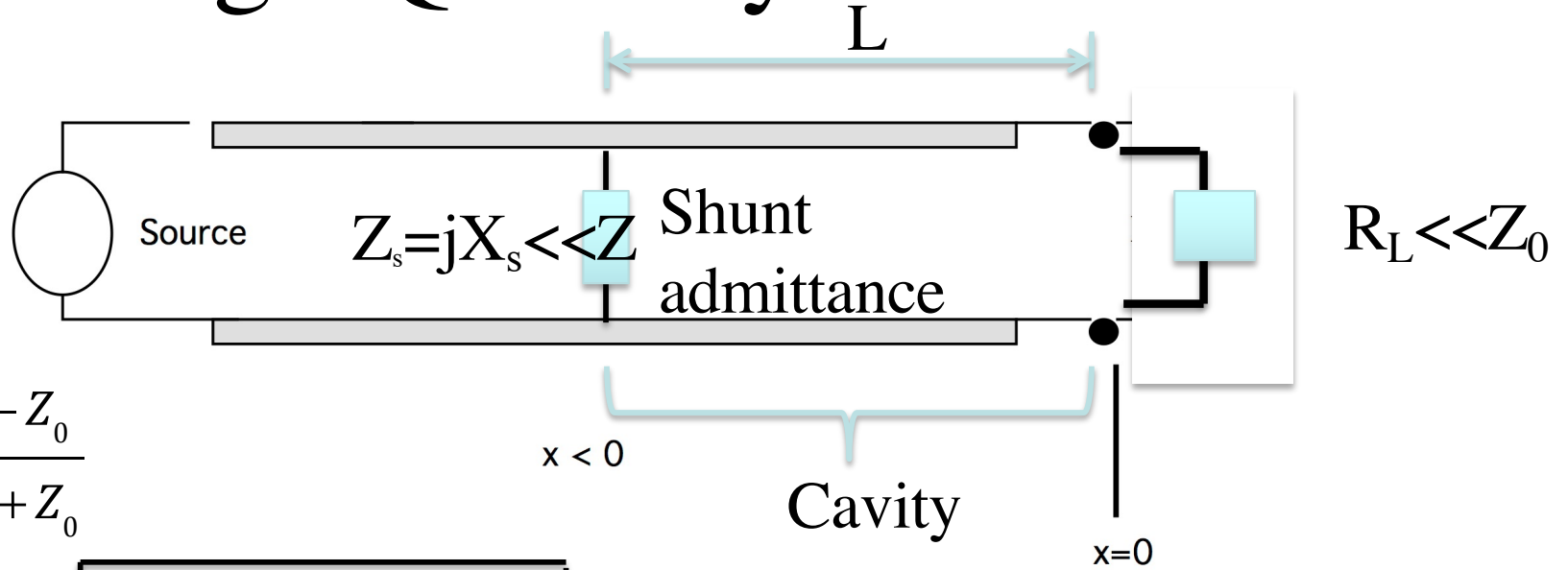
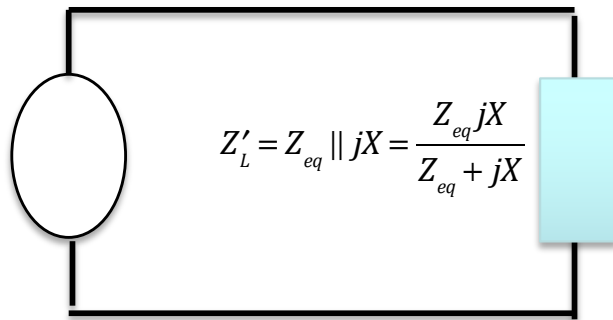
$$\rho_{cav} = \frac{(Z_{eq} \parallel jX_s) - Z_0}{(Z_{eq} \parallel jX_s) + Z_0}$$



$$Z_{eq} = Z_0 \frac{R_L \cos(kL) + jZ_0 \sin(kL)}{jR_L \sin(kL) + Z_0 \cos(kL)} \approx jZ_0 \tan(kL) + R_L$$

$$\rho_{cav} \approx -\frac{j(Z_0 \tan(kL) + X_s) + R_L - X_s^2 / Z_0}{j(Z_0 \tan(kL) + X_s) + R_L + X_s^2 / Z_0} = -\frac{j2(\omega - \omega_c) / \omega_c + Q_{int}^{-1} - Q_{ext}^{-1}}{j2(\omega - \omega_c) / \omega_c + Q_{int}^{-1} + Q_{ext}^{-1}}$$

# Smith Chart

Graphically solves the following bi-linear formulas

$$\frac{Z_{eq}(l)}{Z_0} = \frac{1 + (\rho e^{-2jkl})}{1 - (\rho e^{-2jkl})}$$

$$\rho = \frac{(Z_L / Z_0) - 1}{(Z_L / Z_0) + 1}$$

Note: works for admittance too.

$$\frac{Y_{eq}(l)}{Y_0} = \left( \frac{Z_{eq}(l)}{Z_0} \right)^{-1} = \frac{1 - (\rho e^{-2jkl})}{1 + (\rho e^{-2jkl})}$$


Just switch sign of  $\rho$

$$\rho \rightarrow -\rho$$

Smith chart is the interior of the unit circle in the complex plane

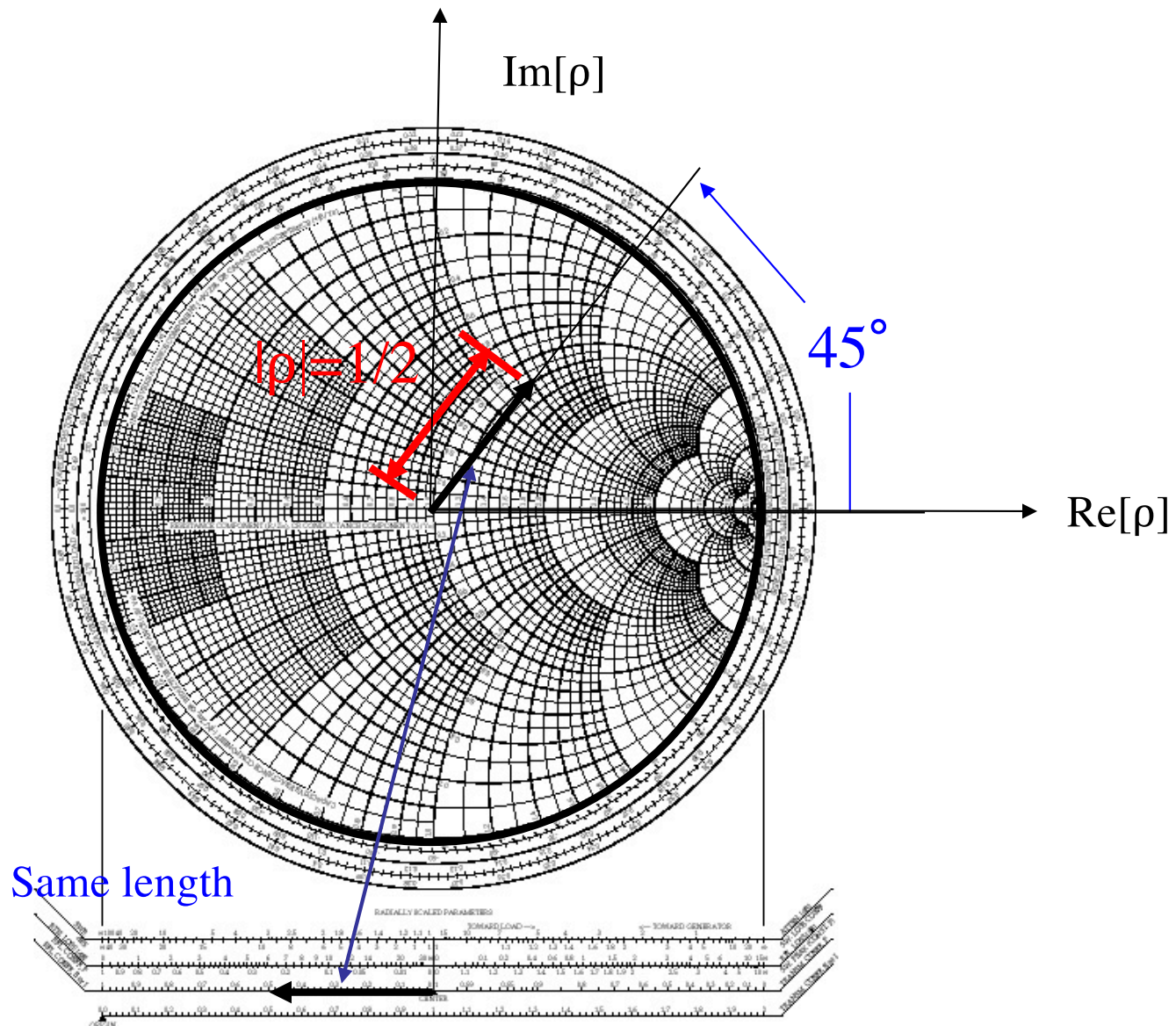Example:


$$\rho = \frac{1}{2} e^{j\frac{\pi}{4}}$$



Find  $Z_L$  given  $\rho$

$$\frac{Z_{eq}(l)}{Z_0} = \frac{1 + (\rho e^{-2jkl})}{1 - (\rho e^{-2jkl})}$$

Note:  $Z_{eq}(l=0) = Z_L$

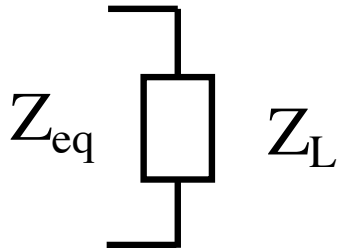


The diagram shows a rectangular box representing a load impedance  $Z_L$ . To the left of the box, there is a vertical line with a horizontal tick at the top and bottom, representing the equivalent impedance  $Z_{eq}$  looking into the port from the left.

Find real and Imaginary parts:

$$\frac{Z_L}{Z_0} = \frac{1 + \rho}{1 - \rho} = R + jX$$

Curves of constant real part: R
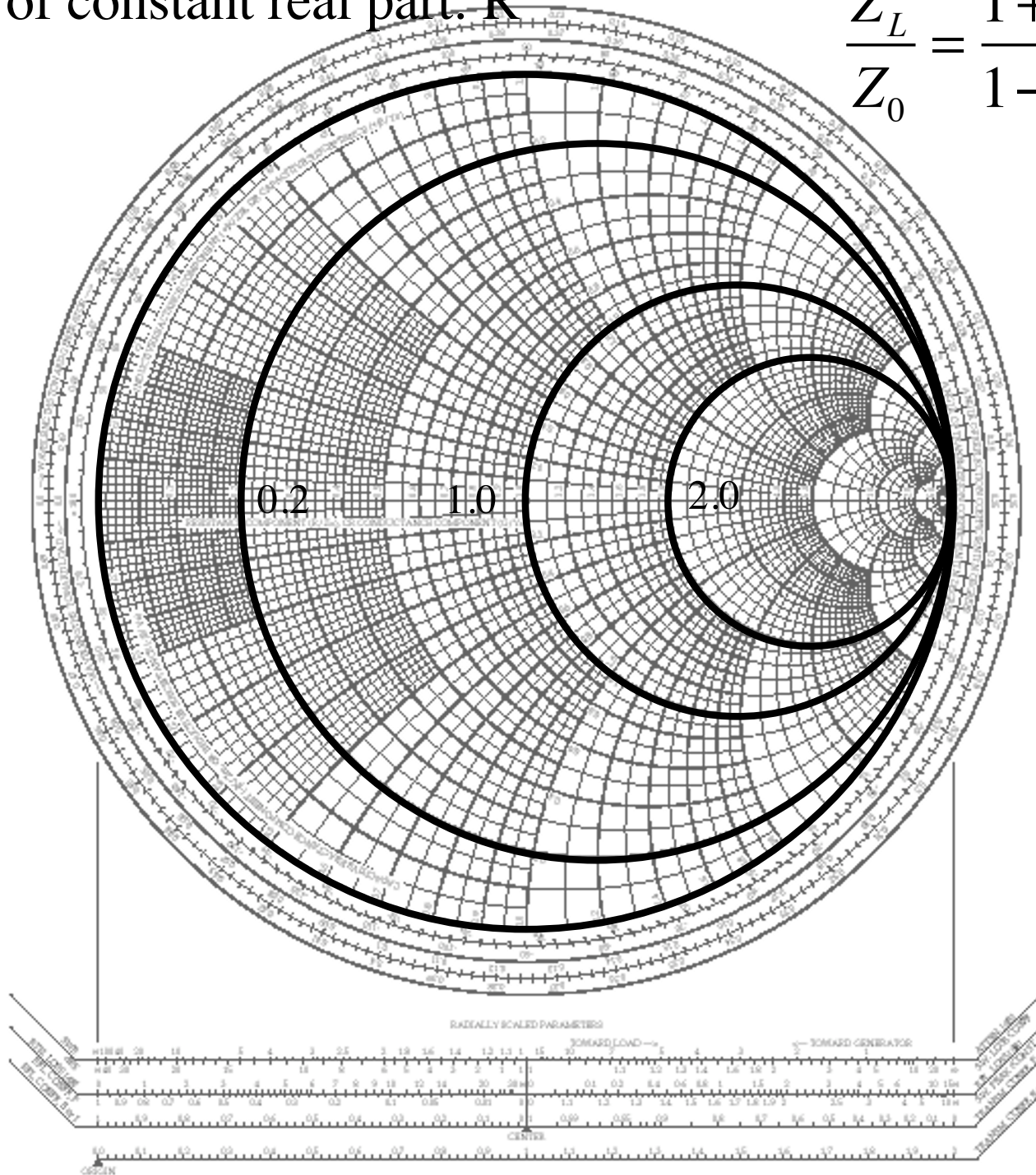
$$\frac{Z_L}{Z_0} = \frac{1 + \rho}{1 - \rho} = R + jX$$





Curves of constant  
imaginary part: X

+0.5

0.0

-0.5

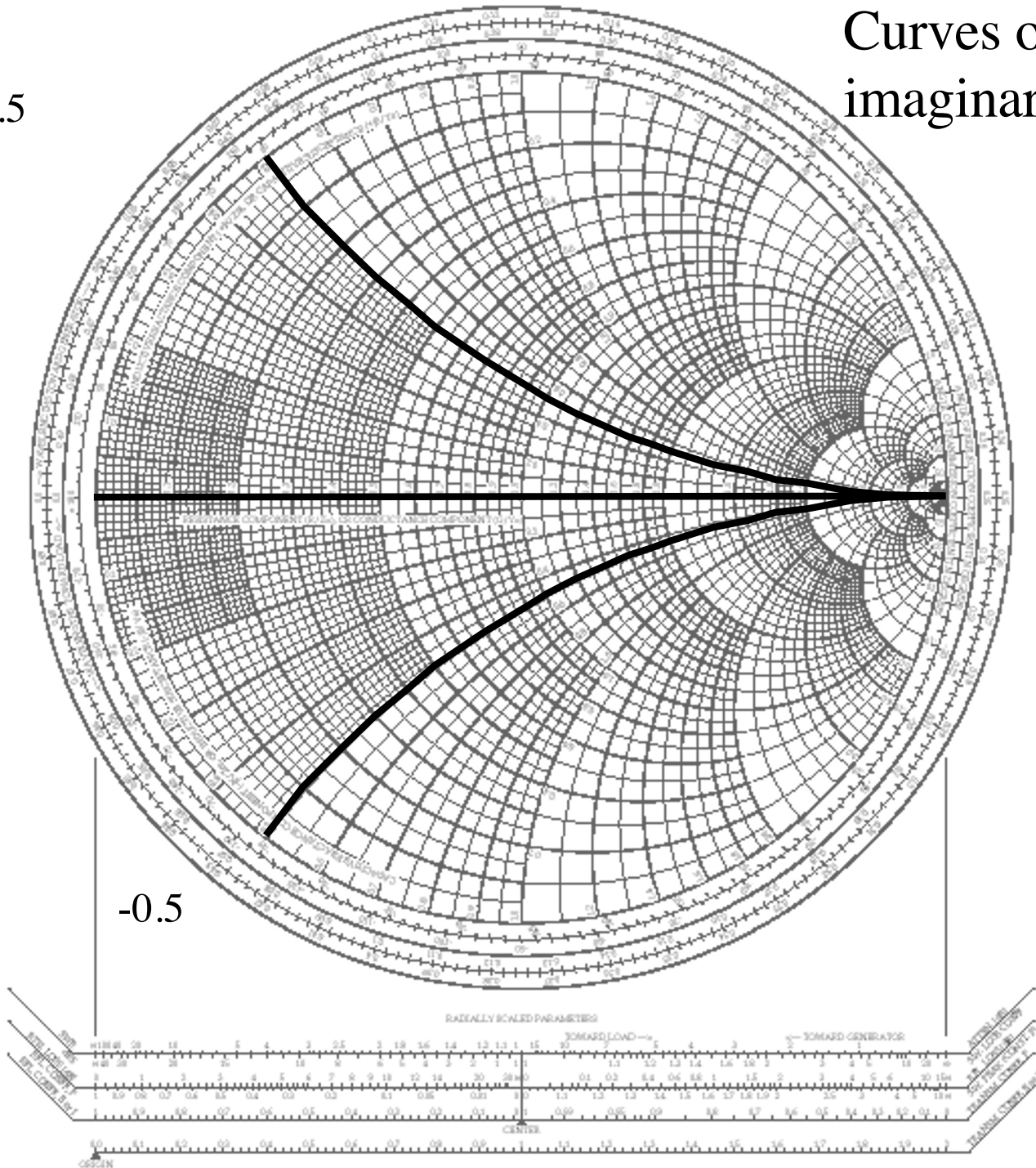


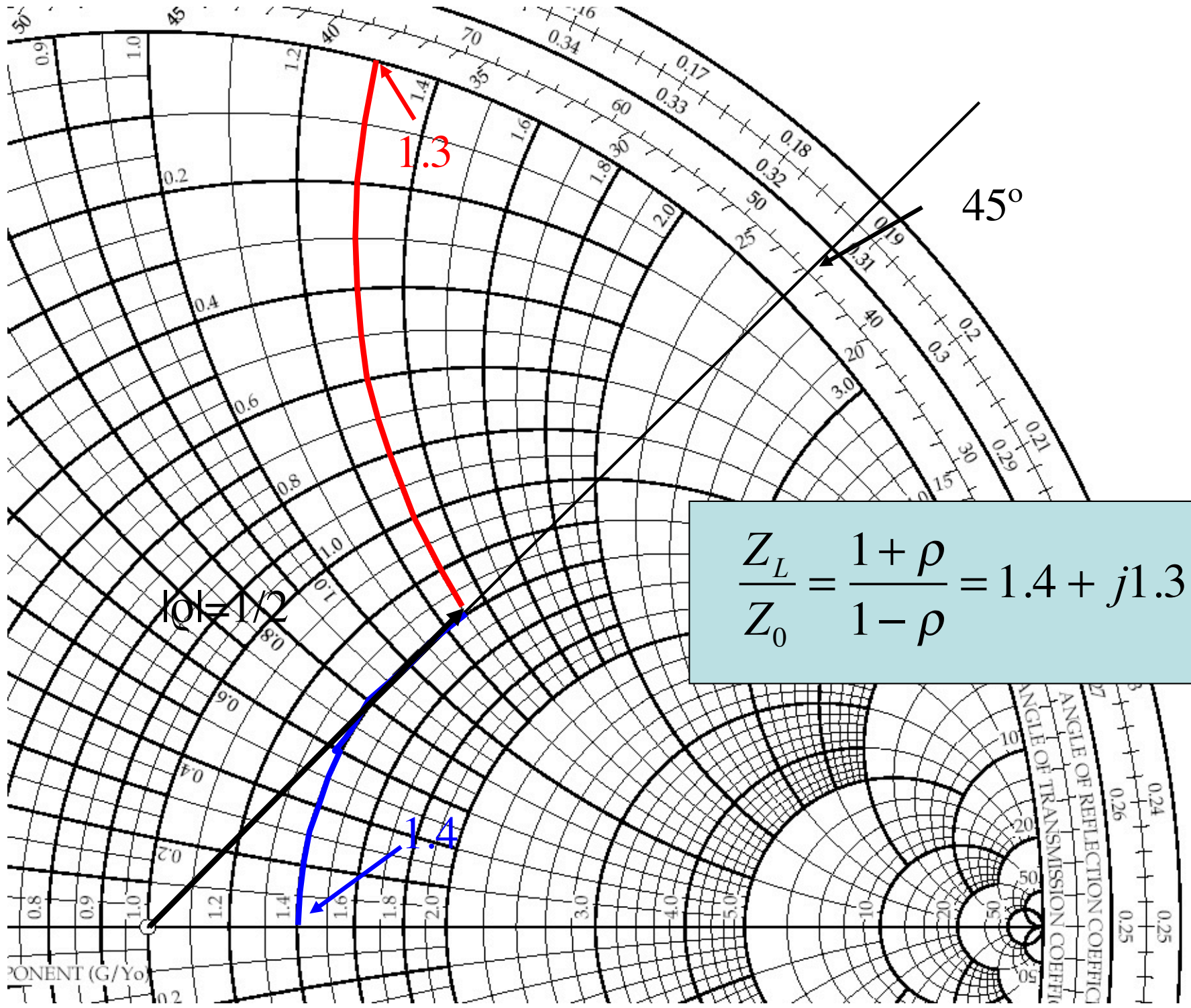

What is  $Z_{eq}$  at  $l = \lambda/4$  from the load?

$$\frac{Z_{eq}(l)}{Z_0} = \frac{1 + (\rho e^{-2jkl})}{1 - (\rho e^{-2jkl})}$$

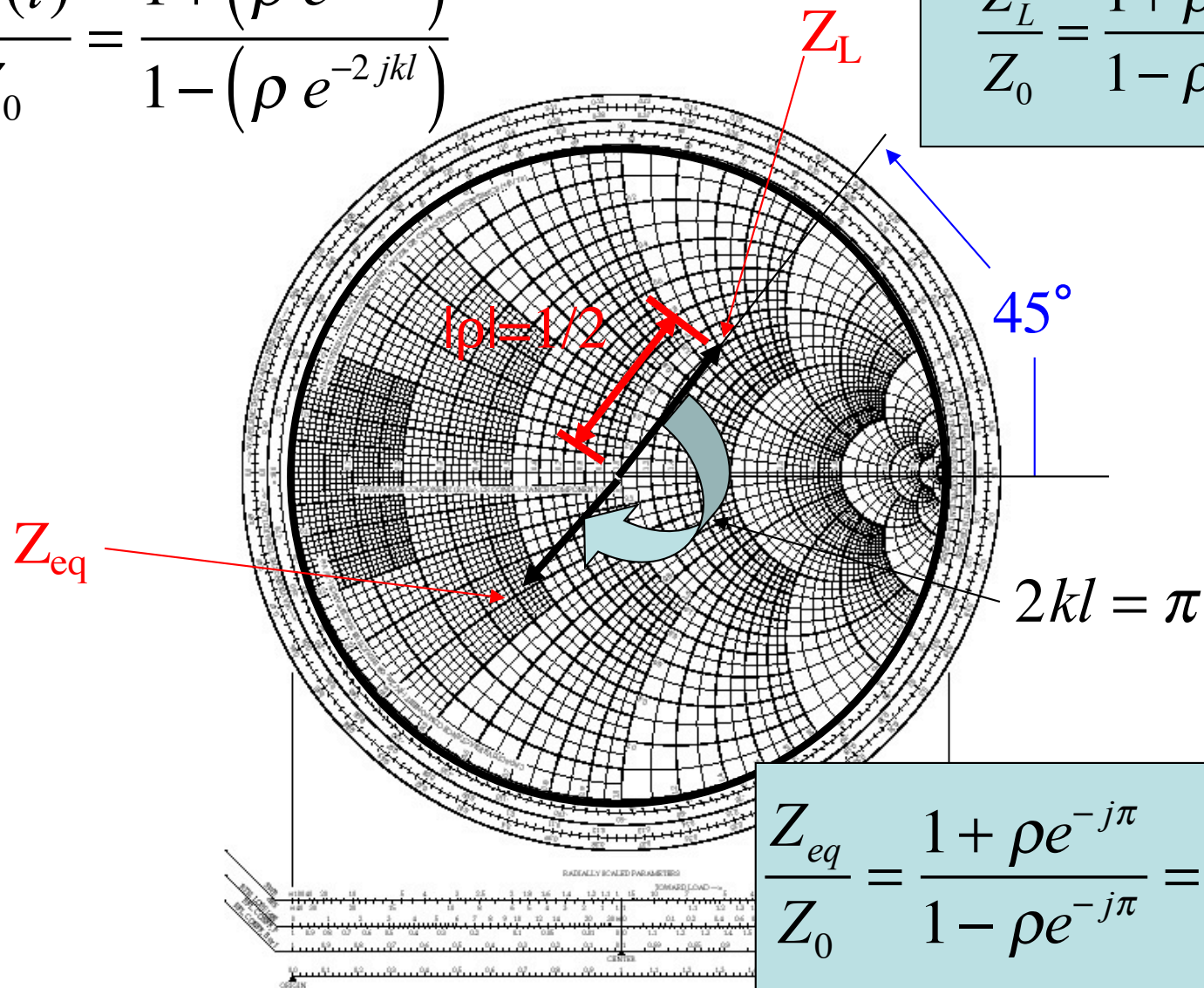
$$\frac{Z_L}{Z_0} = \frac{1 + \rho}{1 - \rho} = 1.4 + j1.3$$



$$\frac{Z_{eq}}{Z_0} = \frac{1 + \rho e^{-j\pi}}{1 - \rho e^{-j\pi}} = .38 - j.34$$



Sample Problem: find  $Z_{eq}$

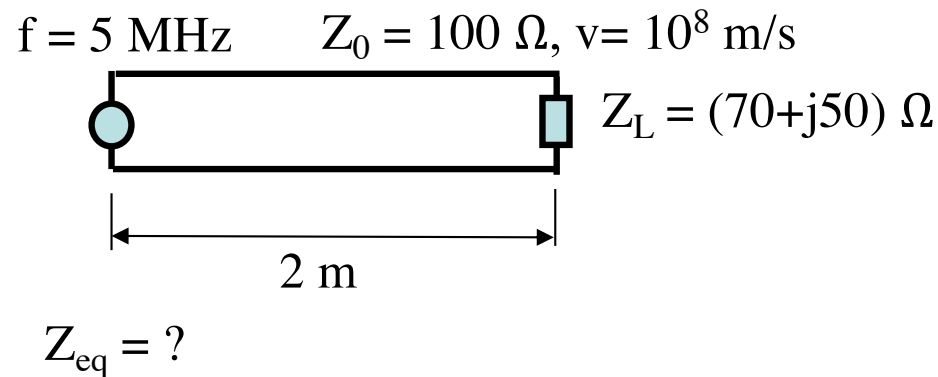

Method 1:

$$Z_{eq}(l) = Z_0 \frac{Z_L \cos kl + jZ_0 \sin kl}{Z_0 \cos kl + jZ_L \sin kl}$$

$$\cos kl = 0.81$$

$$\sin kl = 0.59$$

$$k = 2\pi / \lambda$$

$$\lambda = v / f = 10^8 / 5 \times 10^6 = 20 \text{ m}$$

$$kl = 0.628$$

or

$$l / \lambda = .1$$

$$Z_{eq}(2) = Z_0 \frac{56.63 + j99.5}{51.50 + j41.14}$$


$$Z_{eq}(2) = (161 + j64) \ \Omega$$

# Method 2: Smith Chart


$$Z_L / Z_0 = (70 + j50) / 100$$

$$Z_L / Z_0 = (.7 + j.5)$$

Move  $.1 \lambda$  toward generator

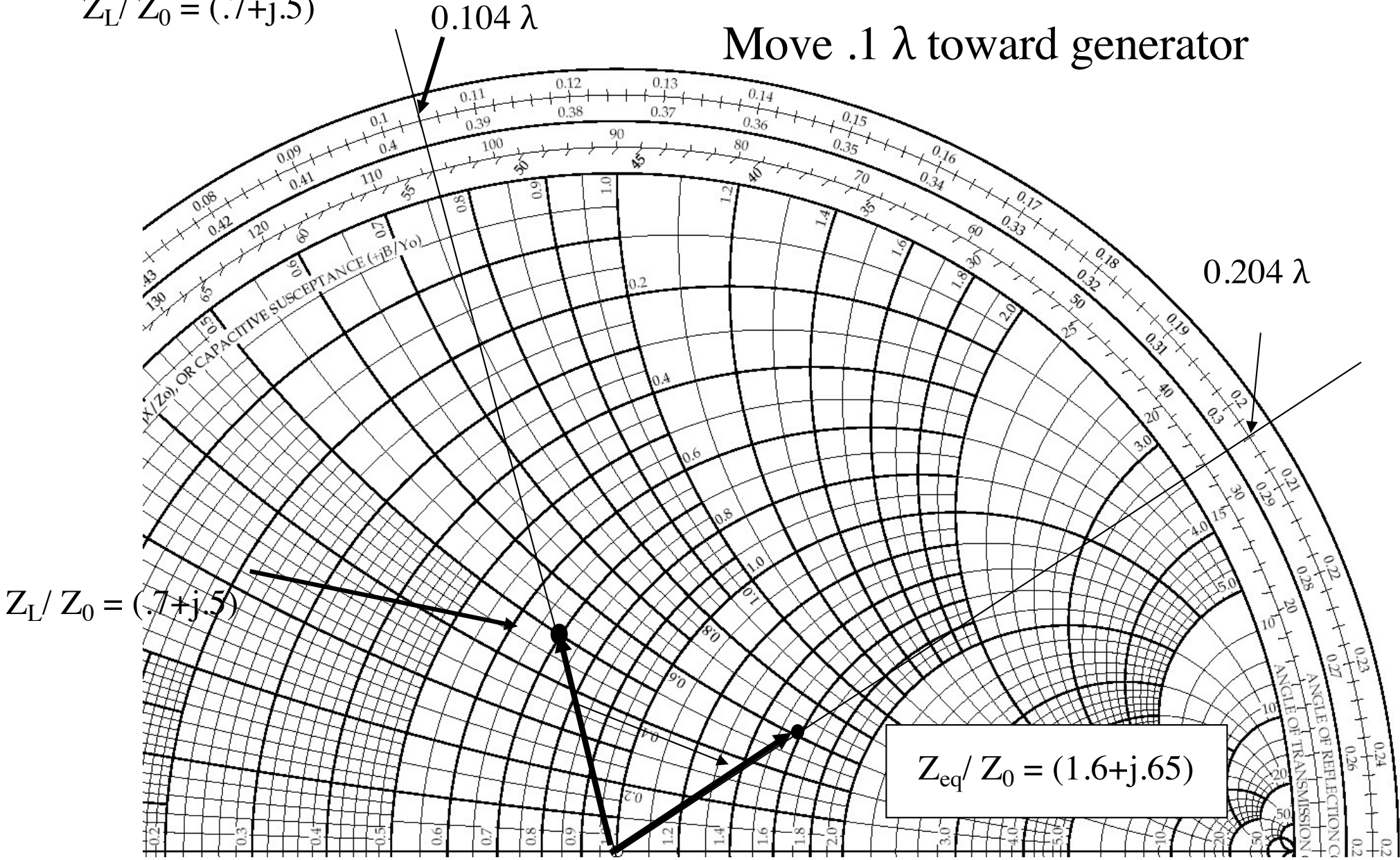


# Standing Wave Problem

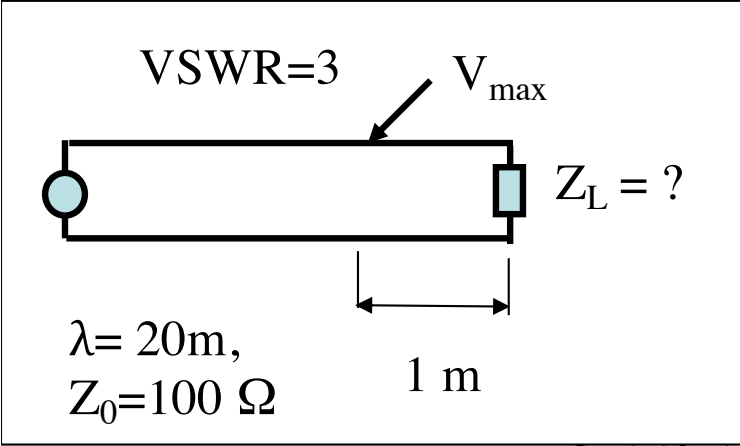

$$\frac{Z_{eq}(l_{max})}{Z_0} = \frac{1 + (\rho e^{-2jkl_{max}})}{1 - (\rho e^{-2jkl_{max}})}$$


$$\frac{Z_{eq}(l_{max})}{Z_0} = \frac{1 + |\rho|}{1 - |\rho|} = VSWR$$

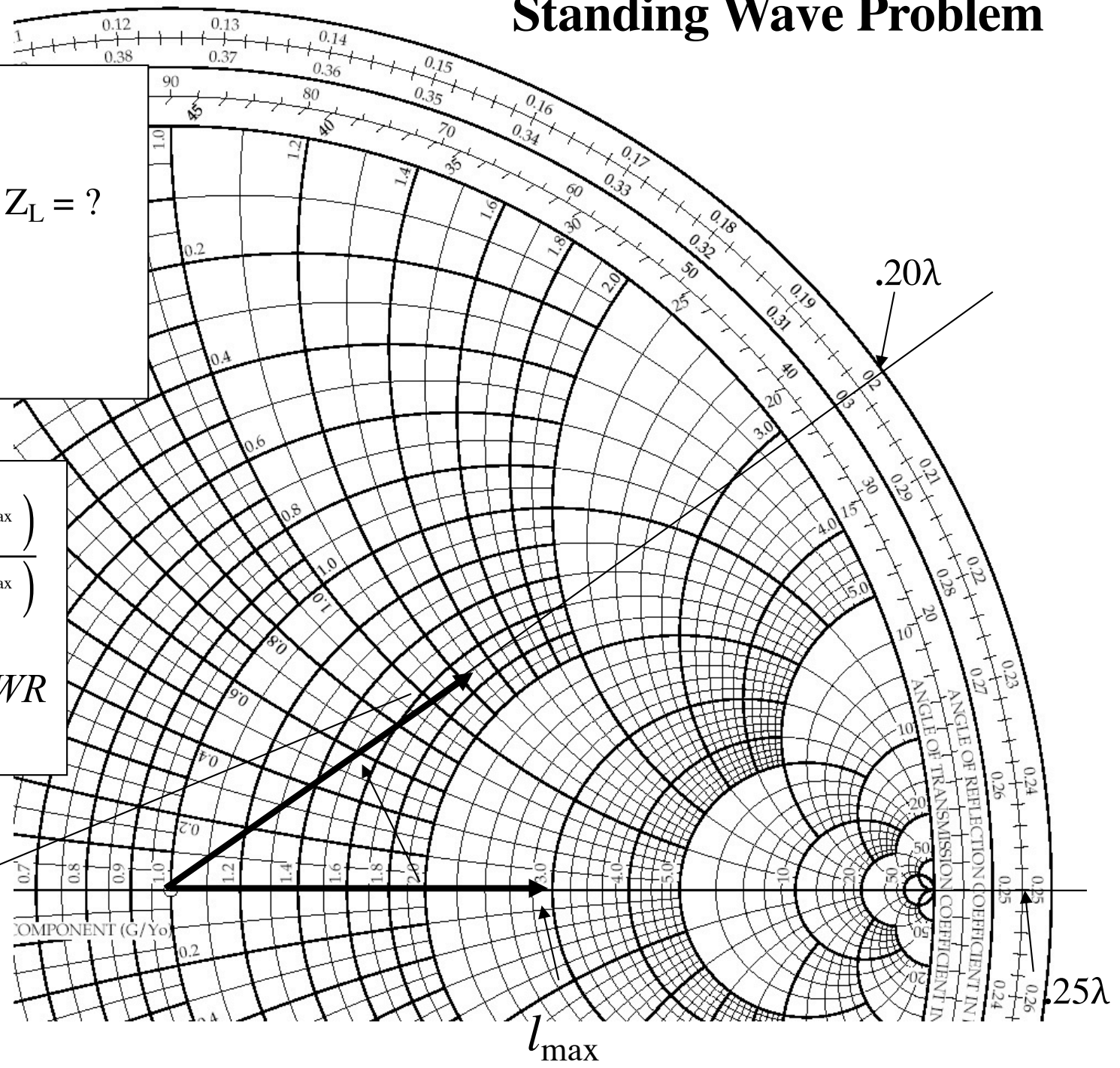$1.7 + j1.3$   
 $Z_L = 170 + j130 \Omega$



$f = 5 \text{ MHz}$

$Z_0 = 100 \Omega, v = 10^8 \text{ m/s}$

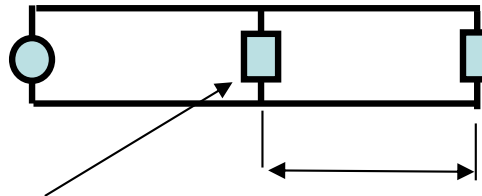

$Z_L = (140 + j130) \Omega$

$Y_s = ?$

$l = ? \text{ m}$


**Matching**

$l/\lambda = .06 + .168 = .228$


$Y_{eq}/Y_0 = (1.0 + j1.2)$   
 $Y_s/Y_0 = (0 - j1.2)$

$Z_L/Z_0 = (1.4 + j1.3)$

$Y_L/Y_0 = (.38 - j.34)$

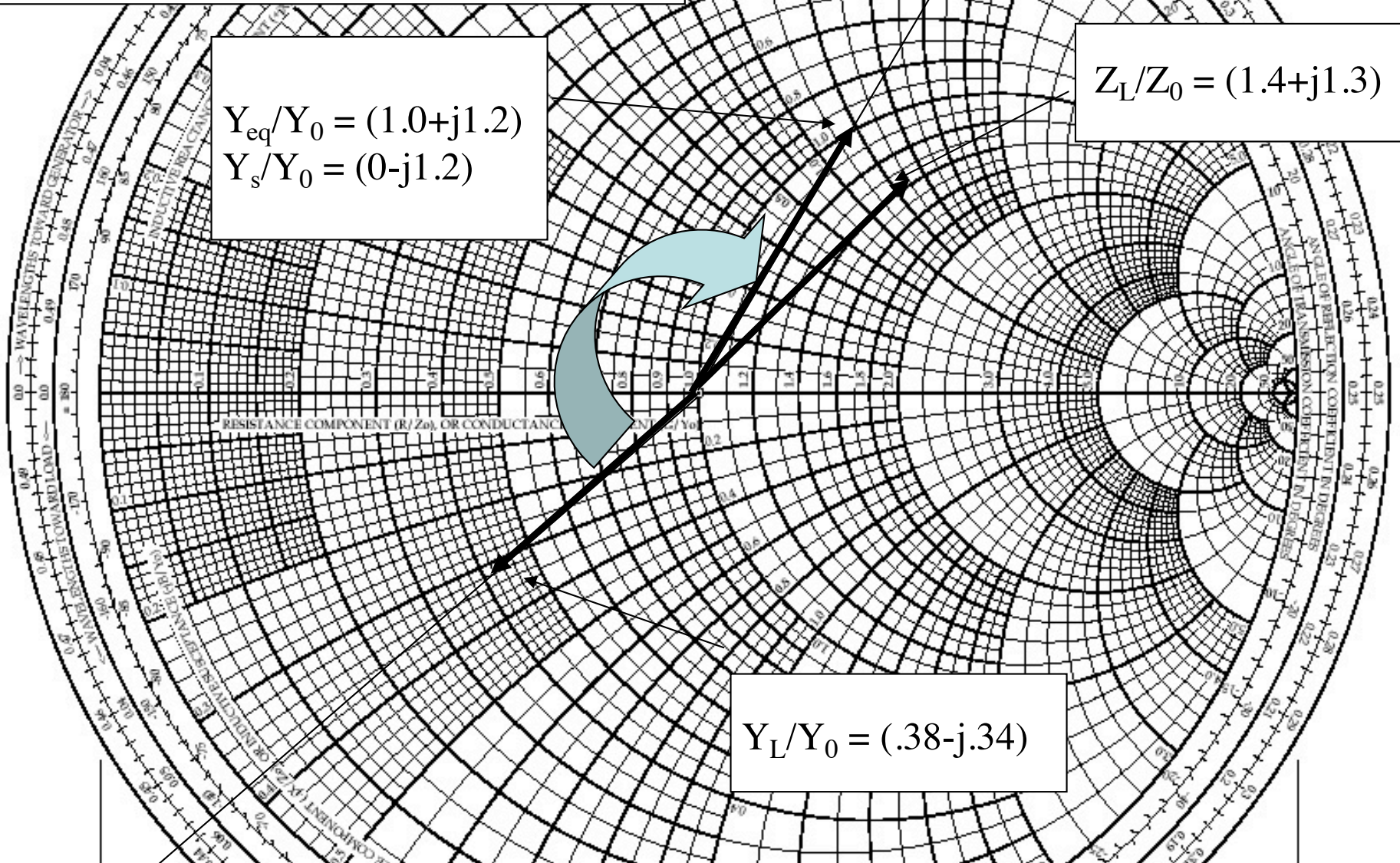

# Shunt admittance

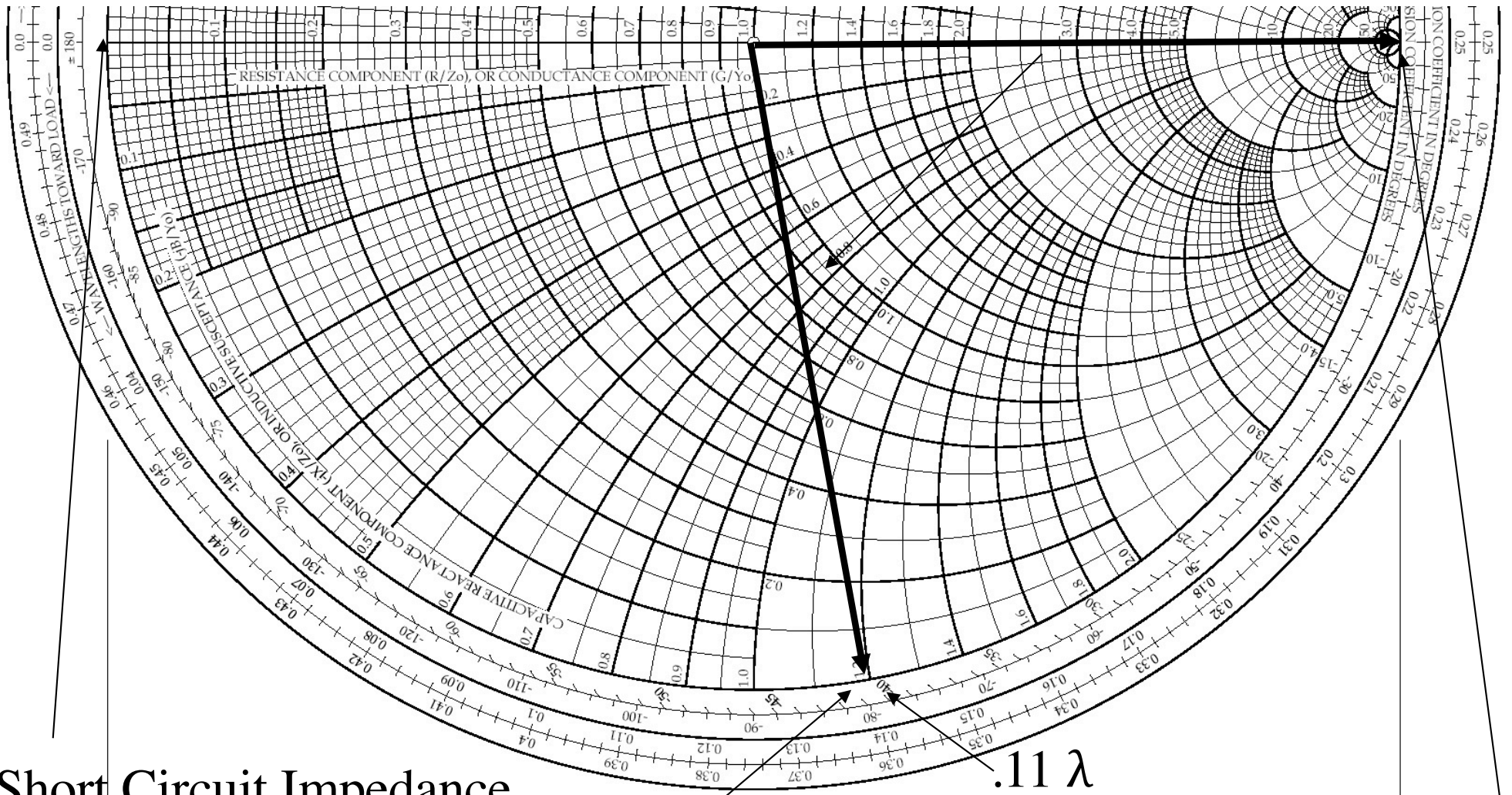

Short Circuit Impedance

$$Y_s/Y_0 = (0 - j1.2)$$

0.11 λ

Short Circuit Admittance