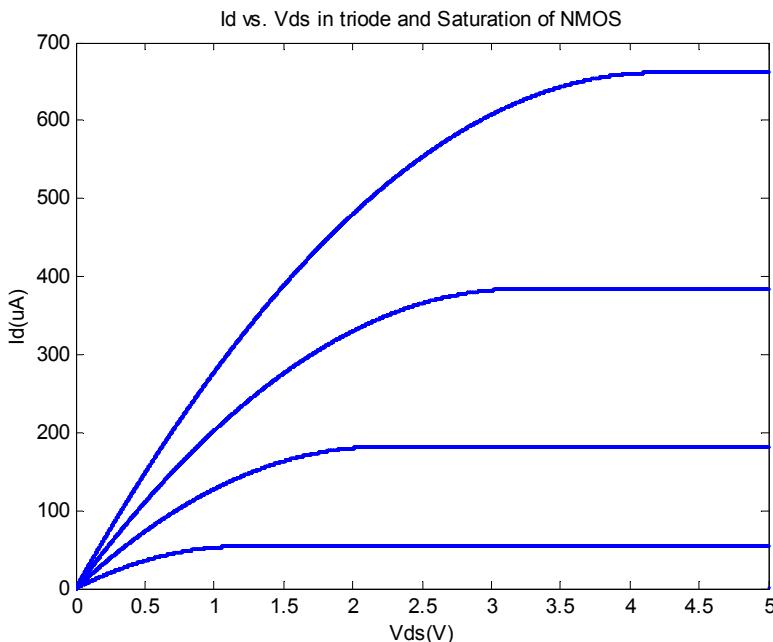


**Problem1**


```
clear all  
L=2;  
W=3;  
VTO=0.8;  
KPn=50;  
  
Vthn=VTO;  
Vds=0.5;  
for Vgs=0.1:0.01:5;  
    if (Vgs-Vthn)>0  
        if (Vds<=(Vgs-Vthn))  
            Id=KPn*(W/L)*((Vgs-Vthn)*Vds-Vds*Vds/2);  
        else  
            Id=KPn/2*(W/L)*(Vgs-Vthn)^2;  
        end  
    else  
        Id0=KPn*0.0259*0.0259*exp(1.8);  
        Id=Id0*(W/L)*exp((Vgs-Vthn)/0.0259);  
    end  
    semilogy(Vgs,Id);  
    hold on  
end  
xlabel('Vgs(V)');  
ylabel('log Id(uA)');  
title('log Id vs. Vgs in subthreshold triode and Saturation of NMOS')
```



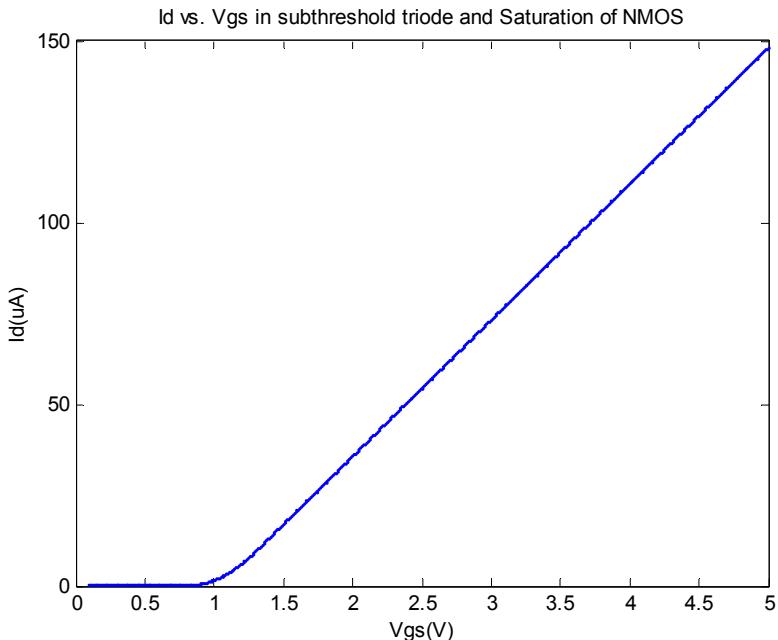**Problem 2:**

```
clear all
L=2;
W=3;
VTO=0.8;
KPn=50;

Vthn=VTO;
Vds=0.5;
for Vgs=0.1:0.01:5;
    if (Vgs-Vthn)>0
        if (Vds<=(Vgs-Vthn))
            Id=KPn*(W/L)*((Vgs-Vthn)*Vds-Vds*Vds/2);
        else
            Id=KPn/2*(W/L)*(Vgs-Vthn)^2;
        end
    else
        Id0=KPn*0.0259*0.0259*exp(1.8);
        Id=Id0*(W/L)*exp((Vgs-Vthn)/0.0259);
    end
    plot(Vgs,Id);
    hold on
end
xlabel('Vgs(V)');
ylabel('Id(uA)');
title('Id vs. Vgs in subthreshold triode and Saturation of NMOS')
```



### Problem 6.5

The drive current of a short-channel MOSFET is given by Eq. (6.41)

$$I_{\text{drive}} = v_{\text{sat}} \times C'_{\text{ox}} \times (V_{\text{GS}} - V_{\text{THN}} - V_{\text{DS,sat}}),$$

$$C'_{\text{ox}} = \epsilon_{\text{ox}} / \text{TOX} = (8.85 \times 3.97 \text{ aF}/\mu\text{m}) / (75 \times 10^{-10} \text{ m}) = 4.685 \text{ fF}/\mu\text{m}^2$$

$$I_{\text{drive}} = 10 \text{ cm/s} \times 4.685 \text{ fF}/\mu\text{m}^2 \times (2.5 - .5 - 1.5) \text{ V} = 234.25 \mu\text{A}/\mu\text{m}$$

For the long channel MOSFET in chapter five, we assume that electron mobility  $\mu$  does not vary with  $V_{\text{DS}}$ . For short-channel MOSFETs,  $V_{\text{DS,sat}}$  is not directly dependent on the  $V_{\text{GS}}$  and  $V_{\text{TH}}$ , but it is used to change the drift velocity. From figure 6.8 and Eq. (6.39), the  $V_{\text{DS,sat}}$  is dependent directly on the critical electrical field which causes the drift velocity to  $v_{\text{sat}}$ . Therefore,  $V_{\text{DS,sat}}$  is not equal to  $V_{\text{GS}} - V_{\text{THN}}$  for short-channel MOSFETs.

### Problem 6.7

From eq. (6.21), the output resistance is given by  $r_o = 1/(\lambda \cdot I_D)$ . Using level 1 MOSFET SPICE model, in saturation region,  $I_D = \text{MUZ} \cdot C_{\text{ox}} \cdot W \cdot (V_{\text{GS}} - V_{\text{THN}})^2 / 2L$

Therefore,

$$r_o = 2L / [\lambda \cdot \text{MUZ} \cdot C_{\text{ox}} \cdot W \cdot (V_{\text{GS}} - V_{\text{THN}})^2]$$

$$\text{Set } K = 2 / [\text{MUZ} \cdot C_{\text{ox}} \cdot W \cdot (V_{\text{GS}} - V_{\text{THN}})^2],$$

$$r_o = L / (\lambda \cdot K)$$

For  $10\mu\text{m}/2\mu\text{m}$  MOSFET, the effective resistance of NMOS is  $R_n = 12\text{k}\Omega \times 2/10 = 2.4\text{k}\Omega$ , and for the PMOS,  $R_p = 36\text{k}\Omega \times 0.2 = 7.2\text{k}\Omega$ . The capacitance between drain to ground is same for both NMOS and PMOS and equal to  $C_{\text{ox}} + 150\text{fF} = 166\text{fF}$ . From eq. (10.8) and (10.9), for NMOS,

$$t_{\text{PLH}} = 2.4\text{k}\Omega \times 166\text{fF} \approx 398\text{ps}, \quad t_{\text{LH}} = 2 \times 2.4\text{k}\Omega \times 166\text{fF} \approx 797\text{ps}$$



for PMOS,

$$t_{\text{PLH}} = 7.2\text{k}\Omega \times 166\text{fF} \approx 1.2\text{ns}, \quad t_{\text{LH}} = 2 \times 7.2\text{k}\Omega \times 166\text{fF} \approx 2.4\text{ns}$$



Simulation:

Trick: need to set the IC value for the Capacitor.

NMOS

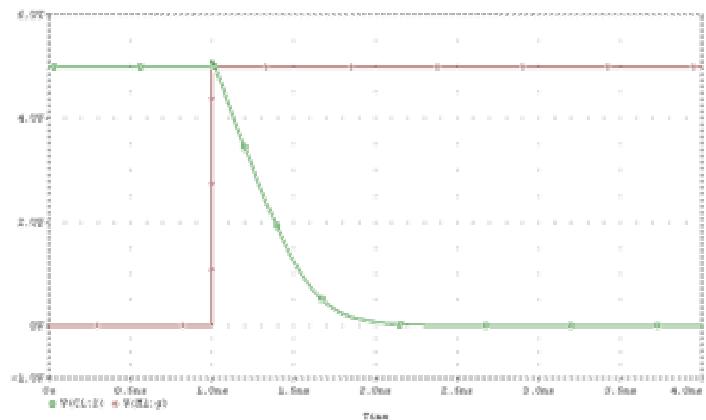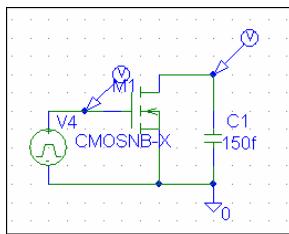

PMOS

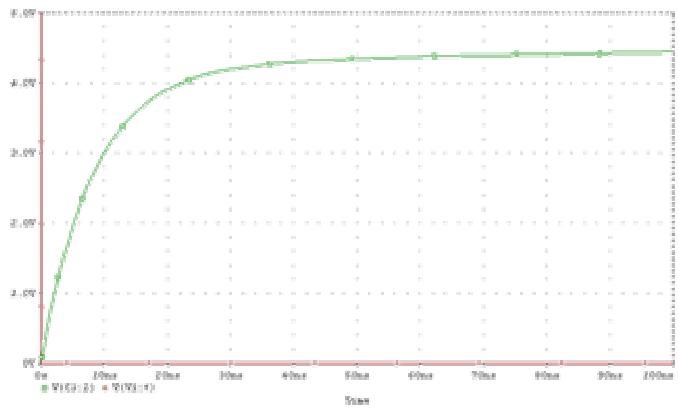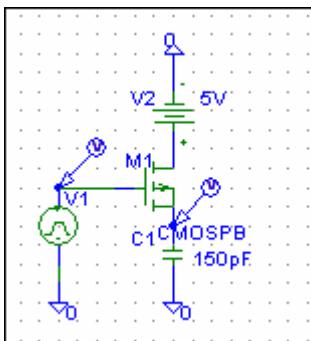

### Problem 10.7


For  $3\mu\text{m}/2\mu\text{m}$  MOSFET, the effective resistance of NMOS is  $R_n = 12\text{k}\Omega \times 2/3 = 8\text{k}\Omega$ , and for the PMOS,  $R_p = 24\text{k}\Omega$ . The capacitance between drain to ground is same for both NMOS and PMOS and equal to  $C_{ox} + 1\text{pF} \approx 1\text{pF}$ . From eq. (10.8) and (10.9), for NMOS,

$$t_{PHL} = 8\text{k}\Omega \times 1\text{pF} = 8\text{ns}, \quad t_{HL} = 2 \times 8\text{k}\Omega \times 1\text{pF} = 16\text{ns}$$


for PMOS,

$$t_{PLH} = 24\text{k}\Omega \times 1\text{pF} = 24\text{ns}, \quad t_{LH} = 2 \times 24\text{k}\Omega \times 1\text{pF} = 48\text{ns}$$


NMOS:

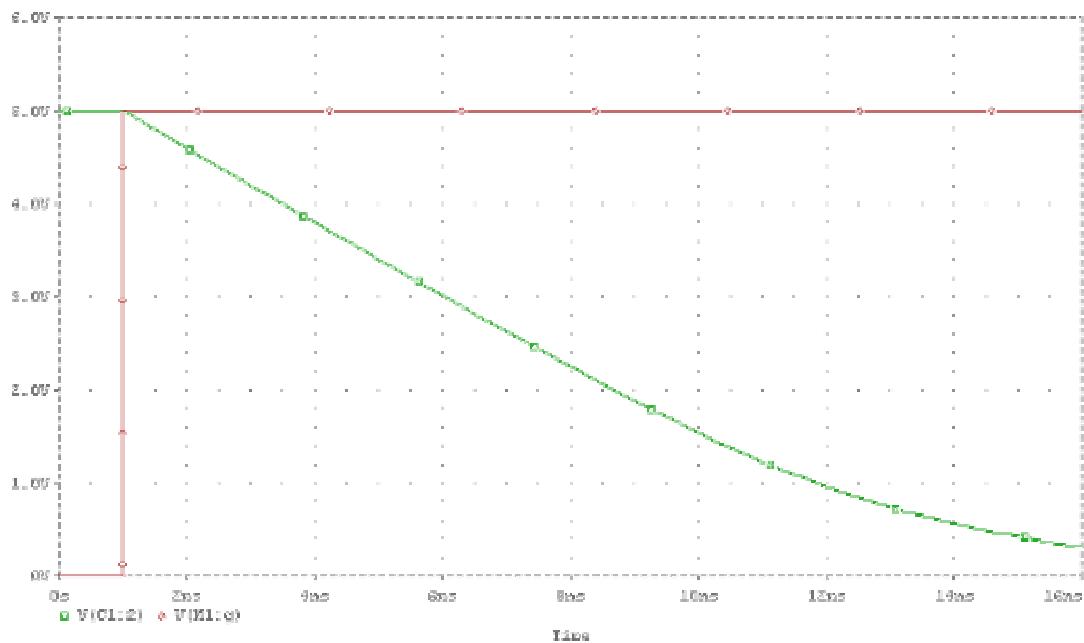

PMOS:

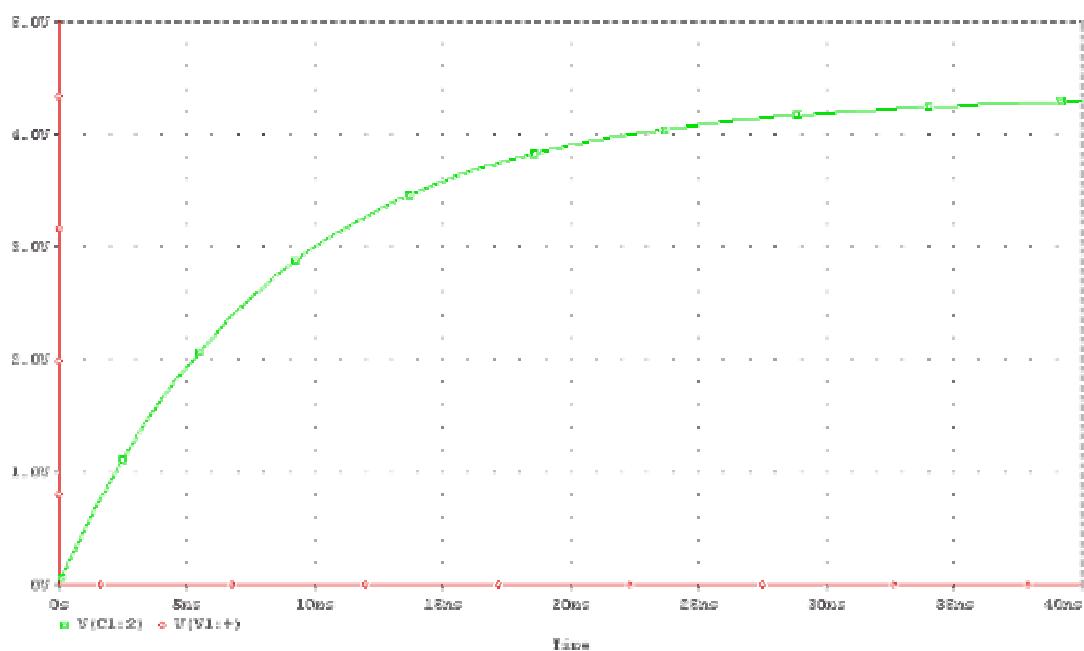

Problem 10.8

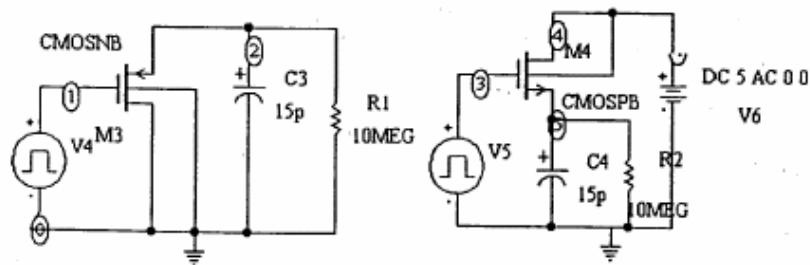

For nmos,  $t_{PLH} \approx 8k\Omega \times 15pF = 120\text{ns}$ ; for pmos,  $t_{PLH} \approx 360\text{ns}$

