Homework 11 Solution

P25.1
SNS: IMA goos through Ms. M1, M2, M3, M4, M7, M8
WA (Iss) through M6

$$g_{m_1} = \sqrt{2 \times 50 \times \frac{17}{1} \times 1} = 17.32 \text{ MA//}$$

 $g_{m_7} = \sqrt{2 \times 17 \times \frac{70}{5} \times 1} = 21.82 \text{ MA//}$
 $r_{02} = r_{09} = r_{08} = \frac{1}{0.06 \times 144} = 16.67 \text{ M2}$
AoL= $g_{m_1} = r_{01} + r_{01} + r_{02} + r_{03} + r_{03}$

$$P_{25:3} \quad ANS$$

$$R_{inMi, 5} = \left(\frac{1+9}{Y_{01}+\frac{1}{2}}\right)^{-1} \approx g_{m_{1}}^{-1} = \frac{1}{g_{m_{1}}}$$

$$\frac{1}{4s_{m_{1}}} \qquad \frac{1}{4s_{m_{1}}} \qquad \frac{1}{s_{m_{2}}} = \frac{1}{s_{m_{2}}}$$

$$R_{inMi, 5} = \left(\frac{1+9}{Y_{01}+\frac{1}{2}}\right)^{-1} = \left(\frac{9}{2}\right)^{-1} = \frac{2}{g_{m_{1}}}$$

$$\frac{1}{2} = \frac{1}{2} \times 50 \ M \ M^{-1}_{2} \times \frac{5}{2} \times \frac{1}{2} \times \frac{1$$

25.5

If the drain current of M6, in Fig. 25.11, is reduced to 5mA, what are the drain currents in M3, M4, M7, and M9?

$$I_{03} = I_{04} = \frac{1}{2}I_{04} = \frac{2.5 \text{ M}}{2}$$

Since $\binom{W}{L}_{4} = \binom{W}{L}_{0}$
 $I_{07} = I_{04} = 2.5 \text{ M}$

For Iog first find Vosqu:

$$2.5\mu = \frac{50\mu}{2} \frac{15}{2} (V_{GSN} - 0.83)^2 = neglecting built effect$$

 $V_{GSQL} = 0.945 V$

Due to symmetry $U_{GSH} = U_{GSQ}$ $I_{Aq} = \frac{50\mu}{2} \frac{150}{2} (0.145 - .83)^2$ $I_{AQ} = 25\mu A$

small signal model:
Rs
+
$$C_1 \prod_{i=1}^{n} \frac{1}{C_{gSI}} \frac{1}{V_{JSI}} \bigoplus_{j=1}^{n} \frac{1}{V_{gSI}} \frac{1}{V_{ag}} \frac{1}{V_{ag$$

$$\frac{N_{out}}{V_{gsi}} = -g_{mi} \left(\frac{1}{\frac{1}{R_{eg}} + jwC_{egz}} \right)$$

$$\frac{V_{fsi}}{V_{iN}} = \frac{\frac{1}{jwC_{egi}}}{\frac{1}{jwC_{egi}} + R_{s}} = \frac{1}{1 + jwC_{egi}R_{s}}$$

$$\frac{N_{our}}{N_{iN}} = \frac{V_{but}}{V_{gsi}} \cdot \frac{N_{fsi}}{V_{iw}} = -g_{mi} \left(\frac{1}{\frac{1}{R_{eg}} + jwC_{egz}} \right) \left(\frac{1}{1 + jwC_{egi}R_{s}} \right)$$

$$\frac{N_{eur}}{V_{im}} = \left(\frac{-g_{mi}R_{eg}}{1 + jwC_{egz}R_{eg}} \right) \left(\frac{1}{1 + jwC_{egi}R_{s}} \right)$$

$$\omega_2 = \frac{9m}{Cgdl}$$