HW5 Solution Mar,2003

Problem1: Describe how MOSFET works, including 4 regions talked in the class.

Main point: list 4 regions (Cutoff, Subthreshold, Triode, Saturation), and give the working conditions for those 4 region and explain it in relative detail, follow the lecture notes.

Note: There is a subtle difference from what we talked Accumulation, Depletion, Weak/Strong Inversion in the MOS cap. Don't mixed those two models up, although they do have strong relationships.

Problem 5.2

Ans: From Eq (5.8), the number of acceptor atoms in the substrate $N_A = n_i \exp(|\phi_F| q/KT) = 8.354 \times 10^{14} \text{ atoms/cm}^3$ Use Eq (5.20), C' $_{ox} = (2 \times q \epsilon_{si} N_A)^{0.5} / \lambda = 369.72 \text{ aF} / \mu m^2$ The KP of this n-channel MOSFET is $KP = \mu_n \times C' _{ox} = 550 \text{ cm}^2 / \text{V} \times 369.72 \text{ aF} / \mu m^2 = 20.33 \mu \text{A} / \text{V}^2$

From Eq. (5.36), $\beta = KP \times W/L = 20.33 \times 10/2 = 101.56$ From Eq. (5.21), $V_{THN} = 0.8V + 0.45 \times ((.57+1)^{0.5} - (.57)^{0.5}) = 1.024V$

Since $V_{DS} > V_{GS} - V_{THN}$ and $V_{GS} > V_{THN}$, the MOSFET is operated in saturation region. With $\lambda=0$, use Eq (5.39),

 $I_{D} = \beta \left(V_{GS} - V_{THN} \right)^{2} / 2 \approx \underline{48.4 \mu A}$

If use CN20 process, the C' $_{ox}$ is 800 $aF/\mu m^2$, and KP = 44 $\mu A/V^2$, $I_D = 104.78\mu A$

For Vsb=0V

Clearly, Vthn=Vthn0=0.8V, and Vgs-Vthn=2-0.8=1.1V, Vds=1.1V, so Vds<Vgs-Vthn, it works in Triode region, so we need to use the equation of Ids in Triode region to calculate Ids, and the result is Ids=72.7uA.

Problem 5.5

C' _{ox} = ϵ_{ox} / TOX = (8.85 × 3.97 aF/µm) / (400×10⁻¹⁰ m) = <u>878.4aF/µm²</u>

Problem 5.8

The electrostatic potential of the oxide semiconductor interface when $VG_S = Vruno$ is: $\phi_S = -\phi_F = \frac{kT}{2} \ln \frac{NA}{N_i}$

Where NA is the number of acceptor atoms in the substrate, Ni is the intrinsic Carrier concentration of silicon. Problem 5.13

Since every MOSFET shown in Figure P5.13 has the same V_{DS} , V_{GS} , KP, L and V_{THN} , the current flowing through every MOSFET is

 $I_{Dn} = (KP \times W_n \times /L) \times [(V_{GS} - V_{THN})V_{DS} - V_{DS}^2/2], n = 1,2, ..., N$ (neglect the body effect and for both triode and saturation region, this equation is effective.)

Therefore, the total current from drain to source is $I_D = [KP \times (W_1 + W_2 + ... + W_N)/L] \times [(V_{GS} - V_{THN})V_{DS} - V_{DS}^2/2]$

This I-V characteristic is the same as one single MOSFET with a width equal to the sum of each individual MOSFET's width.

Problem 5.15

From Figure P5.14, we assume that both MOSFET are in the triode region. Neglecting the body effects,

1) $I_D \times L1/(KP \times W) = (Vgs1 - Vthn) Vds1 - Vds1^2/2 = (Vg - Vthn)V1 - V1^2/2$ 2) $I_D \times L2/(KP \times W) = (Vgs2 - Vthn) Vds2 - Vds2^2/2$ $= (Vg - Vthn - V1)(Vd - V1) - (Vd - V1)^2/2$

1)+2)

 $I_D \times (L2+L1)/(KP\times W) = VgVd-VthnVd-Vd^2/2 = (Vg - Vthn)Vd - Vd^2/2$

Re-arranging this equation,

 $I_D = [KP \times W/(L2+L1)] \times [(V_{GS} - V_{THN})V_{DS} - V_{DS}^2/2]$ From this equation, Figure P5.14 does behave as a single MOSFET with the length equal to the sum of the individual MOSFET's length.

Problem 5.19

For the Fig. P5.19, the layout of an n-channel MOSFET is equal to 5 MOSFETs, each with W/L=4/25, connected serially. Therefore, the device's width is 4 μ m and length is $5\times25=125\mu$ m.

You could relate problem 5.15 with Problem 5.19, just like you could relate the layout example on the book Page 103 with the problem 5.13.