

ENEE 610 Fall 2001 Final exam

2 hours, 100 points total, open book open notes. If stuck on a problem go on to the next.

Shoe your work for partial credit. Good luck!

1. (33points, 30 minutes)

Assume that for the following function $F(s)$, $m=n-1$ and $0 \leq \sigma_1 < \sigma_2 < \dots < \sigma_m < \sigma_n$.

$$F(s) = \frac{(s+\sigma_1)(s+\sigma_3)\dots(s+\sigma_m)}{(s+\sigma_2)(s+\sigma_4)\dots(s+\sigma_n)} = \prod_{k=1}^{n/2} \left(\frac{s+\sigma_{2k-1}}{s+\sigma_{2k}} \right)$$

a) Show that the function can be expanded into a partial fraction expansion as

$$F(s) = K_1 + \frac{K_2}{s+\sigma_2} + \frac{K_4}{s+\sigma_4} + \dots + \frac{K_n}{s+\sigma_n}$$

b) Determine which of the coefficients K_i in this partial fraction expansion are real and positive.

c) Synthesize the following function $F_1(s)$ as an impedance and as an admittance of a network, respectively.

$$F_1(s) = \frac{s(s+5)}{(s+3)(s+8)}$$

2. (35 points, 30 minutes)

Consider the admittance function

$$Y(s) = \frac{s+a}{s+b}$$


where a and b are complex parameters.

a) Determine for which a and b this admittance is positive real.

b) Find the zeros of the even part of $Y(s)$.


c) For $0 < a \leq b$ synthesize $Y(s)$ by using the Richards' function and the following circuit giving passive element values where possible in terms of the parameters a and b .

d) Discuss any anomalies.

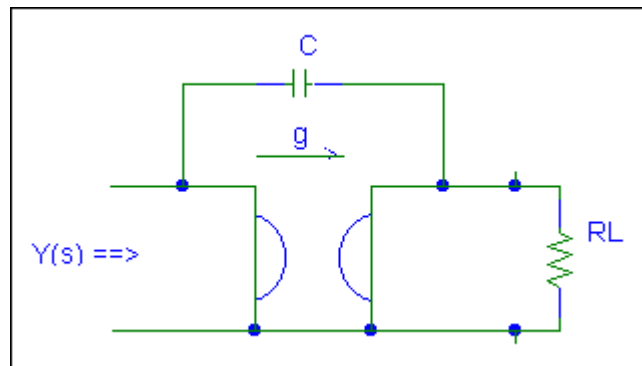

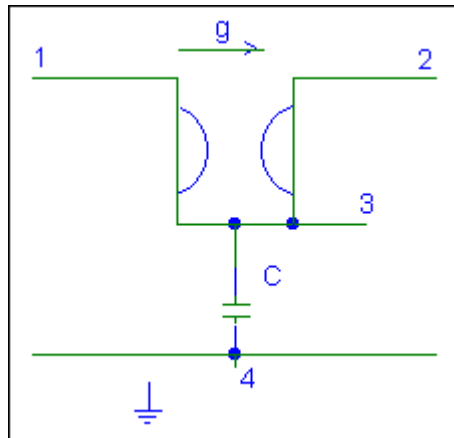3. (32 points, 30 minutes)

For the following circuit all node voltages are measured positive with respect to ground and all external currents enter the numbered nodes.



- Set up the indefinite admittance. Then from it
- Find the admittance matrix when node 4 is grounded.
- With node 4 grounded set up semistate equations using the results of b) along with

$$x = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \text{semistate}, \quad u = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \text{input}, \quad y = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \text{output},$$

where all voltages are measured with respect to the ground node and the input currents enter the correspondingly numbered nodes. (note that in this case $i_3 = 0$)

- By any means find the 2-port admittance $Y(s)$, $y=Y(s)u$, for u and y as in c).