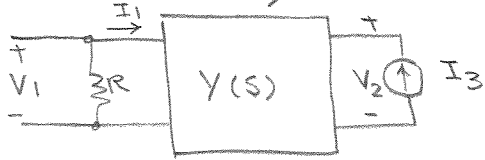


1) (P2, consider 5)



$$V_1 = -I_1 R$$

$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_3 = y_{21} V_1 + y_{22} V_2 \end{cases}$$

10 points

{ 5 → correct basic equation
5 → simplification

$$\Rightarrow I_1 = -\frac{V_1}{R} = y_{11} V_1 + y_{12} V_2 \Rightarrow V_2 = \frac{-V_1/R - y_{11} V_1}{y_{12}}$$

$$I_3 = y_{21} V_1 + y_{22} V_2 = y_{21} V_1 + y_{22} \frac{(-V_1/R - y_{11} V_1)}{y_{12}}$$

$$= \frac{(y_{21} y_{12} - y_{22} y_{11})}{y_{12}} V_1 - \frac{y_{22}}{y_{12}} \times \frac{1}{R} V_1 \Rightarrow \boxed{\frac{V_1}{I_3} = \frac{-R y_{12}}{y_{22} + R(y_{22} y_{11} - y_{21} y_{12})}}$$

2) (P3, Consider 5)

5 points { 3 → R > 0
2 → R < 0

The condition of $T(s) = \frac{V_1}{I_2}$ (for previous problem) to be realizable is the

condition of synthesis of the transfer function:

$$T(s) = \frac{V_1}{I_2} = \frac{-R y_{12}}{y_{22} + R \Delta y} = \frac{-y_{12}/y_{22} \times R}{1 + R \Delta y / y_{22}}$$

a) $Y(s)$ is a lossless ladder & $R > 0$

* $Y(s)$ lossless $\Rightarrow Y(s)$ positive real $\Rightarrow \Delta \geq 0$

$$Y(s) = -Y(-s) \Rightarrow \begin{cases} y_{11}(s) = -y_{11}(-s) ; y_{12}(s) = -y_{12}(-s) \\ y_{21}(s) = -y_{21}(-s) ; y_{22}(s) = -y_{22}(-s) \end{cases}$$

$$* \Delta Y(s) = y_{11}(s) y_{22}(s) - y_{12}(s) y_{21}(s)$$

$$= y_{11}(s) y_{22}(s) - y_{12}(s) y_{21}(s)$$

$$= \Delta(-s)$$

$$\text{Denominator } 1 + \frac{R \Delta Y(s)}{y_{22}} = 0 \Rightarrow y_{22} = -R \Delta y \leq 0$$

\Rightarrow if $R > 0 \Rightarrow$ poles of $T(s)$ are not in the right half plane.


if $R < 0 \Rightarrow$ poles of $T(s)$ could be in the right half plane in which case $T(s)$ wouldn't be positive real or lossless anymore.

3) (consider $G, P3$)

$$Y(s) = \frac{s(s+3)}{3(s+1/3)} \quad \text{poles: } s = -1/3, \quad \text{zeros: } s=0, s=-3$$


$$\text{EV}\{Y(s)\} = \frac{Y(s)+Y(-s)}{2} = \frac{8s^2}{9s^2-1}, \quad \text{zeros: } s=0$$
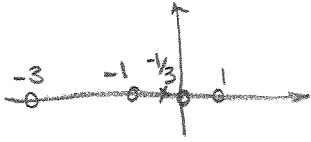
$$\text{Odd}\{Y(s)\} = \frac{Y(s)-Y(-s)}{2} = \frac{3s(s^2-1)}{9s^2-1}, \quad \text{zeros: } s=0, s=\pm 1$$



Pole-zero plot of $Y(s)$
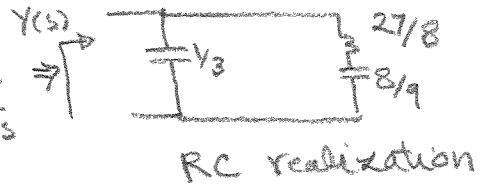
$$Y(s) = \frac{s(s+3)}{3(s+1/3)} = 1/3 s + \frac{8/9 s}{3(s+1/3)} = 1/3 s + \frac{1}{27/8 + 1/8/9s}$$



note: $Z_{LC}(s)$ of the form:

$$\left\{ \begin{array}{l} \frac{H(s^2+\omega_1^2)(s^2+\omega_3^2)\dots}{s(s^2+\omega_2^2)(s^2+\omega_4^2)\dots} \\ \text{or} \\ \frac{Hs(s^2+\omega_2^2)(s^2+\omega_4^2)\dots}{(s^2+\omega_1^2)(s^2+\omega_3^2)\dots} \end{array} \right.$$

to get Z_{RC} from Z_{LC} , replace $1/s$ by R , so $Z_{LC} = Ls + \frac{1}{sC}$ becomes $R + \frac{1}{sC}$, or replace s^2 by s in the above expression for Z_{LC} .

$$Z_{RC}(s) \text{ of the form: } \left\{ \begin{array}{l} \frac{H(s+\alpha_1)(s+\alpha_3)\dots}{s(s+\alpha_2)(s+\alpha_4)\dots} \\ \frac{H(s+\alpha_2)(s+\alpha_4)\dots}{(s+\alpha_1)(s+\alpha_3)\dots} \end{array} \right.$$

$$\Rightarrow Y_{RC} \text{ of the form: } \left\{ \begin{array}{l} \frac{1}{H} \frac{s(s+\alpha_2)(s+\alpha_4)\dots}{(s+\alpha_1)(s+\alpha_3)\dots} \\ \frac{1}{H} \frac{(s+\alpha_1)(s+\alpha_3)\dots}{(s+\alpha_2)(s+\alpha_4)\dots} \end{array} \right.$$

Our function $Y(s) = \frac{s(s+3)}{3(s+1/3)}$ has the Y_{RC} configuration. (can use any of Foster I, Foster II, Cauer I, II synthesis methods for solution).

15 { 5 → poles, zero ^{P2}/₆
10 → driving admittance
up to 5 bonus points for Richard function

3 cont.)

Richard Function Synthesis:

$$y_L = y_{in}(k) \times \frac{ky_{in}(k) - sy_{in}(s)}{ky_{in}(s) - sy_{in}(k)}$$

$$y_L = \frac{k(k+3)}{3(k+1/3)} \times \frac{k \frac{k(k+3)}{3(k+1/3)} - s \frac{s(s+3)}{3(s+1/3)}}{k \frac{s(s+3)}{3(s+1/3)} - s \frac{k(k+3)}{3(k+1/3)}}$$

eliminate (k-s) from numerator & denominator

$$= \frac{k(k+3)}{3(k+1/3)} \times \frac{k^3s + 1/3k^3 + 3k^2s + k^2 - s^3k - 1/3s^3 - 3s^2k - s^2}{k^2s^2 + 1/3ks^2 + 3k^2s + ks - k^2s^2 - 3s^2k - 1/3k^3 - ks}$$

$$= \frac{k(k+3)}{3(k+1/3)} \times \frac{(k-s)(s^2k^2 + ks^2 + 1/3k^2 + 1/3ks + 1/3s^2 + 3ks + k+s)}{3/8 ks(k-s)}$$

eliminate k as well


$$= \frac{1}{8} \frac{k+3}{(k+1/3) \times s} (s^2k^2 + ks^2 + 1/3k^2 + 1/3ks + 1/3s^2 + 3ks + k+s)$$

now let k=0

$$y_L|_{k=0} = \frac{3}{8} \times \frac{1}{s/3} \times s \left(\frac{s}{3} + 1 \right) = \frac{s+3}{8/3} = \frac{3}{8}s + \frac{9}{8}$$


$$g = y_{in}(k) = 0$$

$$C = \frac{k}{y_{in}(k)} \Big|_{k=0} = \frac{0}{0} \xrightarrow{\text{take derivative from num. \& denom. with respect to k}} C = \frac{1}{\frac{1}{3} \frac{(2k+3)(k+1/3) - (k^2+3k)}{(k+1/3)^2}} \Big|_{k=0} = 3$$

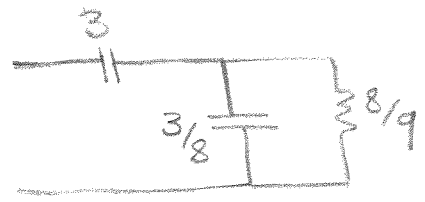

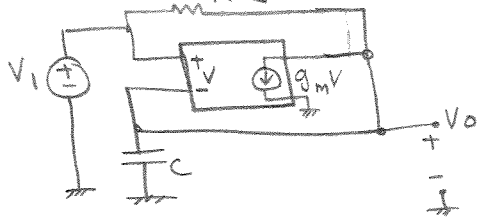4) (P5, consider 6)

15 points } 5 points for each case
 3 points for adjoint from sensitivity
 2 points for direct method



$$\frac{V_0 - V_1}{R} + g_m(V_1 - V_0) + sCV_0 = 0$$

$$\Rightarrow T(s) = \frac{V_0}{V_1} = \frac{1/R - g_m}{1/R - g_m + sC}$$

1- Direct calculation:


$$S_{g_m}^T = \frac{g_m}{T} \frac{\partial T}{\partial g_m} = \frac{-(1/R - g_m + sC) + (1/R - g_m)}{(1/R - g_m + sC)^2} \times \frac{g_m}{\frac{1/R - g_m}{1/R - g_m + sC}} = \frac{-sC g_m}{(g_m + 1/R)(1/R - g_m + sC)}$$

$$S_C^T = \frac{C}{T} \frac{\partial T}{\partial C} = \frac{-s(1/R - g_m)}{(1/R - g_m + sC)^2} \times \frac{C}{\frac{1/R - g_m}{1/R - g_m + sC}} = \frac{-sC}{1/R - g_m + sC}$$


$$S_R^T = \frac{R}{T} \frac{\partial T}{\partial R} = \frac{-1/R^2 (1/R - g_m + sC) + 1/R^2 (1/R - g_m)}{(1/R - g_m + sC)^2} \times \frac{R}{\frac{1/R - g_m}{1/R - g_m + sC}} = \frac{-sC}{(1 - g_m R)(1/R - g_m + sC)}$$

2- Using adjoint circuit:

Adjoint circuit:

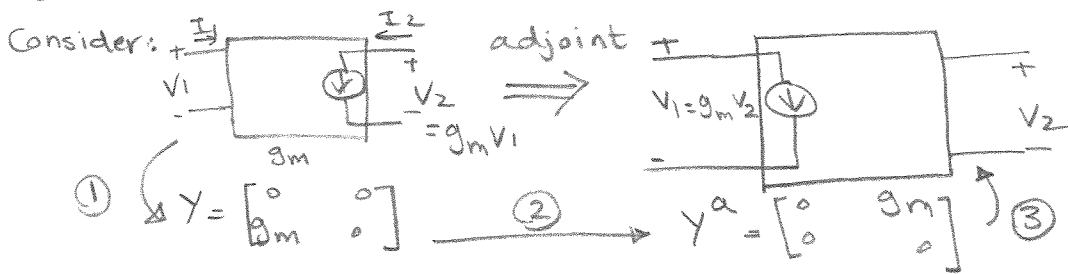

adjoint circuit: V_G^a

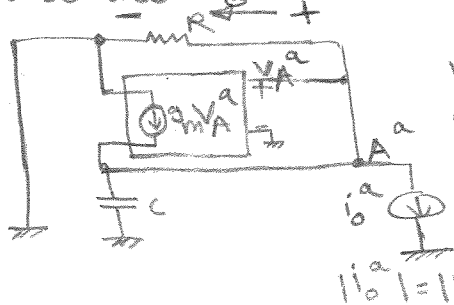

notice, the graph of the original and adjoint circuit stays the same.
 (if one branch for input and one branch for output is considered.)

$$\frac{\partial T}{\partial R} = \frac{\partial T}{\partial G} \times \frac{\partial G}{\partial R} = \frac{-1/R^2}{\frac{\partial V_R}{\partial R} = -1/R^2} \times (V_G \times V_G^a) = \frac{-1}{R^2} (V_0 - V_1) \left(\frac{-1}{sC + 1/R - g_m} \right)$$

KCL @ A: $i_o^a = V_A^a (-sC - 1/R + g_m) \Rightarrow V_A^a = V_G^a = \frac{-1}{sC + 1/R - g_m}$

$\|i_o^a\| = 1$

$$V_G = V_0 - V_1 = T - 1 = \frac{1/R - g_m}{1/R - g_m + sC} - 1 = \frac{-sC}{1/R - g_m + sC}$$

$|V_G| = 1$

$$\Rightarrow S_R^T = \frac{R}{T} \times \frac{\partial T}{\partial R} = \frac{R}{\frac{1/R - g_m}{1/R - g_m + sC}} \times \frac{-sC}{1/R - g_m + sC} \times \frac{-1}{sC + \frac{1}{R} - g_m} \times \frac{-1}{R^2} = \frac{-sC}{(1 - Rg_m)(\frac{1}{R} - g_m + sC)}$$

$$\frac{\partial T}{\partial C} = \frac{\partial T}{\partial y_c} \times \frac{\partial y_c}{\partial C} = S \frac{\partial T}{\partial y_c} = S \times V_{y_c} \times V_{y_c}^a$$

$y_c = sC$

$$V_{y_c} = V_0 = T = \frac{1/R - g_m}{1/R - g_m + sC}$$

$$V_{y_c}^a = V_G^a = \frac{-1}{sC + \frac{1}{R} - g_m}$$

$$\Rightarrow S_C^T = \frac{C}{T} \times \frac{\partial T}{\partial C} = \frac{C}{\frac{1/R - g_m}{1/R - g_m + sC}} \times S \times \frac{1/R - g_m}{1/R - g_m + sC} \times \frac{-1}{sC + \frac{1}{R} - g_m} = \frac{-sC}{sC + \frac{1}{R} - g_m}$$

$$\frac{\partial T}{\partial g_m} = V_A \times V_A^a = (V_1 - V_0) \times V_G^a = (1 - T)(V_G)^a$$

$$\Rightarrow S_{g_m}^T = \frac{g_m}{T} \times \frac{\partial T}{\partial g_m} = \frac{g_m}{\frac{1/R - g_m}{1/R - g_m + sC}} \times (1 - \frac{1/R - g_m}{1/R - g_m + sC}) \times \frac{-1}{sC + \frac{1}{R} - g_m} = \frac{-g_m sC}{(-g_m + \frac{1}{R})(\frac{1}{R} - g_m + sC)}$$


5) (P6, consider 6)

To get the adjoint circuit, the input voltage source is replaced with short in adjoint circuit and the output "open" voltage is replaced by a current source. The graph of the original and adjoint circuit stays the same. Basic rule is: $V_b^T i_b^a - V_b^a i_b^T = 0$ (for all branches), this implies $y_b^a = y_b^T$, which suggests that all ^{passive} 1 port elements like R, C, LG stay the same in both circuits. For n-ports in general, we use $y_b^a = y_b^T$ to extract its adjoint as we did for the G component in previous problem.

For the adjoint of the previous problem, please refer to the previous page.

10 points; G → how to build
 K → contraction on prev. example


5) $f(x) = x(\frac{x^2}{3} - 1)$

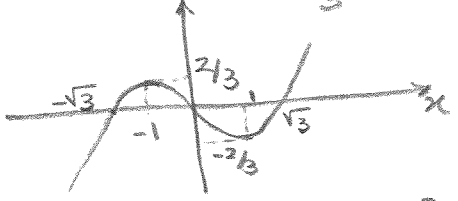

extrema: $(-1, \frac{2}{3})$ and $(1, -\frac{2}{3})$

30 points { 20 part a (limit cycles + f(x))
10 part b Pspice setup
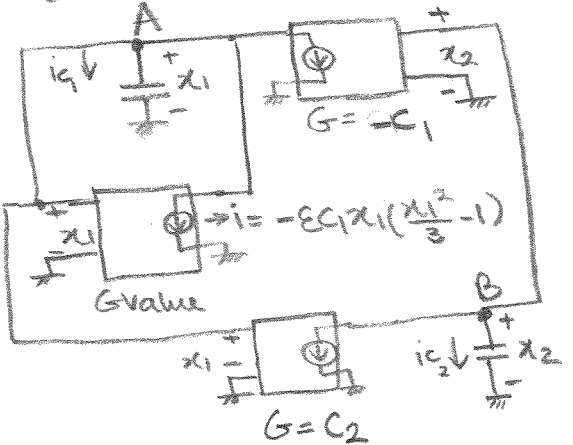
$$\begin{cases} \dot{x}_1 = x_2 + \epsilon x_1 (\frac{x_1^2}{3} - 1) \\ \dot{x}_2 = -x_1 \end{cases} \Rightarrow \begin{cases} C_1 \dot{x}_1 = C_1 x_2 + \epsilon C_1 x_1 (\frac{x_1^2}{3} - 1) = \dot{\lambda}_1 C_1 \\ C_2 \dot{x}_2 = -C_2 x_1 = \dot{\lambda}_2 C_2 \end{cases} \rightarrow 2 \text{ KCLS}$$
 should be realized at points A & B.



* Shape of limit cycle (x_2 versus x_1) sharpens as ϵ increases. (for $\epsilon = .001$, it's oval, for $\epsilon = 1000$ it becomes a square).