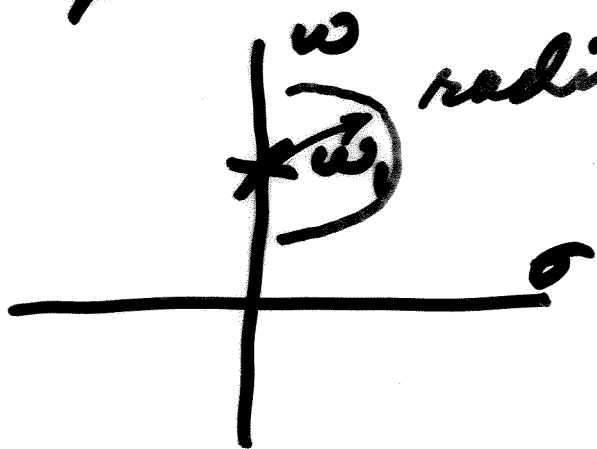


lossless 1-port passive
 synthesis \Rightarrow $z(s)$ rational,
 positive coefficients

$$z(s) = N(s)/D(s)$$

$$z(s) + z(-s) = 0 \text{ lossless}$$

poles are all on the $j\omega$ axis



near a pole at $j\omega_1$
 $z(s)$ near $j\omega_1$
 $\approx \frac{k}{(s - j\omega_1)^m}$

$$2 \operatorname{Re} z(s) \approx \frac{k}{(s - j\omega_1)^m} + \frac{k^*}{(s^* + j\omega_1)^m}$$

$$\approx \frac{|k| e^{j(\angle k - m \angle (s - j\omega_1))}}{|s - j\omega_1|^m}$$

$$\approx \frac{|k|}{r^m} \cos(\angle k - m \angle (s - j\omega_1))$$

$-90^\circ < \angle (s - j\omega_1) < 90^\circ$

as sweep of $\alpha - j\omega_1$

The cos($\alpha t - m \angle [\alpha - j\omega_1]$)
will be negative if $\alpha t \neq 0$
and $m \neq 1$


$$\therefore y(s) \text{ near } j\omega_1 \Rightarrow \frac{|k| = k}{(\alpha - j\omega_1)^1}$$

$$y(s) = \frac{k}{\alpha - j\omega_1} + \frac{k}{\alpha + j\omega_1} + \dots$$

$$= \frac{2k\alpha}{\alpha^2 + \omega_1^2} + \dots$$

$$\therefore y(s) = \frac{k_0}{\alpha} + k_{\infty} \alpha + \sum_{i=1}^n \frac{2k_i \alpha}{\alpha^2 + \omega_i^2}$$

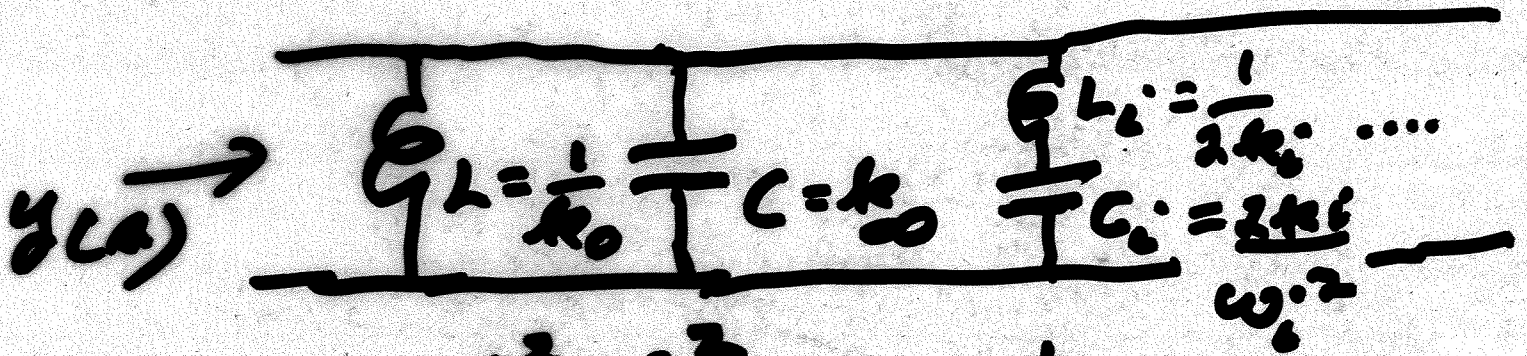
where $k_0 \geq 0$, $k_{\infty} \geq 0$, $k_i \geq 0$



$$Z_i(s) = \frac{s^2 + \omega_i^2}{2k_i s} = \frac{1}{2k_i} + \frac{1}{\frac{2k_i}{\omega_i^2} s}$$

this is a 2nd Foster form

1st Foster:

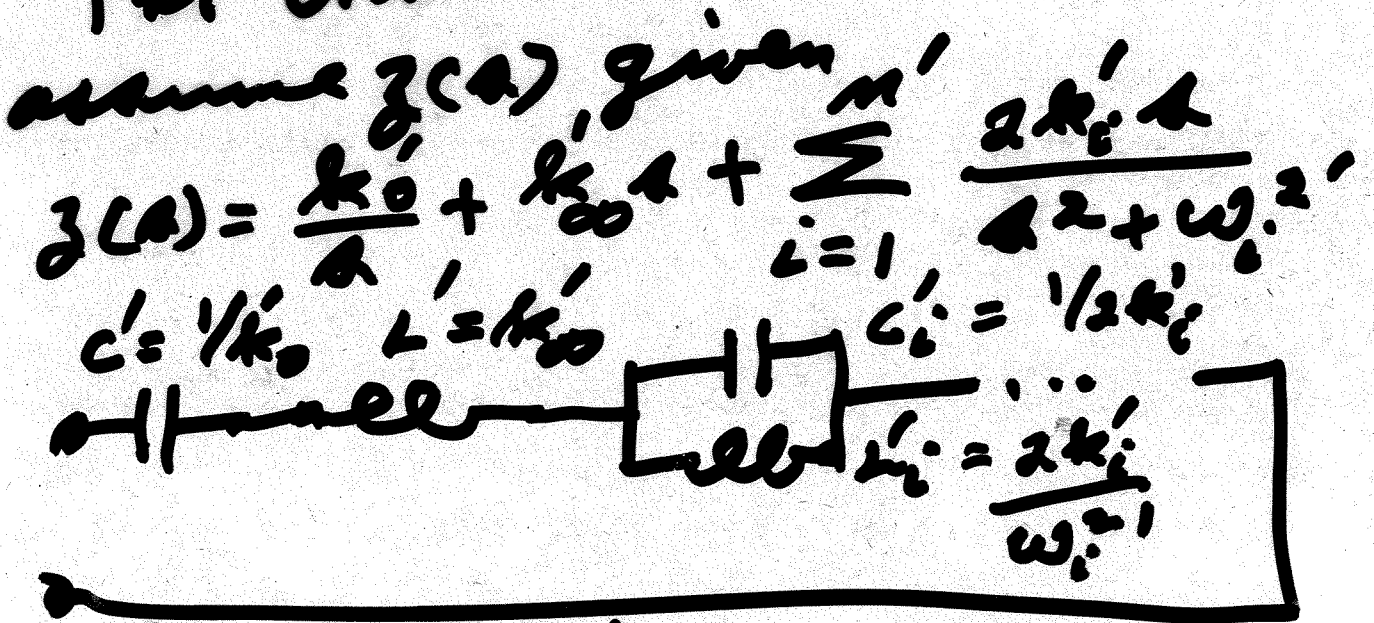

$$Y_i'(s) = \frac{s^2 + \omega_i'^2}{2k_i' s} = \frac{1}{2k_i'} + \frac{1}{\frac{2k_i'}{\omega_i'^2} s}$$

poles of $z(s)$ are

zeros of $y(s) = 1/z(s)$

for lossless, all poles and all zeros are on the $j\omega$ axis and poles and zeros alternate.

$$z(j\omega) = j\omega k_0 + \frac{k_0}{j\omega} + \sum_{i=1}^n \frac{2k_i \cdot j\omega}{\omega_i^2 - \omega^2}$$

$$= jX(\omega)$$

$$\frac{dX(\omega)}{d\omega} = k_0 + \frac{k_0}{\omega^2} + \sum_{i=1}^n \frac{2k_i(\omega_i^2 + \omega^2)}{(\omega_i^2 - \omega^2)^2}$$


$$\frac{d}{d\omega} \frac{\omega}{\omega_i^2 - \omega^2} = \frac{1}{\omega_i^2 - \omega^2} - \frac{\omega(-2\omega)}{(\omega_i^2 - \omega^2)^2}$$

$$= \frac{\omega_i^2 - \omega^2 + 2\omega^2}{(\omega_i^2 - \omega^2)^2} = \frac{\omega_i^2 + \omega^2}{(\omega_i^2 - \omega^2)^2}$$

≥ 0

\therefore slope $\frac{dX(\omega)}{d\omega} \geq 0$ or ∞

1.5

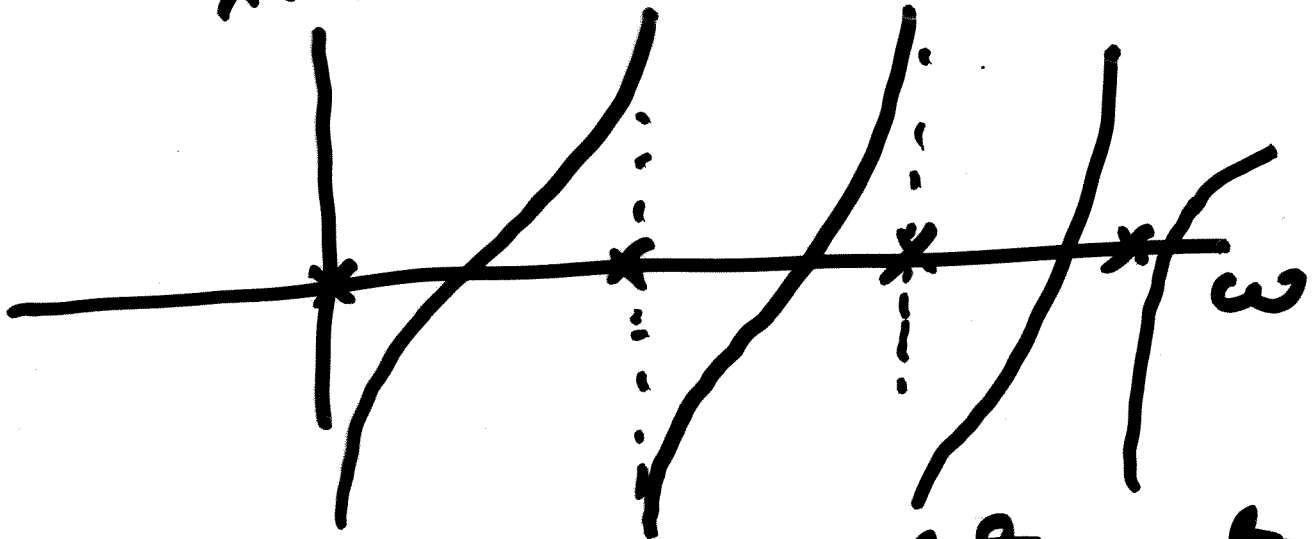

\therefore zeros of $X(\omega)$ alternate with the poles these are zeros of $Z(s)$

\therefore poles and zeros of lossless positive real rational function alternate and are on the $j\omega$ axis.

$$Y(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+2)}$$

this is a lossless admittance

EE 610 10/07/02

1st Order synthesis

r.6

$$Z(s) = \frac{1}{s} = \frac{s(s^2+2)}{(s^2+1)(s^2+4)}$$

$$= \frac{2k_1 s}{s^2+1} + \frac{2k_2 s}{s^2+4}$$

to find k_1 , multiply by $\frac{s^2+1}{s}$


$$\left. \frac{s^2+2}{s^2+4} \right|_{s^2=-1} = 2k_1 + \frac{s^2+1}{s^2+4} \cdot \frac{s}{s} \cdot 2k_2 \Big|_{s^2=-1}$$

0

$$2k_1 = \frac{-1+2}{-1+4} = \frac{1}{3}$$

$$2k_2 = \frac{s^2+2}{s^2+4} \Big|_{s^2=4} = \frac{-2}{-3} = \frac{2}{3}$$
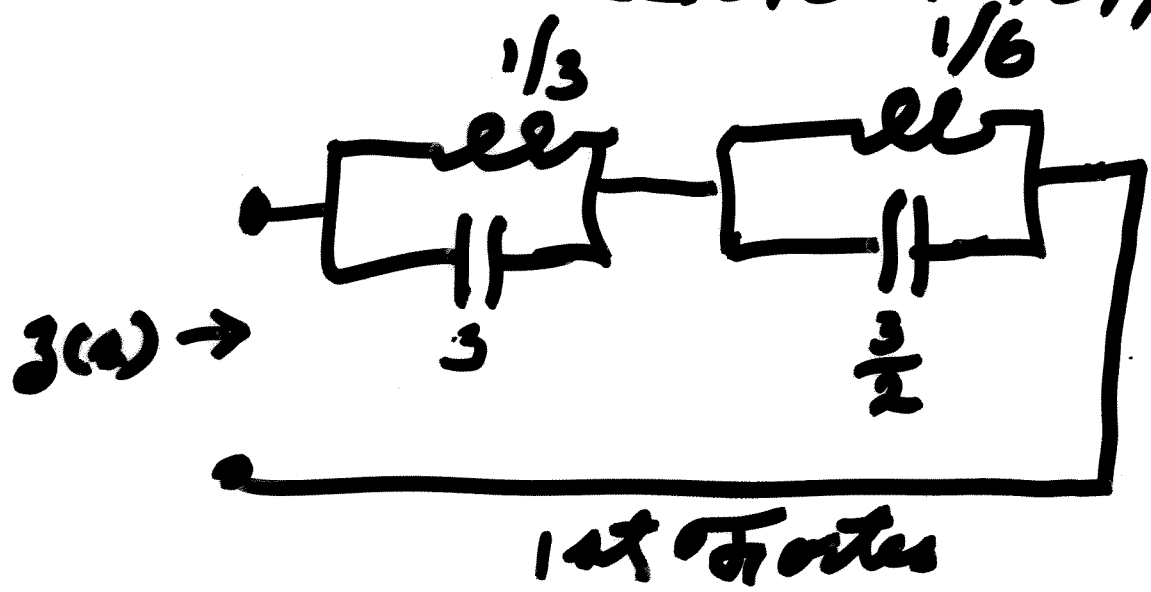
$$Z(s) = \frac{\frac{1}{3}s}{s^2+1} + \frac{\frac{2}{3}s}{s^2+4}$$



2nd Foster


$$y(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+2)}$$

$$= \frac{k_0}{s} + 1 \cdot s + \frac{2ks}{s^2+2}$$

$$= \frac{2}{s} + s +$$

$$2k = \left. \frac{(s^2+1)(s^2+4)}{s^2} \right|_{s^2=-2} = \frac{(-1)(2)}{-2} = 1$$
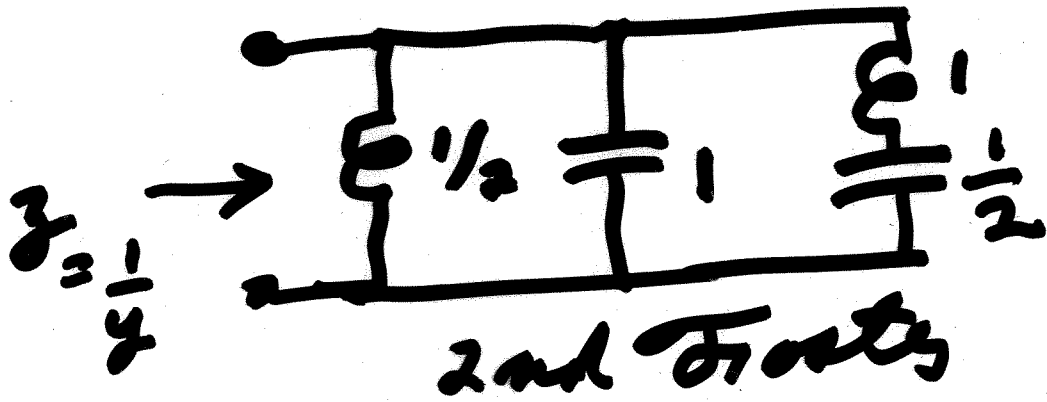
$$y(s) = \frac{2}{s} + s + \frac{s}{s^2+2}$$



1st Layer: removes poles

at ∞

$$y(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+2)} = \frac{s^4+5s^2+4}{s^3+2s}$$

$$\begin{array}{r} s^3+2s \overline{) s^4+5s^2+4} \\ \underline{s^4+2s^2} \\ 3s^2+4 \end{array} \quad \begin{array}{r} \frac{1}{3}s \overline{) s^3+2s} \\ \underline{s^3+\frac{4}{3}s} \\ \frac{2s}{3} \sqrt{3s^2+4} \end{array}$$

$$\begin{array}{r} \frac{2s}{3} \overline{) 3s^2+4} \\ \underline{3s^2+4} \\ 0 \end{array} \quad \begin{array}{r} \frac{2}{3}s \overline{) 2s} \\ \underline{2s} \\ 0 \end{array} \quad \begin{array}{r} \frac{2s}{3} \overline{) 3s^2+4} \\ \underline{3s^2+4} \\ 0 \end{array}$$


$$y(s) = s + \frac{3s^2+4}{s^3+2s} = s + \frac{1}{\frac{s^3+2s}{3s^2+4}}$$

$$y(s) = 1 + \frac{1}{s^2 + 5s + 4}$$

$$s_1 \rightarrow \frac{1}{3}s + \frac{1}{8}$$

$$s_2 \rightarrow \frac{1}{2}s + \frac{1}{12}$$

$y(s) \rightarrow$

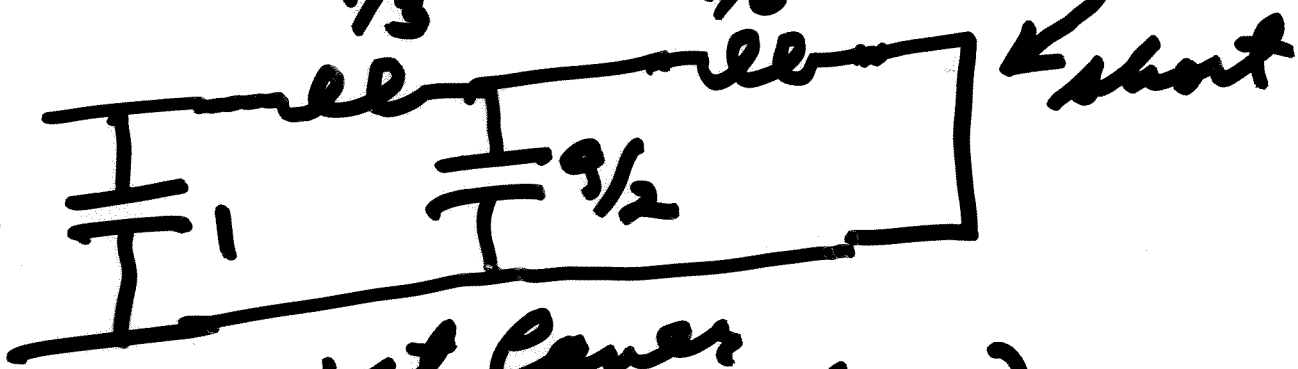

1st Cover
(removes poles at ∞)


2nd Cover - remove poles at zero

$$y(s) = \frac{4 + 5s^2 + s^4}{2s + s^3}$$

$$\begin{array}{r} \frac{4}{2s} \\ \hline 2s + s^3 \sqrt{4 + 5s^2 + s^4} \\ 4 + 2s^2 \\ \hline 3s^2 + s^4 \sqrt{2s + s^3} \\ 2s + \frac{2}{3}s^3 \\ \hline \frac{1}{3}s^3 \sqrt{\frac{1}{3}s^3} \\ \frac{1}{3}s^3 \sqrt{3s^2 + 4} \\ 3s^2 + 4 \\ \hline \frac{1}{3}s^3 \sqrt{\frac{1}{3}s^3} \end{array}$$

$$y(s) = \frac{4}{2s} + \frac{\frac{2}{3s} + \frac{1}{\frac{9}{s} + \frac{1}{\frac{1}{3s+0}}}}$$

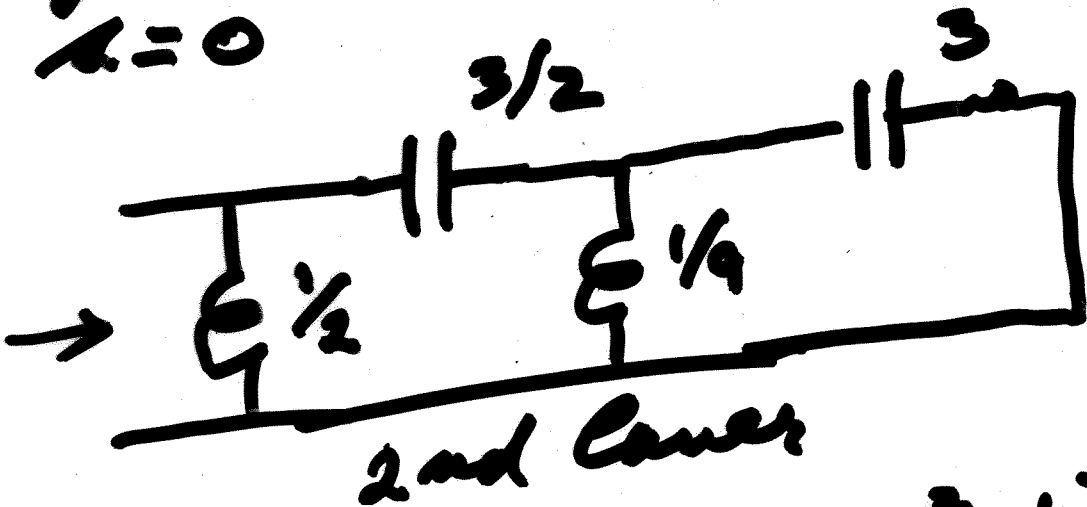a continued fraction expansion about $s=0$



$$y(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+1)}$$


all 4 synthesize this

$$\delta[y] = 4 = \text{degree of } y(s)$$

all are minimal in the number of "reactive" elements

natural frequencies


v.10

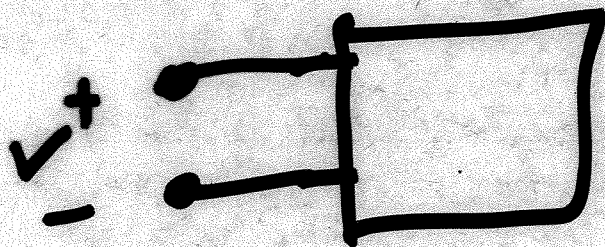

$$V = Z(s) \cdot I \quad \text{if } I = 0 \text{ \& } V \neq 0$$

$$\Rightarrow s \text{ is at a pole of } Z(s)$$

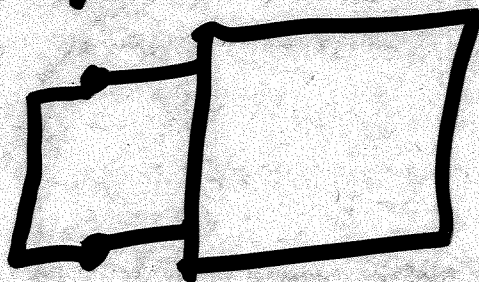
\Rightarrow poles of $Z(s)$ are open circuit ($I=0$) natural frequencies.



$I = Y(s) V \Rightarrow$ if $V = 0, I \neq 0$
 then have $Y(s) \rightarrow \infty$ or
 poles of $Y(s)$ are short
 circuit natural frequencies

EE610 10/07/02 Y.R

O.R. nat. freq. of

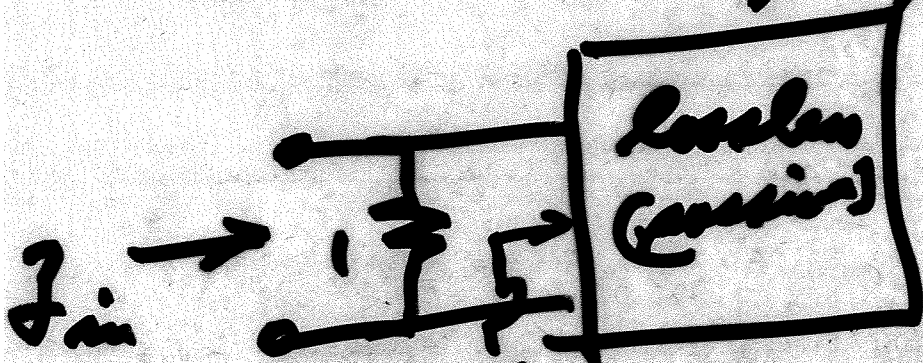

$$\text{desire poles of } Z_{in} = \frac{1}{y_{in}}$$

$$= \frac{1}{1 + y(s)}$$

\therefore O.R. nat. freq. where $y(s) \rightarrow -1$
can't be in RHP if $y(s)$ is P.R.
can't be on $j\omega$ axis if lossless
or $y(j\omega) = jB(\omega)$

\therefore no poles in $s \geq 0$

$$\text{let } y(s) = N/D$$

$Z_{in} = \frac{D}{N+D}$ has $N+D$ as an Hurwitz polynomial