

$$Z = \begin{bmatrix} \frac{1}{c_a} & \frac{1}{c_a} + p \\ \frac{1}{c_a} - p & \frac{1}{c_a} \end{bmatrix} = \begin{bmatrix} k z(k)/a & \frac{k z(k) + z(k)}{a} \\ \frac{k z(k) - z(k)}{a} & \frac{k z(k)}{a} \end{bmatrix} \quad p. 1$$

at $a = k \Rightarrow z_{21}(k) = 0 \Rightarrow$ zero of transmission

$$\text{have } R(a) = \frac{k z(a) - a z(k)}{k z(k) - a z(a)}$$

if $z(k) = -z(-k) \Rightarrow$
 (a) $a = -k$ also get a cancellation

$$R(-k) = \frac{kz(-k) - (-k)z(k)}{kz(k) - (-k)z(-k)} = \frac{-kz(k) + kz(k)}{kz(k) - kz(k)}$$

$$z(k) = -z(-k)$$

$\therefore a = -k$ will also cancel

if $z(k) + z(-k) = 0 \Rightarrow$ if a is a zero of the even part of $z(a)$

By def: $\text{Ev } z(a) = \frac{1}{2}(z(a) + z(-a))$ or $\text{Ev}(z(a)) = \text{Ev}(z(-a))$

$$\text{Od } z(a) = \frac{1}{2}(z(a) - z(-a))$$

$$z(a) = \text{Ev } z + \text{Od } z$$

Exp: $z(s) = \frac{3s+1}{s+2}$ let $k=2; z(k) = 7/4$

$$z_L = V.R(s) = z(k) \cdot \frac{kz(s) - sz(k)}{kz(k) - sz(s)} = \frac{\frac{7}{4} \left(2 \left(\frac{3s+1}{s+2} \right) - s \cdot \frac{7}{4} \right)}{\frac{7}{2} - s(3s+1)}$$

$$= \frac{7}{4} \left(\frac{6s+2 - \frac{7}{4}s^2 - \frac{7}{2}s}{\frac{7}{2} - 3s^2 - s} \right) = \frac{7}{8} \left(\frac{-7s^2 + 10s + 8}{-6s^2 + 5s + 14} \right)$$

$$\begin{array}{r} \underline{s-2} \quad \begin{array}{r} -7s-4 \\ -7s^2+10s+8 \\ -7s^2+14s \end{array} \end{array} = \frac{7}{8} \left(\frac{(s-2)(-7s-4)}{(s-2)(-6s-7)} \right)$$


$$\begin{array}{r} \underline{s-2} \quad \begin{array}{r} -6s-7-4s \\ -6s^2+5s+14 \\ -6s^2+12s \end{array} \end{array}$$

$$= \frac{7}{8} \left(\frac{7s+4}{6s+7} \right); \delta[z_L] = \delta[z] = 1$$

$\delta[\cdot] = \text{degree}$

EE 610, 09/08/03

P. 4

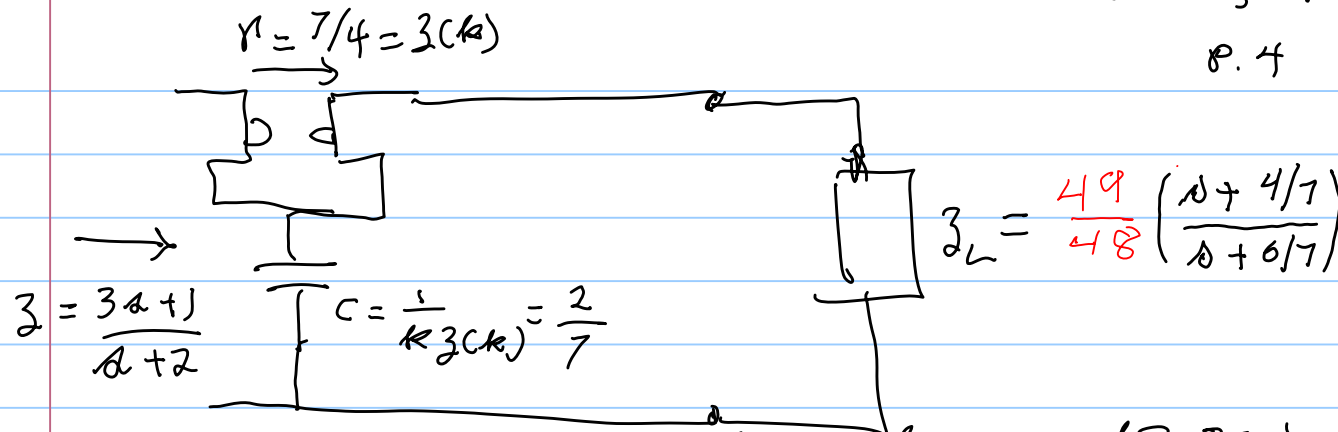

look for a better k : desire $k = \text{zero of } \mathcal{E}_v z(s)$

$$2 \mathcal{E}_v z(s) = z(s) + z(-s) = \frac{3s+1}{s+2} + \frac{-3s+1}{-s+2}$$

$$\Rightarrow \frac{2}{3} \mathcal{E}_v z(s) = \frac{(s+1/3)(-s+2) + (-s+1/3)(s+2)}{(s+2)(-s+2)} = \frac{-2s^2 + 4/3}{D(s)D(-s)}$$

where $D(s) = s+2$

$$\Rightarrow -s^2 + 2/3 \Rightarrow s^2 - 2/3 = 0$$

$$s_{\text{zero}} = \pm \sqrt{2/3} \Rightarrow k = \sqrt{2/3}$$


EE610, 09/08/03
P.5

$$Z(s) = \frac{3s+1}{s+2} \quad ; \quad k = \sqrt{2/3} \quad ; \quad Z(s) = \frac{\sqrt{6}+1}{2+\sqrt{2/3}} = \sqrt{\frac{3}{2}}$$

$$R = \frac{\sqrt{2/3} \cdot \frac{3s+1}{s+2} - s \sqrt{3/2}}{\sqrt{2/3} \cdot \sqrt{3/2} - s \left(\frac{3s+1}{s+2} \right)} = \text{constant as } (s - \sqrt{2/3})(s + \sqrt{2/3}) = s^2 - 2/3$$

will cancel
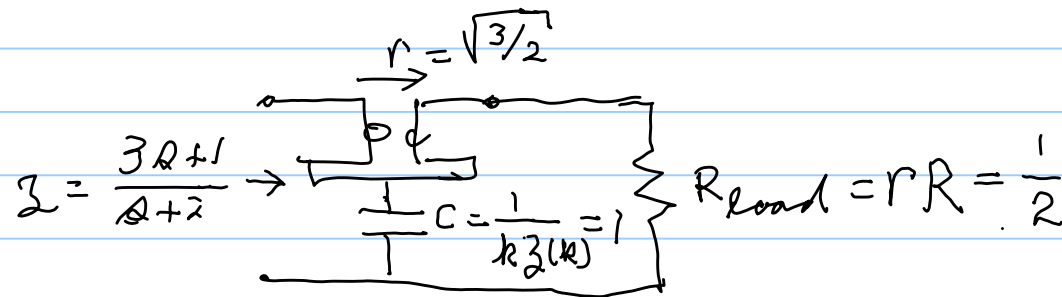
$$= \frac{-\sqrt{3/2} (s^2 - 2/3)}{-3(s^2 - 2/3)} = \frac{1}{\sqrt{6}}$$



EE 610, 09/08/03

P. 6

Lossless circuits - p. 342 (LC = reactance)

$P_{ave}(\omega) |_{\omega = j\omega} = 0 \Rightarrow P_{ave} = \text{average power}$

$$= \operatorname{Re} V^{T*} I = \frac{V^{T*} I + I^{T*} V}{2}$$

assume $Z(j\omega)$ exists; $V = ZI$

$$\begin{aligned} 2 P_{ave}(\omega) &= I^{T*} Z^{T*}(j\omega) I + I^{T*} Z(j\omega) I \\ &= I^{T*} [Z^{T*}(j\omega) + Z(j\omega)] I \end{aligned}$$

lossless $\Rightarrow Z(j\omega) + Z^{T*}(j\omega) = 0_{m \times m}$ if V & I are n -vectors

