

State variable equations - chapter 5 p.1

$$\dot{x} = Ax + Bu$$


$x = \text{state (vector)}$

$$y = Cx + Du$$

A, B, C, D constant
matrices

$u = \text{input}, y = \text{output}$

$x \rightarrow$ inductor currents, capacitor voltages

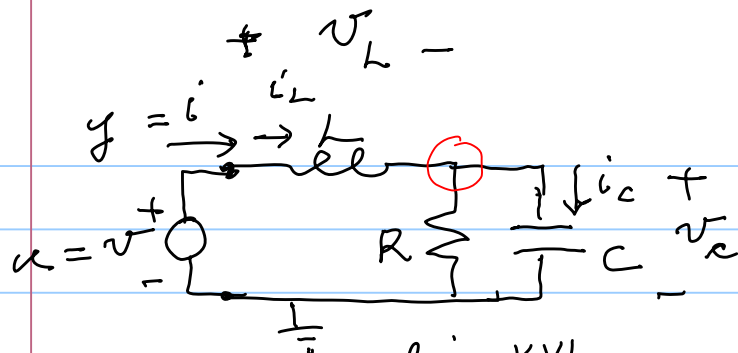

EE610
09/22/03 v.2

$$v_L = L \frac{di_L}{dt} \stackrel{\text{KVL}}{=} v - v_C \Rightarrow \frac{di_L}{dt} = -\frac{1}{L} v_C + \frac{1}{L} v$$

$$i_C = C \frac{dv_C}{dt} \stackrel{\text{KCL}}{=} i_L + (-\frac{1}{R} v_C) \Rightarrow \frac{dv_C}{dt} = -\frac{1}{RC} v_C + \frac{1}{C} i_L$$


$$x = \begin{bmatrix} i_L \\ v_C \end{bmatrix}; \quad \frac{dx}{dt} = \begin{bmatrix} di_L/dt \\ dv_C/dt \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \begin{bmatrix} v \end{bmatrix}$$

$$y = [i] = [i_L] = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$y = i_L = i, \quad u = v$$

EE610
09/22/03 p.3


Indefinite admittance matrix, (s domain)

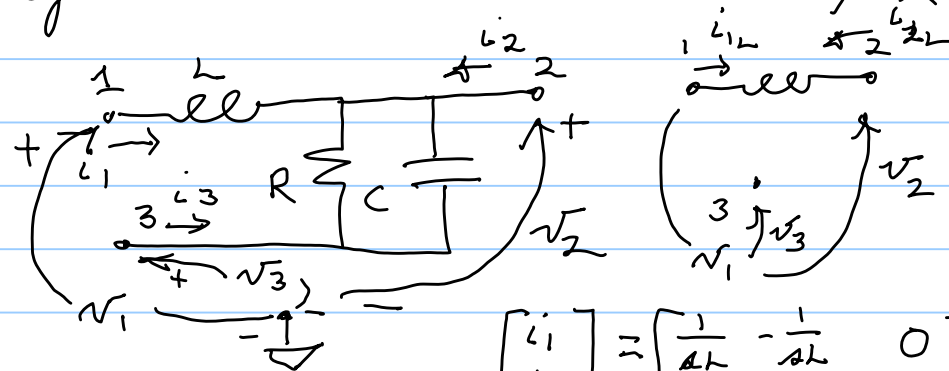


$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} \frac{1}{sL} & -\frac{1}{sL} & 0 \\ -\frac{1}{sL} & \frac{1}{sL} & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

EE610

09/22/03
p.4

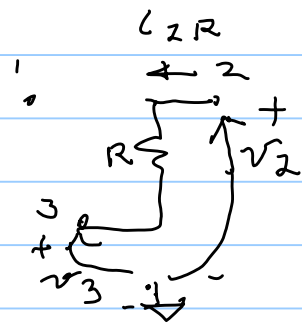
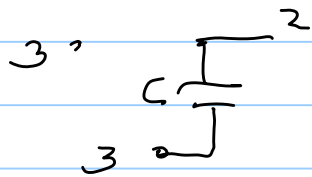
$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_R = \begin{bmatrix} 0 & 0 & 0 \\ 0 & \frac{1}{R} & -\frac{1}{R} \\ 0 & -\frac{1}{R} & \frac{1}{R} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$



$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_C = \begin{bmatrix} 0 & 0 & 0 \\ 0 & sC & -sC \\ 0 & -sC & sC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

indefinite admittance

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_L + \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_R + \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}_C = \begin{bmatrix} \frac{1}{2R} & -\frac{1}{2R} & 0 \\ -\frac{1}{2R} & \frac{1}{2R} + \frac{1}{R} + sC & -\frac{1}{R} - sC \\ 0 & -\frac{1}{R} - sC & \frac{1}{R} + sC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

EE610
09/22/03
p.5

move ground to circuit $\Rightarrow v_3 = 0$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{sL} & -\frac{1}{sL} \\ -\frac{1}{sL} & \frac{1}{sL} + \frac{1}{R} + sC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad \text{ignore } i_3$$

for input admittance set $i_2 = 0$ and eliminate v_2 (= internal node elimination)

$$\frac{1}{sL} v_1 = \left[\frac{1}{sL} + \frac{1}{R} + sC \right] v_2 \Rightarrow v_2 = \frac{1}{sL} \cdot \frac{1}{\frac{1}{sL} + \frac{1}{R} + sC} \cdot v_1$$

$$i_1 = \left[\frac{1}{sL} - \frac{1}{sL} \cdot \frac{1}{sL} \cdot \frac{1}{\frac{1}{sL} + \frac{1}{R} + sC} \right] v_1 = Y_{in}(s) \cdot v_1$$

$$= \left[\frac{\cancel{\frac{1}{sL}} \cdot \cancel{\frac{1}{sL}} + \frac{1}{sL} \cdot \frac{1}{R} + \frac{sC}{sL} - \cancel{\frac{1}{sL}} \cdot \cancel{\frac{1}{sL}} \right] v_1 = \frac{\frac{1}{R} + sC}{s^2 LC + \frac{L}{R} s + 1} v_1$$

EE610
09/22/03 p.6

$$Y_{in}(s) = \frac{C}{LC} \left(\frac{s + 1/RC}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \right)$$

$$s^2 + \frac{\omega_0}{Q}s + \omega_0^2 = s^2 + 2\zeta\omega_n s + \omega_n^2; \quad \omega_0 = \omega_n = \frac{1}{\sqrt{LC}}$$

$$\frac{\omega_0}{Q} = \frac{1}{RC} \Rightarrow Q = \omega_0 RC = R\sqrt{\frac{C}{L}}$$

$$\text{poles are at } s_{1,2} = \frac{-\omega_0}{2Q} \pm \frac{1}{2} \sqrt{\left(\frac{\omega_0}{Q}\right)^2 - 4\omega_0^2} = \frac{\omega_0}{2Q} \left[-1 \pm \sqrt{1 - 4Q^2} \right]$$