
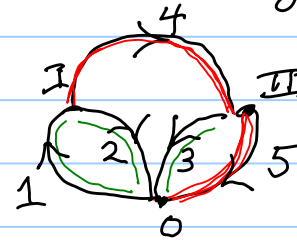



p. 1

Graph theory for circuit analysis

Chapter 3, p. 91

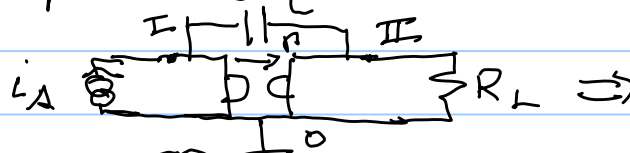

- = tree
- = cotree
- = limbs
- = links

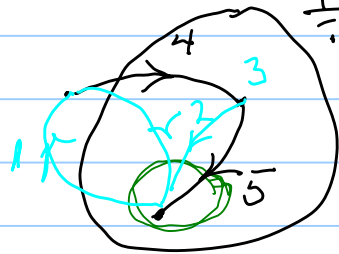

sphere 1

cut set 1 = branches 1, 2, 4

cut set 2 = branches 1, 2, 3, 5

generic branch $\begin{cases} i_a \\ a \end{cases} \begin{matrix} + \\ \downarrow \\ v_a \\ - \end{matrix} \Rightarrow i_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}_b, v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}_b$

EE610
09/29/03
p.2

KCL: at node 1: $0 = -i_1 + i_2 + i_4$
 at node 2: $0 = -i_1 + i_2 + i_3 + i_5 \Rightarrow 0 = C i_b$

$t = \# \text{ of tree branches} = 2$, $n = \# \text{ of nodes} = 3$
 $b = \# \text{ of branches} = 5$, $C = \text{cut set matrix} = t \times b$

$$C = \left[\dots \mid \mathbf{1}_t \right] \Rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \underbrace{\begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 1 \end{bmatrix}}_{\substack{K \\ t \times t}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}}_{\substack{I_2 \\ b}}$$

cut set equations:

KVL: 4

loop 1	$0 = v_1 + v_4 + v_5$
loop 2	$0 = v_2 - v_4 - v_5$
loop 3	$0 = v_3 - v_5$



ΣΣ 610
09/29/03
p.3

$l = \# \text{ of links} = 3$ $\mathcal{O}_l = \mathcal{J} \cdot \mathbf{v}_b$; $\mathcal{J} = \text{the set matrix}$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}_b ; \quad \mathcal{J} = \begin{bmatrix} 1_l & \dots \end{bmatrix}_{l \times b}$$

$$\mathcal{C} = \begin{bmatrix} K \\ \vdots \\ 1_t \end{bmatrix}, \quad \mathcal{J} = \begin{bmatrix} 1_l & -K^T \end{bmatrix}$$


$$\Rightarrow \mathcal{C} \mathcal{J}^T = \begin{bmatrix} K \\ \vdots \\ 1_t \end{bmatrix}_{t \times l} \begin{bmatrix} 1_l \\ \dots \\ -K \end{bmatrix}_{l \times t} = \begin{bmatrix} K - K \end{bmatrix} = \mathbf{0}_{t \times l}$$

$$\mathcal{O}_l = \mathbf{v}_l - K^T \mathbf{v}_t \Rightarrow \mathbf{v}_b = \begin{bmatrix} \mathbf{v}_l \\ \mathbf{v}_t \end{bmatrix} = \begin{bmatrix} K^T \\ 1_t \end{bmatrix} \mathbf{v}_t = \mathcal{C}^T \mathbf{v}_t$$

Laws of connection are KVL & KCL


$$v_b = C^T v_t, \quad i_b = D^T i_t$$

Laws of elements:

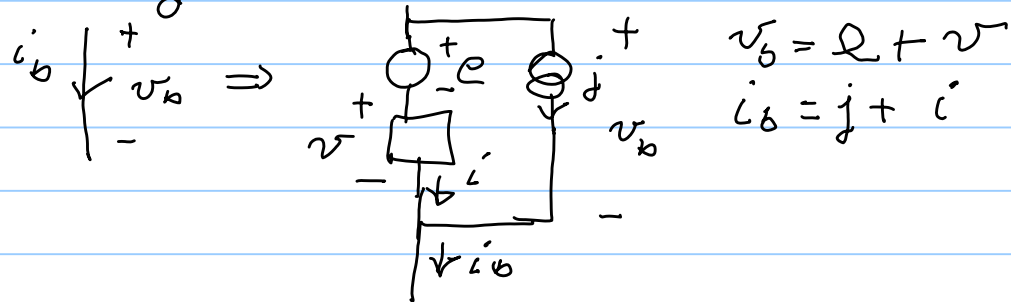

ΣΣ610
09/29/03
p.4

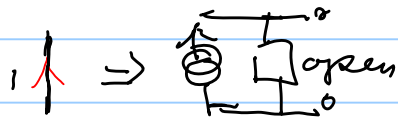i versus v laws: assume every branch is part of an admittance matrix



admittance of v , via i , $\Rightarrow i_i = 0 \cdot v_i$

EE610
09/29/03
p. 5

$$\begin{array}{c} H \\ \downarrow \\ \uparrow \\ H \end{array} = \frac{1}{C} \quad , \quad \begin{array}{c} H \\ \downarrow \\ 0 \\ \uparrow \\ 0 \end{array} \quad z = \frac{1}{R_L}$$

$$\begin{array}{c} \downarrow \\ 2 \\ \downarrow \\ 3 \end{array} \quad Y = \begin{bmatrix} 0 & \frac{1}{r} \\ \frac{1}{r} & 0 \end{bmatrix} \quad \text{all other entries zero}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ \frac{1}{R_L} \\ 0 \end{bmatrix} \quad \Rightarrow \quad i = Y v \quad \begin{matrix} 6 \times 6 \\ 5\text{-vector} \end{matrix}$$

$$e = 0 \quad \leftarrow \text{corrected}$$

$$i = \begin{bmatrix} i_1 \\ i_2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned}
 v_6 &= v \\
 i_6 &= i + c = i + Y_{6 \times 6} v \\
 &= i + Y_{6 \times 6} v_6 = i + Y_{6 \times 6} P^T v
 \end{aligned}$$

also $0_t = e i_b \Rightarrow \begin{matrix} \uparrow \\ e i_b = e_j + e Y_{b \times b} e^T v_t \end{matrix}$ EE610
09/29/03

$-e_j = e Y_{b \times b} e^T \cdot v_t \Rightarrow t \text{ equations in } t \text{ unknowns}$ p6

added material

$$-e_j = - \begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} +i_1 \\ +i_1 \end{bmatrix}$$

$$e Y_{b \times b} e^T = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & -g & & & \\ g & 0 & & & \\ & & \Delta c & & \\ & & & G_L & \\ & & & & \end{bmatrix} \begin{bmatrix} -1 & -1 \\ 1 & 1 \\ 0 & 1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{matrix} j \quad g = 1/r \\ G_L = 1/R_L \end{matrix}$$

$$= \begin{bmatrix} 0 & 0 & -g & \alpha C & 0 \\ 0 & g & -g & 0 & G_L \end{bmatrix} \begin{bmatrix} -1 & -1 \\ 1 & 1 \\ 0 & 1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} \alpha C & -g \\ g & G_L \end{bmatrix} \quad \begin{array}{l} \text{added} \\ \text{p. 7} \\ 09/30/03 \end{array}$$

$$\therefore \begin{bmatrix} i_A \\ i_A \end{bmatrix} = \begin{bmatrix} \alpha C & -g \\ g & G_L \end{bmatrix} \begin{bmatrix} v_4 \\ v_5 \end{bmatrix} ; \left\{ \begin{array}{l} \text{if desire input} \\ \text{I need } v_{in} = -v_1 \\ \text{by } v_6 = C^T v_4 \\ v_{in} = -v_1 = -[-1 \ -1] \begin{bmatrix} v_4 \\ v_5 \end{bmatrix} \\ = v_4 + v_5 \\ = \frac{\alpha C + G_L}{\alpha C G_L + g^2} i_A = 2 i_A \end{array} \right.$$

solving

$$\begin{bmatrix} v_4 \\ v_5 \end{bmatrix} = \frac{1}{\alpha C G_L + g^2} \begin{bmatrix} G_L & g \\ -g & \alpha C \end{bmatrix} \begin{bmatrix} i_A \\ i_A \end{bmatrix} \\ = \frac{i_A}{\alpha C G_L + g^2} \begin{bmatrix} G_L + g \\ \alpha C - g \end{bmatrix}$$