
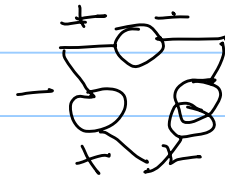


$$P_{in}(t) = v_b^T i_b(t)$$

if finite  $= 0$

$$v_b = C^T v_t, \quad i_b = J^T i_l$$

$$P_{in} = 0 = v_t^T C \cdot J^T i_l$$

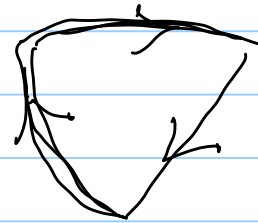


choose  $v_t$  freely by assuming there are voltage sources in the tree & the same for current sources in the links

$$\Rightarrow \quad 0 = C J^T$$

$t \times l$

Tellegen's Theorem, p. 118 is  $v_B^T \hat{L}_B = 0$  p.2  
for the same graph  
but different circuit elements

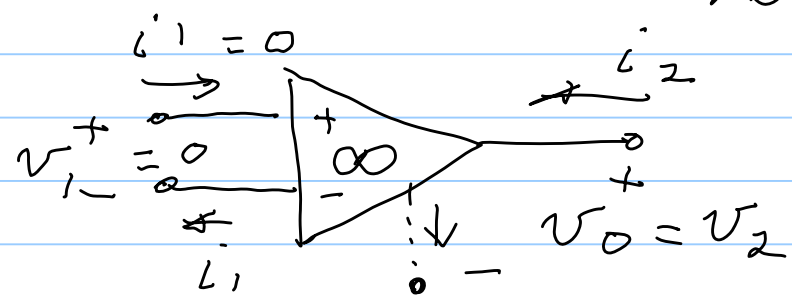circuit without  $Y_{b \times b}$ : ones with <sup>ideal</sup> op-amps





$$\begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

no  $Y$  or  $Z$  matrix  
if "linear"

$$A v = B i \Rightarrow i = Y v$$

$$Y = B^{-1} A$$

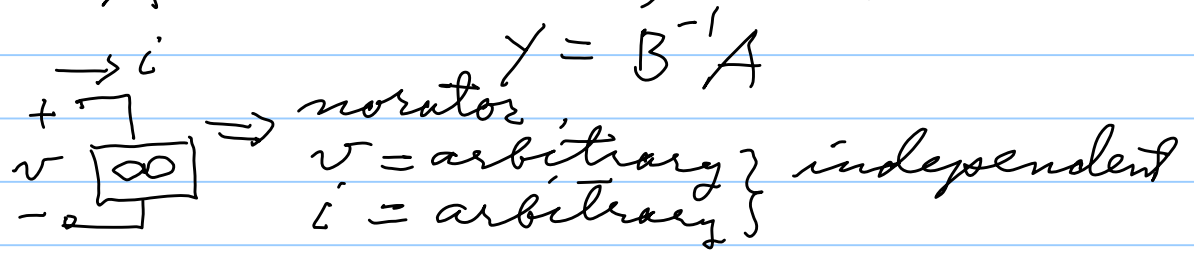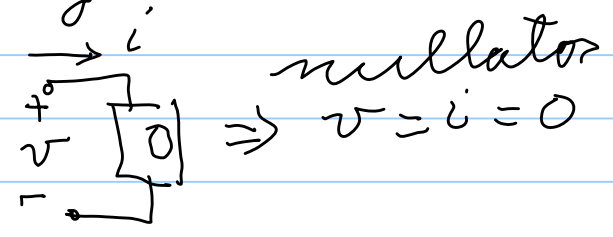

} independent

EE610  
10/01/03  
p.3

$$\begin{bmatrix} 0 \end{bmatrix} \begin{bmatrix} v \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix} \begin{bmatrix} i \end{bmatrix} \Leftarrow \text{no ratos}$$

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} \begin{bmatrix} v \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \begin{bmatrix} i \end{bmatrix} \Leftarrow \text{nullator}$$

----- general theory

$$v_b = e^T v_z \quad i_b = j^T i_\ell \quad v_b = e + v$$

$$i_b = j + i$$

$$A v = B i$$

or

$$A v_b = A e + A v \Rightarrow A v = A v_b - A e = B i = B i_b - B j$$

$$B i_b = B j + B i$$

or


$$A e^T v_z - B j^T i_\ell = A e - B j$$

$$\begin{bmatrix} A e^T & \vdots & -B j^T \end{bmatrix} \begin{bmatrix} v_z \\ \vdots \\ i_\ell \end{bmatrix} = \begin{bmatrix} A & -B \end{bmatrix} \begin{bmatrix} e \\ j \end{bmatrix}$$

as  $b = t + l$   $[v_t, i_l]^T$  is a  $b$ -vector  
 $\Rightarrow$   $b$  unknowns; if  $A$  &  $B$  square have  
 $b$  equations

if  $b$   $\left\{ \begin{array}{c} \underbrace{[A \ C]^T}_{t} \ ; \ \underbrace{[-B \ J]^T}_{l} \end{array} \right\}$  is nonsingular we can  
 solve the circuit  $\Rightarrow$  know  
 $v_t, i_l$ ;  $v_b = C^T v_t$ ,  $i_b = J^T i_l$   
 $b = t + l$

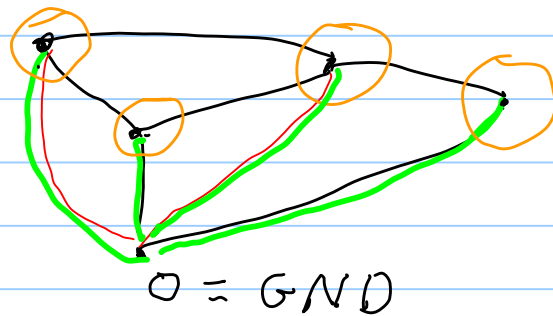For "nodal" analysis take a tree  
 where all of  $v_t$  are voltages of the  
 nodes with respect to ground



fictitious branches are  
 open circuits. Use  
 "nodal analysis"