

Semistate Equations

$$E \dot{x} = Ax + Bu$$

$$y = Cx$$

$$\text{ex } \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} x + \begin{bmatrix} 1 \\ 1 \end{bmatrix} u$$

$$y = \begin{bmatrix} \quad \quad \quad \end{bmatrix} x$$

$$\left\{ \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \right\} X(s) = \begin{bmatrix} 1 \\ 1 \end{bmatrix} U(s)$$

"

$$\begin{bmatrix} -1 & a \\ 0 & -1 \end{bmatrix}^{-1} = \frac{1}{1} \begin{bmatrix} -1 & -a \\ 0 & -1 \end{bmatrix}$$

EE610
10/20/03

$$X(a) = \begin{bmatrix} -1 & -a \\ 0 & -1 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} U(a) = \begin{bmatrix} -1 - a \\ -1 \end{bmatrix} U$$

P.2

$$\begin{aligned} Y(a) &= \begin{bmatrix} -1 & +1 \end{bmatrix} X(a) = a U(a) \\ &= \begin{bmatrix} -1 & +1 \end{bmatrix} \begin{bmatrix} -(1+a) \\ -1 \end{bmatrix} U(a) = [a] U(a) \end{aligned}$$

\therefore

$$\begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} \dot{x} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} x + \begin{bmatrix} 1 \\ 1 \end{bmatrix} u$$

$$y = \begin{bmatrix} -1 & 1 \end{bmatrix} x \quad \Rightarrow \text{differentiator}$$


$$\frac{Y(a)}{U(a)} = a$$

EE610
10/20/03

More general case (nonlinear & time-varying) $\dot{x} = A(x, t) + Bu$
 $y = Cx$

P.3

Toward the scattering matrix
look at a lossless transmission line

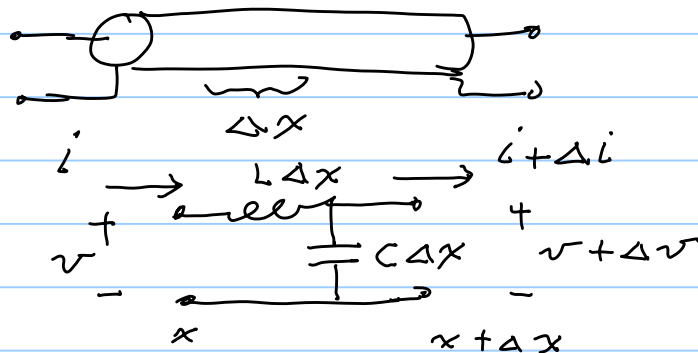

EE610
10/20/03
P. 4

$$v - (v + \Delta v) \approx \Delta x \frac{di'}{dt} \Rightarrow -\frac{\Delta v}{\Delta x} = \Delta \frac{di'}{dt}$$

$$i - (i + \Delta i) = c \Delta x \left(\frac{d(v + \Delta v)}{dt} \right) \Rightarrow -\frac{\Delta i}{\Delta x} = c \frac{dv}{dt} + \frac{d\Delta v}{dt}$$

$$\lim_{\Delta x \rightarrow 0} : \frac{dv}{dx} = -\Delta \frac{di'}{dt}, \quad \frac{di'}{dx} = -c \frac{dv}{dt}$$

$$\begin{aligned} v(t, x) &= v^i(t - \frac{x}{v}) + v^r(t + \frac{x}{v}) \\ \text{2.0 } i(t, x) &= v^i(t - \frac{x}{v}) - v^r(t + \frac{x}{v}) \end{aligned} \left. \begin{array}{l} \text{assume} \\ \text{then} \end{array} \right\}$$


$$\frac{dv}{dx} = -\frac{1}{v} \dot{v}^i(t - \frac{x}{v}) + \frac{1}{v} \dot{v}^r(t + \frac{x}{v}) =$$


$$\text{3.0 } \frac{di}{dt} = \dot{v}^i(t - \frac{x}{v}) - \dot{v}^r(t + \frac{x}{v}) = -v \frac{dv}{dx}$$

EE610
10/20/03 p.5

$$\frac{dv}{dx} = -\frac{Z_0}{v} \frac{di}{dt} \quad ; \quad Z_0 = \sqrt{RL \cdot \frac{1}{c}} \quad ; \quad v = \frac{1}{\sqrt{LC}}$$
$$\frac{Z_0}{v} = \sqrt{\frac{L}{C}} \cdot \sqrt{LC} = L$$

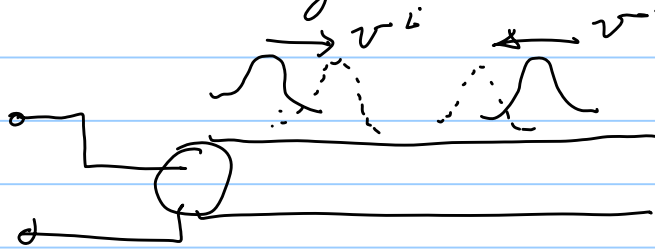\therefore the solution assumed
is valid (after check dL/dx eq.)



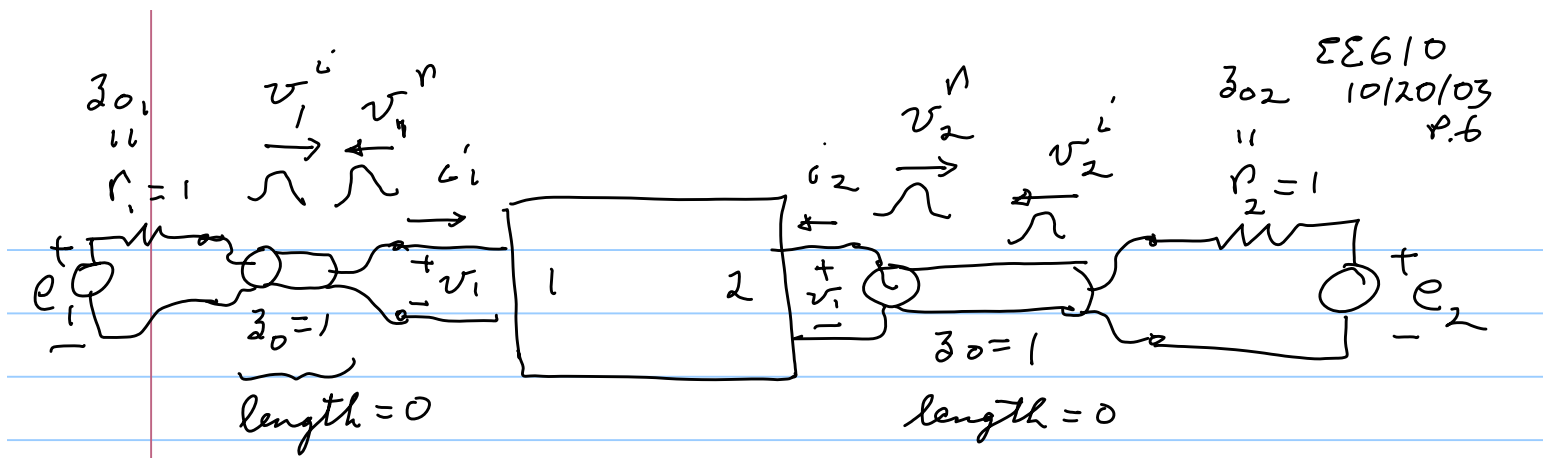

$$\begin{aligned}
 v_1 &= v_1^i + v_1^n & ; & & v_2 &= v_2^i + v_2^n \\
 Z_0 i_1 = i_1 &= v_1^i - v_1^n & & & i_2 &= v_2^i - v_2^n \\
 v &= v^i + v^n & & & & \\
 \left. \begin{aligned} \Gamma_1 &= 0 \\ \Gamma_2 &= 0 \end{aligned} \right\} i = Z_0 i = v^i - v^n & & & & \left. \begin{aligned} 2v^i &= v + Z_0 i \\ 2v^n &= v - Z_0 i \end{aligned} \right\}
 \end{aligned}$$

$S(\omega) = \text{scattering matrix } V^n = S V^i$



EE610
10/20/03

p. 7

$$S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \Rightarrow S_{21} = \frac{V_2^n}{V_1^i} \Big|_{V_2^i = 0} =$$

$$2V_2^i = V_2 + Z_0 I_2 = 0 \Rightarrow V_2 = -Z_0 I_2$$

$$= E_2 = 0$$

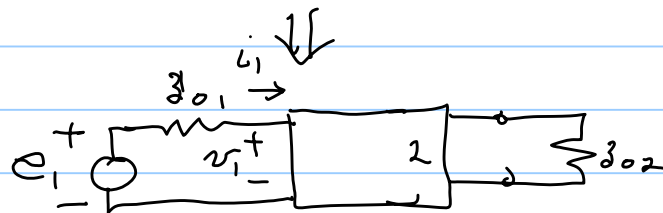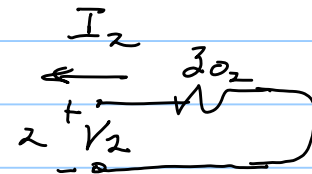

$$2V_1^i = V_1 + Z_{01} I_1 = E_1$$

$$2V_2^n = V_2 - Z_{02} I_2 = 2V_2$$

$$S_{21} = \frac{V_2}{E_1/2} = 2 \frac{V_2}{E_1} \Rightarrow \text{a voltage gain of a terminated 2-port}$$

what does $S_{11} = 0$ mean? nothing out

EE610
10/20/03

in comes back at you.

p.8


$$S_{11} = \left. \frac{V_1^r}{V_1^i} \right|_{V_2^i = 0}$$

$$V_2^i = 0 \Rightarrow E_2 = 0$$

$$2V_1^r = V_1 - Z_0 I_1$$

$$\therefore \text{if } V_1^i = E_1/2 \neq 0 \Rightarrow V_1^r = 0 \Rightarrow V_1 = Z_0 I_1$$

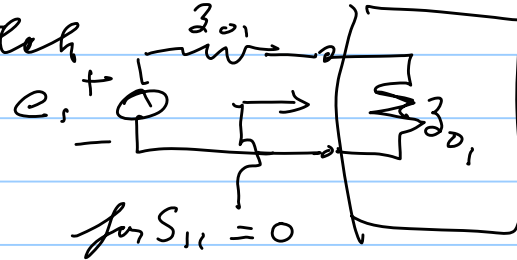that is the input looks like a resistor
of value Z_0 , i.e. a match



Power relations:

$$P_{ave}(\omega) = \operatorname{Re}(V^{T*} I) = \frac{V^{T*} I + I^{T*} V}{2}$$

EE610
10/20/03

$$V = V^i + V^r$$

$$I = V^i - V^r \quad \text{if } Z_0 = \text{identity}$$

10.9

$$2P_{\text{ave}}(\omega) = (V^{i T*} + V^{r T*})(V^i - V^r) + (V^{i* T} - V^{r* T})(V^i + V^r)$$

$$= 2V^{i T*} V^i - 2V^{r T*} V^r$$

$$P_{\text{ave}} = V^{i T*} V^i - V^{r T*} S^T S V^i = V^{i T*} \begin{bmatrix} 1 & \\ & -S^T S \end{bmatrix} V^i$$

$S \rightarrow$ Bounded real if passive.