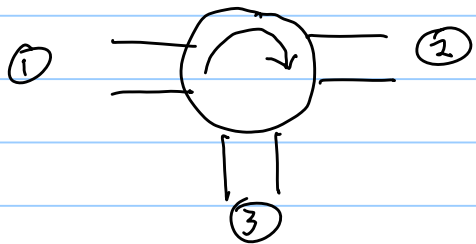


circulator - 3 port

v. 1





$$S = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}; \quad V^n = S V^i$$


$$S^T S = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \mathbf{I}_3$$

lossless

Pr. 2  
 EE610  
 11/03/03

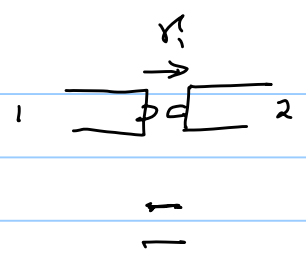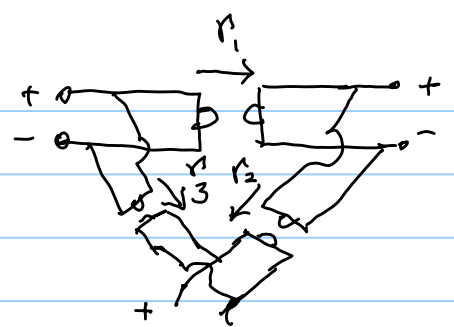
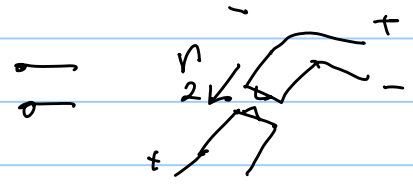
$$Y_1 = \begin{bmatrix} 0 & -g_1 & 0 \\ g_1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$



$$Y_2 = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & -g_2 \\ 0 & g_2 & 0 \end{bmatrix}$$



$$Y_3 = \begin{bmatrix} 0 & 0 & -g_3 \\ 0 & 0 & 0 \\ g_3 & 0 & 0 \end{bmatrix}$$

P.3  
EE610  
11/03/03


$$S = (\mathbf{1}_3 + Y)^{-1} (\mathbf{1}_3 - Y); \quad Y = Y_1 + Y_2 + Y_3 = \begin{bmatrix} 0 & -g_1 & -g_3 \\ g_1 & 0 & -g_2 \\ g_3 & g_2 & 0 \end{bmatrix}$$

$$S = \frac{1}{1 + g_1^2 + g_2^2 + g_3^2} \begin{bmatrix} 1 + g_2^2 - g_1^2 - g_3^2 & 2g_1(1 - g_2g_3) & 2g_3(1 + \frac{g_1g_2}{g_3}) \\ -2g_1(1 + \frac{g_2g_3}{g_1}) & 1 - g_1^2 - g_2^2 + g_3^2 & 2g_2(1 - \frac{g_1g_3}{g_2}) \\ -2g_3(1 - \frac{g_1g_2}{g_3}) & -2g_2(1 + \frac{g_1g_3}{g_2}) & 1 + g_1^2 - g_2^2 - g_3^2 \end{bmatrix}$$

set  $g_1 = g_2 = -1, g_3 = 1$

$$S = \frac{1}{4} \begin{bmatrix} 0 & 0 & 4 \\ 4 & 0 & 0 \\ 0 & 4 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

EE610  
11/03/03  
p.4

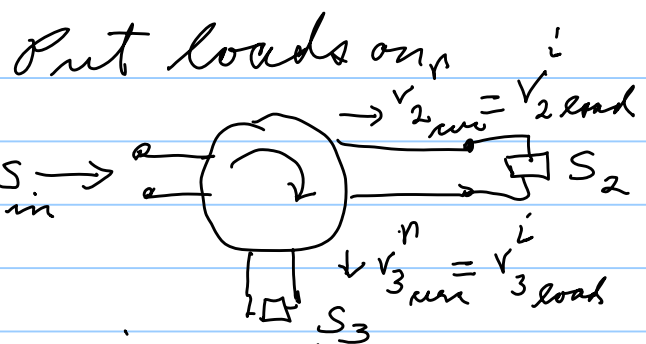

$$S_{in} \Rightarrow V_1^r = S_{in} V_1^i$$

$$V_1^r = V_3^i ; V_3^r = V_2^i \text{ for circulator}$$

$$V_3^i = V_3^r = V_3^{\text{load}}$$

$$V_1^r = V_3^i = S_3 V_3^r = S_3 V_3^{\text{load}}$$

$$= S_3 V_2^i = S_3 V_2^r = S_3 V_2^{\text{load}}$$

$$= S_3 \cdot S_2 \cdot V_1^i \Rightarrow S_{in} = S_3 \cdot S_2$$

$$V_3^r = V_3^i = S_3 V_3^{\text{load}} = S_3 V_3^r$$


$$V_2^{\text{load}} = S_2 V_2^{\text{load}} = S_2 V_2^r$$

$$= S_2 V_1^i \text{ (def of circulator)}$$

EE 610  
11/03/03  
v.5

as circulator is passive, if the two loads are passive so is the circuit  $\Rightarrow$  product of bounded real functions,  $S_2, S_3$ , is <sup>sim</sup> bounded real (not true for positive real functions).

can do with one gyrator:

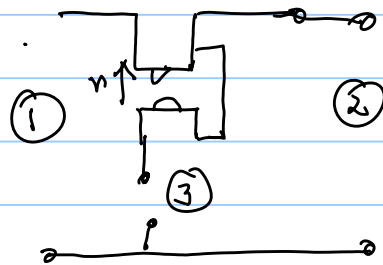


$$S = \frac{1}{3+r^2} \begin{bmatrix} r^2-1 & 2-2r & 2+2r \\ 2+2r & r^2-1 & 2-2r \\ 2-2r & 2+2r & r^2-1 \end{bmatrix}$$

$$\text{if } r=1 \quad S = \frac{1}{4} \begin{bmatrix} 0 & 0 & 4 \\ 4 & 0 & 0 \\ 0 & 4 & 0 \end{bmatrix}$$

resistor

EE610  
11/03/03  
p.6

nullator &  $v_1$

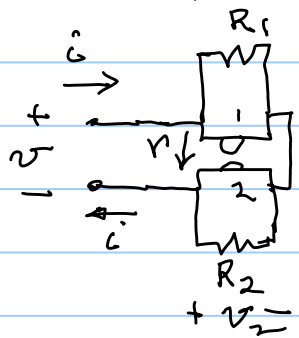

$$v = v_1 - v_2$$

$$i = G_1 v_1 + i_{g_1} = -G_2 v_2 - i_{g_2}$$

$$v_1 = r i_{g_2} ; v_2 = -r i_{g_1}$$

$$\Rightarrow v = r (i_{g_2} + i_{g_1})$$

$$i = G_1 r i_{g_2} + i_{g_1} = +G_2 r i_{g_1} - i_{g_2}$$

$$(G_1 r + 1) i_{g_2} = (G_2 r - 1) i_{g_1}$$

if  $i_{g_2} = -i_{g_1} \Rightarrow v = 0$  &  $0 = [(G_1 r + 1) + (G_2 r - 1)] i_{g_1}$   
 $= r (G_1 + G_2) i_{g_1}$

if also  $G_1 \neq -G_2 \Rightarrow i_{g_1} = 0 = -i_{g_2} = 0 \Rightarrow v_1 = v_2 = 0$   
 $\Rightarrow i = 0, v = 0$  can also guarantee by  $G_1 r + 1 = 0$

Then  $G_1 = -\frac{1}{r}$  ;  $G_2 = -G_1 \Rightarrow$  nullator

EE610  
11/03/03  
r.7

if  $i_{q_2} = i_{q_1} \Rightarrow v = 2r i_{q_1}$   
 $i = (1+G_1)r i_{q_1} \Rightarrow$  allows  $i_{q_1}$  doesn't get anywhere



$G_1 r + 1 = 0, G_2 r - 1 = 0 \Rightarrow i_{q_1} \& i_{q_2}$  can be anything



$\Rightarrow i =$  arbitrary

$v =$  arbitrary independent of  $i$

$\Rightarrow$  norator

$i =$  free  $i =$  arb

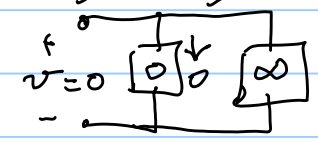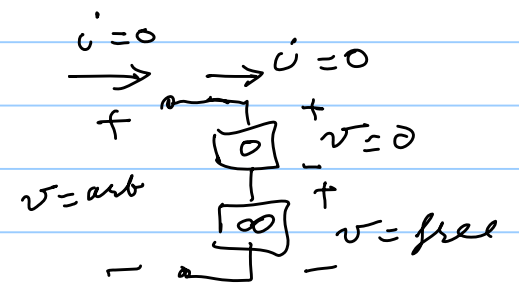

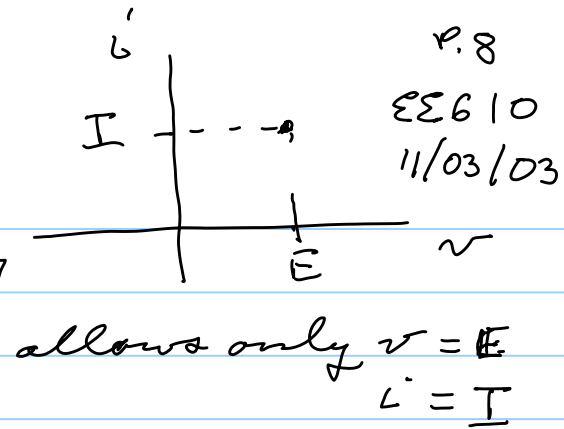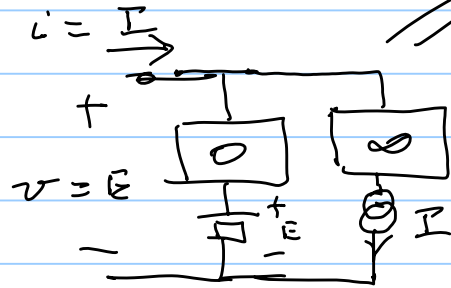

Bilateral Laplace transform  $f(t)$

$$\mathcal{L}[f] = \int_{-\infty}^{\infty} f(t) e^{-\alpha t} dt = \langle f(t), e^{-\alpha t} \rangle_t$$

$$\text{if } f(t) = \delta(t) = \langle \delta, e^{-\alpha t} \rangle_t = e^{-\alpha \cdot 0} = 1$$



EE610  
11/03/03  
r.9

$$\text{for } e^{at} \mathcal{L}\{-t\} \Rightarrow \int_{-\infty}^{\infty} e^{at} e^{-st} \mathcal{L}\{-t\} dt$$

$$= \int_{-\infty}^0 e^{(a-s)t} dt = \frac{1}{a-s} e^{(a-s)t} \Big|_{-\infty}^0$$

$$= \frac{1}{a-s} - \frac{1}{a-s} e^{(a-s)t} \Big|_{-\infty}$$

needs  $\text{Re}(a-s) > 0$


$$\therefore \mathcal{L}[e^{at} \mathcal{L}\{-t\}] = \frac{-1}{a-s} \text{ if } \text{Re } s < \text{Re } a$$

region of convergence  
a left half plane

$$\mathcal{L}[-e^{at} \mathcal{L}\{t\}] = \frac{-1}{a-s} \text{ if } \text{Re } s > \text{Re } a \Rightarrow \text{RHP}$$

EE610  
11/03/03  
p. 10

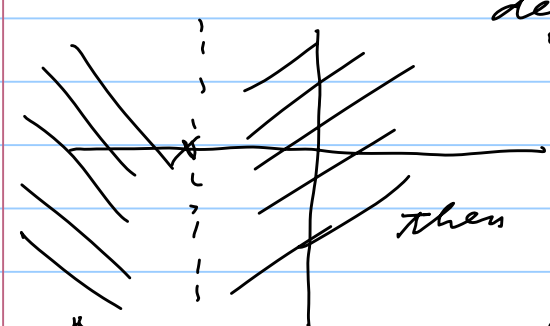$F(s) = \frac{-1}{s-a}$  need region of convergence to determine  $f(t)$



then  $f(t) = -e^{at} u(t)$

↑ here  $f(t) = e^{at} u(-t)$