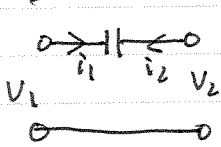


Problem 1. a) (15/25)


left circuit:



$$i_1 = -i_2 = (v_1 - v_2) C s \quad (1)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} C s & -C s \\ -C s & C s \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad (2)$$

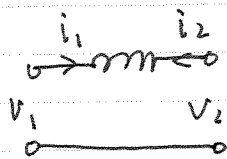
$$Y_c = \begin{bmatrix} C s & -C s \\ -C s & C s \end{bmatrix} \quad (3)$$



$$i_1 = -i_2 = \frac{v_1 - v_2}{R_L} \quad (4)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_L} & -\frac{1}{R_L} \\ -\frac{1}{R_L} & \frac{1}{R_L} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad (5)$$
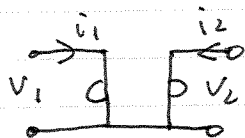
$$Y_L = \begin{bmatrix} \frac{1}{R_L} & -\frac{1}{R_L} \\ -\frac{1}{R_L} & \frac{1}{R_L} \end{bmatrix} \quad (6)$$




$$Z_g = \begin{bmatrix} 0 & r_1 \\ -r_1 & 0 \end{bmatrix} \quad (7)$$

$$Y_g = \begin{bmatrix} 0 & -\frac{1}{r_1} \\ \frac{1}{r_1} & 0 \end{bmatrix} \quad (8)$$

$$Y_1 = Y_c + Y_L + Y_g = \begin{bmatrix} C s + \frac{1}{R_L} & -C s - \frac{1}{R_L} - \frac{1}{r_1} \\ -C s - \frac{1}{R_L} + \frac{1}{r_1} & C s + \frac{1}{R_L} \end{bmatrix} \quad (9)$$


right circuit:

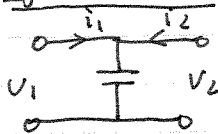

$$v_1 = v_2 = \frac{i_1 + i_2}{C s} \quad (10)$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{C s} & \frac{1}{C s} \\ \frac{1}{C s} & \frac{1}{C s} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad (11)$$

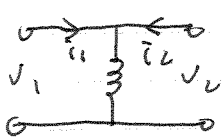
$$Z_c = \begin{bmatrix} \frac{1}{C s} & \frac{1}{C s} \\ \frac{1}{C s} & \frac{1}{C s} \end{bmatrix} \quad (12)$$



$$v_1 = v_2 = (i_1 + i_2) L s \quad (13)$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L s & L s \\ L s & L s \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad (14)$$
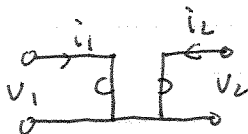
$$Z_L = \begin{bmatrix} L s & L s \\ L s & L s \end{bmatrix} \quad (15)$$



$$Z_g = \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix} \quad (16)$$

$$Z = Z_c + Z_L + Z_g = \begin{bmatrix} L s + \frac{1}{C s} & L s + \frac{1}{C s} + r \\ L s + \frac{1}{C s} - r & L s + \frac{1}{C s} \end{bmatrix} \quad (17)$$

For circuit on the left: $\Delta Y_1 = (C s + \frac{1}{R_L})^2 - (-C s - \frac{1}{R_L} - \frac{1}{r_1})(-C s - \frac{1}{R_L} - \frac{1}{r_1}) = \frac{1}{r_1^2}$

$$Z_1 = Y_1^{-1} = \begin{bmatrix} C_1 r_1^2 s + \frac{r_1^2}{L} \cdot \frac{1}{s} & C s^2 s + \frac{r_1^2}{L} \cdot \frac{1}{s} + r_1 \\ C_1 r_1^2 s + \frac{r_1^2}{L} \cdot \frac{1}{s} + r_1 & C_1 r_1^2 s + \frac{r_1^2}{L} \cdot \frac{1}{s} \end{bmatrix} \quad (19)$$

ENEE 610

HW 2

J.Y. 09/22/03 (2)

Problem 1. b) (10/25)

left circuit:

$$Z_1 = \begin{bmatrix} z'_{11} & z'_{12} \\ z'_{21} & z'_{22} \end{bmatrix} = \begin{bmatrix} C_1 r_1^2 s + \frac{r_1^2}{L_1} \frac{1}{s} & C_1 r_1^2 s + \frac{r_1^2}{L_1} \frac{1}{s} + r_1 \\ C_1 r_1^2 s + \frac{r_1^2}{L_1} \frac{1}{s} - r_1 & C_1 r_1^2 s + \frac{r_1^2}{L_1} \frac{1}{s} \end{bmatrix} \quad (20)$$

right circuit:

$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} Ls + \frac{1}{C} \frac{1}{s} & Ls + \frac{1}{C} \frac{1}{s} + r \\ Ls + \frac{1}{C} \frac{1}{s} - r & Ls + \frac{1}{C} \frac{1}{s} \end{bmatrix} \quad (21)$$

$$Z_1 = Z \Rightarrow z'_{11} = z_{11}, z'_{12} = z_{12}, z'_{21} = z_{21}, z'_{22} = z_{22} \quad (22)$$

$$\therefore \begin{cases} C_1 r_1^2 = L & (23) \\ \frac{r_1^2}{L_1} = \frac{1}{C} & (24) \\ r_1 = r & (25) \end{cases}$$

solve r_1, L_1, C_1 in r, L, C

$$\begin{cases} r_1 = r & (26) \\ C_1 = \frac{L}{r^2} & (27) \\ L_1 = r^2 C & (28) \end{cases}$$

Problem 2. a) (15/25)

$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} zS + \frac{1}{cS} & zS + \frac{1}{cS} + r \\ zS + \frac{1}{cS} - r & zS + \frac{1}{cS} \end{bmatrix} \quad (1)$$

Notice that $z(s) = -z^T(-s)$ lossless (2)

$$z_{in} = \frac{z_{11} z_L + \Delta z}{z_L + z_{22}} \quad (3)$$

$$z_{in} = \frac{(zS + \frac{1}{cS}) z_L + r^2}{z_L + (zS + \frac{1}{cS})}$$

$$Ev z_{in}(s) = \frac{1}{2} \left[\frac{z_{11}(s) z_L(s) + \Delta z(s)}{z_L(s) + z_{22}(s)} + \frac{z_{11}(-s) z_L(-s) + \Delta z(-s)}{z_L(-s) + z_{22}(-s)} \right] \quad (4)$$

$$Nr (Ev z_{in}) = \frac{1}{2} \left\{ [z_{11}(s) z_L(s) + \Delta z(s)] [z_L(-s) + z_{22}(-s)] + [z_{11}(-s) z_L(-s) + \Delta z(-s)] [z_L(s) + z_{22}(s)] \right\} \frac{1}{2}$$

$$= \frac{1}{2} \left\{ \underbrace{z_{11}(s) z_L(-s) z_L(s)}_{(1)} + \underbrace{z_{11}(s) z_{22}(-s) z_L(s)}_{(2)} + \underbrace{\Delta z(s) z_L(-s)}_{(3)} + \underbrace{\Delta z(s) z_{22}(-s)}_{(4)} + \underbrace{z_{11}(-s) z_L(-s) z_L(s)}_{(5)} + \underbrace{z_{11}(-s) z_{22}(s) z_L(-s)}_{(6)} + \underbrace{\Delta z(-s) z_L(s)}_{(7)} + \underbrace{\Delta z(-s) z_{22}(s)}_{(8)} \right\} \frac{1}{2}$$

z is lossless

$$z_{11}(s) = -z_{11}(-s) \quad (b) \quad z_{22}(s) = -z_{22}(-s) \quad (b)$$

$$\Delta z(-s) = \Delta z^T(-s) = \Delta(-z(s)) = (-1)^n \Delta z(s) \quad (n=2) = \Delta z(s) = r^2 \quad (8)$$

terms (1) & (2) cancel, term (3) & (4) cancel

$$Nr (Ev z_{in}) = [-z_{11}(s) z_{22}(s) + \Delta z(s)] [z_L(s) + z_L(-s)] / 2$$

$$= -z_{12}(s) z_{21}(s) \frac{z_L(s) + z_L(-s)}{2}$$

$$= -z_{12}(s) \cdot z_{21}(s) \cdot Ev z_L(s) \quad (9)$$

Zeros of Even part of $z_{in}(s)$ are:

(Zeros of z_{12} , z_{21} and zeros of even part of z_L)

Zeros of z_{12} & z_{21}

$$zS + \frac{1}{cS} \pm r = 0 \quad (10)$$


$$z c S^2 \pm r c S + 1 = 0 \quad (11)$$

$$S = \frac{\pm r c \pm \sqrt{r^2 c^2 - 4 z c}}{2 z c} \quad (12)$$

zeros of z_{21} $\left\{ \frac{r c \pm \sqrt{r^2 c^2 - 4 z c}}{2 z c} \right\}$ (13)

zeros of z_{12} $\left\{ \frac{-r c \pm \sqrt{r^2 c^2 - 4 z c}}{2 z c} \right\}$ (14)

Problem 2. b) (10/25)

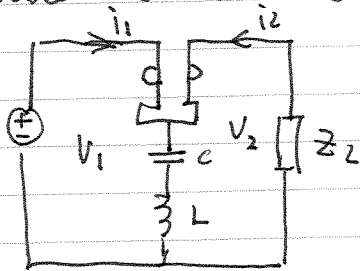

$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} Ls + \frac{1}{Cs} & Ls + \frac{1}{Cs} + r \\ Ls + \frac{1}{Cs} - r & Ls + \frac{1}{Cs} \end{bmatrix} \quad (1)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad (2) \Rightarrow \begin{aligned} V_1 &= z_{11}i_1 + z_{12}i_2 & (3) \\ V_2 &= z_{21}i_1 + z_{22}i_2 & (4) \end{aligned}$$

$$V_2 = -z_{21}i_2 \quad (5) \Rightarrow i_2 = -\frac{V_2}{z_{21}} \quad (6)$$

③ × z₂₁ - ④ × z₁₁

$$z_{21}V_1 - z_{11}V_2 = z_{12}z_{21}i_2 - z_{11}z_{22}i_2 = -\Delta Z i_2 \quad (7)$$

Plug (6) in (7)

$$z_{21}V_1 - z_{11}V_2 = +\frac{\Delta Z}{z_{21}}V_2 \quad (8)$$

$$z_{21}V_1 = \left(z_{11} + \frac{\Delta Z}{z_{21}}\right)V_2 \quad (9)$$

$$\frac{V_2}{V_1} = \frac{z_{21}}{z_{11} + \frac{\Delta Z}{z_{21}}} = \frac{z_{21}z_{21}}{z_{11}z_{21} + \Delta Z} \quad (10)$$

$$z_{21} = Ls + \frac{1}{Cs} - r \quad (11), \quad z_{11} = Ls + \frac{1}{Cs} \quad (12), \quad z_{22} = \frac{Nr(z_c)}{Dm(z_c)} \quad (13), \quad \Delta Z = r^2$$

$$\frac{V_2}{V_1} = \frac{(Ls + \frac{1}{Cs} - r) \frac{Nr(z_c)}{Dm(z_c)}}{(Ls + \frac{1}{Cs}) \frac{Nr(z_c)}{Dm(z_c)} + r^2} = \frac{(Ls^2 - rCs + 1) Nr(z_c)}{(Ls^2 + 1) Nr(z_c) + r^2 Dm(z_c)} = 0 \quad (15)$$

Zeros of $\frac{V_2}{V_1}$ (zeros of transmission) are zeros of z₂₁ and load.

$$Ls^2 - rCs + 1 = 0$$

$$s = \frac{rc \pm \sqrt{r^2c^2 - 4Lc}}{2Lc} \quad (16)$$

$$Nr(z_c) = 0$$

$$\text{Zeros of load} \quad (17)$$

Problem 3. (5 for each synthesis)

$$Z_{in}(s) = \frac{5s(s^2+4)}{(s^2+2)(s^2+8)} \quad (1)$$

a) 1st Foster's

$$Z_{in}(s) = k_{\infty}s + \frac{k_0}{s} + \frac{2k_1s}{s^2+2} + \frac{2k_2s}{s^2+8} \quad (2)$$

$$k_{\infty} = \frac{1}{s} \cdot Z_{in}(s) \Big|_{s \rightarrow \infty} = \frac{5(s^2+4)}{(s^2+2)(s^2+8)} \Big|_{s \rightarrow \infty} = 0 \quad (3)$$


$$k_0 = s \cdot Z_{in}(s) \Big|_{s=0} = \frac{5s^2(s^2+4)}{(s^2+2)(s^2+8)} \Big|_{s=0} = 0 \quad (4)$$

$$2k_1 = \frac{s^2+2}{s} \cdot Z_{in}(s) \Big|_{s^2=2} = \frac{5(s^2+4)}{s^2+8} \Big|_{s^2=2} = \frac{5}{3} \quad (5)$$

$$2k_2 = \frac{s^2+8}{s} \cdot Z_{in}(s) \Big|_{s^2=8} = \frac{5(s^2+4)}{s^2+2} \Big|_{s^2=8} = \frac{10}{3} \quad (6)$$

$$\therefore Z_{in}(s) = \frac{\frac{5}{3} \cdot s}{s^2+2} + \frac{\frac{10}{3} \cdot s}{s^2+8} \quad (7)$$
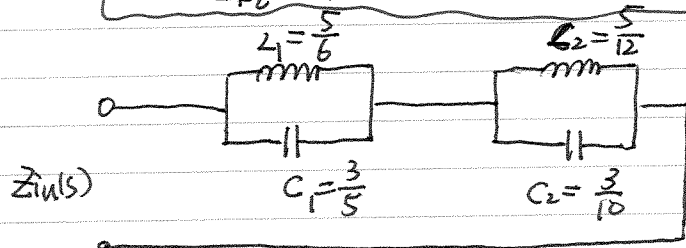
$$\left\{ \begin{array}{l} C_1 = \frac{1}{2k_1} = \frac{3}{5} \quad (9), \quad L_1 = \frac{2k_1}{\omega_1^2} = \frac{5/3}{2} = \frac{5}{6} \quad (10) \\ C_2 = \frac{1}{2k_2} = \frac{3}{10} \quad (11), \quad L_2 = \frac{2k_2}{\omega_2^2} = \frac{10/3}{8} = \frac{5}{12} \quad (12) \end{array} \right.$$



b) 2nd Foster's

$$Y_{in}(s) = \frac{1}{Z_{in}(s)} = \frac{(s^2+2)(s^2+8)}{5s(s^2+4)} \quad (13)$$

$$Y_{in}(s) = k'_{\infty}s + \frac{k'_0}{s} + \frac{2k'_1s}{s^2+4} \quad (14)$$

$$k'_{\infty} = \frac{1}{s} Y_{in}(s) \Big|_{s \rightarrow \infty} = \frac{(s^2+2)(s^2+8)}{5s^2(s^2+4)} \Big|_{s \rightarrow \infty} = \frac{1}{5} \quad (15)$$

$$k'_0 = s \cdot Y_{in}(s) \Big|_{s=0} = \frac{(s^2+2)(s^2+8)}{5(s^2+4)} \Big|_{s=0} = \frac{4}{5} \quad (16)$$

$$2k'_1 = \frac{s^2+4}{s} \cdot Y_{in}(s) \Big|_{s^2=4} = \frac{(s^2+2)(s^2+8)}{5s^2} \Big|_{s^2=4} = \frac{2}{5} \quad (17)$$

ENEE 610

HW 2

J.T. 09/22/03 ⑥


Problem 3

b) (continued)

$$Y_{in}(s) = \frac{1}{5}s + \frac{4}{5} \cdot \frac{1}{s} + \frac{\frac{2}{5} \cdot s}{s^2 + 4} \quad (18)$$

$$C_{\infty} = K_{\infty}' = \frac{1}{5} \quad (19) \quad L_0 = \frac{1}{k_0'} = \frac{5}{4} \quad (20)$$
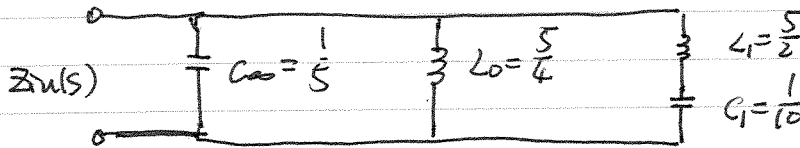
$$L_1 = \frac{1}{2k_1'} = \frac{5}{2} \quad (21) \quad C_1 = \frac{2k_1'}{\omega_1'^2} = \frac{2}{5/4} = \frac{1}{10} \quad (22)$$



c) 1st Cauer's

$$Z_{in}(s) = \frac{5s(s^2+4)}{(s^2+2)(s^2+8)} = \frac{5s^3+20s}{s^4+10s^2+16} \quad (23) \quad \text{Order}(\text{Nuc}(Z_{in})) > \text{Order}(\text{Den}(Z_{in}))$$

$$\frac{1}{5}s \sqrt{s^4+10s^2+16}$$

$$-) \frac{s^4+4s^2}{s^4+10s^2+16}$$

$$\frac{5}{6}s \sqrt{5s^3+20s}$$

$$-) \frac{5s^3+\frac{40}{3}s}{5s^3+20s}$$

$$\frac{20}{3}s \sqrt{6s^2+16}$$

$$-) \frac{6s^2}{6s^2+16}$$


$$\frac{5}{12}s \sqrt{\frac{20}{3}s}$$

$$-) \frac{5s}{\frac{20}{3}s}$$

$$\frac{0}{0}$$

(24)

$$Z_{in}(s) = \frac{1}{\frac{1}{5}s + \frac{1}{\frac{5}{6}s + \frac{1}{\frac{9}{10}s + \frac{1}{\frac{5}{12}s}}}}} \quad (25)$$

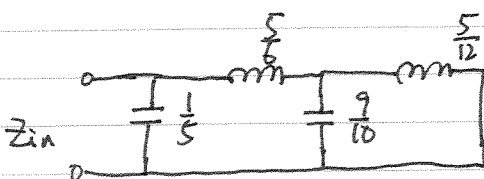

ENFE610

HW 2

J.T. 09/24/03 (7)

d) 2nd Cauer's

$$Z_{in}(s) = \frac{5s(s^2+4)}{(s^2+2)(s^2+8)} = \frac{20s + 5s^3}{16 + 10s^2 + s^4} \quad (26)$$

$$\begin{array}{r} \frac{4}{5}s^{-1} \\ 20s + 5s^3 \sqrt{16 + 10s^2 + s^4} \\ -) \underline{16 + 4s^2} \qquad \frac{10}{3}s^{-1} \\ 6s^2 + s^4 \sqrt{20s + 5s^3} \\ -) \underline{20s + \frac{10}{3}s^3} \qquad \frac{18}{5}s^{-1} \\ \frac{5}{2}s^3 \sqrt{6s^2 + s^4} \\ -) \underline{6s^2} \qquad \frac{5}{3}s^{-1} \\ s^4 \sqrt{\frac{5}{3}s^3} \\ -) \underline{\frac{5}{3}s^3} \\ 0 \end{array} \quad (27)$$

$$Y_{in}(s) = \frac{1}{Z_{in}(s)} = \frac{16 + 10s^2 + s^4}{20s + 5s^3} \quad (28)$$

$$\begin{aligned} Y_{in}(s) &= \frac{4}{5}s^{-1} + \frac{1}{\frac{10}{3}s^{-1} + \frac{1}{\frac{18}{5}s^{-1} + \frac{1}{\frac{5}{3}s^{-1}}}} \\ &= \frac{1}{\frac{5}{4}s} + \frac{1}{\frac{3}{10}s + \frac{1}{\frac{5}{18}s + \frac{1}{\frac{3}{5}s}}} \end{aligned} \quad (29)$$

