
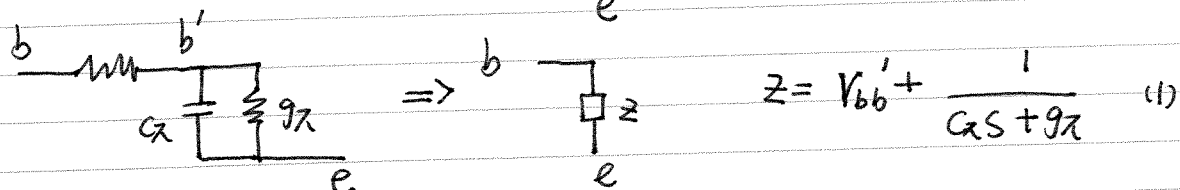


ECEE 610

HW 3

Problem 1 a)

J.Y. 09/29/03 (1)

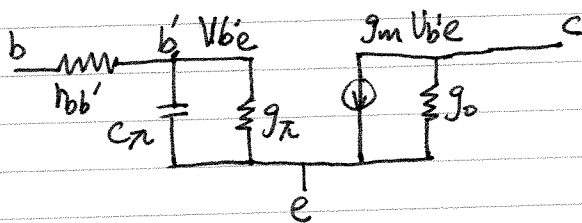

$$Z = r_{bb}' + \frac{1}{C_{\pi}S + g_{\pi}} \quad (1)$$

$$V_{b'e} = \frac{1}{r_{bb}' + \frac{1}{C_{\pi}S + g_{\pi}}} V_{be} = \frac{V_{be}}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} \quad (2)$$

$$V_1 = V_{be}, \quad V_2 = V_{ce}, \quad i_1 = i_b, \quad i_2 = i_c \quad (3)$$

$$i_1 = i_b = \frac{V_{be}}{Z} = \frac{C_{\pi}S + g_{\pi}}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} V_1 \quad (4)$$

$$i_2 = i_c = g_m V_{b'e} + g_o V_{ce} = \frac{g_m}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} V_{be} + g_o V_{ce}$$

$$= \frac{g_m}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} V_1 + g_o V_2 \quad (5)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{C_{\pi}S + g_{\pi}}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} & 0 \\ \frac{g_m}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} & g_o \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad (6)$$

$$Y = \begin{bmatrix} \frac{C_{\pi}S + g_{\pi}}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} & 0 \\ \frac{g_m}{r_{bb}'(C_{\pi}S + g_{\pi}) + 1} & g_o \end{bmatrix} = \begin{bmatrix} \frac{C_{\pi}S + g_{\pi}}{r_{bb}'C_{\pi}S + (r_{bb}'g_{\pi} + 1)} & 0 \\ \frac{g_m}{r_{bb}'C_{\pi}S + (r_{bb}'g_{\pi} + 1)} & g_o \end{bmatrix} \quad (7)$$

$$= \begin{bmatrix} s + \frac{g_{\pi}}{C_{\pi}} & 0 \\ \frac{g_m}{r_{bb}'C_{\pi}} \cdot \frac{1}{(s + \frac{r_{bb}'g_{\pi} + 1}{r_{bb}'C_{\pi}})} & g_o \end{bmatrix}$$

HW3

Problem 1 b)

$$V_T = 26 \text{ mV}, \quad I_C = 2 \text{ mA}, \quad V_A = 100 \text{ V}, \quad \beta = 50, \quad r_{bb}' = 10 \Omega, \quad C_\pi = 20 \text{ pF} \quad (1)$$

$$g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} = 7.69 \times 10^{-2} \Omega^{-1} \quad (2)$$

$$g_o = \frac{I_C}{V_A} = \frac{2 \text{ mA}}{100 \text{ V}} = 2 \times 10^{-5} \Omega^{-1} \quad (3)$$

$$g_\pi = \frac{g_m}{\beta} = \frac{7.69 \times 10^{-2} \Omega^{-1}}{50} = 1.538 \times 10^{-3} \Omega^{-1} \quad (4)$$

$$\frac{g_\pi}{C_\pi} = \frac{1.538 \times 10^{-3} \Omega^{-1}}{20 \times 10^{-12} \text{ F}} = 7.69 \times 10^7 (\Omega \text{ F})^{-1} \quad (5)$$

$$\frac{r_{bb}' g_\pi + 1}{r_{bb}' C_\pi} = \frac{10 \Omega \cdot 1.538 \times 10^{-3} \Omega^{-1} + 1}{10 \Omega \cdot 20 \times 10^{-12} \text{ F}} = 5.077 \times 10^9 (\Omega \text{ F})^{-1} \quad (6)$$

$$\frac{g_m}{r_{bb}' C_\pi} = \frac{7.69 \times 10^{-2} \Omega^{-1}}{10 \Omega \cdot 20 \times 10^{-12} \text{ F}} = 3.85 \times 10^{10} \frac{1}{\Omega \text{ F}} \quad (7)$$

$$\therefore Y = \begin{bmatrix} \frac{s + 7.69 \times 10^7 (\Omega \text{ F})^{-1}}{10 \Omega (s + 5.077 \times 10^9 \Omega \text{ F}^{-1})} & 0 \\ 3.85 \times 10^{10} \frac{1}{\Omega \text{ F}} \cdot \frac{1}{(s + 5.077 \times 10^9 \Omega \text{ F}^{-1})} & 2 \times 10^5 \Omega^{-1} \end{bmatrix}$$

d) Transistor — Passive

Small signal hybrid- π equivalent circuit not passive

since not all connections and bias are shown in the model.

E0EE610

J.Y. 09/29/03 (3)

HW3

Problem 1 c)

$$H(Y) = \frac{1}{2}(Y + Y^*T) \quad R(Y) = \frac{1}{2}(Y + Y^*) \quad (1)$$

$$Y = \begin{bmatrix} \frac{1}{A} \cdot \frac{(s+a)}{(s+b)} & 0 \\ B \cdot \frac{1}{(s+b)} & g_0 \end{bmatrix} \quad (2)$$

with $A = 10\Omega$, $B = 3.85 \times 10^{10} \frac{1}{\Omega^2 F}$, $a = 7.67 \times 10^7 (\Omega F)^{-1}$, $b = 5.077 \times 10^9 (\Omega F)^{-1}$

and $g_0 = 2 \times 10^{-5} \Omega^{-1}$ (3)

$$H(Y)_{11} = \frac{1}{2}(Y_{11} + Y_{11}^*) = \frac{1}{2A} \left(\frac{s+a}{s+b} + \frac{s^*+a}{s^*+b} \right) = \frac{1}{A} \cdot \frac{|s|^2 + (a+b)\text{Re}(s) + ab}{|s|^2 + 2b\text{Re}(s) + b^2} \quad (4)$$

$$H(Y)_{12} = \frac{1}{2}(Y_{12} + Y_{21}^*) = \frac{B}{2} \cdot \frac{1}{s^*+b} \quad (5)$$

$$H(Y)_{21} = \frac{1}{2}(Y_{21} + Y_{12}^*) = \frac{B}{2} \cdot \frac{1}{s+b} \quad (6)$$

$$H(Y)_{22} = \frac{1}{2}(Y_{22} + Y_{22}) = g_0 \quad (7)$$

$$R(Y_{11}) = \frac{1}{2}(Y_{11} + Y_{11}^*) = H(Y)_{11} \quad (8)$$

$$R(Y_{12}) = \frac{1}{2}(Y_{12} + Y_{12}^*) = 0 \quad (9)$$

$$R(Y_{21}) = \frac{1}{2}(Y_{21} + Y_{21}^*) = \frac{B}{2} \left(\frac{1}{s+b} + \frac{1}{s^*+b} \right) = B \cdot \frac{\text{Re}(s) + b}{|s|^2 + 2b\text{Re}(s) + b^2} \quad (10)$$

$$R(Y_{22}) = \frac{1}{2}(Y_{22} + Y_{22}^*) = H(Y)_{22}$$

$$H(Y) = \begin{bmatrix} \frac{1}{10} \cdot \frac{|s|^2 + 5.154 \times 10^9 \text{Re}(s) + 3.904 \times 10^{17}}{|s|^2 + 1.015 \times 10^{10} \text{Re}(s) + 2.578 \times 10^{19}} & 1.925 \times 10^{10} \frac{1}{s^* + 5.077 \times 10^9} \\ \frac{1}{1.925 \times 10^{10}} \frac{1}{s + 5.077 \times 10^9} & 2 \times 10^{-5} \end{bmatrix} \quad (11)$$

$$R(Y) = \begin{bmatrix} \frac{1}{10} \cdot \frac{|s|^2 + 5.154 \times 10^9 \text{Re}(s) + 3.904 \times 10^{17}}{|s|^2 + 1.015 \times 10^{10} \text{Re}(s) + 2.578 \times 10^{19}} & 0 \\ 3.85 \times 10^{10} \cdot \frac{\text{Re}(s) + 5.077 \times 10^9}{|s|^2 + 1.015 \times 10^{10} \text{Re}(s) + 2.578 \times 10^{19}} & 2 \times 10^{-5} \end{bmatrix} \quad (12)$$

ENEE 610

HW3

J.Y. 09/29/03 (4)

Problem 2 a)

$$Z(s) = \frac{2s(s+2)}{(s+8)(s^2+25)} \quad (1)$$

$$u=i, \quad y=V \quad (2) \quad \frac{Y(s)}{U(s)} = Z(s) = \frac{N(s)}{D(s)} \quad (3)$$

$$N(s) = 2s^2 + 4 \quad (4)$$

$$D(s) = s^3 + 8s^2 + 25s + 200 \quad (5)$$

$$\left\{ \begin{array}{l} U(s) = D(s) X(s) \quad (6) \\ Y(s) = N(s) X(s) \quad (7) \end{array} \right.$$

$$\text{define: } X^{(n)} = \frac{dx}{dt} \quad (8)$$

$$\text{state variables: } x_1 = X, \quad x_2 = \dot{x}^{(1)}, \quad x_3 = \dot{x}^{(2)} \quad (9)$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -200 & -25 & -8 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} u \quad (10)$$

$$y = \begin{bmatrix} 0 & 4 & 2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} \quad (11)$$

$$\left\{ \begin{array}{l} \dot{x}_1 = x_2 \\ \dot{x}_2 = x_3 \\ \dot{x}_3 = -200x_1 - 25x_2 - 8x_3 + u \end{array} \right. \quad (12)$$

$$y = 4x_2 + 2x_3 \quad (13)$$