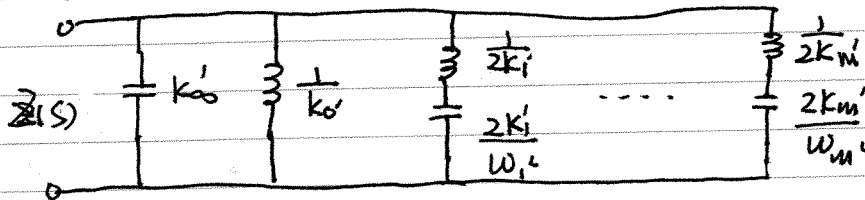


Problem 1:

Lossless Passive finite Circuit:

$$Y(s): Y(s) = k_0' s + \frac{k_0'}{s} + \sum_{i=1}^m \frac{2k_i' s}{s^2 + \omega_i^2} \quad (1)$$

Second Foster realization: (LC)



⑩ a) $Y(s) = -Y(-s) \quad (2)$

$$sY(s) = k_0' s^2 + k_0' + \sum_{i=1}^m \frac{2k_i' s^2}{s^2 + \omega_i^2} \quad (3)$$

$$y(s) = k_0' s + k_0' + \sum_{i=1}^m \frac{2k_i' s}{s + \sigma_i} \quad (4) \quad \text{with } \sigma_i = \omega_i^2 \quad (5)$$

clearly, $y(s^2) = sY(s) \quad (6)$

$\therefore sY(s)$ is a rational function $y(\cdot)$ of s^2 , $y(s^2) = sY(s)$

⑪ b) prove $y(s)$ is positive real.

I. Using Definition

① $y(s) = k_0' s + k_0' + \sum_{i=1}^m \frac{2k_i' s}{s + \sigma_i}$ is real when s is real.

$s = \sigma + j\omega \quad (7)$

$$\begin{aligned} \textcircled{2} y(s) &= k_0'(\sigma + j\omega) + k_0' + \sum_{i=1}^m \frac{2k_i'(\sigma + j\omega)}{(\sigma + \sigma_i) + j\omega} \\ &= k_0'(\sigma + j\omega) + k_0' + \sum_{i=1}^m \frac{2k_i' [\sigma(\sigma + \sigma_i) + \omega^2 + \sigma_i j\omega]}{(\sigma + \sigma_i)^2 + \omega^2} \end{aligned} \quad (8)$$

$$\therefore \text{Re}[y(s)] = k_0' \sigma + k_0' + \sum_{i=1}^m \frac{2k_i' [\sigma(\sigma + \sigma_i) + \omega^2]}{[(\sigma + \sigma_i)^2 + \omega^2]} \quad (9)$$

$\text{Re}[y(s)] \geq 0$ when $\sigma \geq 0$

\therefore by definition of positive real

$y(s)$ is positive real.

Problem 2: b) (continued)

II. Using Theorem 8.2-2

$$Y(s) = k_0' s + k_0' + \sum_{i=1}^m \frac{2k_i' s}{s + \sigma_i} \quad (10)$$

① $Y(s)$ has no poles in right half of s plane, $\sigma_i > 0$


② $Y(s)$ has no poles at $j\omega$ axis

$$\begin{aligned} \textcircled{3} \quad Y(j\omega) &= k_0'(j\omega) + k_0' + \sum_{i=1}^m \frac{2k_i' j\omega}{j\omega + \sigma_i} \\ &= k_0'(j\omega) + k_0' + \sum_{i=1}^m \frac{2k_i' [\omega^2 + j\sigma_i \omega]}{\sigma_i^2 + \omega^2} \end{aligned} \quad (11)$$

$$R[Y(j\omega)] = k_0' + \sum_{i=1}^m \frac{2k_i' \omega^2}{\sigma_i^2 + \omega^2} \quad (12)$$

$\therefore R[Y(j\omega)] \geq 0$ for all $0 \leq \omega < \infty$
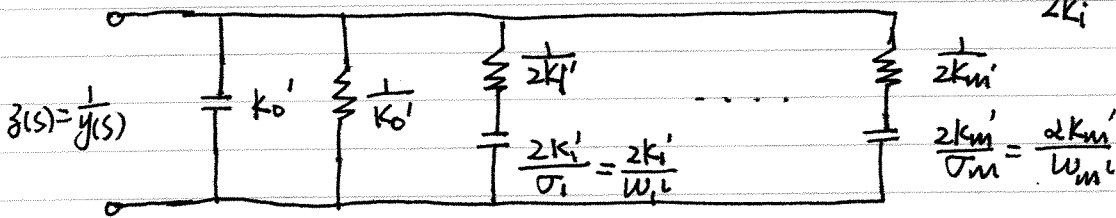
$$\therefore Y(s) \text{ is positive real} \quad Y(s) = k_0' s + k_0' + \sum_{i=1}^m \frac{1}{\frac{1}{2k_i'} + \frac{1}{\sigma_i} s} \quad (13)$$




RC realization


Comparing with $Y(s)$ realization: replacing Z by R with the same value.

Problem 2: (5)

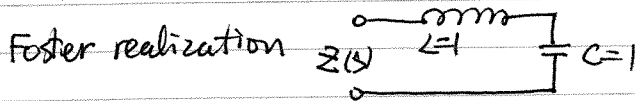a) example: $Y(s) = \frac{s}{s^2+1}$ (1) $Z(s) = s + \frac{1}{s}$ (2)



By replacing $L=1$ by $R=1$

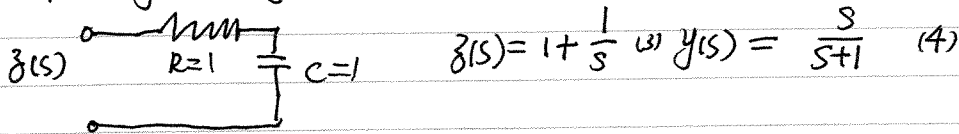


clearly $y(s^2) = \frac{s^2}{s^2+1} = s \cdot Y(s)$ (5)

If Richard's function is used.



$Z(s) = -Z(-s)$ (6) $Z(s) + Z(-s) = 0$ (7) k can be any value

choose $k=1$ $Z(s)|_{s=1} = 2$ (8)

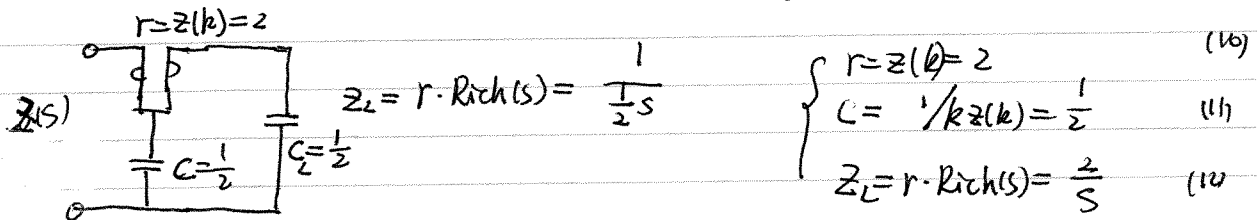Rich(s) = $\frac{kZ(s) - sZ'(k)}{kZ'(k) - sZ(s)} = \frac{s + \frac{1}{s} - 2s}{2 - s \cdot (s + \frac{1}{s})} = \frac{1-s^2}{(1-s^2) \cdot s} = \frac{1}{s}$ (9)



there is no L to be replaced.

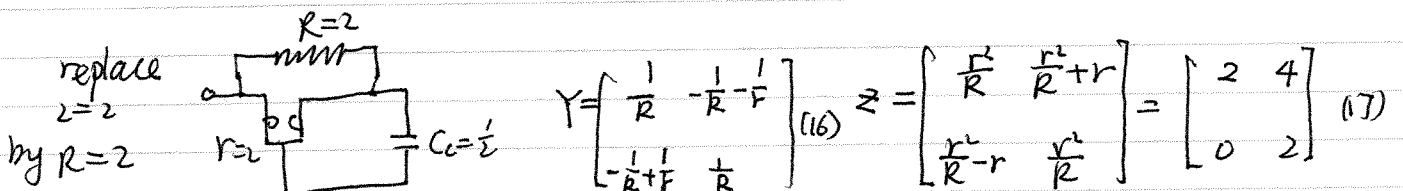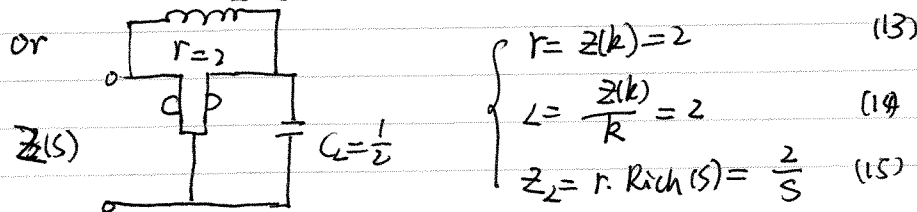

$Z(s) = Z_{in} = \frac{Z_{11}Z_L + Z_{22}}{Z_L + Z_{22}} = \frac{2 \cdot \frac{2}{s} + 4}{\frac{2}{s} + 2} = 2$ (18) $Y(s) = \frac{1}{s}$ (19)

clearly $y(s^2) \neq s \cdot Y(s)$ (20)

Problem 2. b) (5)

The reason for non-synthesizable by degree one real Richards' section zeros of even part of $Z(s)$ are complex number, not real number.

example: $Z(s) = \frac{(s+1)(s+2)}{(s+3)(s+4)}$ (1)

$Z(s)$ is positive real (checked in text book Example 8.2-1 (6), p. 41)

$$\text{even}(Z(s)) = \frac{1}{2} \left[\frac{(s+1)(s+2)}{(s+3)(s+4)} + \frac{(s+1)(s+2)}{(s+3)(-s+4)} \right] = \frac{N_v(s)}{D_v(s)} \quad (2)$$

$$N_v(s) = \frac{1}{2} \left[(s^2+3s+2)(s^2-7s+12) + (s^2-3s+2)(s^2+7s+12) \right] \quad (3)$$

$$N_v(s) = s^4 - 7s^2 + 24 \quad (4)$$

$$N_v(s) = 0 \quad s^2 = \frac{1}{2} \cdot (7 \pm j\sqrt{47}) \quad (5)$$

$$s_{1,2,3,4} = \pm \frac{\sqrt{7 \pm j\sqrt{47}}}{2} \quad (6) \quad \text{zeros are not real numbers}$$

since $\begin{cases} r = z(k) & (7) \\ c = \frac{1}{kz(k)} & (8) \\ z_L = z(k) \text{ Rich}(s) & (9) \end{cases}$ r & c are not real numbers

\therefore not synthesizable by degree one real Richards' section