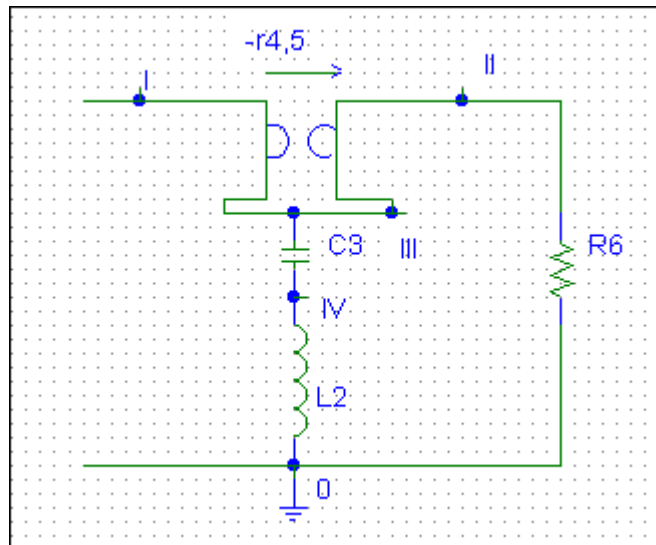


a) (10)

$$\text{YN} := \begin{bmatrix} \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 \\ 0 & s \cdot C & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{-1}{r} & 0 \\ 0 & 0 & \frac{1}{r} & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{R} \end{bmatrix} \quad \text{YNa} := \begin{bmatrix} \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 \\ 0 & s \cdot C & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{r} & 0 \\ 0 & 0 & \frac{-1}{r} & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{R} \end{bmatrix}$$

Adjoint circuit:




b) (10)

$$T(s) := \frac{VII}{II}$$

Input: I1
Output: VII (V2)

Terminate original and adjoint circuit:

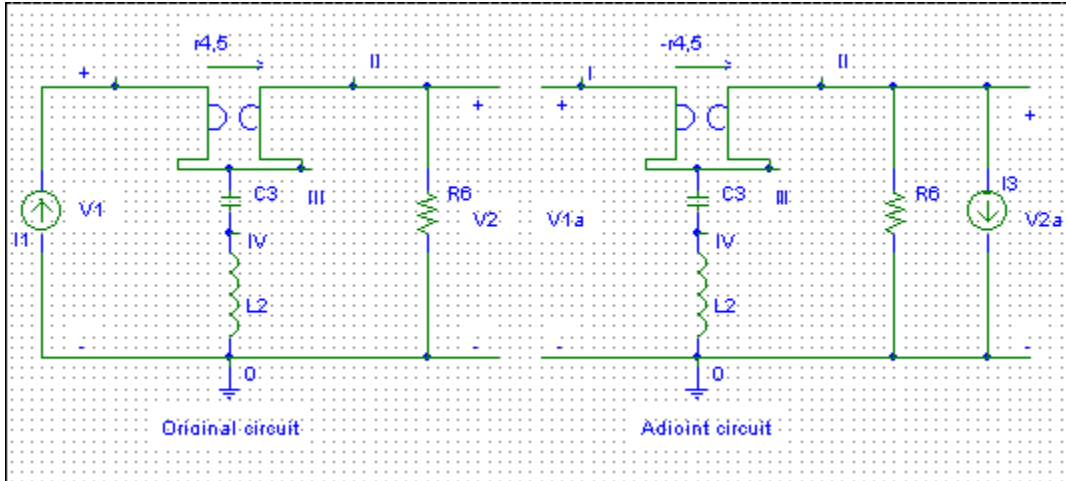

$$V_1 * i_1^a + V_2 * i_2^a - V_1^a * i_1 - V_2^a * i_2 = -[i_N^{aT} * V_N - i_N^T * V_N^a]$$

Clearly $i_1^a = i_2 = 0$

$$\text{So } V_2 * i_2^a - V_1^a * i_1 = -[i_N^{aT} * V_N - i_N^T * V_N^a]$$

Since i_1 is fixed in a , and nothing varies in N^a ,
then $di_1/da = 0$, $di_2^a/da = 0$, and $dV_1^a/da = 0$,


$$\text{So } i_2^a * dV_2/da = -[i_N^{aT} * V_N - i_N^T * V_N^a]$$

$$\text{Then } dV_2/da = -[i_N^{aT} * V_N - i_N^T * V_N^a] / i_2^a = [V_N^{aT} * (dY_N/da) * V_N] / i_2^a$$

$$dT(s)/da = dV_2/da = [V_N^{aT} * (dY_N/da) * V_N] / i_2^a \text{ by setting } I1=1$$

$$II := 1 \quad \frac{dT(s)}{da} := \frac{1}{I2a} \cdot \left(V_N^{aT} \cdot \frac{dY_N}{da} \cdot V_N \right)$$

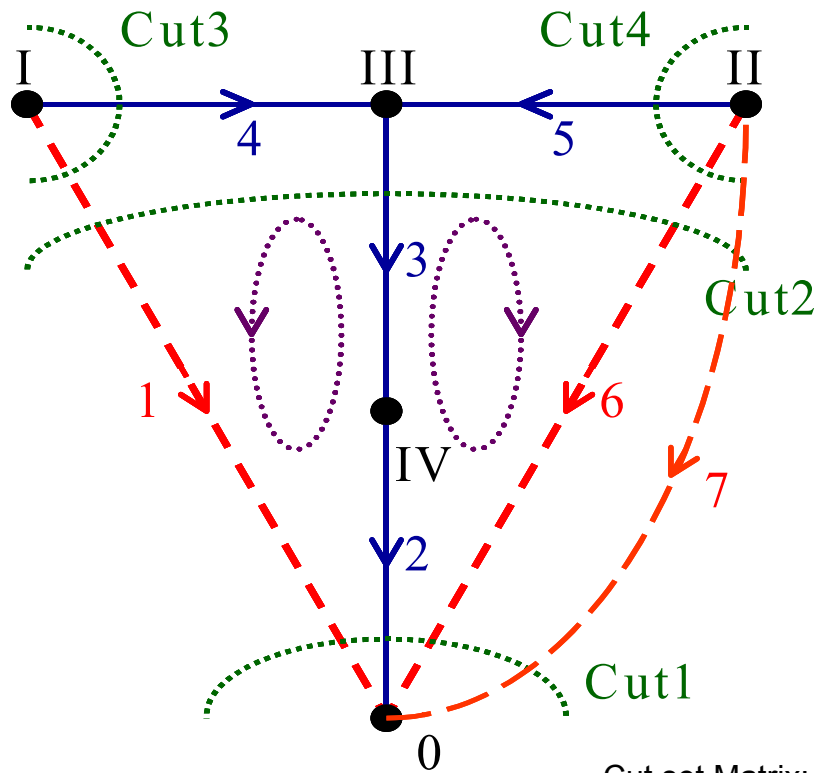c) (15) Circuit annalysis of the original and adjoint circuit: (10)
They are have the same graph.



Tree branches: 2, 3, 4, 6

Cut set 1: (1, 2, 6, 7) $i_1+i_2+i_6+i_7=0$
 Cut set 2: (1, 3, 6, 7) $i_1+i_3+i_6+i_7=0$
 Cut set 3: (1, 4) $i_1+i_4=0$
 Cut set 4: (5, 6, 7) $i_5+i_6+i_7=0$

Cut set Matrix:

$$C := \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix}$$

Tie set Matrix:

Tie set 1: (1, 2, 3, 4) $V_1-V_2-V_3-V_4=0$
 Tie set 2: (2, 3, 5, 6) $-V_2-V_3-V_5+V_6=0$

$$T := \begin{bmatrix} 1 & -1 & -1 & -1 & 0 & 0 & 0 \\ 0 & -1 & -1 & 0 & -1 & 1 & 0 \\ 0 & -1 & -1 & 0 & -1 & 0 & 1 \end{bmatrix}$$

Using equality $-C*j = -C*Y_{bb}*C^T*V_t$

$$j := \begin{bmatrix} -I_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Left := $-C*j$

I2a

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \cdot \begin{bmatrix} -I1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ I2 \end{bmatrix} = \begin{bmatrix} -I1 + I2a \\ -I1 + I2a \\ -I1 \\ I2a \end{bmatrix}$$

For original circuit, $I1=1, I2a=0$

Admittance matrix:

$$Y_{bb} := \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & s \cdot C & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{-1}{r} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{r} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{R} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

Evaluate $CY_{bb}C^T = C \cdot Y_{bb} \cdot C^T$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \cdot \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & s \cdot C & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{-1}{r} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{r} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{R} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 1 & 1 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} \frac{1}{s \cdot L} + \frac{1}{R} & \frac{1}{R} & 0 & \frac{1}{R} \\ \frac{1}{R} & s \cdot C + \frac{1}{R} & 0 & \frac{1}{R} \\ \frac{1}{R} & 0 & 0 & \frac{-1}{r} \\ 0 & 0 & 0 & \frac{1}{R} \\ \frac{1}{R} & \frac{1}{R} & \frac{1}{r} & \frac{1}{R} \end{bmatrix}$$

$$-C^*j = CY_{bbCT}^* V_b$$

$$\begin{bmatrix} I1 \\ I1 \\ I1 \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{1}{s \cdot L} + \frac{1}{R} & \frac{1}{R} & 0 & \frac{1}{R} \\ \frac{1}{R} & s \cdot C + \frac{1}{R} & 0 & \frac{1}{R} \\ 0 & 0 & 0 & -\frac{1}{r} \\ \frac{1}{R} & \frac{1}{R} & \frac{1}{r} & \frac{1}{R} \end{bmatrix} \times \begin{bmatrix} V2 \\ V3 \\ V4 \\ V5 \end{bmatrix}$$

$$CY_{bbCT}^{-1} = \begin{bmatrix} \frac{L \cdot (s \cdot C \cdot R + 1) \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{-L \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{r \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & 0 \\ \frac{-L \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{(R + s \cdot L)}{(s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C)} & \frac{r}{(s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C)} & 0 \\ \frac{-r \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{-r}{(s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C)} & \frac{r^2 \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & r \\ 0 & 0 & -r & 0 \end{bmatrix}$$

$$\begin{bmatrix} V2 \\ V3 \\ V4 \\ V5 \end{bmatrix} := CY_{bbCT}^{-1} \cdot \begin{bmatrix} I1 \\ I1 \\ I1 \\ 0 \end{bmatrix} \quad V6 := V2 + V3 + V5$$

For I1=1:

$$\begin{bmatrix} V2 \\ V3 \\ V4 \\ V5 \end{bmatrix} := CY_{bbCT}^{-1} \cdot \begin{bmatrix} 1 \\ 1 \\ 1 \\ 0 \end{bmatrix}$$

$$\begin{aligned}
 V2 &:= \frac{(R+r) \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 V3 &:= \frac{R+r}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 V4 &:= \frac{-r \cdot L \cdot C \cdot s^2 - r + r^2 \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 V5 &:= -r \\
 V6 &:= \frac{R \cdot L \cdot C \cdot s^2 + R - R \cdot r \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}
 \end{aligned}
 \quad
 VN := \left[\begin{array}{c}
 \frac{(R+r) \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 \frac{R+r}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 \frac{-r \cdot L \cdot C \cdot s^2 - r + r^2 \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\
 -r \\
 \frac{R \cdot L \cdot C \cdot s^2 + R - R \cdot r \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}
 \end{array} \right]$$

For adjoint circuit, $I_1=0$

Admittance matrix: $Y_{bba} := Y_{bb}^T$

Evaluate $CY_{bba}C^T = C \cdot Y_{bba} \cdot C^T$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \cdot \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & s \cdot C & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{r} & 0 & 0 \\ 0 & 0 & 0 & -\frac{1}{r} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{R} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 1 & 1 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix} = \begin{array}{cccc}
 \frac{1}{s \cdot L} + \frac{1}{R} & \frac{1}{R} & 0 & \frac{1}{R} \\
 \frac{1}{R} & s \cdot C + \frac{1}{R} & 0 & \frac{1}{R} \\
 0 & 0 & 0 & \frac{1}{r} \\
 \frac{1}{R} & \frac{1}{R} & -\frac{1}{r} & \frac{1}{R}
 \end{array}$$

Clearly:

$$CY_{bba}C^T := CY_{bb}C^T$$

$$-C^*j = CYbbaCT^*Vb$$

$$\begin{bmatrix} -I2a \\ -I2a \\ 0 \\ I2a \end{bmatrix} = \begin{bmatrix} \frac{1}{s \cdot L} + \frac{1}{R} & \frac{1}{R} & 0 & \frac{1}{R} \\ \frac{1}{R} & s \cdot C + \frac{1}{R} & 0 & \frac{1}{R} \\ 0 & 0 & 0 & \frac{1}{r} \\ \frac{1}{R} & \frac{1}{R} & -\frac{1}{r} & \frac{1}{R} \end{bmatrix} \times \begin{bmatrix} V2a \\ V3a \\ V4a \\ V5a \end{bmatrix}$$

$$CYbbaCT^{-1} = \begin{bmatrix} \frac{L \cdot (s \cdot C \cdot R + 1) \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{-L \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{-r \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & 0 \\ \frac{-L \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{s \cdot L + R}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{-r}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & 0 \\ \frac{r \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{r}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & \frac{r^2 \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} & -r \\ 0 & 0 & r & 0 \end{bmatrix}$$

$$\begin{bmatrix} V2a \\ V3a \\ V4a \\ V5a \end{bmatrix} := CYbbaCT^{-1} \cdot \begin{bmatrix} -I2a \\ -I2a \\ 0 \\ -I2a \end{bmatrix} \quad V6a := V2a + V3a + V5a$$

$$V2a := \frac{-R \cdot L \cdot C \cdot s^2 \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}$$

$$V5a := 0$$

$$V3a := \frac{-R \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}$$

$$V6a := \frac{-R \cdot (L \cdot C \cdot s^2 + 1) \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}$$

$$V4a := \frac{R \cdot r \cdot C \cdot s \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}$$

$$Y_{Na} := \begin{bmatrix} \frac{-R \cdot L \cdot C \cdot s^2 \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ \frac{-R \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ \frac{R \cdot r \cdot C \cdot s \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ 0 \\ \frac{-R \cdot (L \cdot C \cdot s^2 + 1) \cdot I2a}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \end{bmatrix} \quad VN := \begin{bmatrix} \frac{(R + r) \cdot L \cdot C \cdot s^2}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ \frac{R + r}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ \frac{-r \cdot L \cdot C \cdot s^2 - r + r^2 \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \\ -r \\ \frac{R \cdot L \cdot C \cdot s^2 + R - R \cdot r \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C} \end{bmatrix}$$

$$\frac{dT}{da} := \frac{1}{I2a} \cdot \left[VN_{NaT} \cdot \left(\frac{dY_N}{da} \right) \cdot VN \right]$$

Calculate sensitivity with respect to r: (5) $S(C) := \frac{r}{T} \cdot \frac{dT}{dr}$

$$a := r \quad \frac{dY_N}{dr} := \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{r^2} & 0 \\ 0 & 0 & -\frac{1}{r^2} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \frac{dT}{dr} := \frac{1}{I2a \cdot r^2} \cdot (V4a \cdot V5 - V5a \cdot V4)$$

$$\frac{dT}{dr} := \frac{-R \cdot C \cdot s}{s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C}$$

$$S(C) := \frac{-r \cdot C \cdot s}{L \cdot C \cdot s^2 + 1 - r \cdot C \cdot s}$$

d) (5) Calculate sensitivity with respect to C $S(C) := \frac{C}{T} \cdot \frac{dT}{dC}$

$$a := C \quad \frac{dY_N}{dC} := \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & s & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \frac{dT}{dC} := \frac{1}{I2a} \cdot V3a \cdot s \cdot V3 \quad \frac{dT}{dC} := \frac{-R \cdot (R + r) \cdot s}{(s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C)^2}$$

$$S(C) := \frac{-(R + r) \cdot C \cdot s}{(s \cdot C \cdot R + 1 + s^2 \cdot L \cdot C) \cdot (L \cdot C \cdot s^2 + 1 - r \cdot C \cdot s)}$$