

Tree branches: 2, 3, 4, 6

Cut set 1: (1, 2, 6)  $i_1+i_2+i_6=0$   
 Cut set 2: (1, 3, 6)  $i_1+i_3+i_6=0$   
 Cut set 3: (1, 4)  $i_1+i_4=0$   
 Cut set 4: (5, 6)  $i_5+i_6=0$

Cut set Matrix:

$$C := \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

Tie set 1: (1, 2, 3, 4)  $V_1-V_2-V_3-V_4=0$   
 Tie set 2: (2, 3, 5, 6)  $-V_2-V_3-V_5+V_6=0$

Tie set Matrix:

$$T := \begin{bmatrix} 1 & -1 & -1 & -1 & 0 & 0 \\ 0 & -1 & -1 & 0 & -1 & 1 \end{bmatrix}$$

a) (10)  
 State Vector:  $X := \begin{bmatrix} V3 \\ i2 \\ V6 \end{bmatrix}$

KCL:  $i2 - i3 := 0 \quad i3 := i2$

$i3 := C \cdot s \cdot V3$

Equation 1):  $s \cdot V3 := \frac{1}{C} \cdot i2$

KVL:  $-V2 - V3 - V5 + V6 := 0 \quad V2 := -V3 - V5 + V6$

$$\begin{bmatrix} V4 \\ V5 \end{bmatrix} := \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix} \cdot \begin{bmatrix} i4 \\ i5 \end{bmatrix} \quad \begin{bmatrix} V4 \\ V5 \end{bmatrix} := \begin{bmatrix} r \cdot i5 \\ -r \cdot i4 \end{bmatrix}$$

$V2 := V3 - r \cdot i4 - V6$

KCL:  $i1 + i4 := 0 \quad i4 := -i1 \quad i1 := -I1 \quad i4 := I1$

$V2 := -V3 + V6 + r \cdot I1$

$V2 := L \cdot s \cdot i2$

Equation 2):  $s \cdot i2 := \left( \frac{-1}{L} \cdot V3 + \frac{1}{L} \cdot V6 \right) + \frac{r}{L} \cdot I1$

KCL:  $i1 + i2 + i6 := 0 \quad i1 := -I1 \quad i6 := \frac{V6}{R}$

Equation 3):  $R \cdot i2 + V6 - R \cdot I1 := 0$

$$s \cdot \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V6 \end{bmatrix} := \begin{bmatrix} 0 & \frac{1}{C} & 0 \\ \frac{-1}{L} & 0 & \frac{1}{L} \\ 0 & R & 1 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V6 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{r}{L} \\ -R \end{bmatrix} \cdot I1$$

Semistate Equations:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \frac{d}{dt} \begin{bmatrix} V3 \\ i2 \\ V6 \end{bmatrix} := \begin{bmatrix} 0 & \frac{1}{C} & 0 \\ \frac{-1}{L} & 0 & \frac{1}{L} \\ 0 & R & 1 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V6 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{r}{L} \\ -R \end{bmatrix} \cdot I1$$

$y := (0 \ 0 \ 1) \cdot X$

b) (15)  
 State Vector:  $X := \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix}$

KVL:  $V1 - V4 + V5 - V6 := 0$

$$\begin{bmatrix} V4 \\ V5 \end{bmatrix} := \begin{bmatrix} r \cdot i5 \\ -r \cdot i4 \end{bmatrix} \quad V6 := V1 - r \cdot (i4 + i5)$$

KCL:  $i4 + i5 - i3 := 0 \quad i4 + i5 := i2$

$$i2 - i3 := 0$$

$$V6 := V1 - r \cdot i2$$

Plug V6 in equation 2) and 3):

Equation 1): stays the same:  $s \cdot V3 := \frac{1}{C} \cdot i2$

Equation 4) (from Equation 2)):

$$s \cdot i2 := \left( \frac{-1}{L} \cdot V3 - \frac{r}{L} \cdot i2 + \frac{1}{L} \cdot V1 \right) + \frac{r}{L} \cdot I1$$

Equation 5) (from Equation 3)):

$$(R - r) \cdot i2 + V1 - R \cdot I1 := 0$$

$$s \cdot \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} := \begin{bmatrix} 0 & \frac{1}{C} & 0 \\ \frac{-1}{L} & \frac{-r}{L} & \frac{1}{L} \\ 0 & R - r & 1 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{r}{L} \\ -R \end{bmatrix} \cdot I1$$

Semistate Equations:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix} \cdot \frac{d}{dt} \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} := \begin{bmatrix} 0 & \frac{1}{C} & 0 \\ \frac{-1}{L} & \frac{-r}{L} & \frac{1}{L} \\ 0 & R - r & 1 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{r}{L} \\ -R \end{bmatrix} \cdot I1$$

$$y := (0 \ 0 \ 1) \cdot X$$

$$\begin{bmatrix} s & -\frac{1}{C} & 0 \\ \frac{1}{L} & s + \frac{r}{L} & -\frac{1}{L} \\ 0 & r - R & -1 \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} := \begin{bmatrix} 0 \\ \frac{r \cdot I1}{L} \\ -R \cdot I1 \end{bmatrix}$$

$$\begin{bmatrix} V3 \\ i2 \\ V1 \end{bmatrix} := \begin{bmatrix} \frac{(s \cdot L + R) \cdot C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{L}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{-1}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} \\ \frac{-C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{s \cdot L \cdot C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{-s \cdot C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} \\ \frac{(R - r) \cdot C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{-s \cdot (R - r) \cdot L \cdot C}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} & \frac{-(s^2 \cdot C \cdot L + s \cdot C \cdot r + 1)}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ \frac{r \cdot I1}{L} \\ -R \cdot I1 \end{bmatrix}$$

$$V1 := \frac{R \cdot L \cdot C \cdot s^2 + r^2 \cdot C \cdot s + R}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1} \cdot I1 \quad Z_{in} := \frac{V1}{I1}$$

Input impedance:

$$Z_{in} := \frac{R \cdot L \cdot C \cdot s^2 + r^2 \cdot C \cdot s + R}{s^2 \cdot C \cdot L + s \cdot C \cdot R + 1}$$

Equation 1):  $s \cdot V3 := \frac{1}{C} \cdot i2$

Equation 5):  $(R - r) \cdot i2 + V1 - R \cdot I1 := 0$

$V1 := -(R - r) \cdot i2 + R \cdot I1$  Plug in Equation 4.

Equation 6) (from Equation 4)

$$s \cdot i2 := \left( \frac{-1}{L} \cdot V3 - \frac{R}{L} \cdot i2 \right) + \frac{R + r}{L} \cdot I1$$

State Equations:

$$\frac{d}{dt} \begin{bmatrix} V3 \\ i2 \end{bmatrix} := \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \cdot \begin{bmatrix} V3 \\ i2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{R + r}{L} \end{bmatrix} \cdot I1$$

c) and d) (15)

$$\begin{bmatrix} x_1 \\ x_2 \end{bmatrix} := \begin{bmatrix} V_3 \\ i_2 \end{bmatrix} \quad \begin{matrix} r := 2 & L := 2 \\ C := 2 & R := 2 \end{matrix}$$


$$\text{Output } V_1(t) = V_6 = -R \cdot i_2 + R \cdot I_1$$

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} := \begin{bmatrix} 0 & 0.5 \\ -0.5 & -1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} \cdot I_1$$

$$\frac{dx_1}{dt} := 0.5 \cdot x_2$$

$$\frac{dx_2}{dt} := -0.5 \cdot x_1 - x_2 + 2 \cdot I_1$$
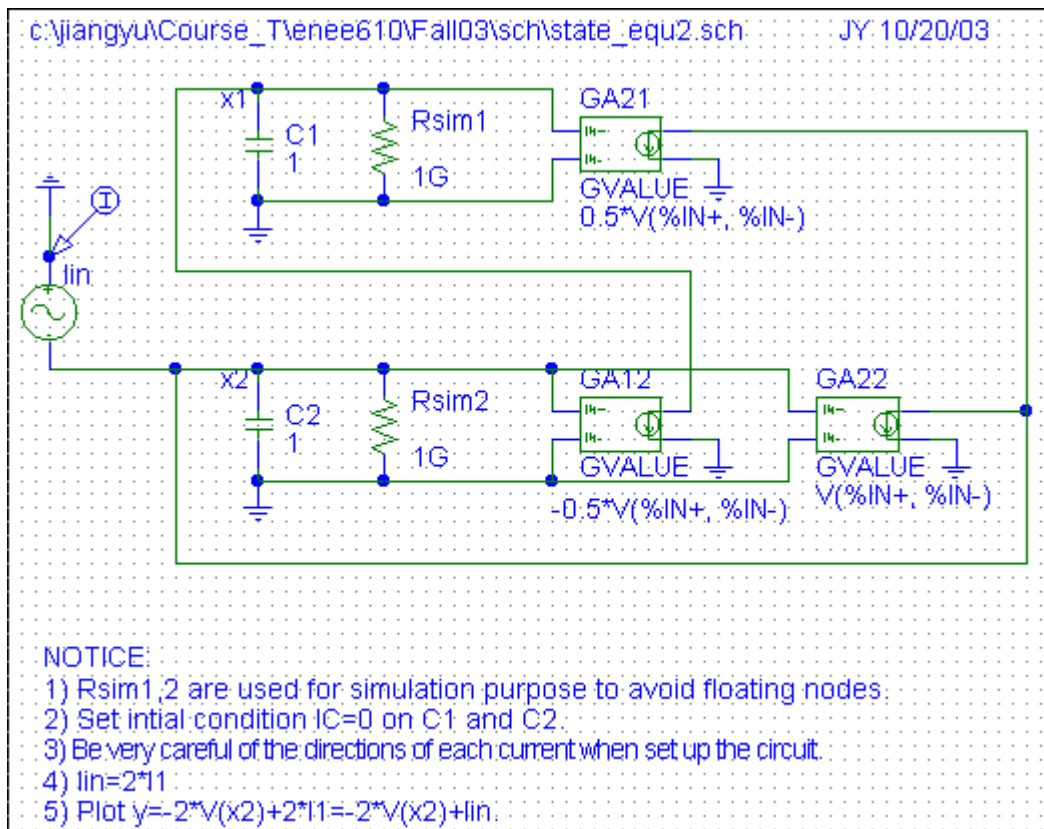
$$y := (0 \quad -2) \cdot X + 2 \cdot u$$



Simulation results:

