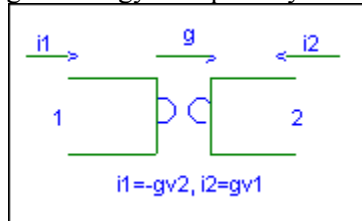


ENEE 610 Fall 2003 Final exam

2 hours (=120minutes), 120 points total, open book, open notes. If stuck on a problem, go on to the next. Show your work for partial credit. Good luck!

For the following use the gyrator polarity as



1. (40points, 30 minutes) [PR and synthesis]



Consider the rational driving point admittance where n and d are finite real parameters:

$$y(s) = \frac{ns^2 + 3s + 1}{ds + 1}$$

- Give the set of n and d such that this y(s) is positive real.
- Give the set of n and d such that this y(s) is lossless.
- Give a synthesis for all y(s) that are positive real.
- Give a synthesis for all y(s) including those which are not positive real.

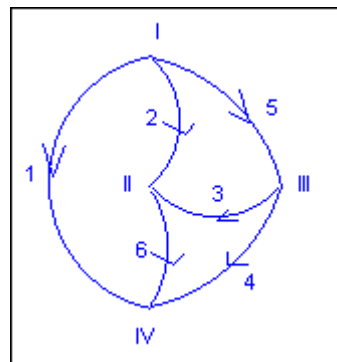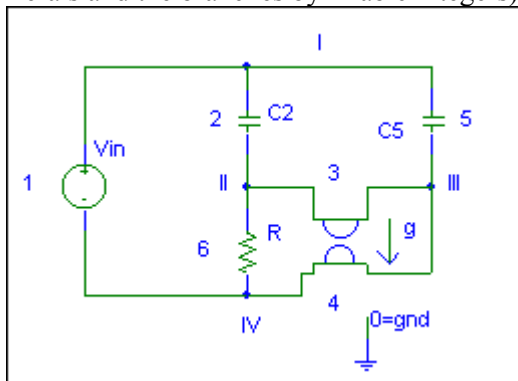2. (40points, 40 minutes) [graph, admittance matrices, transfer function]

For the following bridge circuit and the corresponding given graph (the nodes are numbered by Roman numerals and the branches by Arabic integers) [choose branches 1, 2, 3 as the tree]




- Give the cut-set matrix.
- Give the tie-set matrix.
- Give the indefinite admittance matrix, Y_{ind} , for the circuit to the right of V_{in} .
- Give the resulting 3-terminal Y matrix when node $IV=0=gnd$.
- Assuming $C2=C5=C>0$ find the transfer function V_o/V_{in} where $V_o=v_{III}-v_{II}$ (with $v_{IV}=v_{gnd}=0$).
- Assuming that g can vary find those g and s for which the bridge is balanced, that is $V_o=0=i_3$, and from that state a use for the circuit.

3. (40points, 40 minutes) [from papers presented] Choose one of the following two (I or II)

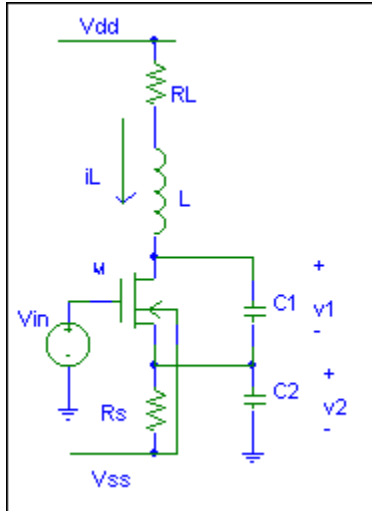I. [nonlinear state variables]

For the Colpitts Oscillator chaos generator of M. P. Kennedy, in the paper presented by A. Jaleel, replace the BJT by an NMOS transistor and add an input $v_{in}=u$ as shown below.



Assume that there is some nonlinear function $f(\dots)$ such that the transistor is described by

$$i_G = i_B = 0$$

$$i_D = f(v_{GS}, v_{DS})$$

a) Using the drain voltage (with respect to ground) as the output, $y=v_1+v_2$, set up the state variable equations in the form

$$\frac{dx}{dt} = Ax + F(x, u) + Bu, \quad x = \begin{bmatrix} i_L \\ v_1 \\ v_2 \end{bmatrix}, u = v_{in}$$


$$y = Cx$$

b) Under the assumptions that the nonlinear transistor is replaced by a linear voltage controlled current source with $i_G=0$, $i_D=g_m v_{GS}$ and that $v_{in}=0$, can the resulting circuit exhibit chaos?

II. [synthesis with op-amps]

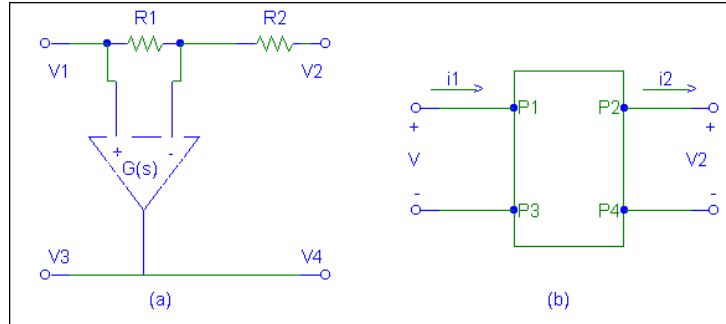
- a) For the following circuit on the left, find the mixed matrix A_1 for $\begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = A_1 \cdot \begin{bmatrix} V_2 \\ V_4 \end{bmatrix}$. The op-amp has

$$V_o = G(s) \cdot (V_+ - V_-) \text{ with } G(s) = \frac{G_0}{a \cdot s + 1}.$$



- b) For the network (b) on the right of the above, if $\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = A_1 \cdot \begin{bmatrix} V_2 \\ i_2 \end{bmatrix}$ with the matrix A_1 found in a), give an RL synthesis and give the value of each element in terms of the circuit elements in (a). V_1 , i_1 , V_2 , and i_2 , have the signs and directions as shown in the right circuit above.

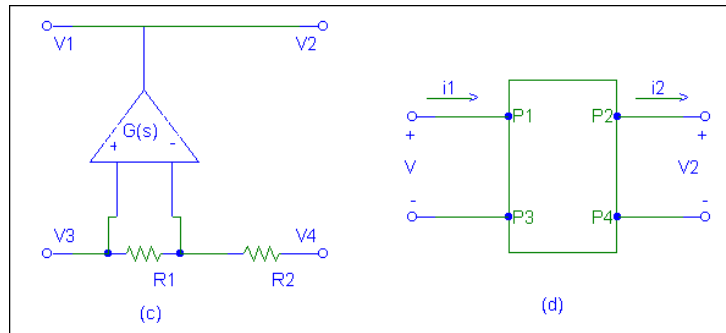- c) For the following circuit find the mixed matrix A_2 $\begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = A_2 \cdot \begin{bmatrix} V_2 \\ V_4 \end{bmatrix}$.



- d) For the network in (d) of the last figure, if $\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = A_2 \cdot \begin{bmatrix} V_2 \\ i_2 \end{bmatrix}$ with the matrix A_2 found in c), give an RC synthesis and the value of each element in terms of the circuit elements in (c).

- e) For the following circuit, find the transfer function $T(s) = \frac{V_o}{V_{in}}$.

