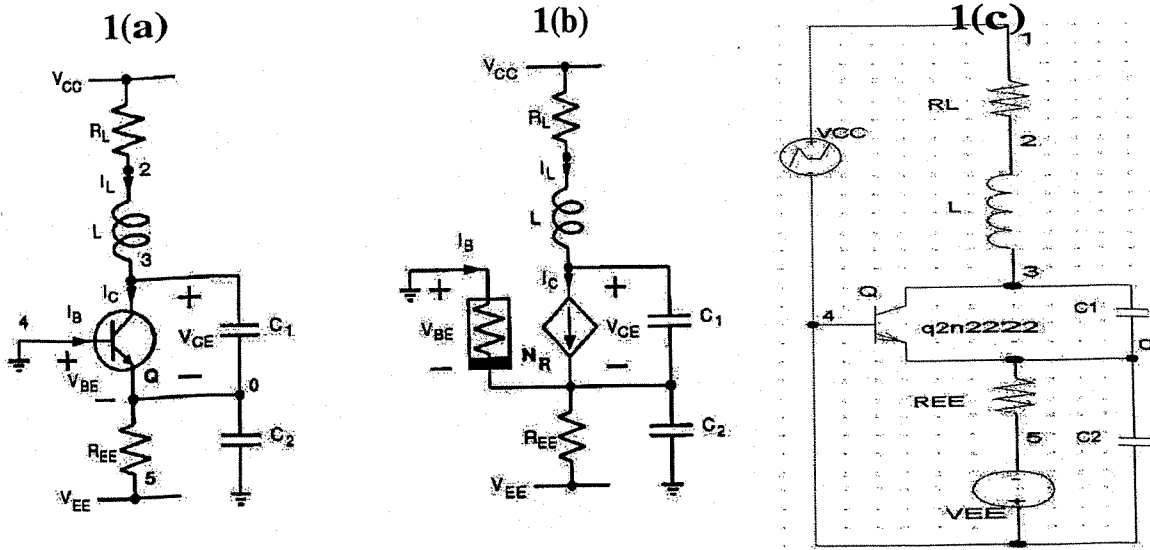


# Chaos in the Colpitts Oscillator

Michael Peter Kennedy -- Presented By Aamer Jaleel



## 1 Objective:

- Colpitts Oscillator can exhibit chaos
- Chaos is NOT a parasitic effect
- Present a 3rd order autonomous circuit model using a two-segment piecewise-linear resistor

## 2 Colpitts Oscillator

### BJT Circuit 1(a) , Pspice Schematic 1(c)

- BJT biased in active region via  $V_{EE}$ ,  $R_{EE}$ , and  $V_{CC}$ .
- Feedback network consists of inductor  $L$  with series resistance  $R_L$ , and capacitive divider  $C_1$  and  $C_2$ .

### Equivalent Circuit

- Assume BJT operates as a purely resistive element
- BJT operates in two regions: forward active and cutoff, oscillator can be modeled using **Figure 1(b)** where BJT is modeled as a linear current-controlled current source  $I_C$ , and a single voltage-controlled **nonlinear** resistor  $N_R$ .

$$I_B = \begin{cases} 0 & \text{if } V_{BE} < V_{TH} \\ \frac{V_{BE} - V_{TH}}{R_{ON}} & \text{if } V_{BE} > V_{TH} \end{cases} \quad I_C = \beta_F \cdot I_B$$

## 3 Circuit Equations

- Three state variables:  $V_{C1}(x_1) = V_{CE}$ ,  $V_{C2}(x_2) = -V_{BE}$ ,  $I_L(x_3)$

$$C_1 \cdot \dot{x}_1 = x_3 - I_C \quad C_2 \cdot \dot{x}_2 = \frac{V_{EE} + V_{BE}}{R_{EE}} + x_3 - I_B \quad L \cdot \dot{x}_3 = V_{CC} - x_1 + x_2 - x_3 R_L$$

- Third order circuit model in terms of  $V_{BE}$ :

$$A \ddot{x}_2 + B \dot{x}_2 + C \cdot x_2 - (\alpha \cdot f(x_2)) = 0$$