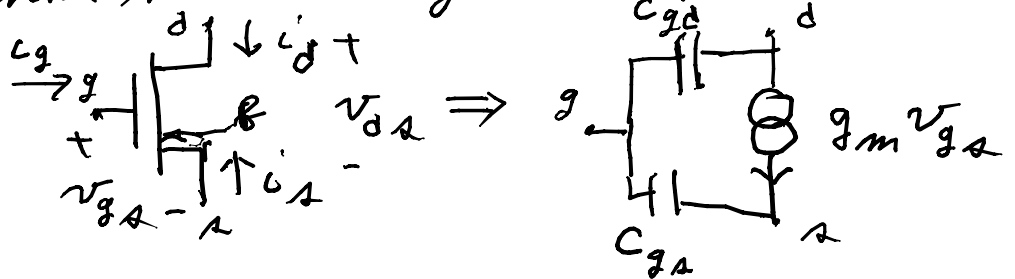


Small signal behaviors for the previous circuit



For small frequencies - ignore the capacitors
 assume transistors in saturation, ignore
 Early effect $\Rightarrow \lambda = 0$

$$i_D = \beta (v_{GS} - V_{th})^2 = I_D + \left. \frac{\partial I_D}{\partial v_{GS}} \right|_{(v_{GS} - V_{th})} + \dots$$

$$i_d = i_D - I_D = \left. \frac{\partial I_D}{\partial v_{GS}} \right|_{v_{GS} \text{ bias}} + (\text{higher order})$$

\rightarrow ignore for $|v_{gs}|$ small



$$\approx g_m v_{gs}$$

g_m is found at $I_D = I_0$


$$g_m = 2\beta (v_{GS} - V_{th}) \Big|_{v_{GS} = V_{GS}} = \frac{2I_0}{(v_{GS} - V_{th})}, \quad v_{GS} - V_{th} = \sqrt{\frac{I_0}{\beta}}$$

$$\beta = \frac{K_P W}{2L}, \quad V_{th} = V_{TO}$$
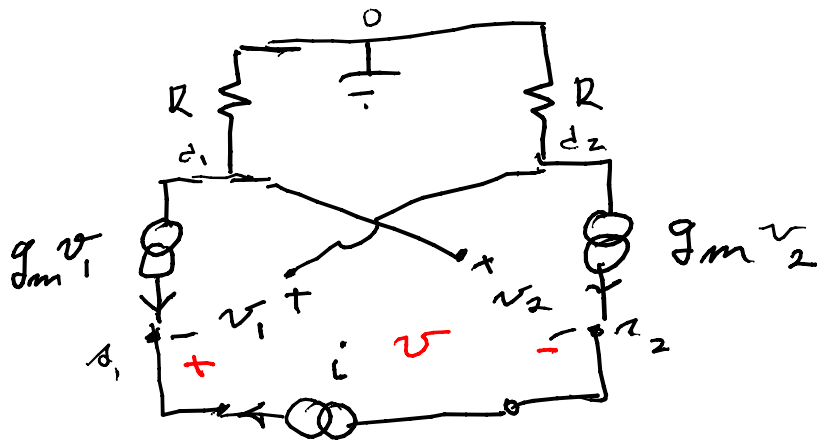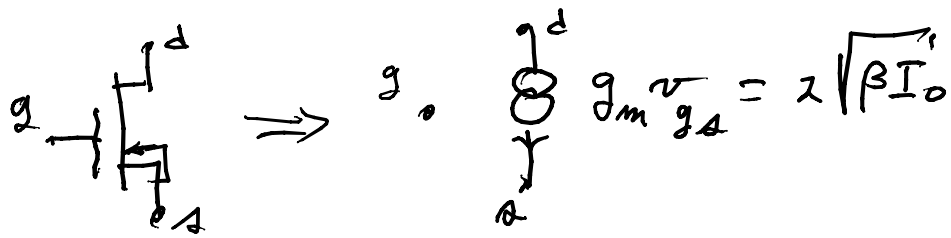
$$= \frac{2I_0}{\sqrt{I_0/\beta}} = 2\sqrt{\beta I_0}$$



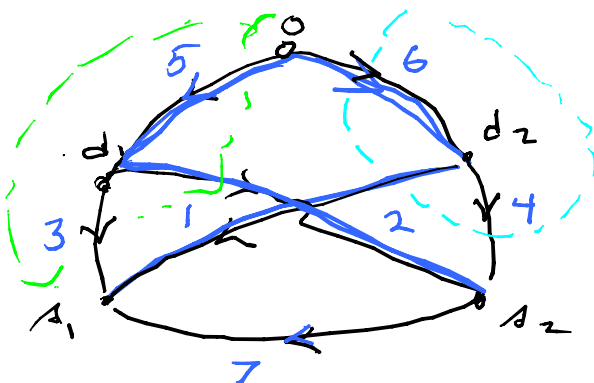$\frac{v}{i} = Z_{in}$ seen by the capacitor




$b = 7$
 $n = 5, t = 4 = n - 1$
 $l = 3, l = b - t$

Cut set eqs:
$$\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix} \Rightarrow 0 = C i_b$$

Tie set eqs.
$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & -1 & 0 & 1 & -1 & 1 & 0 \\ -1 & 1 & 0 & 0 & +1 & -1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \end{bmatrix} \Rightarrow 0 = T v_b$$

$$p = v_b^T i_b = v_t^T C v^T i_R = 0$$
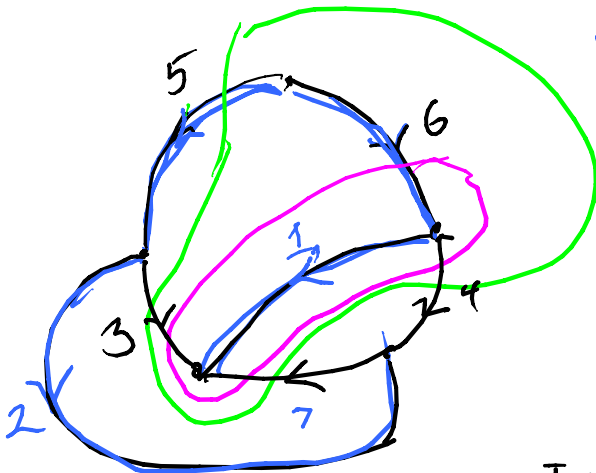
$$= \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} -1 & 0 & -1 \\ 0 & -1 & -1 \\ -1 & -1 & -1 \\ 0 & 0 & -1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & -1 \end{bmatrix}$$



3rd eq

$$0 = [0 \ 0 \ -1 \ 1 \ 1 \ 0 \ -1] i_b$$

4th eq.

$$0 = [0 \ 0 \ 1 \ -1 \ 0 \ 1 \ 1] i_b$$

$$v_b = C^T v_t, \quad i_b = v^T i_R$$

Component equations: $i_{1b} = 0, \quad i_{2b} = 0$ as opens

$$\frac{i}{(b)} = Y_{b \times b} \cdot v_{(b)}$$

$$i_{3b} = g_m v_{1b}, \quad i_{4b} = g_m v_{2b}$$

$$G = 1/R \quad i_{5b} = G v_{5b}, \quad i_{6b} = G v_{6b}$$

$$i_{b7} = 0 + i$$

here

$$Y_{b \times b} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ g_m & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & G & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}; \quad i = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ i \end{bmatrix}$$

$$\begin{aligned}
 v_b = v + e = 0 & \quad ; \quad i_b = i + j & \quad ; \quad 0 = e i_b \\
 = v & & = \sum_{b \times b} y_{b \times b} v + j \\
 = e^T v_t & & = \sum^T i_g \\
 & \downarrow & \\
 e i_b = 0 = \underbrace{e y_{b \times b} e^T}_{t \times t} v_t + e j
 \end{aligned}$$

t eqs in t

unknowns, v_t ; t eqs in t unknowns

$$-e j = (e y_{b \times b} e^T) v_t$$

equivalent
sources in
tree branches

tree branch
admittance