

corrected

610_091504 e

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ g_m & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & G & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & G \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & -1 & -1 & 1 \end{bmatrix} = e y e^T$$

$$= \begin{bmatrix} g_m & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 & 0 & 0 & 0 \\ -g_m & g_m & 0 & 0 & G & 0 & 0 \\ g_m & -g_m & 0 & 0 & 0 & G & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & -1 & -1 & 1 \end{bmatrix} = \begin{bmatrix} g_m & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 \\ -g_m & g_m & G & 0 \\ g_m & -g_m & 0 & G \end{bmatrix}$$

$$-e_j = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ i \end{bmatrix} = \begin{bmatrix} -i \\ i \\ i \\ i \\ -i \end{bmatrix}$$

$\therefore -e_j = e y_{br6} e^T v_t$ is
to solve for v_t

$$\begin{bmatrix} -i \\ i \\ i \\ i \\ -i \end{bmatrix} = \begin{bmatrix} g_m & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 \\ -g_m & g_m & G & 0 \\ g_m & -g_m & 0 & G \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_5 \\ v_6 \end{bmatrix}$$

add 1st row to 3rd
then subtract 2nd from 3rd, then add 2nd to fourth
and finally subtract 1st row from 4th

This gives

$$\begin{bmatrix} -i \\ i \\ -i \\ i \end{bmatrix} = \begin{bmatrix} g_m & 0 & 0 & 0 \\ 0 & g_m & 0 & 0 \\ 0 & 0 & G & 0 \\ 0 & 0 & 0 & G \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_5 \\ v_6 \end{bmatrix} \Rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} -i/g_m \\ i/g_m \\ -i/G \\ i/G \end{bmatrix}$$



From the tie set matrix $0 = -v_1 + v_2 + v_5 - v_6 + v_7$

$$\text{or } v_7 = -v_2 = -v_1 + v_2 + v_5 - v_6 = \frac{i}{g_m} + \frac{i}{g_m} - \frac{i}{G} - \frac{i}{G} = \left(\frac{2}{g_m} - \frac{2}{G}\right)i$$

$$\text{or } \frac{v}{i} = Z_{in} = 2\left(\frac{1}{g_m} - \frac{1}{G}\right) \quad \text{note: } Z_{in} < 0 \text{ if } R > 1/g_m$$

$$= 2\left(\frac{1}{g_m} - R\right)$$

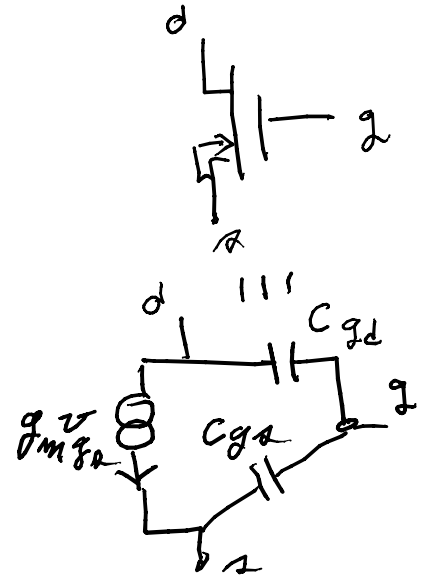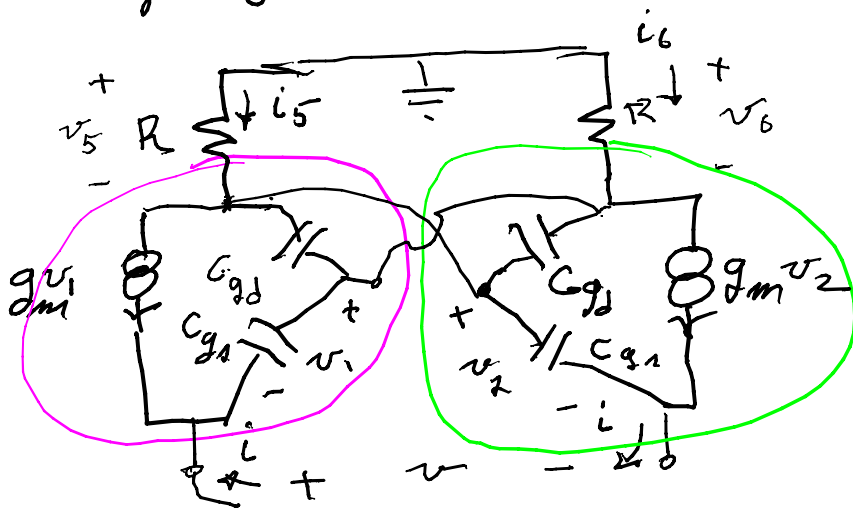To get $Z(s)$, insert transistor capacitors (small signal)



$$1) \quad i = -g_m v_1 - sC_{gs} v_1 = -(g_m + sC_{gs}) v_1$$

$$= g_m v_2 + sC_{gs} v_2 = (g_m + sC_{gs}) v_2 \Rightarrow v_2 = -v_1$$

$$2) \quad 0 = -v - v_1 - v_6 + v_5 + v_2 \Rightarrow v = -2v_1 + v_5 - v_6$$

$$i_5 = (R)v_5 = g_m v_1 + sC_{gd}(v_2 - v_1) + sC_{gd}(v_2 - v_1) + sC_{gs} v_2$$

$$= (g_m - 4sC_{gd} - sC_{gs}) v_1 - 2sC_{gd} v$$

$$3) \quad i_6 = (R)v_6 = (g_m v_2 + sC_{gd}(v_1 - v_2) + sC_{gd}(v_1 - v_2) + sC_{gs} v_1) + 2sC_{gd} v$$

$$= (-g_m + 4sC_{gd} + sC_{gs}) v_1 = -i_5 \Rightarrow v_5 = -v_6$$

$$2) \quad v = -2v_1 + v_5 - v_6 = -2v_1 - 2v_6 = -2(v_1 + v_6)$$

inserted page

4) from 3) $i_6 = -i_5$, $v_8 = -v_5$, $v_6 = [-g_m R + \alpha R(4C_{gd} + C_{gs})]v_1 + 2R\alpha C_{gd}v$


5) from 2) & 1) $v = -2[1 - g_m R + \alpha R(4C_{gd} + C_{gs})] \left[\frac{-i}{g_m + \alpha C_{gs}} \right] - 4\alpha R C_{gd} v$

which is

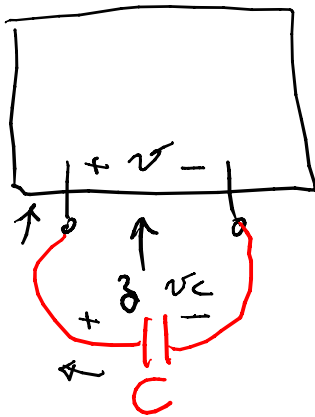6) $\frac{v}{i} = z(s) = \frac{2[(1 - g_m R) + \alpha R(4C_{gd} + C_{gs})]}{(g_m + \alpha C_{gs})(1 + \alpha 4RC_{gd})}$

two real LHP poles, at $s_1 = -\frac{g_m}{C_{gs}}$ & $s_2 = -\frac{1}{4RC_{gd}}$

one zero at ∞ and one real zero, at $s_3 = -\frac{(1 - g_m R)}{R(4C_{gd} + C_{gs})}$ [may be in RHP if $g_m R > 1$]



$$v - v_c = 0 \Rightarrow \left(z(s) + \frac{1}{sC} \right) \cdot i = 0$$

$$\begin{matrix} \text{"} & \text{"} \\ z(s) \cdot i & -\frac{1}{sC} \cdot i \end{matrix}$$

look for zeros of $\left(z(s) + \frac{1}{sC} \right)$; nonzero i can then flow

i.e. zeros of $z(s) + \frac{1}{sC}$ are the natural frequencies

from 6)

$$\frac{2[(1 - g_m R) + \alpha R(4C_{gd} + C_{gs})]}{(g_m + \alpha C_{gs})(1 + \alpha 4RC_{gd})} + \frac{1}{sC} = \frac{N(s)}{D(s)}$$

Zeros are zeros of

7) $N(s) = 2sC[(1 - g_m R) + \alpha R(4C_{gd} + C_{gs})] + [g_m + \alpha(C_{gs} + 4g_m RC_{gd}) + \alpha^2 4RC_{gs}C_{gd}]$
 $= \alpha^2 [2RC(4C_{gd} + C_{gs}) + 4RC_{gs}C_{gd}] + \alpha [2C(1 - g_m R) + C_{gs} + 4g_m RC_{gd}] + g_m$

For $N(s) = \alpha[s^2 + \omega_0^2]$, oscillations, we want the coefficient of $\alpha \Rightarrow 0$:

8) $\therefore 2C(1 - g_m R) + (C_{gs} + 4g_m RC_{gd}) = 0$

which is

$$9) \quad g_m R = \frac{-2C - C_{gs}}{-2C + 4C_{gd}} \Rightarrow R = \frac{1}{g_m} \cdot \frac{2C + C_{gs}}{2C - 4C_{gd}} > \frac{1}{g_m}$$

as $R > 1/g_m$ is the condition for $\Re(\omega) < 0$ we see it is the negative resistance which allows small signal oscillations. Under the condition 9) the oscillation frequency is, from 7)

$$10) \quad \omega_0 = 2\pi f_0 = \sqrt{\frac{g_m}{2R [C(4C_{gd} + C_{gs}) + 2C_{gs}C_{gd}]}}$$
$$= g_m \sqrt{\frac{2C - 4C_{gd}}{2(2C + C_{gs}) [C(4C_{gd} + C_{gs}) + 2C_{gs}C_{gd}]}}$$

which, as, $g_m = 2\sqrt{\beta I_0}$, can be adjusted by I_0 (if also R is, by 9))