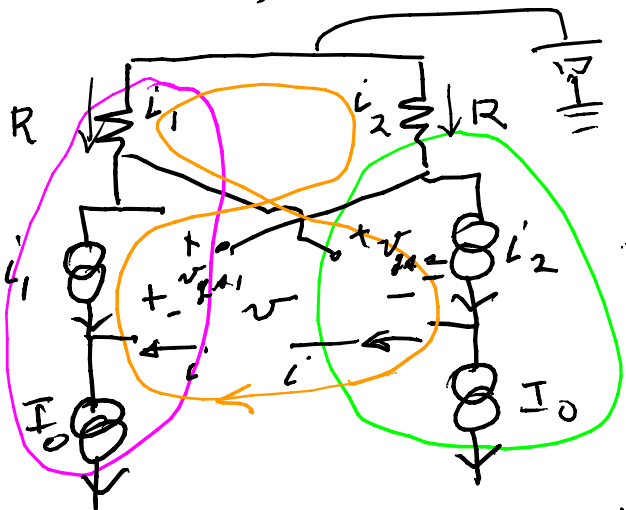


at DC, nonlinear



$$i_1 = I_0 - i = \beta (v_{gs1} - V_{th})^2$$

$$i_2 = I_0 + i = \beta (v_{gs2} - V_{th})^2$$

$$\Rightarrow v_{gs1} = V_{th} + \sqrt{\frac{I_0 - i}{\beta}} = V_{th} + \sqrt{\frac{I_0}{\beta}} \sqrt{1 - \frac{i}{I_0}}$$

$$v_{gs2} = V_{th} + \sqrt{\frac{I_0 + i}{\beta}} = V_{th} + \sqrt{\frac{I_0}{\beta}} \sqrt{1 + \frac{i}{I_0}}$$

$$g_m = 2\sqrt{\beta I_0}$$

KVL  $\Rightarrow 0 = -v - v_{gs1} - Ri_2 + Ri_1 + v_{gs2}$


$$\Rightarrow v = \sqrt{\frac{I_0}{\beta}} \left( \sqrt{1 + \frac{i}{I_0}} - \sqrt{1 - \frac{i}{I_0}} \right) + R(i_1 - i_2)$$

$$= R(-2i) + \frac{2}{2} \sqrt{\frac{I_0^2}{\beta I_0}} \left( \sqrt{1 + \frac{i}{I_0}} - \sqrt{1 - \frac{i}{I_0}} \right)$$

$$= 2 \left\{ -Ri + \frac{I_0}{g_m} \left( \sqrt{1 + \frac{i}{I_0}} - \sqrt{1 - \frac{i}{I_0}} \right) \right\}$$

near  $i = 0$ ;  $|i/I_0| \ll 1 \in$  small


$$\sqrt{1+x} = 1 + \frac{x}{2} + \dots, \quad |x| \text{ small}$$

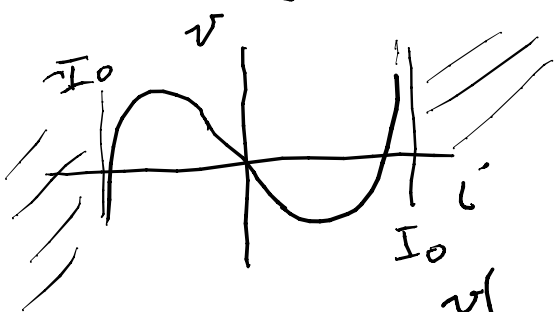

$$v \Big|_{\text{small}} = 2 \left( -Ri + \frac{I_0}{g_m} \left[ 1 + \frac{1}{2} \frac{i}{I_0} - \left( 1 - \frac{1}{2} \frac{i}{I_0} \right) \right] \right)$$

$$= 2 \left( -Ri + \frac{I_0}{g_m} \left[ \frac{i}{I_0} \right] \right) = 2i \left( -R + \frac{1}{g_m} \right)$$

Ideal transformer

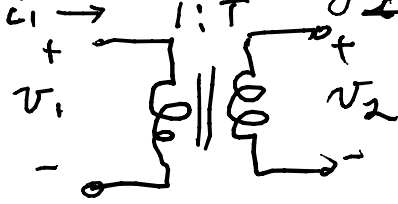

$$v_2 = T v_1 \Rightarrow T v_1 - v_2 = 0$$

$$P_{in} = 0 = v_1 i_1 + v_2 i_2$$

$$= v_1 i_1 + T v_1 i_2$$

$$= v_1 (i_1 + T i_2)$$

if for any  $v_1$ , then


$$i_1 + T i_2 = 0 \Rightarrow i_1 = -T i_2$$

$$i \neq Y v; \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = i, \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = v$$

$$\begin{bmatrix} T & -1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & T \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow \boxed{A v = B i}$$

$$i = Y v \Rightarrow B^{-1} B i = B^{-1} A v = i; Y = B^{-1} A$$

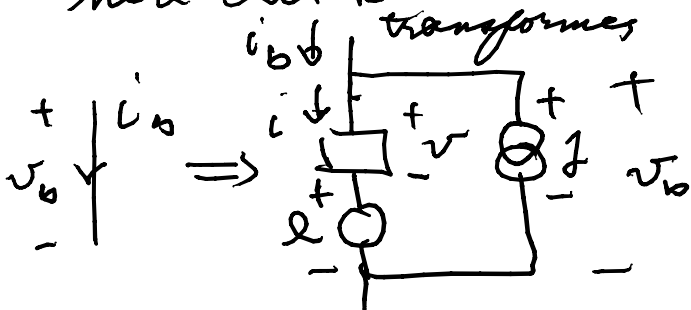here  $\det B = 0$  so no  $B^{-1}$  exists



$$v_b = v + \ell \quad \ell = "e"$$

$$i_b = i + j$$

$$0 = e i_b \quad v_b = e^T v_t$$

$$0 = \sigma v_b \quad i_b = \sigma^T i_\ell$$

$$A v = A(v_b - \ell) \Rightarrow A(e^T v_t - \ell) = B(\sigma^T i_\ell - j)$$

$$B i = B(i_b - j)$$

$$A e^T v_t - B \sigma^T i_\ell = A \ell - B j$$



$$b \left\{ \begin{bmatrix} A e^T & -B \sigma^T \end{bmatrix} \begin{bmatrix} v_t \\ i_\ell \end{bmatrix} = A \ell - B j = \text{source terms} \right.$$

$\underbrace{\quad}_t \quad \underbrace{\quad}_\ell$   
 $b = t + \ell$



gives  $b$  equations in  $b$  unknowns ( $v_t$  &  $i_\ell$ )

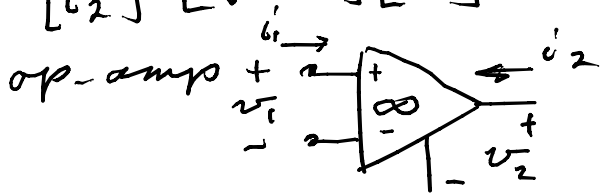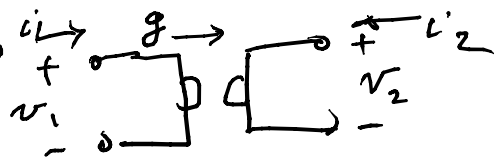Example: use a gyrator  $i_1 \rightarrow$   $g \rightarrow$   $i_2$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


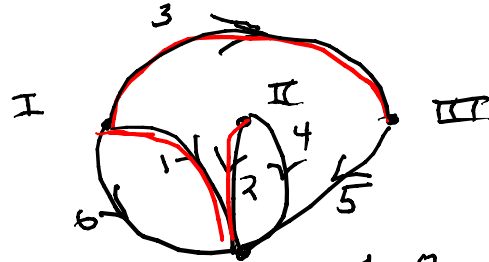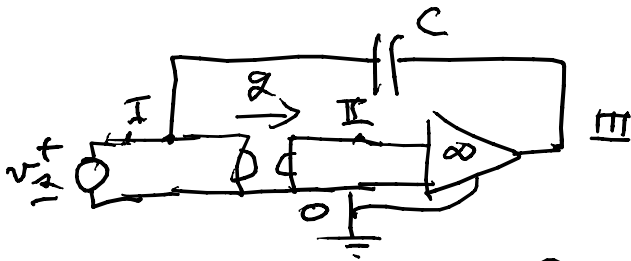
$$\begin{matrix} v_1 = 0 \\ i_1 = 0 \end{matrix} \Rightarrow \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ -g & g & 0 & 0 & 0 & 0 \\ 0 & 0 & AC & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} \quad \begin{matrix} j=0 \\ r=0 \end{matrix} \quad \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\text{KVL: } \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \underline{0} = C i_6$$

For homework, problem #1, use branches 3, 4, 5, 6 as the tree