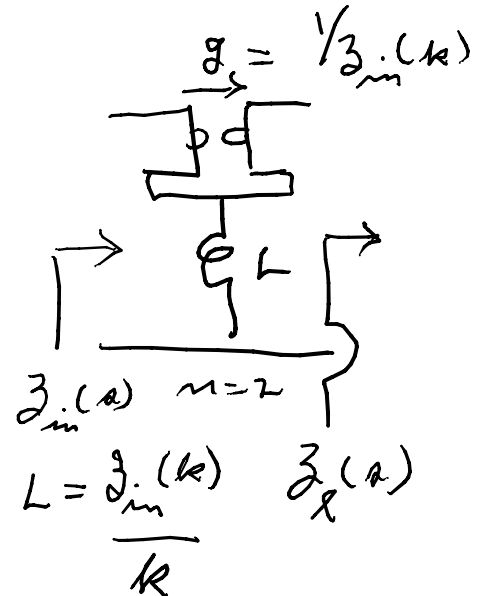


$$Z_L(s) = Z_{in}(k) \left[\frac{\left(\frac{a}{k}\right) \left(\frac{Z_{in}(s)}{Z_{in}(k)}\right) - 1}{\left(\frac{a}{k}\right) - \left(\frac{Z_{in}(s)}{Z_{in}(k)}\right)} \right]$$



if $Z_{in}(k) + Z_{in}(-k) = 2 \operatorname{Re} Z_{in}(a) \Big|_{a=k}$

then $\delta[Z_L(s)] = \delta[Z_{in}(s)] - 1$

If $k > 0$ then if $Z_{in}(s)$ is PR then $Z_L(s)$ is PR


define PR like p. 338 " positive real

PR \rightarrow can make a circuit with its input impedance $Z_{in}(s)$ by using only passive elements

Positive real, $Z(s)$ a square $n \times n$ matrix

1. $Z(\sigma)$ is real $\sigma > 0$
(real elements)
2. $Z(s)$ is analytic in $\sigma > 0$
(stable)

$$\sigma = \operatorname{Re} s$$

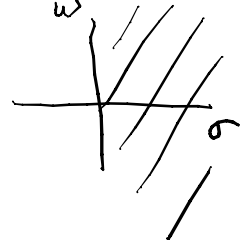

3. $Z(s) + Z^{T*}(s) \geq 0$ in $\sigma > 0$
(passivity)

(Hermitian part) \uparrow positive semi-definite

$$\begin{aligned}
 P(j\omega) &= \operatorname{Re}(V^{T*} I) = \frac{V^{T*} I + I^{T*} V}{2} \\
 &= \frac{1}{2} \left[I^{T*} Z(j\omega) I + I^{T*} Z(j\omega) I \right] \\
 &= \frac{1}{2} I^{T*} \left[Z(j\omega) + Z(j\omega)^{T*} \right] I \geq 0 \text{ if} \\
 &\hspace{15em} \text{passive} \\
 &\hspace{15em} \text{for all } I
 \end{aligned}$$

For the above 2-port

$$Z(s) = \begin{bmatrix} aL & aL-n \\ aL+n & aL \end{bmatrix} \text{ is PR}$$

1. $Z(s)$ is real $Z(s) = \begin{bmatrix} L\sigma & \sigma L-n \\ \sigma L+n & \sigma L \end{bmatrix}$ is real if L, n are real

2. $Z(s)$ has poles at $s = \infty$ (take on $j\omega$ axis on left half plane)

$$Z(\infty) \rightarrow a \begin{bmatrix} L & L \\ L & L \end{bmatrix}$$

3) $Z(s) + Z^{T*}(s)$ in $\operatorname{Re} s > 0$

$$\begin{bmatrix} aL & aL-n \\ aL+n & aL \end{bmatrix} + \begin{bmatrix} a^*L & a^*L+n \\ a^*L-n & a^*L \end{bmatrix} \quad \begin{matrix} s = \sigma + j\omega \\ \sigma > 0 \end{matrix}$$

$$= (a+a^*)L \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} = 2\sigma L \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} = 2\sigma L \begin{bmatrix} 1 \\ 1 \end{bmatrix} \begin{bmatrix} 1 & 1 \end{bmatrix}$$


$$\begin{aligned}
 x^{T*} [Z(s) + Z^{T*}(s)] x &= 2\sigma L \begin{bmatrix} x_1^* & x_2^* \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} \begin{bmatrix} 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} \\
 &= 2\sigma L \begin{bmatrix} x_1 + x_2 \end{bmatrix}^* \begin{bmatrix} x_1 + x_2 \end{bmatrix} = 2\sigma L |x_1 + x_2|^2 \geq 0 \text{ for all } x_1, x_2
 \end{aligned}$$

(complex X_1, X_2), $L > 0, C > 0$


Ex: $Z(s) = \frac{1}{s+4} + \frac{1}{s+1} + 1-b$ for what b is this PR

$\underbrace{\hspace{2em}}_{Z_1}$ $\underbrace{\hspace{2em}}_{Z_2}$ $\underbrace{\hspace{2em}}_{Z_3}$

$\frac{1}{s_1} = Z_1 \rightarrow Y_1 = s+4 \Rightarrow$ 

$\frac{1}{s_2} = \frac{1}{s_2} = s+1 \Rightarrow$ 

$Z_3 = 1-b \Rightarrow$ 

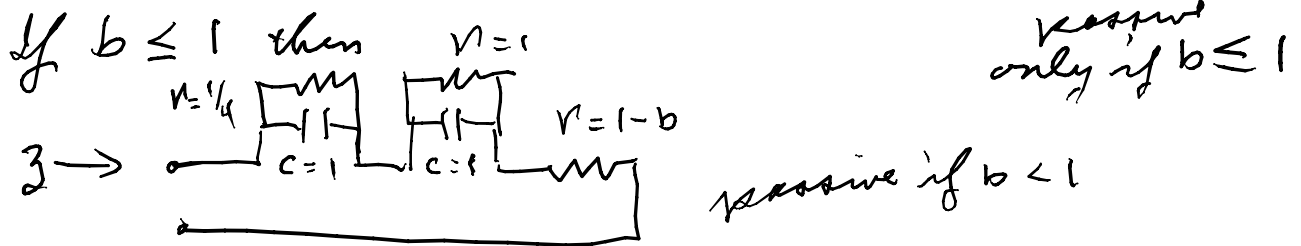

lets check $Z + Z^*$ in $\sigma > 0$

$Z + Z^* |_{A=s} = \frac{1}{s+4} + \frac{1}{s+1} \rightarrow b+1$ for $\sigma > 0, \sigma$ very large

then $Z + Z^* \rightarrow 1-b$

$\Rightarrow 1-b > 0$ for Z to be PR

$\therefore Z(s) = \frac{1}{s+4} + \frac{1}{s+1} + 1-b$ is PR iff $b \leq 1$ & then we can synthesize by a passive circuit

see p. 338 to "start" this

Lossless circuits $P_{ave}(j\omega) \equiv 0$ for any input I

$$I^{T*} [Z(j\omega) + Z^{T*}(j\omega)] I = 0$$

$$\therefore Z(j\omega) = -Z^{T*}(j\omega)$$

if Z is real-rational $= -Z^T(-j\omega)$


$$\Rightarrow Z(j\omega) + Z^T(-j\omega) = 0_{n \times n}$$

let $\omega = \sigma/j \Rightarrow$ analytic continuation

$$Z(\sigma) + Z^T(-\sigma) \equiv 0_{n \times n}$$

$$Z(\sigma) = -Z^T(-\sigma) \text{ in the whole } \sigma \text{ plane}$$

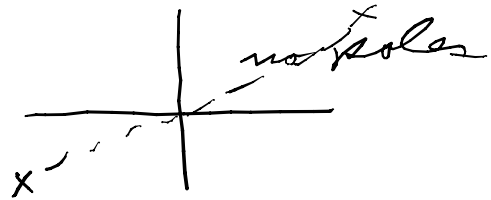if PR & rational $Z(\sigma)$ has no poles in $\sigma > 0$ as $Z(\sigma)$ is analytic there



If a pole in $\sigma < 0$ then it would be in the right half plane & this is not possible in a PR matrix \Rightarrow all poles of a lossless $Z(\sigma)$ are on $j\omega$ axis (& PR)

Ex: $Z(\sigma) = \frac{1}{\sigma}$

$$Z(\sigma) + Z(-\sigma) = \frac{1}{\sigma} + \frac{1}{-\sigma} \equiv 0 = 2\text{Re}(Z(\sigma))$$

$$2\text{Re}(Z(\sigma)) = \frac{1}{\sigma + j\omega} + \frac{1}{\sigma - j\omega} = \frac{2\sigma}{\sigma^2 + \omega^2} > 0 \text{ in } \sigma > 0$$

Result is for a scalar: If lossless all poles are on $j\omega$ axis


poles on the $j\omega$ are simple
 & residues are real and positive

$$Z(s) = \frac{k_0}{s} + k_\infty s + \underbrace{\frac{k}{s+j\omega_1} + \frac{k}{s-j\omega_1}}_{\frac{2k s}{s^2 + \omega_1^2}} + \dots + \sum \frac{2k_i s}{s^2 + \omega_i^2}$$

does have $Z(s) = -Z(-s)$
 i.e. this is an odd function

$\frac{1}{Z(s)} = Y(s)$ is PR if $Z(s)$ is PR; $Y(s) = -Y(-s)$ if lossless

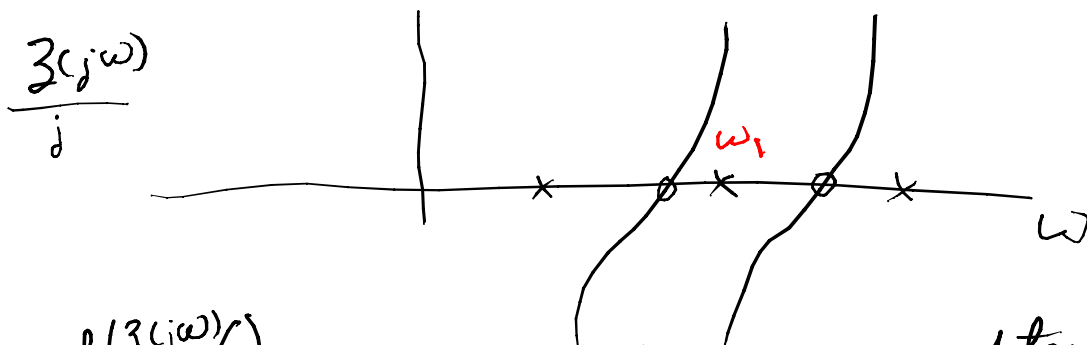there poles and zeros of $Z(s)$ lie on $j\omega$ axis and are all simple (& they alternate)



if $\frac{d(Z(j\omega)/j)}{d\omega} > 0$ then poles & zeros alternate
 but \nearrow This is true

$$\frac{Z(j\omega)}{j} = \frac{k_0}{-\omega} + k_\infty \omega + \frac{k(2\omega)}{-\omega^2 + \omega_1^2} + \dots$$

$$\frac{dZ(j\omega)/j}{d\omega} = \frac{k_0}{\omega^2} + k_\infty + \underbrace{\left[\frac{2k}{-\omega^2 + \omega_1^2} - \frac{2k\omega(2\omega)}{(\omega^2 + \omega_1^2)^2} \right]}_{\dots} + \dots$$

$$+ 2k \left[\frac{\omega^2 + 2\omega^2 + \omega_1^2}{(\omega^2 + \omega_1^2)^2} \right] > 0$$

≥ 0

Ex:

$$Z(s) = \frac{s(s^2 + 2)}{(s^2 + 1)} \quad \text{this is lossless}$$

$$= s + \frac{2ks}{s^2 + 1} = \frac{s^3 + s + 2ks}{s^2 + 1} \Rightarrow \begin{matrix} 2k + 1 = 2 \\ k = 1/2 \end{matrix}$$

$$= s + \frac{1}{s^2 + 1}$$

