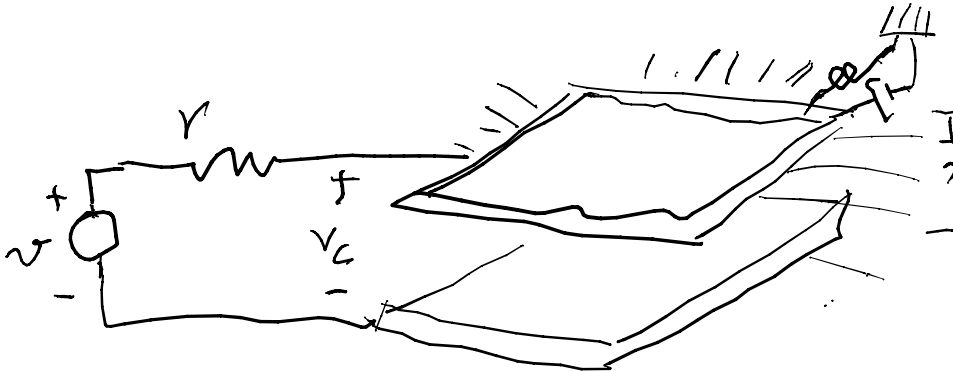


modified  
10/14/04

$L_0 =$  plate separation when  $Q=0$ , i.e.  $v=v_c=0$

$$m \ddot{x} = -kx - b \dot{x} + \frac{Q^2}{\epsilon A}$$

$$C v_c = Q$$

$$C = \frac{\epsilon A}{L_0 - x}$$

$$v = v_i + v_c = r \dot{Q} + \frac{Q}{C} = r \dot{Q} + \frac{(L_0 - x) Q^2}{\epsilon A}$$

set for state  $\underline{x} = [x, \dot{x}, Q]^T$   $\underline{V} = \text{transpose}$

$$\begin{aligned} \dot{x}_1 &= \dot{x} \\ \dot{x}_2 &= \ddot{x} \\ \dot{x}_3 &= \dot{Q} \end{aligned} \quad \begin{bmatrix} 1 & 0 & 0 \\ 0 & m & 0 \\ 0 & 0 & r \end{bmatrix} \begin{bmatrix} \dot{x} \\ \ddot{x} \\ \dot{Q} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ -k & -b & 0 \\ 0 & 0 & -\frac{L_0}{\epsilon A} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ x_3^2 / \epsilon A \\ x_1 x_3 / \epsilon A \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} v$$

$$\dot{\underline{x}} = \begin{bmatrix} 0 & 1 & 0 \\ -\frac{k}{m} & -\frac{b}{m} & 0 \\ 0 & 0 & -\frac{L_0}{\epsilon A r} \end{bmatrix} \underline{x} + \begin{bmatrix} 0 \\ x_3^2 / (\epsilon A m) \\ \frac{x_1 x_3}{\epsilon A r} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1/r \end{bmatrix} u$$

$$u = v$$

$$\underline{x} = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$\dot{\underline{x}} = A \underline{x} + f(\underline{x}) + B u \quad \text{state variable}$$



if desire  $v_c$  as the output;  $v_c = \frac{Q}{C} = \frac{x_3 (L_0 - x_1)}{\epsilon A}$

$$y = v_c = g(\underline{x})$$

To get  $E \dot{\underline{x}} = A(\underline{x}) + B u$ ,  $y = C \underline{x}$ ,  $\underline{x}_E = \begin{bmatrix} \underline{x} \\ v_c \end{bmatrix}$

$$\underline{x}_E = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix}; \quad \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \dot{\underline{x}}_E = \begin{bmatrix} 0 & 1 & 0 & 0 \\ -\frac{k}{m} & -\frac{b}{m} & 0 & 0 \\ 0 & 0 & -\frac{L_0}{\epsilon A r} & 0 \\ 0 & 0 & +\frac{L_0}{\epsilon A} & -1 \end{bmatrix} \underline{x}_E + \begin{bmatrix} 0 \\ x_3^2 / (\epsilon A m) \\ x_1 x_3 / (\epsilon A r) \\ -x_1 x_3 / (\epsilon A) \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 1/r \\ 0 \end{bmatrix} u$$
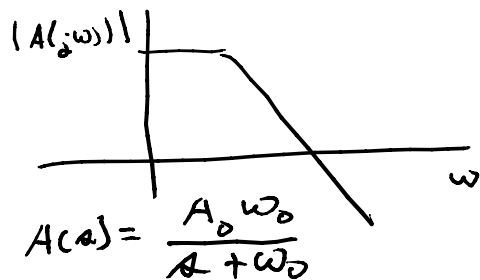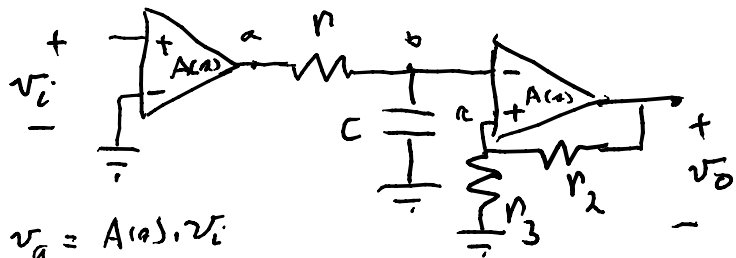
$$y = v_c = [0 \ 0 \ 0 \ 1] \underline{x}_E$$



$$v_a = A(s) \cdot v_i = \frac{A_0 \omega_0}{s + \omega_0} \cdot v_i$$

$$s v_a = -\omega_0 v_a + A_0 \omega_0 v_i$$

1452 op amp  
 $A_0 \approx 10^5$   
 $\omega_0 \approx 10 \text{ Hz}$

$$v_b = \frac{1/rc}{r + 1/rc} \cdot v_a = \frac{1}{rcA + 1} \cdot v_a \Rightarrow s v_b = -\frac{1}{rc} v_b + \frac{1}{rc} v_a$$

$$v_o = A(s)(v_c - v_b) = \frac{A_0 \omega_0}{s + \omega_0} \left( \frac{r_3}{r_2 + r_3} v_o - v_b \right)$$

$$s v_o = (-\omega_0) \left( 1 - \frac{A_0 r_3}{r_2 + r_3} \right) v_o - A_0 \omega_0 v_b$$

$$x = \begin{bmatrix} v_a \\ v_b \\ v_o \end{bmatrix} \Rightarrow \dot{x} = \begin{bmatrix} -\omega_0 & 0 & 0 \\ 1/rc & -1/rc & 0 \\ 0 & -A_0 \omega_0 & -\omega_0 \left( 1 - \frac{A_0 r_3}{r_2 + r_3} \right) \end{bmatrix} x + \begin{bmatrix} A_0 \omega_0 \\ 0 \\ 0 \end{bmatrix} v_i$$

$$v_o = y = [0 \ 0 \ 1] x$$

$$T(s) = \frac{V_o(s)}{V_i(s)} = [0 \ 0 \ 1] \begin{bmatrix} s + \omega_0 & 0 & 0 \\ -1/rc & s + 1/rc & 0 \\ 0 & -A_0 \omega_0 & s + \omega_0 \left( 1 - \frac{A_0 r_3}{r_2 + r_3} \right) \end{bmatrix}^{-1} \begin{bmatrix} A_0 \omega_0 \\ 0 \\ 0 \end{bmatrix}$$

$$= [1] \left\{ \frac{(3,1) \text{ entry of inverse}}{(1,3) \text{ cofactor}} \right\} [A_0 \omega_0] = \frac{1 \cdot (A_0 \omega_0 / rc)}{(s + \omega_0) \left( s + \frac{1}{rc} \right) \left( s + \omega_0 \left( 1 - \frac{A_0 r_3}{r_2 + r_3} \right) \right)} (A_0 \omega_0)$$

$$(1,3) \text{ cofactor} = (-1)^{1+3} \begin{vmatrix} -1/rc & s + 1/rc \\ 0 & -A_0 \omega_0 \end{vmatrix} =$$

$$T(s) = \frac{k}{s^3 + d_2 s^2 + d_1 s + d_0} = \frac{(A_0 \omega_0)^2 / (rc)}{s^3 + \left[ \left( \omega_0 + \frac{1}{rc} \right) + \omega_0 (1 - A_0 \hat{r}) \right] s^2 + \left[ \frac{\omega_0}{rc} + \left( \omega_0 + \frac{1}{rc} \right) \omega_0 (1 - A_0 \hat{r}) \right] s + \frac{\omega_0^2}{rc} (1 - A_0 \hat{r})}$$

for oscillations  $v_o = v_i$  with  $\hat{r} = r_3 / (r_2 + r_3)$

$$V_o = T(s) \cdot V_i = V_i \quad (1 - T(s)) V_i = 0 \quad \text{if } V_i \neq 0$$

have a natural response

at  $s$  such that  $1 - T(s) = 0$

i.e. zeros of  $s^3 + d_2 s^2 + d_1 s + (d_0 - k) = 0$

for sinusoidal oscillations,  $s = j\omega \Rightarrow \text{EoS and both} = 0$

$$\begin{cases} -\omega^3 + d_1 \omega = 0 \\ -d_2 \omega^2 + d_0 - k = 0 \end{cases} \text{ need both of these}$$

$\Rightarrow \omega_{osc}^2 = d_1, \quad d_1 d_2 = d_0 - k$   
gives 2 eqs., 3 things free to satisfy them:  $\omega_{osc}, PC, \hat{\eta} < 1$

Scattering variables:

$$2v^i = v + z_0 i$$

$$2v^n = v - z_0 i$$

assume  $z_0$  real  
normalize to  $1\Omega$

$$\begin{aligned} 2v^i &= v + i \\ 2v^n &= v - i \end{aligned}$$

$$\begin{aligned} v &= v^i + v^n \\ i &= v^i - v^n \end{aligned}$$

