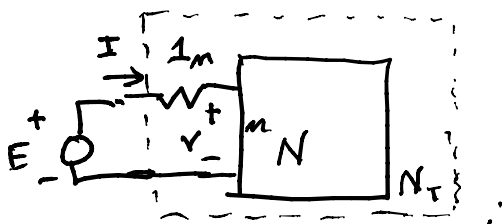


p. 178 = scattering matrix

$$V^n = S(\alpha) V^i$$



$$2V^i = V + I$$

$$2V = 2V^i + 2V^n$$

$$2V^n = V - I$$

$$2I = 2V^i - 2V^n$$

$$V = V^i + V^n$$

$$I = V^i - V^n$$

$$E = V + I = 2V^i$$

$$I = Y_T \cdot E$$

$$V = E - I = E - Y_T E = (1_m - Y_T) E$$

$$(1_m - Y_T) Y_T = Y_T - Y_T^2 = Y_T (1_m - Y_T)$$

$$\therefore (1_m - Y_T) I = (1_m - Y_T) Y_T E = Y_T (1_m - Y_T) E = Y_T V$$


$$AV = BI; \quad A = Y_T, \quad B = (1_m - Y_T)$$

$$A(V^i + V^n) = B(V^i - V^n) \Rightarrow (B + A)V^n = (B - A)V^i$$


$$V^n = (B + A)^{-1} (B - A) V^i = S V^i$$

$$S = (B + A)^{-1} (B - A) = [(1_m - Y_T) + Y_T]^{-1} [(1_m - Y_T) - Y_T]$$

$$= 1_m - 2Y_T$$

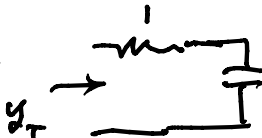$n=1$ , capacitor   $\Rightarrow y_T = \frac{1}{1 + j\omega C} = \frac{\omega C}{1 + \omega C}$

$$d_c(\alpha) = 1 - 2 \left( \frac{\omega C}{1 + \omega C} \right) = \frac{1 - \omega C}{1 + \omega C}$$

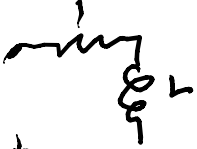  $\Rightarrow y_T = \frac{1}{1 + \omega L}$

$$d_L(\alpha) = 1 - 2 \left( \frac{1}{1 + \omega L} \right) = \frac{-1 + \omega L}{1 + \omega L}$$

no poles on  $\alpha = j\omega$

$$AV = BI \quad S = (B+A)^{-1}(B-A)$$

$$Y = B^{-1}A, \quad Z = A^{-1}B$$

$$S = (B[1_m + B^{-1}A])^{-1}(B[1_m - B^{-1}A]) = ([1_m + B^{-1}A] \cancel{B^{-1}} \cancel{B} [1_m - B^{-1}A])^{-1}$$


$$= (1_m + Y)^{-1}(1_m - Y) = (1_m - Y)(1_m + Y)^{-1}$$

$$(1_m + Y)(1_m - Y) \stackrel{\uparrow}{=} \stackrel{\leftarrow}{=} 1_m - Y^2 = (1_m - Y)(1_m + Y)$$

$$S = (Z - 1_m)(Z + 1_m)^{-1} = (Z + 1_m)^{-1}(Z - 1_m)$$


For the dual circuit  $V \rightarrow I, I \rightarrow V; I^d = V, V^d = I$

$$S^d = -S$$

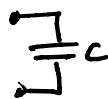

$$Y_c = sC$$

$$S_c = (1 + sC)^{-1}(1 - sC)$$

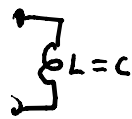

$$Z_L = sL$$

$$S_L = (sL - 1)(sL + 1)^{-1}$$

$$S_L^d = (sC - 1)(sC + 1)^{-1} = -S_c$$

If  $Z(s)$  is lossless then

$$Z(s) + Z^T(-s) = 0_m$$

but  $S(Z + 1_m) = Z - 1_m \Rightarrow Z - SZ = S + 1_m$   
 $(1_m - S)Z = S + 1_m$

$$Z = (1_m - S)^{-1}(S + 1_m) = (S + 1_m)(1_m - S)^{-1}$$

$$Z(s) + Z^T(-s) = (1_m - S)^{-1}(S + 1_m) + [(1_m - S(-s))^{-1}(1_m + S(-s))]^T$$

$$= (1_m - S(s))^{-1}(S(s) + 1_m) + (1_m + S^T(-s))(1_m - S^T(-s))^{-1} = 0_m$$

$$(S(s) + 1_m)(1_m - S^T(-s)) = -(1_m - S(s))(1_m + S^T(-s))$$

$$1_m + S(s) - S^T(-s) - S(s)S^T(-s) = -1_m + S(s) - S^T(-s) + S(s)S^T(-s)$$

$$2(1_m - S(s)S^T(-s)) = 0_m$$

$\therefore$  lossless condition on  $S(s)$ :  $S(s)S^T(-s) = 1_m$

$$\therefore S^T(-s) = S^T(-s)$$

(also  $S^T(-s)S(s) = 1_m$ )

note  $A_c(s) = \frac{1-sc}{1+sc}$ ,  $A_c(-s) = \frac{1+sc}{1-sc} \Rightarrow A_c(s)A_c(-s) = 1$

$$S = (z+1_m)^{-1}(z-1_m)$$

for a passive circuit  $S$  is analytic in  $\text{Re } s > 0$   
 if (real) rational " " " " on  $\text{Re } s = 0$

$$1_m - S(s)S^T(s) \geq 0_m \text{ in } \text{Re } s > 0 \text{ if real rational}$$

$$2 \text{Re } V^T I = V^T I + V^T I^* = V^T I + I^{T*} V \quad (s = j\omega)$$

$$= (V^L + V^N)^T (V^L - V^N) + (V^L - V^N)^T (V^L + V^N)$$

$$= [V^{L^T} V^L - V^{L^T} V^N + V^{N^T} V^L - V^{N^T} V^N] = 2(V^{L^T} [1_m - S(s)] S(s)^T V^L + V^{N^T} V^N)$$

$$+ [V^{L^T} V^L + V^{L^T} V^N - V^{N^T} V^L - V^{N^T} V^N]$$

$$= 2 V^{L^T} [1_m - S(s)] V^L \geq 0 \text{ if passive}$$

$s = j\omega$

bounded for  $s = j\omega$  if passive

$$= 2 [V^{L^T} V^L - V^{N^T} V^N] \quad (\text{sums of } | \cdot |^2 \text{ terms})$$

Ex:  $S_c(s) = \frac{1-sc}{1+sc}$  passive if  $c \geq 0$ ,  $s = -\frac{1}{c}$  a pole

$$1 - S_c^*(s) S_c(s) = 1 - \left( \frac{1-s^*c}{1+s^*c} \right) \left( \frac{1-sc}{1+sc} \right)$$

$$= 1 - \left( \frac{1 - c^2 \text{Re } s + c^2 |s|^2}{1 + c^2 \text{Re } s + c^2 |s|^2} \right) \geq 0 \quad \text{checks passive condition}$$

