

Lossless 1-port synthesis pp. 342-348
 (call $Z(a)$ a reactance function)

PR, $Z(a) = -Z^T(-a)$

$Z^T(-a) = Z_a^*$

i.e. $Z = -Z_a^*$

$*$ = complex conjugate

\wedge^* = Hermitian conjugate

4 classical syntheses

1. 1st Foster \rightarrow partial fraction of Z
2. 2nd Foster \rightarrow " " of $Y = 1/Z$
3. 1st Cauer \rightarrow continued fraction expansion about ∞
4. 2nd Cauer \rightarrow " " " " 0

Ex: $Z(a) = \frac{a(a^2+1)}{(a^2+1/2)(a^2+2)}$

1st Foster: $Z(a) = \frac{k_1}{a+j\sqrt{1/2}} + \frac{k_1^*}{a-j\sqrt{1/2}} + \frac{k_2}{a+j\sqrt{2}} + \frac{k_2^*}{a-j\sqrt{2}}$
 $= \frac{(k_1+k_1^*)a + j(\frac{-k_1+k_1^*}{\sqrt{2}} + \frac{k_2^*}{\sqrt{2}})}{a^2+1/2} + \frac{(k_2+k_2^*)a + j(-\sqrt{2}k_2 + \sqrt{2}k_2^*)}{a^2+2}$

but j terms must disappear
 $k_1^* = k_1, k_2^* = k_2$


$= \frac{2k_1 a}{a^2+1/2} + \frac{2k_2 a}{a^2+2}$

need k_1 & k_2 : $\frac{a^2+1/2}{a} Z(a) = 2k_1 + 2k_2 \frac{(a^2+1/2)}{(a^2+2)}$ set $a^2 = -1/2$

$= \frac{a^2+1/2}{a} \times \frac{a(a^2+1)}{(a^2+1/2)(a^2+2)} \Rightarrow \frac{-1/2+1}{(-1/2+2)} = 2k_1 + 0$

$\therefore 2k_1 = \frac{1/2}{3/2} = 1/3$; $2k_2 = \frac{a(a^2+1)}{(a^2+1/2)(a^2+2)} \times \frac{a^2+2}{a} \Big|_{a^2=-2} = \frac{-2+1}{-2+1/2} = \frac{-1}{-3/2} = \frac{2}{3}$

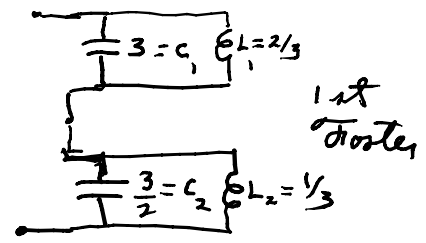
$Z(a) = \frac{a(a^2+1)}{(a^2+1/2)(a^2+2)} = \frac{1/3 a}{a^2+1/2} + \frac{2/3 a}{a^2+2} = \frac{1}{\frac{3}{2}a + \frac{3}{2a}} + \frac{1}{\frac{3}{2}a + \frac{3}{2a}} = Z_1 + Z_2$



$$y(s) = \frac{1}{z(s)} = \frac{(s^2 + \frac{1}{2})(s^2 + 2)}{s(s^2 + 1)} = \frac{k_0}{s} + \frac{2k_1 s}{s^2 + 1} = \frac{1}{s} + \frac{\frac{1}{2}s}{s^2 + 1} + A$$

$$k_0 = \frac{(0 + \frac{1}{2})(0 + 2)}{(0 + 1)} = 1$$

$$2\hat{k}_1 = \frac{(s^2 + \frac{1}{2})(s^2 + 2)}{s^2} \Big|_{s^2 = -1} = \frac{(-\frac{1}{2})(1)}{(-1)} = \frac{1}{2}$$

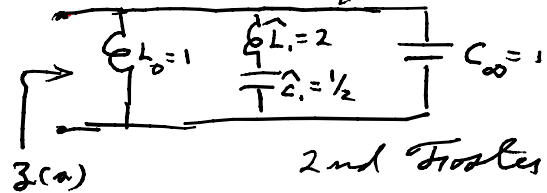

1st Cover - remove poles at ∞


$$z(s) = \frac{s(s^2 + 1)}{(s^2 + \frac{1}{2})(s^2 + 2)} = \frac{1}{\frac{s^4 + \frac{5}{2}s^2 + 1}{s^3 + s}} = \frac{1}{s + \frac{\frac{3}{2}s^2 + 1}{s^3 + s}}$$

$$\begin{array}{r} s \\ s^3 + s \end{array} \overline{) \frac{s^4 + \frac{5}{2}s^2 + 1}{s^3 + s}} \quad \begin{array}{l} 2s/3 \\ \underline{2s/3} \\ \frac{3}{2}s^2 + 1 \end{array}$$

$$\begin{array}{r} \frac{3}{2}s^2 + 1 \\ \frac{3}{2}s^2 + s \end{array} \overline{) \frac{s^3 + s}{s^3 + s}} \quad \begin{array}{l} \frac{1}{3}s \\ \underline{\frac{1}{3}s} \\ 0 \end{array}$$

$$= \frac{1}{s + \frac{1}{\frac{2}{3}s + \frac{1}{\frac{3}{2}s^2 + 1}}} = \frac{1}{s + \frac{1}{\frac{2}{3}s + \frac{1}{\frac{9}{2} + \frac{1}{3}s}}}$$
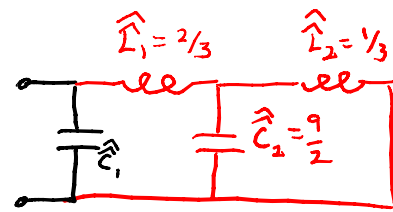
$$z(s) = \frac{1}{s + \frac{1}{\frac{2}{3}s + \frac{1}{\frac{9}{2} + \frac{1}{3}s}}}$$



1st Cover
(removed poles at ∞)
(good for low pass)

2nd Cover - remove poles at $s=0$


$$z(s) = \frac{s(s^2 + 1)}{(s^2 + \frac{1}{2})(s^2 + 2)} = \frac{1}{\frac{s^4 + \frac{5}{2}s^2 + 1}{s^3 + s}} = \frac{1}{\frac{1}{s} + \frac{1}{\frac{1}{\frac{3}{2}s} + \frac{1}{\frac{1}{\frac{3}{2}s} + \frac{1}{\frac{1}{3}s}}}}$$

continued fraction expansion about $s=0$


$$\begin{array}{r} \frac{1}{s} \\ s + s^3 \end{array} \overline{) \frac{1 + \frac{5}{2}s^2 + s^4}{1 + s^2}} \quad \begin{array}{l} \frac{1}{3}s \\ \underline{\frac{1}{3}s} \\ \frac{3}{2}s^2 + s^4 \end{array}$$

$$\begin{array}{r} \frac{3}{2}s^2 + s^4 \\ \frac{3}{2}s^2 + s^3 \end{array} \overline{) \frac{s + s^3}{s + \frac{2}{3}s^3}} \quad \begin{array}{l} \frac{9}{2s} \\ \underline{\frac{9}{2s}} \\ \frac{1}{3}s^3 \end{array}$$
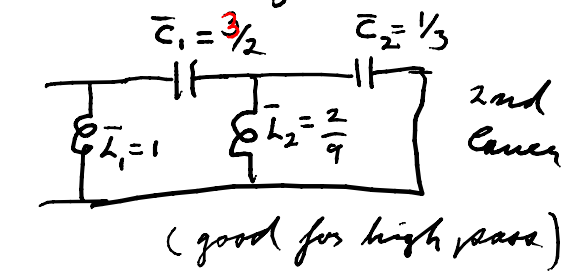
$$\begin{array}{r} \frac{1}{3}s^3 \\ \frac{1}{3}s^3 \end{array} \overline{) \frac{s^4}{s^4}} \quad \begin{array}{l} \frac{1}{3s} \\ \underline{\frac{1}{3s}} \\ 0 \end{array}$$



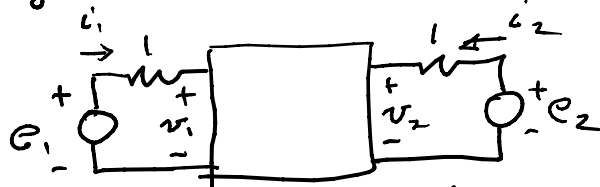Here we have 4 circuits using the minimum number of reactive elements, the minimum number degree of $Z(z) = 4$, called canonical



$$2v^i = v + i = e$$


$$2v^n = v - i$$

here when $e_2 = 0$

$$2v_2^n = v_2 - i_2 = 2v_2$$

$$v_2^n = v_2$$

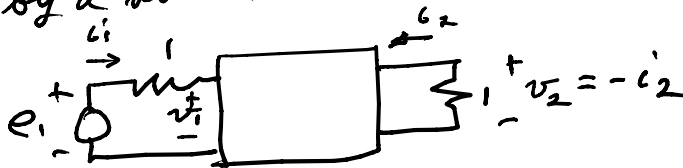if $e_2 = 0$ get "a load" on port 2 fed by a source on port 1



$$2v_1^i = e_1$$

$$V^n = S V^i$$

here $2v_2^i = v_2 + i_2 = 0$

$$\left. \begin{aligned} V_2^n &= S_{21} V_1^i + S_{22} V_2^i \\ &= S_{21} V_1^i \text{ as here } V_2^i = 0 \end{aligned} \right\}$$

$$V_2 = S_{21} \frac{E_1}{2}$$

$$\therefore S_{21} = 2 \frac{V_2}{E_1}$$

$$S_{11} = \left. \frac{V_1^n}{V_1^i} \right|_{V_2^i = 0} = \text{reflection coefficient (when port 2 is terminated in } Z_0 = 1)$$