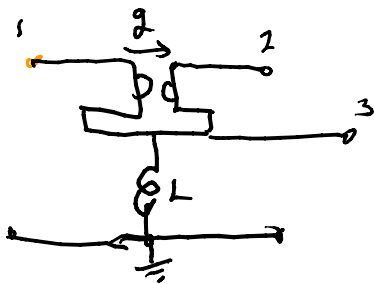


$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}, \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = Y_{ind} V$$


$$Y_{ind} = \begin{bmatrix} 0 & g & g & 0 \\ -g & 0 & g & 0 \\ g & -g & g + \frac{1}{sL} & 0 \\ 0 & 0 & -\frac{1}{sL} & \frac{1}{sL} \end{bmatrix}$$

Set $V_4 = 0$ multiplies last column by 0

$$Y_{def} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 1/sL \end{bmatrix}; \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{def} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$



if desire the 2-port Y

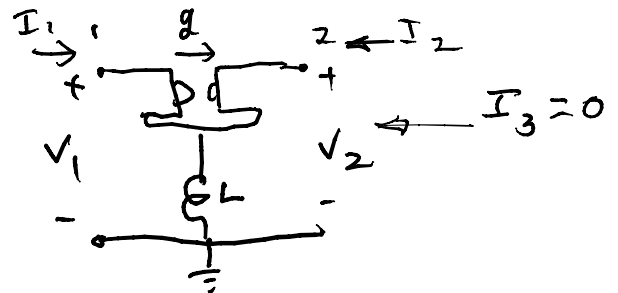

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 1/sL \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} I \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V \\ V_3 \end{bmatrix}$$

Solve for V_3

$$0 = Y_{21}V + Y_{22}V_3$$


$$\Rightarrow V_3 = -Y_{22}^{-1}Y_{21}V$$

$$I = Y_{11}V + Y_{12}V_3 = [Y_{11} - Y_{12}Y_{22}^{-1}Y_{21}]V$$

$$\therefore I = YV \Rightarrow Y = Y_{11} - Y_{12}Y_{22}^{-1}Y_{21}$$


$$= \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} - \begin{bmatrix} -g \\ g \end{bmatrix} [sL] \begin{bmatrix} g & -g \end{bmatrix}$$
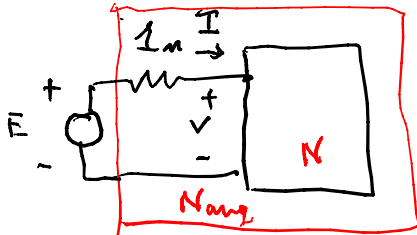
$$Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} - aL \begin{bmatrix} -g^2 & +g^2 \\ g^2 & -g^2 \end{bmatrix} = \begin{bmatrix} aLg^2 & g - aLg^2 \\ -g - aLg^2 & aLg^2 \end{bmatrix}$$



$$S = \mathbf{1}_n - 2Y_{avg}$$

Ex:

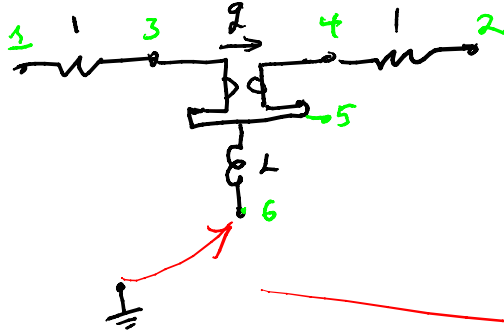

$$Y_{nod} = \begin{bmatrix} 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & 1+g & g & -g & 0 \\ 0 & -1 & -g & 1+g & +g & 0 \\ 0 & 0 & g & -g & 1/aL & -1/aL \\ 0 & 0 & 0 & 0 & -1/aL & 1/aL \end{bmatrix}$$

gnd node 6 \rightarrow removes row 6 & col. 6
to get Y_{avg} eliminate nodes 3, 4, 5

$$Y_{avg} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} 1 & g & -g \\ -g & 1 & +g \\ g & -g & 1/aL \end{bmatrix}^{-1} \begin{bmatrix} -1 & 0 \\ 0 & -1 \\ 0 & 0 \end{bmatrix}$$

$$\det Y_{22} = \frac{1}{aL} - g^3 + g^3 + g^2 + g^2 + g^2/aL = \frac{1}{aL} (1 + g^2) + 2g^2$$

$$\Delta_{11} = \frac{1}{aL} + g^2 \quad \Delta_{21} = (-1)^{2+1} \begin{bmatrix} g & -g^2 \\ aL \end{bmatrix}$$

$$\Delta_{12} = (-1)^{1+2} \begin{bmatrix} -g & -g^2 \\ aL \end{bmatrix} \quad \Delta_{22} = \frac{1}{aL} + g^2$$


$$\therefore Y_{avg} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \frac{1}{\frac{1}{aL}(1+g^2) + 2g^2} \begin{bmatrix} \frac{1}{aL} + g^2 & -\frac{g}{aL} + g^2 \\ \frac{g}{aL} + g^2 & \frac{1}{aL} + g^2 \end{bmatrix} ; S = \mathbf{1}_2 - 2Y_{avg}$$

$$S = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix} + \frac{2aL}{2g^2L a + (1+g^2)} \begin{bmatrix} 1 + ag^2L & -g + ag^2L \\ g + ag^2L & 1 + ag^2L \end{bmatrix}$$

should have $S^T(-a) \cdot S(a) = \mathbf{1}_2$ as lossless

this is bounded
real as a
passive
2-port

Power gain:

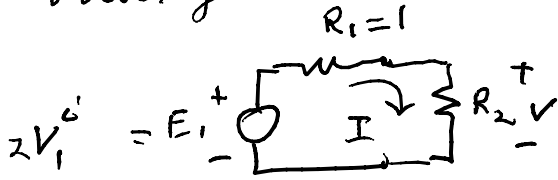


for max power into R_2
 derive $R_2 = R_1 \Rightarrow$ means
 reflection coefficient
 for $R_2 = 0$

$$I = \frac{E}{R_1 + R_2}, \quad V = \frac{R_2}{R_1 + R_2} E, \quad P_{max} = VI = \frac{R_2}{(R_1 + R_2)^2} E^2$$

$\frac{1}{E^2} \frac{dP}{dR_2} = 0$ to maximize:

$$= \frac{1}{(R_1 + R_2)^2} - \frac{2 \cdot R_2}{(R_1 + R_2)^3} = \frac{1}{(R_1 + R_2)^3} [R_1 + R_2 - 2R_2] = 0$$

$R_2 = R_1$

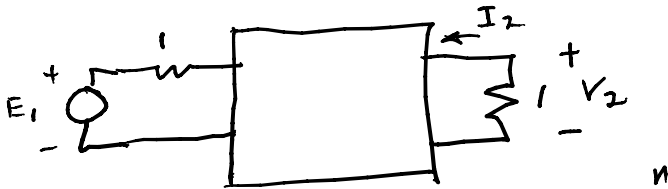

$$2V_2^i = V_2 + I_2 = 0 \quad ; \quad I_2 = -V_2 = -V_2^n$$

$$2V_2^n = V_2 - I_2 = 2V_2$$


$$S_{21}(a) = \left. \frac{V_2^n}{V_1^i} \right|_{V_2^i = 0} \Rightarrow V_2^n = S_{21} V_1^i$$

$$P(j\omega) = \text{Re}(V_2^* I_2) = \text{Re}(V_2^n V_2^n) = |V_2^n(j\omega)|^2 = |S_{21} V_1^i(j\omega)|^2$$

$$\therefore \frac{\text{Power to load}}{\text{Power available from source}}(j\omega) = \frac{|S_{21}(j\omega) V_1^i(j\omega)|^2}{\frac{R_1}{(R_1 + R_1)^2} E^2} = \frac{|S_{21}(j\omega)|^2 |V_1^i(j\omega)|^2}{(2)^2 \cdot (2V_1^i)^2} = |S_{21}(j\omega)|^2$$

$$= |S_{21}(j\omega)|^2 = \text{insertion power gain}$$

$$= S_{21}(-j\omega) S_{21}(j\omega) = \left. \frac{S_{21}(-a) S_{21}(a)}{a=j\omega} \right|$$

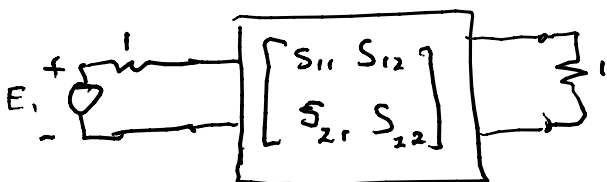

$$\Sigma = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \text{ if lossless}$$

$$\Sigma^T(-a) \Sigma(a) = \mathbf{1}_m$$

here $\mathbf{1}_2$

$$\begin{bmatrix} S_{11}^T(-a) & S_{21}^T(-a) \\ S_{12}^T(-a) & S_{22}^T(-a) \end{bmatrix} \begin{bmatrix} S_{11}(a) & S_{12}(a) \\ S_{21}(a) & S_{22}(a) \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \Rightarrow \Sigma^T(-a)\Sigma(a) = I_n$$

$$1 = S_{11}^T(-a)S_{11}(a) + S_{21}^T(-a)S_{21}(a) \Rightarrow S_{11}^T(-a)S_{11}(a) = 1 - S_{21}^T(-a)S_{21}(a)$$

can factor $1 - S_{21}^T(-a)S_{21}(a)$ into $A^T(-a)A(a)$

$$(1,2) = 0 = S_{11}^T(-a)S_{12}(a) + S_{21}^T(-a)S_{22}(a)$$

$$(2,1) = 0 = S_{12}^T(-a)S_{11}(a) + S_{22}^T(-a)S_{21}(a)$$

$$(2,2) = 1 = S_{12}^T(-a)S_{12}(a) + S_{22}^T(-a)S_{22}(a)$$

$$\text{try } \Sigma(a)\Sigma^T(-a) = I_n \Rightarrow 1 = S_{11}(a)S_{11}^T(-a) + S_{12}(a)S_{12}^T(-a)$$

$$\Rightarrow S_{12}(a)S_{12}^T(-a) = 1 - S_{11}(a)S_{11}^T(-a)$$

gives S_{12} as know S_{21} which gave S_{11}

$$\text{then } S_{22}^T(-a)S_{22}(a) = 1 - S_{12}^T(-a)S_{12}(a) \Rightarrow S_{22} \text{ by factoring } 1 - S_{12}^T(-a)S_{12}(a)$$

gives a lossless 2-port

(and the transpose is not needed here as S_{12} is a 1×1 matrix)

added example 10/28/04

$$\text{Let } |S_{21}(j\omega)|^2 = \frac{1/4}{\omega^2 + 1} = S_{21}(-a)S_{21}(a) \Big|_{a=j\omega} \Rightarrow S_{21} = \frac{\pm 1/2}{a+1}$$

$$\text{choose } S_{21}(a) = \frac{\pm 1/2}{a+1} \text{ (the choice } \frac{-1/2}{a+1} \text{ is also valid)}$$

$$1 - S_{21}(-a)S_{21}(a) = 1 - \frac{1/4}{1-a^2} = \frac{3/4 - a^2}{1-a^2} = S_{11}(-a)S_{11}(a) = \frac{(\frac{\sqrt{3}}{2} - a)(\frac{\sqrt{3}}{2} + a)}{(1-a)(1+a)}$$

$$\text{factor to } S_{11}(a) = \frac{\frac{\sqrt{3}}{2} + a}{1+a} \text{ (the choices } \frac{\pm\sqrt{3}}{2} - a \text{ are also possible but not } (1-a) \text{ in denominator)}$$

$$\text{also } S_{12}(a)S_{12}(-a) = 1 - S_{11}(a)S_{11}(-a) \text{ (= here } S_{21}(-a)S_{12}(a) \text{ since } S_{11} \text{ is } 1 \times 1)$$

$$\text{so we can choose } S_{12}(a) = S_{21}(a) \text{ or } S_{12}(a) = A(a)S_{21}(a) \text{ with } A(a) \text{ all-pass including } A(a) = -1$$

$$\text{Choose } S_{12}(a) = S_{21}(a) \text{ [guarantees a symmetric } \Sigma(a) \text{ that is, a reciprocal 2-port]} \\ = \frac{1/2}{a+1}$$

$$\text{Next find } S_{22}(a) \text{ from } S_{22}(-a)S_{22}(a) = 1 - S_{12}(-a)S_{12}(a) = \frac{3/4 - a^2}{1-a^2} = S_{11}^* S_{11}$$

choose $S_{22}(s) = -S_{11}(s) = -\left(\frac{\frac{\sqrt{3}}{2} + s}{1+s}\right)$ (can also insert an all-pass in the factor but that can increase the degree)

Finally we have the lossless coupling 2-port described by

$$\Sigma(s) = \begin{bmatrix} \frac{s + \sqrt{3}/2}{s+1} & \frac{1/2}{s+1} \\ \frac{1/2}{s+1} & -\left(\frac{s + \sqrt{3}/2}{s+1}\right) \end{bmatrix}$$

(this should be bounded real and satisfy $\Sigma^T(-s)\Sigma(s) = \mathbf{I}_2$ as the lossless condition)

If we synthesize this 2-port $S(s) = \Sigma(s)$ then we obtain the insertion power "gain" $G(\omega) = |S_{21}(j\omega)|^2 = \frac{1/4}{\omega^2 + 1}$

