

EE 610 Final – Fall2004

100 points, 120 minutes, work all problems; if stuck go on to next part

1. 30 points (30 minutes)


For the polynomial

$$P(s) = s^6 + 3s^5 + 4s^4 + 6s^3 + 5s^2 + 3s + 2$$

- Form  $z(s) = \text{Ev}P(s)/\text{Od}P(s)$
- Determine if  $z(s)$  is a reactance function (= positive-real & lossless)
- If  $z(s)$  is a reactance function give a First Cauer synthesis while if it is not give the reason why it is not.
- Using  $z(s)$  determine if  $P(s)$  is a Hurwitz polynomial (no zeros in  $\text{Re}s > 0$  and only simple ones on  $\text{Re}s = 0$ ).

2. 35 points (30 minutes)


For the following 2-port

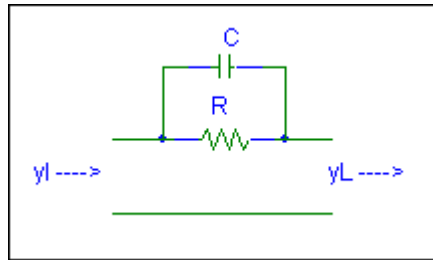

- Find the 2-port admittance matrix  $Y(s)$  and give its determinant  $\Delta(s)$
- Find the load admittance  $y_L(s)$  in terms of  $\Delta(s)$ , the entries of  $Y(s)$ , and the loaded input admittance  $y_I(s)$ .
- Determine necessary and sufficient conditions on a rational positive-real  $y_I(s)$  such that  $y_L(s)$  is positive-real and one degree lower than  $y_I(s)$ .

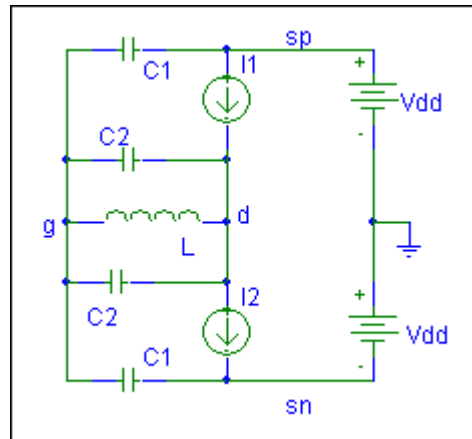3. 35 points (30 minutes)

For one of the Colpitts oscillators presented in class the following is an equivalent circuit.



Here the voltages  $v_g$ ,  $v_d$ ,  $v_{sp}=V_{dd}$ ,  $v_{sn}=-V_{dd}$  (for gate, drain, source\_p and source\_n) are measured with respect to ground. Using  $\beta = \frac{KP}{2} \frac{W}{L}$ , assume the drain current source values are given by

$$-i_{Dp} = i1 = \beta(v_g - v_{sp} - V_{TO})^2$$

$$i_{Dn} = i2 = \beta(v_g - v_{sn} - V_{TO})^2$$

- Let  $i_L$  and  $v_L=v_g-v_d$  be inductor current and voltage. Set up state variable equation using  $x=[i_L, v_g, v_L]^T$  as the state variable.
- Linearize the state variable equations and find the characteristic polynomial  $[= \det(sI_3-A)]$ . From this find the natural frequencies.
- Show that this circuit can be an oscillator and find the oscillation frequency in terms of the circuit parameters.