

ENEE 610
Homework Problems for Grading, Set 2 (60 points)
Due at class M 09/27/04
Linear and nonlinear $v(i)$

1. (20 points)

For the MOS circuit discussed in class with DC equations set up on 09/13/04 choose branches ~~1,2~~, 3, 4, **5,6** (with the same orientation as in class) for the tree.

a) Draw the new graph highlighting the new tree and from it obtain the new cut-set and tie-set matrices.

b) For this tree give the branch by branch admittance and from it the input admittance, i/v .

c) Insert gate-source and gate-drain capacitance and replace the capacitor C (between the two transistor sources) by an inductor L. For the resulting circuit find the natural frequencies.

2. (20) points

For the same circuit as in problem 1 above, place a capacitor C_d between the two transistor drains. In the presence of the gate-source and gate-drain capacitors, find the new driving point impedance $z(s)=v/i$. Give impulse responses under the condition that all capacitances and R are normalized to 1 with g_m as a parameter.

3. (20) points

For the same circuit as in problem 1 above, place a resistor R_d between the two transistor drains. Assuming DC operation find the nonlinear $v(i)$ description. Plot v versus i for normalized $R_d=R=1$, $I_o=1$ and three values of g_m ($1/g_m <, =, > R$).