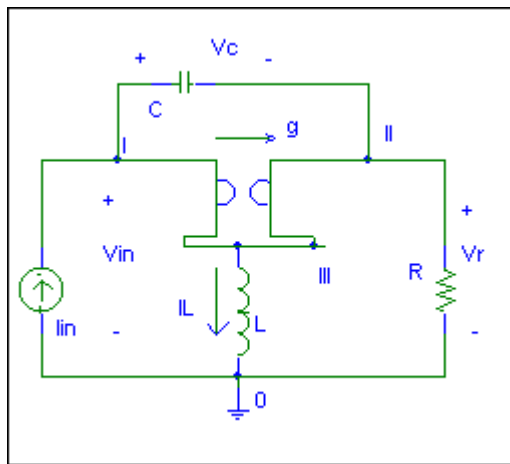


ENEE 610
 Homework Problems for Grading, Set 3 (60 points)
 Due at class M 10/11/04
 Sensitivity, state, input $y(s)$

1.(20 points)

For the following circuit

- a) draw the adjoint as needed for the sensitivity of the input admittance, $y_{in}(s) = I_{in}(s)/V_{in}(s)$ seen by the current source, to C, to L, and to R.
- b) use the adjoint to calculate the sensitivities listed in part a).
- c) check by straight differentiation.



2. (20) points

For the same circuit as in problem 1 above, give state variable equations using the state as $x = [v_C, i_L]^T$, input $u = I_{in}$, and output $y = [V_{in}, V_r]^T$

3. (20) points

For the same circuit as in problem 1 above,

- a) find the 2-port $Y(s)$ matrix for the 2-port formed by L, C, and the gyrator (that is, the 2-port seen by the external I_{in} and R).
- b) replace R by a load $y_L(s)$ and calculate $y_{in}(s)$ versus $y_L(s)$ and L, C, and g using the $Y(s)$ found in a)
- c) from the result of b) find $y_L(s)$ in terms of $y_{in}(s)$, L, C, and g.