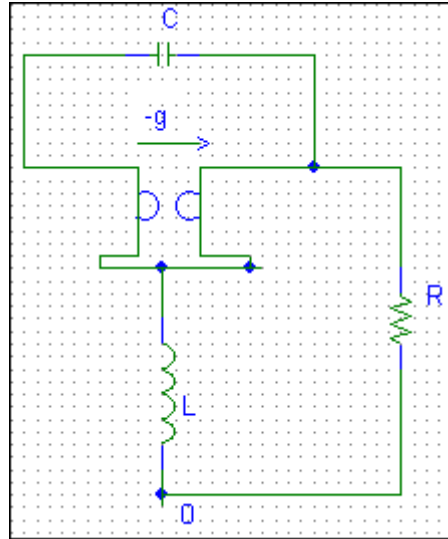


a) (5)


The adjoint circuit:



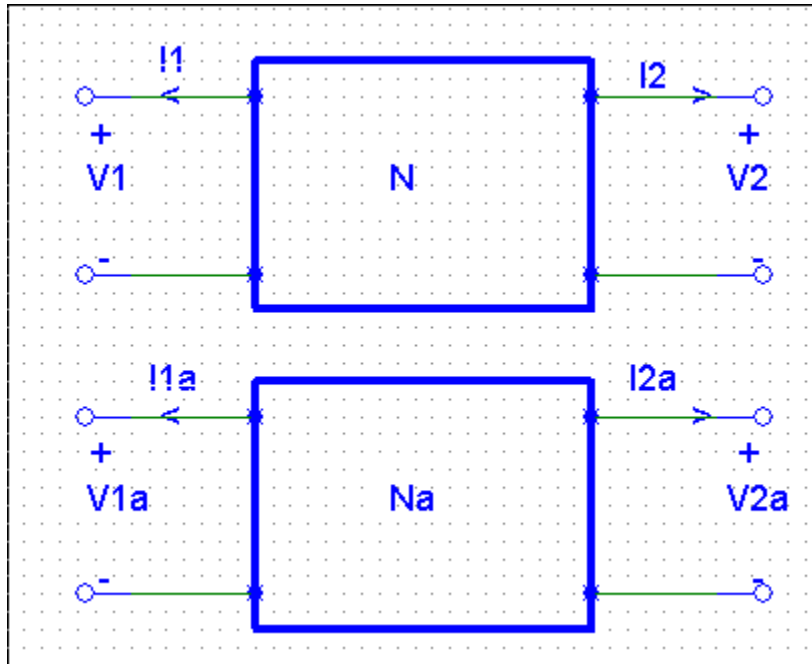b) (10)

The key point of calculating the sensitivity is to find how to terminated the original and adjoint circuit.

In this case, $y_{in}(s) = i_{in}(s)/V_{in}(s)$:




We have to start with: realizing that all the voltage signs and current directions are show above.

$$V_1 * i_1^a + V_2 * i_2^a - V_1^a * i_1 - V_2^a * i_2 = -[i_N^a T * V_N - i_N^T * V_N^a]$$

To find sensitivity of $Y(s) = -i_1/V_1$, The original and adjoint circuits are terminated in a way that sets $V_1 = V_1^a = 1$, and $i_2 = i_2^a = 0$. There for, $Y(s) = -i_1$, and $dY(s)/da = -di_1/da$.

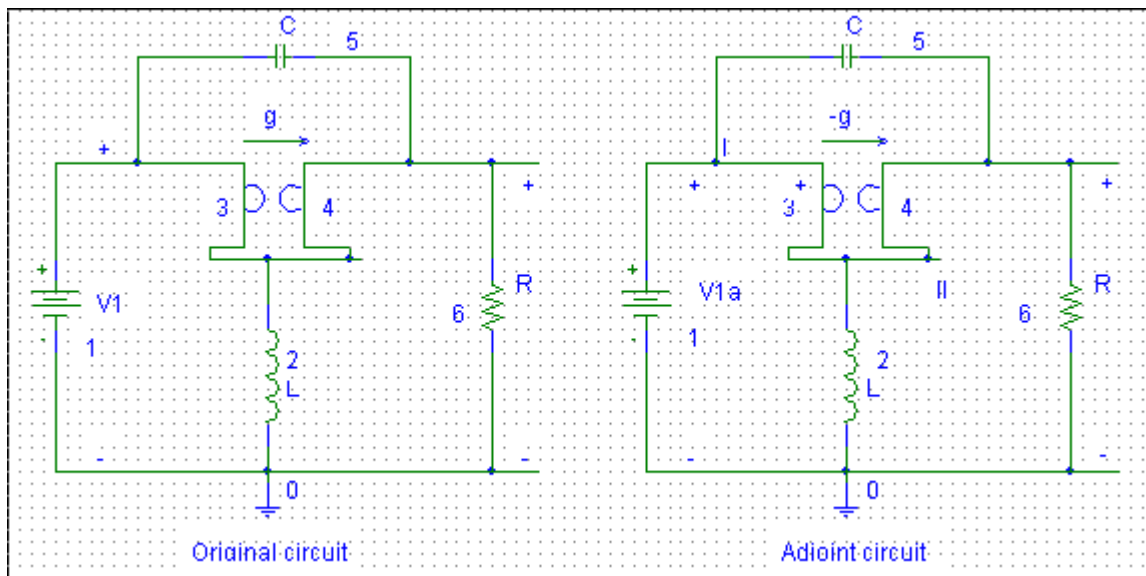The original and adjoint circuits are terminated as shown below.



Clearly $i_2 = i_2^a = 0$

$$\text{So } V_1 * i_1^a - V_1^a * i_1 = -[i_N^a T * V_N - i_N^T * V_N^a]$$

Since is V_1 fixed in a, and nothing varies in N^a ,
then $dV_1/da = 0$, $dV_1^a/da = 0$, and $di_1^a/da = 0$,

$$\text{So } -V_1^a * di_1/da = -[i_N^a T * V_N - i_N^T * V_N^a]$$

$$\text{Then } di_1/da = d[i_N^a T * V_N - i_N^T * V_N^a]/da / V_1^a = [V_N^a T * (dY_N/da) * V_N] / V_1^a$$

$$Y(s) = -i_1/V_1$$

$$dY(s)/da = -di_1/da = -[V_N^a T * (dY_N/da) * V_N] \text{ by setting } V_1 = V_1^a = 1$$

$$ST(a) = -(a/i_1) * (di_1/da)$$

Circuit analysis of the original and adjoint circuit:

They have the same graph.

Choose 2, 3, 4 to be the tree branch.

Cut set Matrix:
$$C := \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 \end{bmatrix}$$

Tie set Matrix:
$$T := \begin{bmatrix} 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & -1 & 0 & -1 & 0 & 1 \end{bmatrix}$$

Using equality $-C*j = -C*Y_{bb}*C^T*V_t$

$$j := (i_{OR} \ i_a \ 0 \ 0 \ 0 \ 0)^T$$

Left := $-C*j$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 \end{bmatrix} \cdot \begin{bmatrix} i_{OR} \ i_a \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \cdot (-1) \quad -C*j = \begin{bmatrix} -i_{OR} - i_a \\ -i_{OR} - i_a \\ 0 \end{bmatrix}$$

For original circuit, I1 to make $V_1=1, I_2=0$

Admittance matrix:
$$Y_{bb} := \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & g & 0 & 0 \\ 0 & 0 & -g & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & s \cdot C & 0 \\ 0 & 0 & 0 & 0 & 0 & R \end{bmatrix}$$

Evaluate $CY_{bb}C^T = C \cdot Y_{bb} \cdot C^T$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 \end{bmatrix} \cdot \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & g & 0 & 0 \\ 0 & 0 & -g & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & s \cdot C & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{R} \end{bmatrix} \cdot \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & -1 \\ 1 & 0 & 1 \end{bmatrix} = \begin{matrix} CY_{bb}C^T = \\ \left[\begin{array}{ccc} \frac{1}{(s \cdot L)} + \frac{1}{R} & 0 & \frac{1}{R} \\ 0 & s \cdot C & g - s \cdot C \\ \frac{1}{R} & -g - s \cdot C & s \cdot C + \frac{1}{R} \end{array} \right] \end{matrix}$$

$$\begin{bmatrix} \frac{1}{(s \cdot L)} + \frac{1}{R} & 0 & \frac{1}{R} \\ 0 & s \cdot C & g - s \cdot C \\ \frac{1}{R} & -g - s \cdot C & s \cdot C + \frac{1}{R} \end{bmatrix} \cdot \begin{bmatrix} V1 \\ V2 \\ V3 \end{bmatrix} = \begin{bmatrix} -i1 \\ -i1 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V2 \\ V3 \\ V4 \end{bmatrix} := \begin{bmatrix} \frac{s \cdot (L \cdot R \cdot g^2 - L \cdot g)}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + 1}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + R \cdot g}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \end{bmatrix} \cdot (-i1)$$

$$VN := \begin{bmatrix} \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (L \cdot R \cdot g^2 - L \cdot g)}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + 1}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + R \cdot g}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{1 - R \cdot g}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \\ \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + R \cdot g}{(s \cdot (C + L \cdot g^2) + R \cdot g^2)} \end{bmatrix} \cdot (-i1)$$

Since $V1=1$

$$i1 := \frac{-(s \cdot (C + L \cdot g^2) + R \cdot g^2)}{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1}$$

$$Y_{in}(s) := \frac{s \cdot (C + L \cdot g^2) + R \cdot g^2}{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1}$$

$$VN := \begin{bmatrix} 1 \\ \frac{s \cdot (L \cdot R \cdot g^2 - L \cdot g)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + 1}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{1 - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \end{bmatrix}$$

For adjoint circuit, I1a to make $V2a=1$, $I2a=0$

Admittance matrix :

$$Y_{bba} := \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{s \cdot L} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -g & 0 & 0 \\ 0 & 0 & g & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & s \cdot C & 0 \\ 0 & 0 & 0 & 0 & 0 & R \end{bmatrix}$$

Very similar to the original circuit, just replace g by $-g$
The results of the adjoint circuits are:

$$\begin{bmatrix} \text{Va2} \\ \text{Va3} \\ \text{Va4} \end{bmatrix} := \begin{bmatrix} \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{L} \cdot \mathbf{g})}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) + 1}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) - \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \end{bmatrix} \cdot (-i1a) \quad \text{VNa} := \begin{bmatrix} \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{L} \cdot \mathbf{g})}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) + 1}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) - \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{1 + \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \\ \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) - \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2)} \end{bmatrix} \cdot (-i1a)$$

Since V1a=1

$$\text{I1a} := \frac{-s \cdot (\mathbf{C} + \mathbf{L} \cdot \mathbf{g}^2) + \mathbf{R} \cdot \mathbf{g}^2}{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1} \quad \text{VNa} := \begin{bmatrix} 1 \\ \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{L} \cdot \mathbf{g})}{(s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) + 1}{(s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1)} \\ \frac{s \cdot (\mathbf{R} \cdot \mathbf{C} - \mathbf{L} \cdot \mathbf{g}) - \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1)} \\ \frac{1 + \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1)} \\ \frac{s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) - \mathbf{R} \cdot \mathbf{g}}{(s \cdot (\mathbf{L} \cdot \mathbf{R} \cdot \mathbf{g}^2 + \mathbf{R} \cdot \mathbf{C}) + 1)} \end{bmatrix}$$

The solutions for both the original the adjoint circuit:

$$\text{VN} := \begin{bmatrix} 1 \\ \frac{s \cdot (L \cdot R \cdot g^2 - L \cdot g)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + 1}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C + L \cdot g) + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{1 - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \end{bmatrix} \quad \text{VNa} := \begin{bmatrix} 1 \\ \frac{s \cdot (L \cdot R \cdot g^2 + L \cdot g)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C - L \cdot g) + 1}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (R \cdot C - L \cdot g) - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{1 + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \\ \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \end{bmatrix}$$

$$\text{Yin}(s) := \frac{s \cdot (C + L \cdot g^2) + R \cdot g^2}{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1}$$

Calculate sensitivity with respect to L: $\text{SY}(C) := \frac{L}{Y} \cdot \frac{dY}{dL}$

$$\frac{dY_{22}}{dL} := \frac{-1}{s \cdot L^2} \quad \text{All the other terms are zero}$$

$$\text{V2} := \frac{s \cdot (L \cdot R \cdot g^2 - L \cdot g)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \quad \text{V2a} := \frac{s \cdot (L \cdot R \cdot g^2 + L \cdot g)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)}$$

$$\text{SY}(L) := \frac{-s \cdot L \cdot g^2 \cdot (R^2 \cdot g^2 - 1)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$

Calculate sensitivity with respect to C: $\text{SY}(C) := \frac{C}{Y} \cdot \frac{dY}{dC}$

$$\frac{dY_{55}}{dC} := s \quad \text{All the other terms are zero}$$

$$\text{V5} := \frac{1 - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \quad \text{V5a} := \frac{1 + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)}$$

$$SY(C) := \frac{-s \cdot C \cdot (R^2 \cdot g^2 - 1)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$

Calculate sensitivity with respect to R: $SY(C) := \frac{R}{Y} \cdot \frac{dY}{dR}$

$\frac{dY}{dC} := \frac{-1}{R^2}$ All the other terms are zero

$$V6 := \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)} \quad V6a := \frac{s \cdot (L \cdot R \cdot g^2 + R \cdot C) - R \cdot g}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1)}$$

$$SY(R) := \frac{-R \cdot (s^2 \cdot (L \cdot g^2 - C)^2 - g^2)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$

c) (5)

Calculate sensitivity directly from Yin(s)

$$Yin(s) := \frac{s \cdot (C + L \cdot g^2) + R \cdot g^2}{s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1}$$

$$SY(L) := \frac{-s \cdot L \cdot g^2 \cdot (R^2 \cdot g^2 - 1)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$

$$SY(C) := \frac{-s \cdot C \cdot (R^2 \cdot g^2 - 1)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$

$$SY(R) := \frac{-R \cdot (s^2 \cdot (L \cdot g^2 - C)^2 - g^2)}{(s \cdot (L \cdot R \cdot g^2 + R \cdot C) + 1) \cdot (s \cdot (C + L \cdot g^2) + R \cdot g^2)}$$