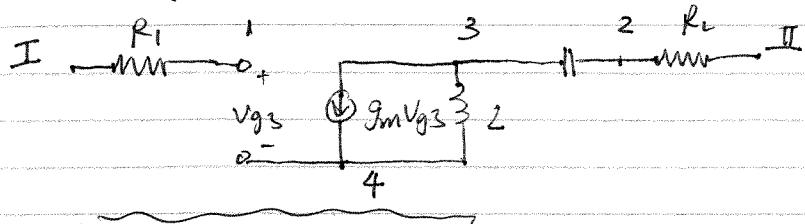


Problem 1.

$$I_d = \frac{k_p}{2} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$V_{th} = 1 \text{ V}, \quad k_p = 10^{-5} \text{ A/V}^2, \quad W/L = 10$$

10' a) small signal equivalent circuit:



$$\boxed{g_m = k_p \frac{W}{L} (V_{gs} - V_{th})}$$

10' b) Yind matrix between node 1, 2 and ground.

$$I_1 = 0$$

$$I_2 = (V_2 - V_3) \cdot SC = SC V_2 - SC V_3$$

$$I_3 = g_m V_{gs} + \frac{1}{SC} V_{34} + SC \cdot V_{32}$$

$$I_3 = g_m V_1 - SC V_2 + (\frac{1}{SC} + SC) V_3 - (g_m + \frac{1}{SC}) V_4$$

$$I_4 = -g_m V_{gs} + \frac{1}{SC} V_{43} = -g_m V_1 - \frac{1}{SC} V_3 + (g_m + \frac{1}{SC}) V_4$$

$$\therefore \boxed{\boxed{Y_{ind} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & SC & -SC & 0 \\ g_m & -SC & \frac{1}{SC} + SC & -(g_m + \frac{1}{SC}) \\ -g_m & 0 & -\frac{1}{SC} & g_m + \frac{1}{SC} \end{bmatrix}} \quad \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = Y_{ind} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}}$$

12' c) ground 4 to ground $V_4 = 0$

$$Y_{def} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & SC & -SC \\ g_m & -SC & \frac{1}{SC} + SC \end{bmatrix}$$

$$\begin{aligned} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} &= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} & Y_{11} &= \begin{bmatrix} 0 & 0 \\ 0 & SC \end{bmatrix} \\ & T_{12} = \begin{bmatrix} 0 \\ -SC \end{bmatrix} & T_{12} &= \begin{bmatrix} 0 \\ -SC \end{bmatrix} \\ & Y_{21} = \begin{bmatrix} g_m - SC \end{bmatrix} & Y_{22} &= \frac{1}{SC} + SC \end{aligned}$$

$$I_3 = 0$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = Y \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} = \begin{bmatrix} 0 & 0 \\ 0 & SC \end{bmatrix} - \begin{bmatrix} 0 \\ -SC \end{bmatrix} \cdot \frac{1}{(\frac{1}{SC} + SC)} \cdot [g_m - SC]$$

$$\therefore \boxed{Y = \begin{bmatrix} 0 & 0 \\ \frac{S^2 C g_m}{1 + S^2 C} & \frac{SC}{1 + S^2 C} \end{bmatrix}}$$

Problem 1 (continued)

12' d) $R_1 = R_2 = 1$ Yang-ind for the two ports between node I and II.

$$I_I = (V_I - V_1)/R_1 = V_I - V_1$$

$$I_{II} = (V_{II} - V_2)/R_2 = V_{II} - V_2$$

$$I_1 = (V_1 - V_I)/R_1 = -V_I + V_1$$

$$I_2 = (V_2 - V_{II})/R_2 + (V_2 - V_3) \cdot SC = -V_{II} + (1+SC)V_2 - SCV_3$$

$$I_3 = g_m V_1 - SCV_2 + (\frac{1}{SC} + SC)V_3 - (g_m + \frac{1}{SC})V_4$$

$$I_4 = -g_m V_1 - \frac{1}{SC}V_3 + (g_m + \frac{1}{SC})V_4$$

I II 1 2 3 4

$$\left\{ \begin{array}{l} \text{Yang-ind} = \\ \left| \begin{array}{cccccc} 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1+SC & -SC & 0 \\ 0 & 0 & g_m & -SC & SC + \frac{1}{SC} & -(g_m + \frac{1}{SC}) \\ 0 & 0 & -g_m & 0 & -\frac{1}{SC} & g_m + \frac{1}{SC} \end{array} \right| \end{array} \right\}$$

12' e) ground 4, $V_4 = 0$

$$\text{Yang-dif} = \left| \begin{array}{ccccc} 1 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1+SC & -SC \\ 0 & 0 & g_m & -SC & SC + \frac{1}{SC} \end{array} \right| = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} I_I \\ I_{II} \\ I_1 \\ I_2 \\ I_3 \end{bmatrix} = \text{Yang-dif} \cdot \begin{bmatrix} V_I \\ V_{II} \\ V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} I_I \\ I_{II} \end{bmatrix} = \text{Yang} \cdot \begin{bmatrix} V_I \\ V_{II} \end{bmatrix}$$

$$\text{Yang} = Y_{11} - Y_{12}Y_{22}^{-1}Y_{21} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1+SC & -SC \\ g_m - SC & SC + \frac{1}{SC} & 1 \end{bmatrix}^{-1} \begin{bmatrix} -1 & 0 \\ 0 & -1 \\ 0 & 0 \end{bmatrix}$$

$$\therefore \left\{ \begin{array}{l} \text{Yang} = \begin{bmatrix} 0 & 0 \\ \frac{S^2 2 C g_m}{HSC + S^2 C} & \frac{-SC}{1+SC+S^2 C} \end{bmatrix} \end{array} \right\}$$

Problem 1. (continuous)

$$n^f) Y = \begin{bmatrix} 0 & 0 \\ \frac{s^2 c g_m}{1+s^2 C} & \frac{sc}{1+s^2 C} \end{bmatrix} \quad Y_{aug} = \begin{bmatrix} 0 & 0 \\ \frac{s^2 c g_m}{1+s^2 C} & \frac{sc}{1+s^2 C} \end{bmatrix}$$

$$\text{Method 1)} \quad S(s) = (H R^{-1} Y)^{-1} (I - R^{-1} Y)$$

$$\therefore S(s) = \begin{bmatrix} 1 & 0 \\ \frac{s^2 c g_m}{1+s^2 C} & \frac{H C + s^2 L C}{1+s^2 C} \end{bmatrix}^{-1} \cdot \begin{bmatrix} 1 & 0 \\ -\frac{s^2 c g_m}{1+s^2 C} & \frac{1-s C + s^2 C}{1+s^2 C} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{-2s^2 c g_m}{1+s^2 C + s^2 L C} & \frac{1-s C + s^2 C}{1+s^2 C + s^2 L C} \end{bmatrix}$$

$$\text{Method 2)} \quad S(s) = I - 2 Y_{aug}$$

$$\therefore S(s) = \boxed{\begin{bmatrix} 1 & 0 \\ \frac{-2s^2 c g_m}{1+s^2 C + s^2 L C} & \frac{1-s C + s^2 C}{1+s^2 C + s^2 L C} \end{bmatrix}}$$

clearly, two methods agree.

 $n^g)$ $S(s)$ is bounded-real means:

$$X^{T^*} (I_2 - S^{T^*}(s) S(s)) X \geq 0 \quad \text{in } \text{Re}s \geq 0$$

for $s = jw$

$$I_2 - S^{T^*}(jw) S(jw) = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 1 & \frac{2w^2 c g_m}{(1-w^2 C) - jw^2} \\ 0 & e^{-jw} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{2w^2 c g_m}{(1-w^2 C) + jw^2} & e^{jw} \end{bmatrix}$$

$$e^{jw} = \frac{(1-w^2 C) - jw^2}{(1-w^2 C) + jw^2}, \quad b = \frac{2w^2 c g_m}{[(1-w^2 C) + jw^2]}$$

$$\text{then } I_2 - S^{T^*}(jw) S(jw) = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 1 & b^* \\ 0 & e^{-jw} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ b & e^{jw} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 1+|b|^2 & b^* e^{jw} \\ b e^{-jw} & 1 \end{bmatrix}$$

$$\therefore I_2 - S^{T^*}(jw) S(jw) = \begin{bmatrix} -|b|^2 & b^* e^{jw} \\ b e^{-jw} & 0 \end{bmatrix}$$

$$\det(I_2 - S^{T^*}(jw) S(jw)) = -|b|^2 \leq 0$$

so. for any $b \neq 0$, $S(s)$ is not bounded-realto make $S(s)$ bounded real, $\boxed{b=0, \omega=0 \text{ or } C=0}$

$$2=0 \quad S(s) = \begin{bmatrix} 1 & 0 \\ 0 & \frac{1-sC}{1+s^2 C} \end{bmatrix} \quad \text{or } C=0 \quad \boxed{S(s) = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}}$$

Problem 2:

$P(s)$ has no zeros at $\text{Re}s > 0$, $\Rightarrow Z(s)$ has Hurwitz property

$$P(s) = \text{even}(s) + \text{odd}(s)$$

If $Z(s) = \frac{\text{even}(s)}{\text{odd}(s)}$ (or $\frac{\text{odd}(s)}{\text{even}(s)}$) is lossless, which means it can be synthesized with LC elements, the $P(s)$ has Hurwitz property

$$16' a) P_1(s) = s^6 + 6s^5 + 5s^4 + 4s^3 + 3s^2 + 2s + 1 \quad Z(s) = \frac{s^6 + 5s^4 + 3s^2 + 1}{6s^5 + 4s^3 + 2s}$$

1st caner:

$$\begin{aligned} & \frac{1}{6s^5 + 4s^3 + 2s} \sqrt{s^6 + 5s^4 + 3s^2 + 1} \\ & \frac{s^6 + \frac{2}{3}s^4 + \frac{1}{3}s^2}{\frac{13}{3}s^4 + \frac{8}{3}s^2 + 1} \sqrt{6s^4 + 4s^3 + 2s} \\ & \frac{6s^5 + \frac{48}{13}s^3 + \frac{18}{13}s}{\frac{169}{12}s} \\ & \frac{\frac{4}{13}s^3 + \frac{8}{13}s}{\sqrt{\frac{13}{3}s^4 + \frac{8}{3}s^2 + 1}} \\ & \frac{\frac{13}{3}s^4 + \frac{26}{3}s^2}{-\frac{18}{3}s^2 + 1} \quad -\frac{2}{37}s \\ & \frac{4}{13}s^3 - \frac{2}{37}s \quad (-9s) \\ & \frac{2}{3}s \sqrt{-6s^2 + 1} \\ & -6s^2 \quad 1 \quad \sqrt{\frac{2}{3}s} \\ & \frac{2}{3}s \end{aligned}$$

$Z(s)$ not synthesizable with LC, $P_1(s)$ doesn't have Hurwitz property

$$16' b) P_2 = s^5 + 2s^4 + 3s^3 + 4s^2 + 5 \quad Z(s) = \frac{s^5 + 3s^3 + 0s}{2s^4 + 4s^2 + 5}$$

1st caner:

$$Z(s) = \frac{1}{2s} + \frac{1}{2s + \frac{1}{\frac{1}{2}s + \frac{1}{-\frac{162}{55}s + \frac{1}{-\frac{11}{8}s}}}}$$

$P_2(s)$ doesn't have Hurwitz property