

with modified input 09/07/05


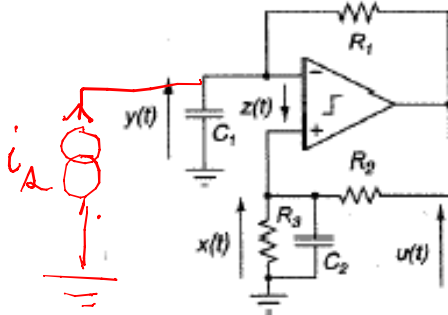


Fig. 1. Schematic of a relaxation oscillator. The comparator is assumed to be ideal.

Use KCL, KVL, laws of elements

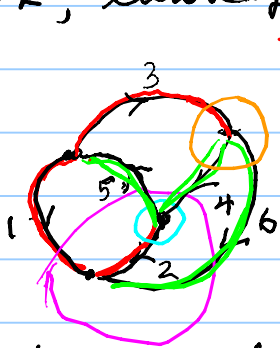

tree branches
 cutset (links) $l_3 = 1 + t$
 KCL

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & | & 1 & -1 & 1 \\ 0 & 1 & 0 & | & -1 & 1 & 0 \\ 0 & 0 & 1 & | & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$t = \#$ of tree branches

$l = \#$ of links

KVL

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & | & 1 & 0 & 0 \\ 1 & -1 & 0 & | & 0 & 1 & 0 \\ -1 & 0 & 1 & | & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$$

$0 = C i_b$

1×2 cut set matrix

$0 = T v_b$
 tie set matrix

Laws of the elements, $a = l/t$

$$\begin{bmatrix} \Delta C_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & \Delta C_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & \Delta R_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & \Delta R_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & \Delta C_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & \Delta C_6 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$v_b = K(v_s)$ opt - amp gain (nonlinear) P.2

$$v_b = \begin{bmatrix} v_t \\ v_r \end{bmatrix}; \quad v_b = \begin{bmatrix} v_t \\ v_r \end{bmatrix}$$

$b =$ branches, # of branches
 $t =$ trees, # of tree branches
 $r =$ links, # of links
 $b = b, t = 3, r = 3 \cdot b = t + r$
 $n = \#$ of nodes $= b + 1$

$$0 = C v_b = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_t \\ v_t \\ v_r \end{bmatrix}$$

$$v_t = -K v_r$$

$$0 = \sigma v_b = \begin{bmatrix} -K & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_t \\ v_t \\ v_r \end{bmatrix}$$

to remove

$$v_r = K^{-1} v_t$$

$$v_b = \begin{bmatrix} v_t \\ v_r \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ K & 1 \end{bmatrix} v_t$$

$$v_b = \begin{bmatrix} -K & 1 \\ 1 & 1 \end{bmatrix} v_r$$

$$\text{or } \mathcal{V}_b = \mathcal{Q}^T \mathcal{V}_T, \quad \mathcal{L}_b = \mathcal{J}^T \mathcal{L}_T; \quad A \mathcal{V}_T = B \mathcal{L}_T, \quad K(\mathcal{V}_T) = \mathcal{V}_b$$

$$\text{or } A \mathcal{Q}^T \mathcal{V}_T = B \mathcal{J}^T \mathcal{L}_T + \text{irrelevant terms}$$

$-B \mathcal{J}^T$

$$\mathcal{L}' = \mathcal{L}_b - \mathcal{J}; \quad \mathcal{J} = \text{irrelevant current}$$
$$= [-i_a, 0 \dots 0]^T$$