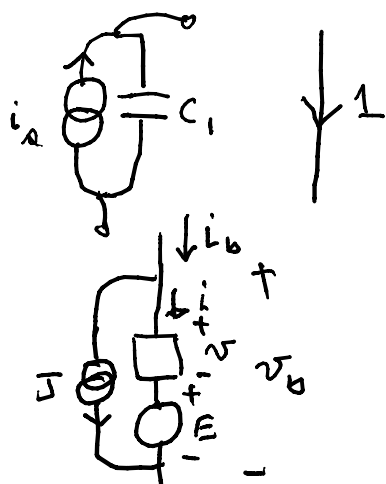


09/07/05



$v_b =$ graph branch voltage

$i_b =$ graph branch currents

our example as modified

$$E = \underline{0} \quad (\text{a b-vector})$$

$$J = \begin{bmatrix} -i_a \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$Av = Bi \\ = B(i_b - J)$$

$$\begin{bmatrix} sC_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & sC_2 + g_1 & 0 & 0 & 0 & 0 \\ 0 & 0 & g_2 & 0 & 0 & 0 \\ 0 & 0 & 0 & g_1 & 0 & 0 \\ 0 & 0 & 0 & 0 & g_1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \left\{ \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} - \begin{bmatrix} -i_a \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \right\}$$

$K(v_5) = v_6$ *op-amp voltage gain*

$$v_b = e^T v_t, \quad i_b = g^T i_a$$

$$\begin{bmatrix} sC_1 \\ sC_2 + g_1 \\ g_1 \\ g_2 \\ 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & -1 \\ -1 & 1 & 0 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \\ 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \left\{ \begin{bmatrix} -1 & 1 & -1 \\ 1 & -1 & 0 \\ 1 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_4 \\ i_5 \\ i_6 \end{bmatrix} + \begin{bmatrix} i_a \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \right\}$$

$K(v_2 - v_1) = v_1 - v_3$

General but linear, time invariant:

$$v_b = e^T v_t \quad i_b = \sigma^T i_r \quad Av = Bi_j$$

$$v_b = v + E, \quad i_b = i + J$$

$$Av = A(v_b - E) = Bi = B(i_b - J)$$

$$= Ae^T v_t - AE = B\sigma^T i_r - BJ$$

$$(Ae^T v_t - B\sigma^T i_r) = AE - BJ$$

$$\Rightarrow \begin{bmatrix} Ae^T & -B\sigma^T \end{bmatrix} \begin{bmatrix} v_t \\ i_r \end{bmatrix} = \underbrace{AE - BJ}_{\text{sources (assume known)}}$$

$x = \text{unknowns} \rightarrow a \text{ } b\text{-vector}$

if $[Ae^T \quad -B\sigma^T]^{-1}$ exists, can solve for x

$$x = [Ae^T \quad -B\sigma^T]^{-1} [A \quad -B] \begin{bmatrix} E \\ J \end{bmatrix}$$

input u


if isolate capacitors into the tree with loops of capacitors

$$\begin{bmatrix} C_{cap} & 0 \\ 0 & 0 \end{bmatrix} x = \begin{bmatrix} A_{const} \\ \text{elem} \end{bmatrix} x + \begin{bmatrix} B_{coef.} \\ \text{elem} \end{bmatrix} u$$

$$y = [C_{out}] x$$

Ex:
$$\begin{bmatrix} c_1 & 0 & 0 & 0 & 0 \\ 0 & c_2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \\ \quad \\ \quad \\ \quad \\ \quad \end{bmatrix} x + \begin{bmatrix} \quad \\ \quad \\ \quad \\ \quad \\ \quad \\ \quad \end{bmatrix} \begin{bmatrix} i_a \end{bmatrix}$$

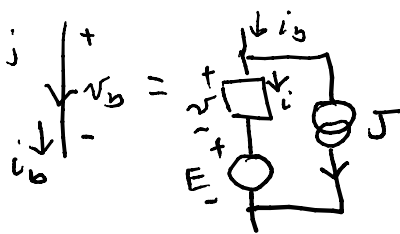Call x the state = $\begin{bmatrix} v_t \\ i_r \end{bmatrix}$ as an example



for b branches
 A generally is $\hat{b} \times \hat{b}$
 B " " $\hat{b} \times \hat{b}$

$$b = t + r$$

generally $E \frac{dx}{dt} = A(x,t) + Bu$ assumes constant linear capacitors
 $y = Cx$

if linear and time invariant $A(x,t) = A \cdot x$
 \uparrow constant matrix

$$sE x = E \frac{dx}{dt} = A x + B u$$

$$y = C x$$

$$\Rightarrow (sE - A)x = B u ; (sE - A)^{-1} B u = x \text{ if inverse exists}$$

$$y = \{C (sE - A)^{-1} B\} u \Rightarrow T(s) = C (sE - A)^{-1} B$$

if $E = \text{identity}$, then at $s = \infty$, $T(s) = 0$

But if $E \neq 1_D$ then $T(s) = s$ is possible

Ex: $s \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} x = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u$

$$y = [0 \ 1] x$$

$$T(s) = [0 \ 1] \begin{bmatrix} 0 & 1 \\ -1 & s \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = s$$

$$(sE - A) = \begin{bmatrix} s & -1 \\ 1 & 0 \end{bmatrix}$$

$$(sE - A)^{-1} = \frac{1}{1} \begin{bmatrix} 0 & 1 \\ -1 & s \end{bmatrix}$$

Ex: $s \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} x = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u$

$$y = [0 \ 1] x$$

$$T(s) = \frac{s}{s^2 + 1} \rightarrow T(\infty) = 0$$

$$sE - A = \begin{bmatrix} s & -1 \\ 1 & s \end{bmatrix}$$

$$(sE - A)^{-1} = \frac{1}{s^2 + 1} \begin{bmatrix} s & 1 \\ -1 & s \end{bmatrix}$$