

For the previous example; "linear" part:

09/12/05

$$Ae^T v_t = \begin{bmatrix} \Delta C_1 & 0 & 0 \\ 0 & \Delta C_2 + g_3 & 0 \\ 0 & 0 & g_1 \\ g_2 & -g_2 & -g_2 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -1 & 1 & -1 \\ 1 & -1 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_4 \\ i_5 \\ i_6 \end{bmatrix} + \begin{bmatrix} i_4 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = B^T i_l - B J \quad \text{corrected}$$

(here $v_t \in i_l$ are for the full branches; subscript b left off for ease of writing)

nonlinear part: $K(v_5) = v_6 \Rightarrow K(v_2 - v_1) = v_1 - v_3$

Rewritten:

$$\begin{bmatrix} \Delta C_1 & 0 & 0 & | & 1 & -1 & 1 \\ 0 & \Delta C_2 + g_3 & 0 & | & -1 & 1 & 0 \\ 0 & 0 & g_1 & | & -1 & 0 & -1 \\ g_2 & -g_2 & -g_2 & | & -1 & 0 & 0 \\ 0 & 0 & 0 & | & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} i_4 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$v_3 = v_1 - K(v_2 - v_1) \Rightarrow 0 = v_1 - v_3 - K(v_2 - v_1)$$

Choose also $y = v_6 = v_1 - v_3$

Rewritten to isolate derivatives and get $E\dot{x} = A(x) + Bu, y = Cx, x = \text{semistate}$

$$A \begin{bmatrix} C_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & C_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} x = \begin{bmatrix} 0 & 0 & 0 & -1 & 1 & -1 \\ 0 & -g_3 & 0 & 1 & -1 & 0 \\ 0 & 0 & -g_1 & 1 & 0 & 1 \\ -g_2 & g_2 & g_2 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 0 \end{bmatrix} x + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -K(v_2 - v_1) \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} u; \quad x = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$u = [i_4]$
 $y = [v_6]$

For state equations need to eliminate 4 variables (normally keep capacitor voltages as the state variables) by solving the last 4 equations [note here exactly $i_5 = 0, v_3 = v_1 - K(v_2 - v_1)$ then solve for $[i_4, i_6]^T = F([v_1, v_2]^T)$]



close a finite circuit by a sphere

$\rho(t)$ into the sphere $\equiv 0$

if use $i_b(t), v_b(t)$ then $\rho(t) = i_b^T v_b(t) = 0$

assume $v_b = e^T v_t; i_b = J^T i_l \Rightarrow \rho(t) = i_l^T J \cdot e^T v_t = 0$

as for a generic graph can choose the v_{i_t} independent & same for i_{i_l} (link current components)

\therefore can cancel v_t & $i_l \Rightarrow \mathcal{J} \cdot e^T = 0_{l \times t}$

If choose the same tree for forming e and \mathcal{J} ; $e = [1_t \vdots K]$, $\mathcal{J} = [k_{\mathcal{J}} \vdots 1_l]$


$$\begin{bmatrix} k_{\mathcal{J}} & \vdots & 1_l \end{bmatrix} \begin{bmatrix} 1_t \\ \vdots \\ K^T \end{bmatrix} = 0_{l \times t} = k_{\mathcal{J}} \cdot 1_t + 1_l \cdot K^T \Rightarrow -k_{\mathcal{J}} = K^T$$

\therefore KVL \Leftrightarrow KCL

note $i_b^T(t_1) \cdot v_b(t_2) = 0$ or $\sum_{b \in \text{circuit 1}} i_b^T \cdot \sum_{b \in \text{circuit 2}} v_b = 0$ if the two circuits have the same graph even if $t_1 \neq t_2$

(used to calculate sensitivities using a circuit that is the adjoint of another)

ideal transformer - 2-port

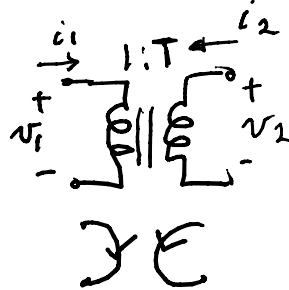

instantaneously lossless

sum of amp turns = 0
 $1 \cdot i_1 + T i_2 = 0$
 $v_2 = T v_1$


$$P(t) = [i_1, i_2] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = i_1 v_1 + i_2 v_2 = -T i_2 v_1 + i_2 v_2 \stackrel{!}{=} 0$$

assume $i_2 \neq 0$
 $T v_1 = v_2$


$$\begin{bmatrix} T & -1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & T \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



note this is $AV = Bi$ and $\det A = 0 = \det B$

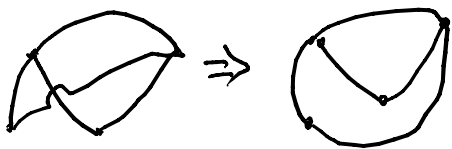 planar graph \Rightarrow projection on a plane has no crossing branches




see fig. P 3.6 for a nonplanar

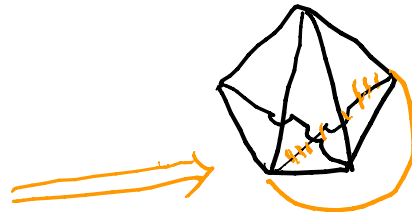

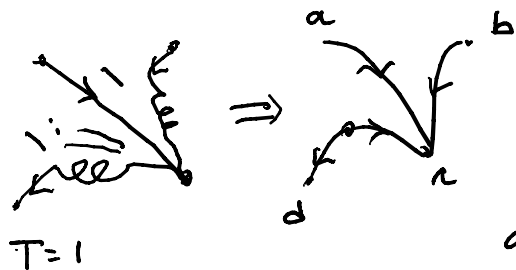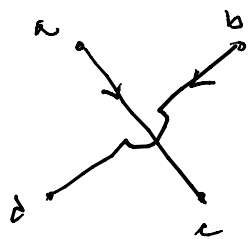

allows a circuit to always have an equivalent with a planar graph

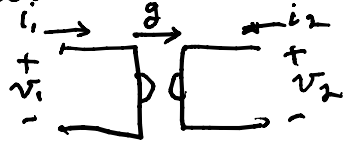To work with admittances - use gyrators
 $g = \text{gyration conductance}$



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & g \\ g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \begin{aligned} i_1 &= +g v_2 \\ i_2 &= -g v_1 \end{aligned}$$

*

$$\left. \begin{aligned} v_1 i_1 &= +g v_1 v_2 \\ v_2 i_2 &= -g v_1 v_2 \end{aligned} \right\} p = [i_1 \ i_2] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = -g v_1 v_2 + g v_1 v_2 \equiv 0$$

also instantaneously lossless


a short circuit has no admittance

an open circuit has an admittance

$$\left. \begin{aligned} v &= 0 \\ i &= \text{arbitrary} \end{aligned} \right\}$$

$$\left. \begin{aligned} i &= 0 \\ v &= \text{arbitrary} \end{aligned} \right\}$$



here $Y=0$ is its admittance

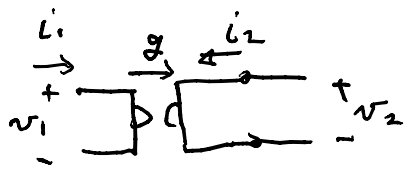

$$\begin{aligned} i_2 &= 0 \\ &= -g v_1 \Rightarrow v_1 = 0 \text{ if } g \neq 0 \end{aligned}$$

||| a short
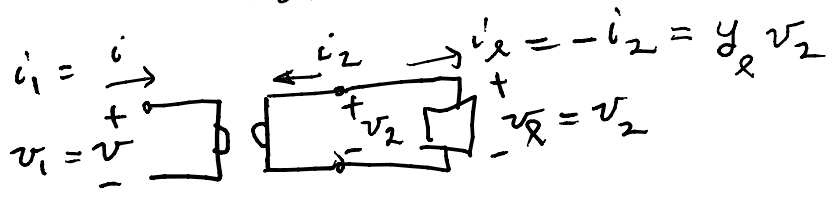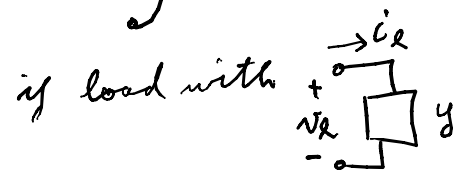
$$\begin{aligned} v_2 &= \text{arbitrary} \\ i_1 &= -g v_2 \Rightarrow i_1 = \text{arbitrary if } g \neq 0 \end{aligned}$$



$$i_1 = -g v_2$$

$$v_1 = -\frac{1}{g} i_2$$

$$= -\frac{1}{g} (-Y v_2) = +\frac{1}{g} Y \left(+\frac{1}{g} i_1 \right) = \frac{Y}{g^2} i_1 = Z_{in} i_1 = v_1$$

$$Z_{in} = \frac{Y}{g^2}$$