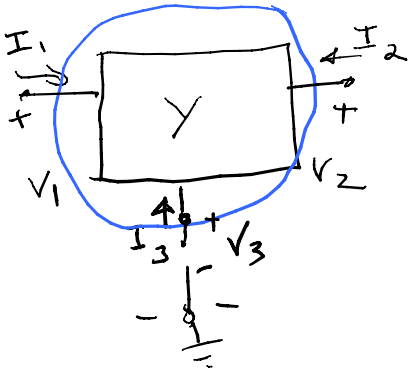


09/14/05
EE610



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = Y \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{ind} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$I_1 + I_2 + I_3 = 0$$

look when $V_2 = V_3 = 0$

$$I_1 + I_2 + I_3 = y_{11}V_1 + y_{21}V_1 + y_{31}V_1 = (y_{11} + y_{21} + y_{31})V_1 = 0$$

for any V_1

similarly $\sum_{i=1}^3 y_{ij} = 0$ for each j


$$\sum_{i=1}^3 y_{i1} = 0$$

add E a fixed number to all V 's replaces $V_1 \rightarrow V_1 + E$
 $V_2 \rightarrow V_2 + E$
 $V_3 \rightarrow V_3 + E$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{ind} \begin{bmatrix} V_1 + E \\ V_2 + E \\ V_3 + E \end{bmatrix} = Y_{ind} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} + Y_{ind} \begin{bmatrix} E \\ E \\ E \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} \sum_{j=1}^3 y_{1j} E \\ \sum_{j=1}^3 y_{2j} E \\ \sum_{j=1}^3 y_{3j} E \end{bmatrix} \Rightarrow \sum_{j=1}^3 y_{ij} = 0 \text{ for any } i$$


Y_{ind} has rows & columns sum to zero

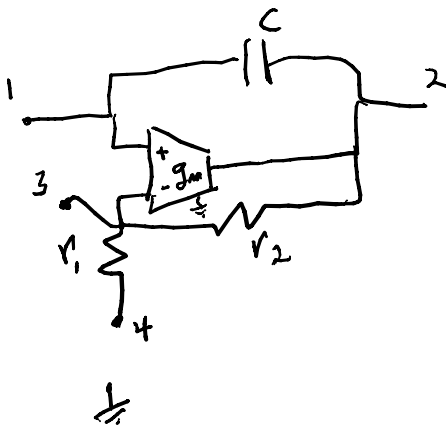

Y_{ind} is 4×4




$$Y_{ind} = \begin{bmatrix} sC & -sC & 0 & 0 \\ -sC & sC & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

DVCCS \Leftrightarrow OTA

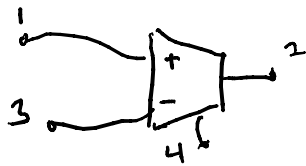

transconductance amplifier
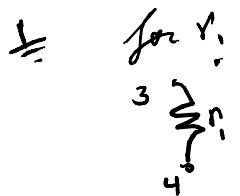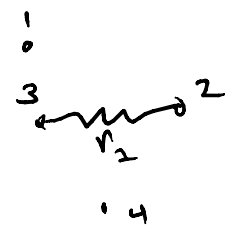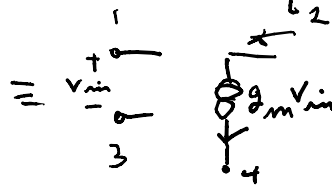
$$Y_{ing} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & g_2 & -g_2 & 0 \\ 0 & -g_2 & g_2 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$



$$Y_{ind} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ g_m & 0 & -g_m & 0 \\ 0 & 0 & 0 & 0 \\ -g_m & 0 & g_m & 0 \end{bmatrix}$$

$$Y_{ing}^T = \begin{bmatrix} 0 & g_m & 0 & -g_m \\ 0 & 0 & 0 & 0 \\ 0 & -g_m & 0 & g_m \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

||

Y_{ind} g_m

$$Y_{ind} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & g_1 & -g_1 \\ 0 & 0 & -g_1 & g_1 \end{bmatrix}$$

$$Y_{ind} = Y_{ind_c} + Y_{ind_{g_m}} + Y_{ind_{g_1}} + Y_{ind_{g_2}}$$

$$= \begin{bmatrix} g_c & -g_c & 0 & 0 \\ -g_c + g_m & g_c + g_2 & -g_m - g_2 & 0 \\ 0 & -g_2 & g_2 + g_1 & -g_1 \\ -g_m & 0 & g_m - g_1 & g_1 \end{bmatrix}$$

if ground node 4 $\rightarrow v_4 = 0$, if ignore $I_4 (= -I_1 - I_2 - I_3)$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} g_c & -g_c & 0 \\ -g_c + g_m & g_c + g_2 & -g_m - g_2 \\ 0 & -g_2 & g_1 + g_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = Y_{nodal} \cdot V = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

if don't use node 3 externally, $I_3 = 0$


$$\text{gives } 0 = y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + y_{22} v_3 = \begin{bmatrix} 0 & -g_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} g_1 + g_2 \end{bmatrix} v_3 = 0$$

$$v_3 = -y_{22}^{-1} y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & \frac{+g_2}{g_1 + g_2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\text{Then } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = y_{11} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + y_{12} \cdot \left(-y_{22}^{-1} y_{21} \right) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow Y_{term} = y_{11} - y_{12} y_{22}^{-1} y_{21}$$

$$Y_{\text{term}} = \begin{bmatrix} sC & -sC \\ -sC + g_m & sC + g_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -g_m - g_2 \end{bmatrix} (g_1 + g_2)^{-1} \begin{bmatrix} 0 & -g_2 \end{bmatrix}$$
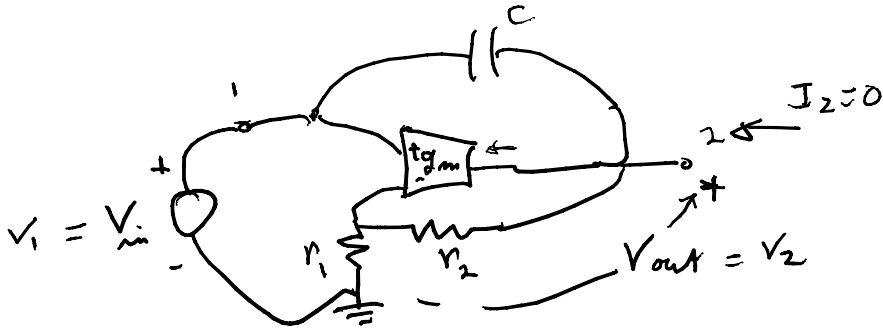
$$= \begin{bmatrix} sC & -sC \\ -sC + g_m & sC + g_2 - \frac{(g_m + g_2)g_2}{g_1 + g_2} \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = Y_{\text{term}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$\text{as } I_2 = 0$$

$$0 = Y_{21} V_1 + Y_{22} V_2$$

$$V_{out} = -Y_{22}^{-1} Y_{21} V_1$$

$$\frac{V_{out}}{V_{in}} = -Y_{22}^{-1} Y_{21} = \frac{(sC - g_m)}{sC + g_2 \left(\frac{g_1 - g_m}{g_1 + g_2} \right)}$$

$$\text{zero} \Rightarrow s = g_m / C$$

$$\text{poles} \Rightarrow s = -\frac{g_2}{C} \left(\frac{g_1 - g_m}{g_1 + g_2} \right)$$

if $g_1 > g_m$

