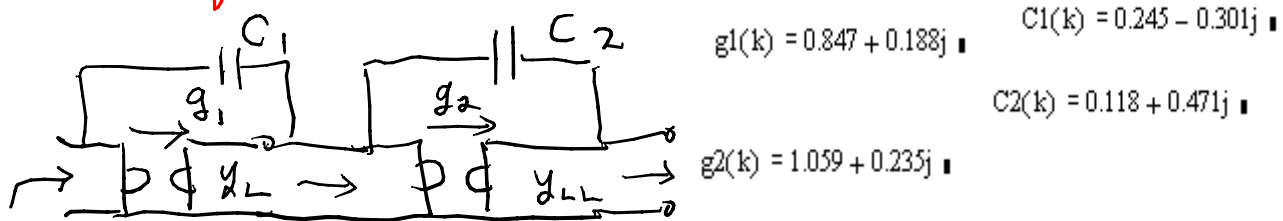


$\frac{dX}{dt}$, $X = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{bmatrix}$ in homework 10/12/05
 $X(0) = [\dots]^T$
 = initial conditions


most A, W are constants \Rightarrow G works in PS since
 A_{44} & $w \Rightarrow$ G value works
 with these as parameters

Returning to cascade synthesis see file even part.pdf for detailed calculations




$$Y(s) = \frac{s^2 + as + b}{s^2 + cs + d} = \frac{s^2 + 2s + 4}{s^2 + 2.125s + 6.25}$$

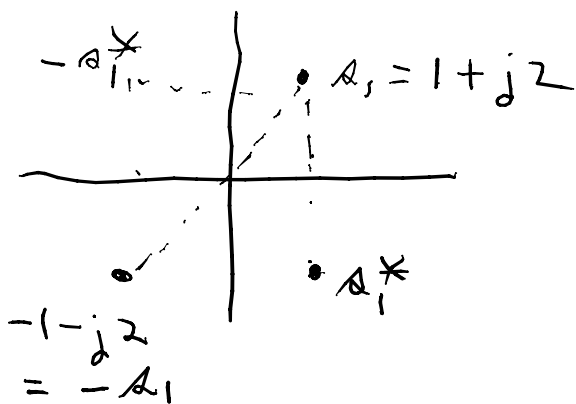; Ev $y(s) = 0$
 $\Rightarrow s = \pm(1 + j2)$
 $\& \pm(1 - j2)$



$$Y(s) = C s \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + g \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} + \frac{1}{Ls} \begin{bmatrix} 1 & -\frac{1}{T} \\ -\frac{1}{T} & \frac{1}{T^2} \end{bmatrix}$$
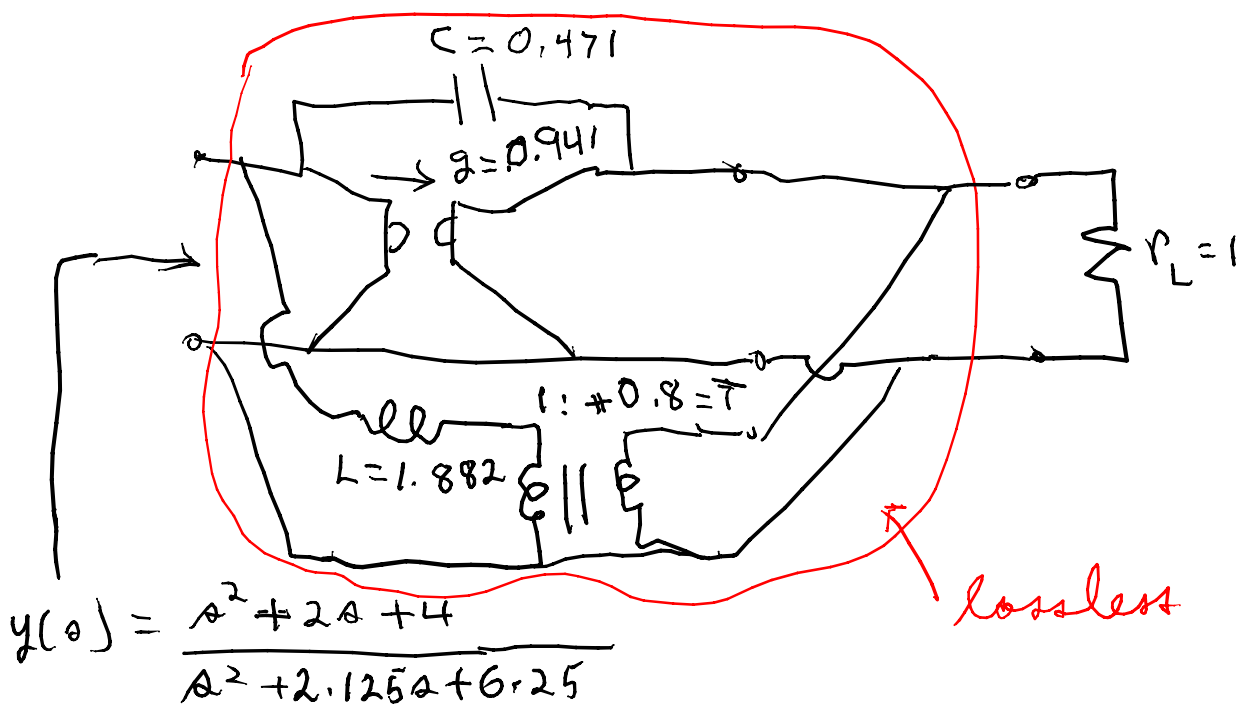
$$= 0.471s \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + 0.941 \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} + \frac{1}{1.882s} \begin{bmatrix} 1 & -\frac{1}{0.8} \\ -\frac{1}{0.8} & \frac{1}{0.64} \end{bmatrix}$$



Lossless: $P_{ave}(j\omega) \equiv 0$ for almost all ω
 $s = \sigma + j\omega$ with $\sigma = 0$

Ex: admittance

$$\begin{aligned}
 P_{ave}(j\omega) &= \operatorname{Re}(V_{C_j\omega}^{T*} I(j\omega)) \\
 &= \frac{1}{2} [V_{C_j\omega}^{T*} I(j\omega) + I(j\omega)^T V_{C_j\omega}] \\
 &= 2 [V_{C_j\omega}^{T*} Y(j\omega) V_{C_j\omega} + V_{C_j\omega}^{T*} Y(j\omega)^T V_{C_j\omega}] \\
 &= V_{C_j\omega}^{T*} \left[\frac{1}{2} (Y(j\omega) + Y(j\omega)^T) \right] V_{C_j\omega} = \mathbf{0}_{1 \times 1}
 \end{aligned}$$

\uparrow
lossless

holds for all $V(j\omega)$ & "all" ω :

$$\therefore Y(j\omega) + Y(j\omega)^T = 0$$

if $Y(s)$ has real coefficients then $Y(j\omega)^* = Y(-j\omega)$

if rational also then this is zero on a dense set of s on $s = j\omega$; here $Y(-s)$ & $Y(s)$ are analytic functions $\Rightarrow Y(s) + Y^T(-s) \equiv 0_n$ for all s .

For transistor models see the VLSI page accessed via the 610 web page (at bottom).