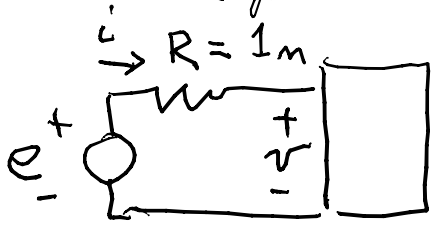


p. 342 lossless synthesis
(of reactance functions)

10/17/05



$e \in \mathcal{L}_2 = \text{Lebesgue}$

$$\|e\|_{\mathcal{L}_2}^2 = \int_{-\infty}^{\infty} e^{T*}(t) e(t) dt < \infty$$

$$e = v + i$$

$$e^{T*} e = (v+i)^{T*} (v+i) = v^{T*} v + i^{T*} i + v^{T*} i + i^{T*} v$$

$$\|e\|_{\mathcal{L}_2}^2 = \|v\|_{\mathcal{L}_2}^2 + \|i\|_{\mathcal{L}_2}^2$$

$$+ 2 \operatorname{Re} \int_{-\infty}^{\infty} v^{T*}(t) i(t) dt \quad \text{if } \operatorname{Re} \int_{-\infty}^{\infty} v^{T*} i \geq 0$$

(passive)

then $v, i \in \mathcal{L}_2$

Lossless means $\int_{-\infty}^{\infty} v^{T*} i dt = 0$

\Rightarrow energy is dissipated in terminating R

$$\text{Lossless} \Rightarrow Y(j\omega) + Y^{T*}(j\omega) = 0_n$$

if $Y(s)$ are rational with real coefficients then


$$* \text{ goes onto } j\omega \Rightarrow Y(j\omega) + Y^T(-j\omega) = 0_n$$

if rational can extend to $s = \sigma + j\omega$ by setting $\omega = s/j$ valid in all $s = \sigma + j\omega$ except at poles.

$$Y(s) + Y^T(-s) = 0_n \quad (\text{except possibly at poles})$$

$$Y(s) = -Y^T(-s) = -Y_*^T(s) \quad \leftarrow \text{Hurwitz conjugate}$$

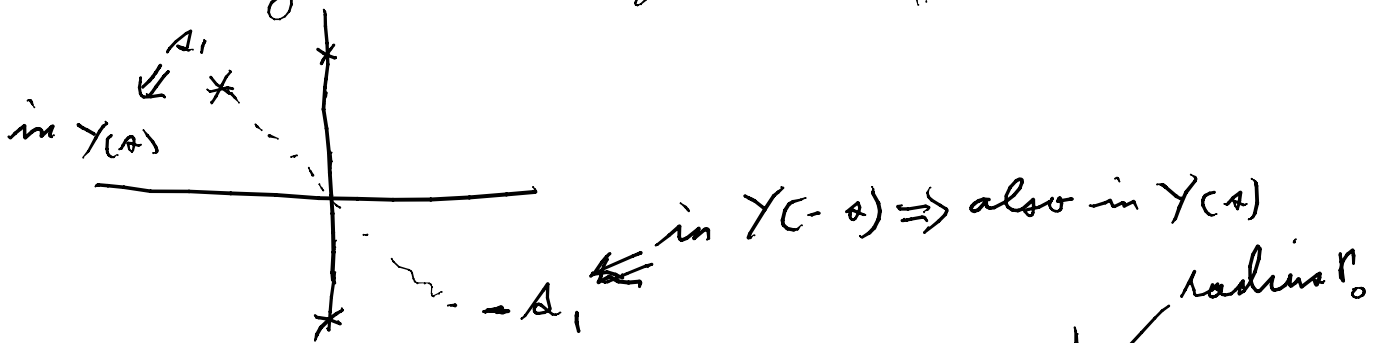all poles of X are on the $j\omega$ axis, if positive-real



\therefore no poles in $\sigma > 0$ or $\sigma < 0$

For $n=1$, $Y(s) = -Y(-s)$

near a pole $Y(s) \sim \frac{a}{(s+j\omega_0)^k}$

$$k \sim \operatorname{Re} \left(\frac{a}{(s+j\omega_0)^k} \right) = \operatorname{Re} \frac{|a|e^{j\angle a}}{r e^{j(\angle a - \omega_0)k}}$$

$\angle a = 0$ & $k=1$ if pos. real

\Rightarrow poles on $j\omega$ axis are simple and residues (a)

are positive (real)

Ex: $Y(s) = \frac{2s}{s^2+4}$; $Y(s) = -Y(-s)$

$$= \frac{a_1}{s+j2} + \frac{a_1^*}{s-j2}$$

$$a_1 = (s+j2) \left[\frac{2s}{s^2+4} - \frac{a_1^*}{s-j2} \right] = \frac{2s}{s-j2} + (s+j2) \left(\frac{-a_1^*}{s-j2} \right)$$


as $a_1 = \text{const}$ set $s = -j2$

$$= \frac{-j4}{2(-j2)} + 0 = 1$$

$$y(s) = \frac{1}{s + j2} + \frac{1}{s - j2} = \frac{2s}{s^2 + 4}$$


$\therefore y(s)$ is a lossless PR function
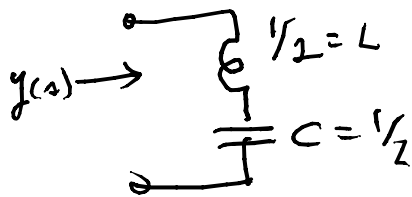
$$y(s) = \frac{2s}{s^2 + 4} = \frac{1}{\frac{s^2}{2s} + \frac{4}{2s}} = \frac{1}{\frac{s}{2} + \frac{2}{s}} \quad \text{imp. admittance}$$



for a Richards' function synthesis can use any k as $y(s)$ has an identically zero even part.

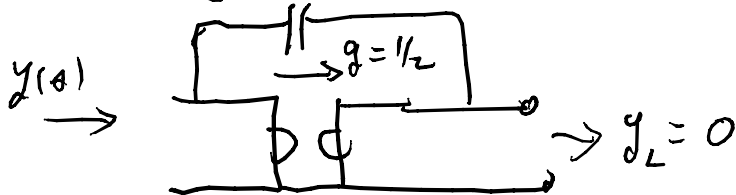Ex: $k=2$ $y(k) = \frac{2k}{k^2 + 4} = \frac{4}{8} = 1/2$, $g = y(k) = 1/2$
 $C = 1/4$ $C = y(k)/k = 1/4$



Ex: If $y(s)$ is PR then so is $\frac{1}{y(s)} = z(s)$

$y(s) = \frac{2s^2}{s^2 + 4}$; not lossless as not odd
 $z(s) \neq -z(-s) = \frac{-2s^2}{s^2 + 4}$

$z(s) = \frac{s^2 + 4}{2s^2}$; has a double pole at $s=0$
 so can not be PR


\therefore no passive circuit exists for this $y(s)$

If $Y(s)$ is lossless, poles and zeros alternate on the $j\omega$ axis:

$$Y(s) = k_{\infty} s + \frac{k_0}{s} + \sum_{i=1}^m \frac{2k_i s}{s^2 + \omega_{k_i}^2} \quad \text{for } k_i's \geq 0$$

$$Y(j\omega) = jk_{\infty} \omega - j\frac{k_0}{\omega} + \sum_{i=1}^m \frac{j 2k_i \omega}{-\omega^2 + \omega_{k_i}^2} = jX(\omega)$$
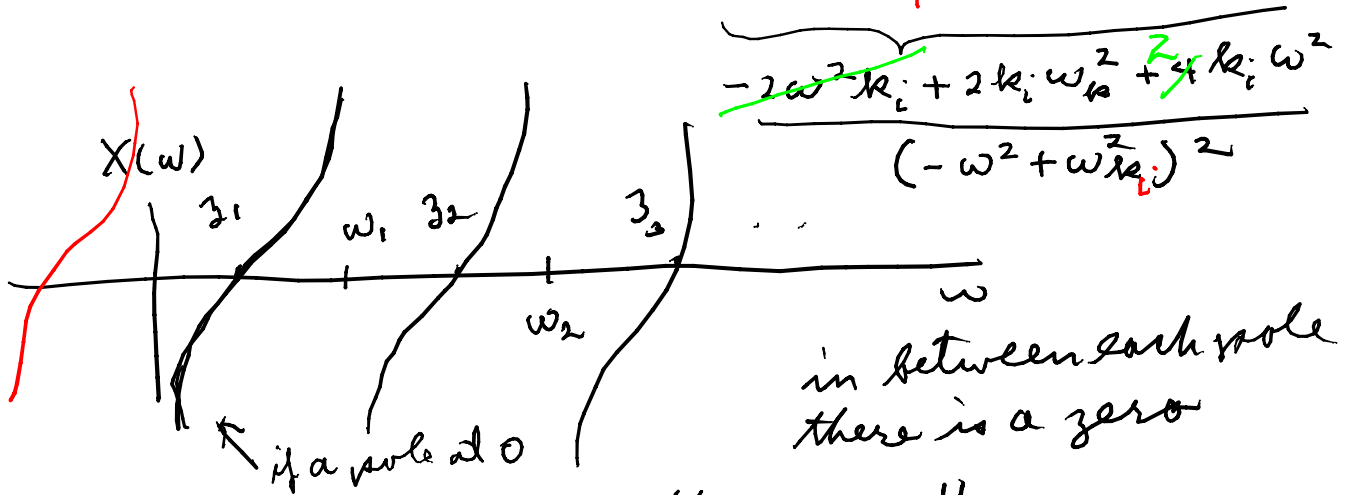
$$\frac{dX(\omega)}{d\omega} = k_{\infty} + \frac{k_0}{\omega^2} + \sum_{i=1}^m \frac{2k_i}{(-\omega^2 + \omega_{k_i}^2)} - \frac{2k_i \omega (-2\omega)}{(-\omega^2 + \omega_{k_i}^2)^2} \geq 0$$



$X(\omega) = -X(-\omega)$ is the "reactance"

\therefore
 Ex: $Y(s) = \frac{s(s^2+3)}{s^2+1}$ is PR & lossless

but $Y(s) = \frac{s(s^2+3)}{s^2+5}$ is not as poles and zeros do not alternate

$Y(s) = \frac{s(s^2+3)^2}{s^2+1}$ is not as $Y(s) = 1/s$ has a double pole at $s = \pm j\sqrt{3}$

$Y(s)$ lossless (PR) yields

2nd Foster form =

partial fraction expansion of $Y(s)$



$$Y_i(s) = \frac{2k_i s}{s^2 + \omega_{k_i}^2} = \frac{1}{\frac{s}{2k_i} + \frac{\omega_{k_i}^2}{2k_i s}}$$

$$C_i = \frac{2k_i}{\omega_{k_i}^2}, \quad L_i = \frac{1}{2k_i}$$


1st Foster \Rightarrow partial fraction expansion of $Z(s)$

$$Z(s) = \frac{1}{Y(s)} = \hat{k}_\infty s + \frac{\hat{k}_0}{s} + \sum_{i=1}^{\hat{m}} \frac{2\hat{k}_i s}{s^2 + \hat{\omega}_i^2}$$

$$L = \hat{k}_\infty \quad C = 1/\hat{k}_0$$


$$L_i = 2\hat{k}_i / \hat{\omega}_i^2$$

$$C_i = \frac{1}{2\hat{k}_i}$$

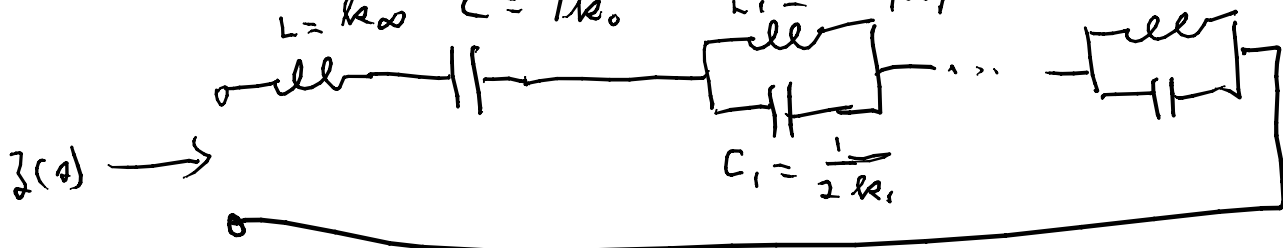

2 other Canonical forms are those due to Cauer

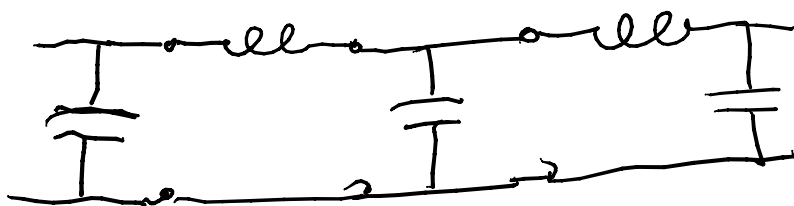1st; removes poles at ∞ , makes a continued fraction expansion:



gives this ladder structure

removing poles at zero

gives 2nd order

