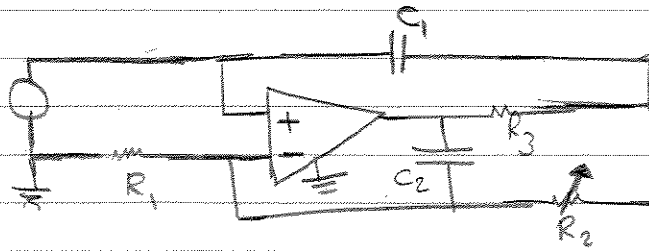


(2) (a), (b)



KCL:

$$i_1 + i_6 - i_7 = 0$$

$$i_2 + i_3 + i_6 = 0$$

$$i_3 + i_5 + i_8 = 0$$

$$i_4 - i_5 - i_6 + i_7 - i_8 = 0$$

KVL: $-v_2 - v_3 + v_4 + v_5 = 0$

$$-v_1 - v_2 + v_4 + v_6 = 0$$

$$v_1 - v_4 + v_7 = 0$$

$$-v_3 + v_4 + v_8 = 0$$

a: $v_i = B_i i_i$ so: device equations are as follows:

$$S C_1 v_1 = i_1$$

$$v_5 = k v_4$$

$$S C_2 v_2 = i_2$$

$$G_3 v_6 = i_6$$

$$v_3 = v + 0.1 i_3$$

$$G_2 v_7 = i_7$$

$$i_3 = -i$$

$$G_1 v_8 = i_8$$

$$i_4 = 0$$

So from the above device equations:

$$\begin{bmatrix}
 sC_1 & & & & & & & & \\
 & sC_2 & & & & & & & \\
 & & 1 & & & & & & \\
 & & & k & & & & & \\
 & & & & -1 & & & & \\
 & & & & & G_3 & & & \\
 & & & & & & G_2 & & \\
 & & & & & & & G_1 & \\
 & & & & & & & & G_1
 \end{bmatrix}
 \begin{bmatrix}
 v_1 \\
 v_2 \\
 v_3 \\
 v_4 \\
 v_5 \\
 v_6 \\
 v_7 \\
 v_8
 \end{bmatrix}
 +
 \begin{bmatrix}
 0 \\
 0 \\
 -v \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{bmatrix}
 =
 \begin{bmatrix}
 1 & & & & & & & & \\
 & 1 & & & & & & & \\
 & & 0 & & & & & & \\
 & & & 1 & & & & & \\
 & & & & 1 & & & & \\
 & & & & & 1 & & & \\
 & & & & & & 1 & & \\
 & & & & & & & 1 & \\
 & & & & & & & & 1
 \end{bmatrix}$$

$$\begin{bmatrix}
 i_1 \\
 i_2 \\
 i_3 \\
 i_4 \\
 i_5 \\
 i_6 \\
 i_7 \\
 i_8
 \end{bmatrix}$$

From KCL:

$$\left[\begin{array}{cccc|cccc}
 1 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\
 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0 \\
 0 & 0 & 1 & 0 & 1 & 0 & 0 & 1 \\
 0 & 0 & 0 & 1 & -1 & -1 & 1 & -1
 \end{array} \right] i_b = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow C = \text{cutset Matrix} = \left[\begin{array}{cccc|cccc}
 1 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\
 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0 \\
 0 & 0 & 1 & 0 & 1 & 0 & 0 & 1 \\
 0 & 0 & 0 & 1 & -1 & -1 & 1 & -1
 \end{array} \right]$$

From KVL:

$$\left[\begin{array}{cccc|cccc}
 0 & -1 & -1 & 1 & 1 & 0 & 0 & 0 \\
 -1 & -1 & 0 & 1 & 0 & 1 & 0 & 0 \\
 1 & 0 & 0 & -1 & 0 & 0 & 1 & 0 \\
 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1
 \end{array} \right] v_b = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow T = \left[\begin{array}{cccc|cccc}
 0 & -1 & -1 & 1 & 1 & 0 & 0 & 0 \\
 -1 & -1 & 0 & 1 & 0 & 1 & 0 & 0 \\
 1 & 0 & 0 & -1 & 0 & 0 & 1 & 0 \\
 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1
 \end{array} \right]$$

from ket:

hw #1

ENEE 610

Sana Z Adil
10/18/05

$$i_t = \begin{bmatrix} 0 & -1 & 1 & 0 \\ -1 & -1 & 0 & 0 \\ -1 & 0 & 0 & -1 \\ 1 & 1 & -1 & 1 \end{bmatrix} i_l$$

from kvl

$$v_l = \begin{bmatrix} 0 & 1 & 1 & -1 \\ 1 & 1 & 0 & -1 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 \end{bmatrix} v_t$$

$$a \begin{bmatrix} v_t \\ v_l \end{bmatrix} - ae = b \begin{bmatrix} i_t \\ i_l \end{bmatrix} \Rightarrow a \begin{bmatrix} I_t \\ k_t \end{bmatrix} v_t - e = b \begin{bmatrix} -k_t^T \\ I_l \end{bmatrix} i_l$$

$$0 = i_l^T v = i_l^T \begin{bmatrix} v_t \\ k_t v_t \end{bmatrix} = i_l^T [k_l^T + k_t] v_t$$

d, e, f

$$-v_2 - v_3 + (k+1)v_4 = 0 \quad \text{if } k \neq -1, v_4 = \frac{1}{k+1} (v_2 + v_3)$$

$$v_3 = v$$

$$G_1 v_3 - G_1 v_4 = G_1 v - \frac{G_1}{1+k} (v_2 + v) = i_8$$

$$i_6 = G_3 (v_1 + v_2 - v_4) = G_3 \left(v_1 + v_2 - \frac{1}{1+k} (v_2 + v_3) \right)$$

$$i_7 = G_2 (-v_1 + v_4) = G_2 \left(-v_1 + \frac{1}{1+k} (v_2 + v_3) \right)$$

$$i_5 + i_6 - i_7 + i_8 = 0 \Rightarrow i_5 = i_7 - i_6 - i_8 = -G_3 \left(v_1 + v_2 - \frac{1}{1+k} (v_2 + v_3) \right)$$

$$-G_2 \left(-v_1 + \frac{1}{1+k} (v_2 + v_3) \right) + G_1 v - \frac{G_1}{1+k} (v_2 + v)$$

10/18/05

$$\textcircled{1} \quad sCv_1 = -i5 + i7 = -G_3 \left(v_1 + v_2 - \frac{1}{1+k} [v_2 + v] \right) + G_2 \left(-v_1 + \frac{1}{1+k} [v_2 + v] \right)$$

$$\textcircled{2} \quad sCv_2 = -i5 - i6 = -[-i5 + i7 - i8] - i6 = -i7 + i8$$

$$= -G_2 \left[-v_1 + \frac{1}{1+k} [v_2 + v] \right] + G_1 \left(v - \frac{1}{1+k} [v_2 + v] \right)$$

$$\Rightarrow sCv_2 = G_2 v_1 + \left[-G_2 - G_1 \right] \frac{1}{1+k} v_2 + (-G_2 - G_1) \frac{1}{1+k} v + G_1 v$$

$$i = -i3 = -(-i5 - i8) = -i6 - i7 - i8 + i8 = -i6 - i7$$

$$= -G_3 \left(v_1 + v_2 - \frac{1}{1+k} [v_2 + v] \right) - G_2 \left(-v_1 + \frac{1}{1+k} [v_2 + v] \right)$$

So

$$\begin{bmatrix} c_1 & 0 \\ 0 & c_2 \end{bmatrix} s \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -(G_2 + G_3) & -G_3 + \frac{G_2 + G_3}{1+k} \\ G_2 & -G_1 - G_2 \\ & \frac{-G_1 - G_2}{1+k} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$+ \begin{bmatrix} \frac{G_2 + G_3}{1+k} \\ G_1 + \frac{G_1 - G_2}{1+k} \end{bmatrix} v$$

$$i = \begin{bmatrix} G_2 - G_3 & -G_3 + \frac{G_3 - G_2}{1+k} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} G_3 - G_2 \\ \frac{G_3 - G_2}{1+k} \end{bmatrix} v$$

$$\Rightarrow Y = \begin{bmatrix} \frac{G_3 - G_2}{1+k} \end{bmatrix} + \begin{bmatrix} G_2 - G_3 & -G_3 + \frac{G_3 - G_2}{1+k} \\ -G_2 & -G_3 + \frac{G_3 - G_2}{1+k} \end{bmatrix} \begin{bmatrix} sCv_1 + \frac{G_2 + G_3}{1+k} v \\ sCv_2 + \frac{G_2 + G_1}{1+k} v \end{bmatrix}$$

$$\begin{bmatrix} \frac{G_2 + G_3}{1+k} \\ G_1 + \frac{G_2 + G_1}{1+k} \end{bmatrix}$$

HW#1

ENEE 610

Sana Z Adl
10/19/05

5

if $k \rightarrow \infty$ then $Y \approx \begin{bmatrix} G_2 - G_3 & -G_3 \end{bmatrix} \begin{bmatrix} sC_1 + (G_2 + G_3) & G_3 \\ -G_2 & sC_2 \end{bmatrix} \begin{bmatrix} 0 \\ G_1 \end{bmatrix}$

$$Y = \begin{bmatrix} G_2 - G_3 & -G_3 \end{bmatrix} \begin{bmatrix} -G_3 G_1 \\ sC_1 + (G_2 + G_3)/G_1 \end{bmatrix} \frac{1}{s^2 C_1 C_2 + sC_2 (G_2 + G_3) + G_2 G_3}$$

for $C_1 \gg C_2$, $G_3 \gg G_2 \sim G_1 \Rightarrow Y = -\frac{G_3}{3} \begin{bmatrix} 1 & 1 \end{bmatrix} \begin{bmatrix} -G_3 G_1 \\ sC_1 G_1 \end{bmatrix} \frac{1}{-G_2 G_3}$

$$\approx \frac{G_1 s C_1}{G_2}$$