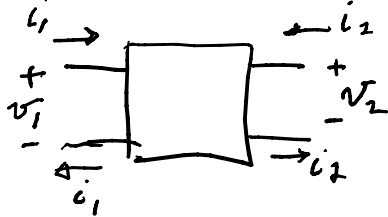


EE610
09/05/07


admittance matrix 2-port



$$P_{in}(t) = v_1(t)i_1(t) + v_2(t)i_2(t)$$

$s = \sigma + j\omega$, d/dt , Laplace transform variable, s in e^{st}
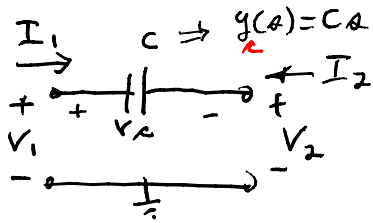
$$Y(s) V(s) = I(s); \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$





$$I_1 = -I_2$$


$$V_1 = V_C + V_2 = \frac{I_C}{y_C(s)} + V_2 = \frac{I_1}{C s} + V_2$$

$$\begin{aligned} I_1 &= C s (V_1 - V_2) \\ I_2 &= -C s (V_1 - V_2) \end{aligned} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} C s & -C s \\ -C s & C s \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow Y(s) = C s \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$

VCCS \Rightarrow C of Spice

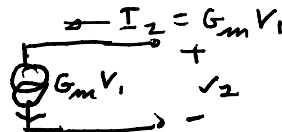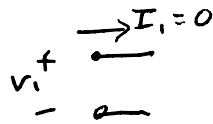

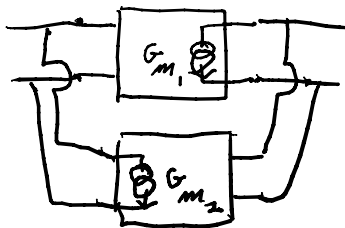
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ G_m & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$Y = Y_{G_{m1}} + Y_{G_{m2}} = \begin{bmatrix} 0 & 0 \\ G_{m1} & 0 \end{bmatrix} + \begin{bmatrix} 0 & G_{m2} \\ 0 & 0 \end{bmatrix}$$


useful to choose $G_{m2} = -G_{m1} = g$
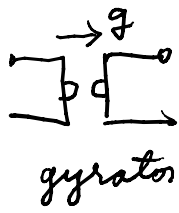
$$\begin{aligned} \text{since } P_{in}(t) &= v_1 i_1 + v_2 i_2 = v_1 \cdot G_{m2} v_2 + v_2 \cdot G_{m1} v_1 = v_2 v_1 (G_{m2} + G_{m1}) \\ &= 0 \text{ if } G_{m2} = -G_{m1} \end{aligned}$$



$$\Rightarrow Y = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} = -Y^T \quad (\text{skew-symmetric matrix})$$

\Rightarrow basic nonreciprocal element

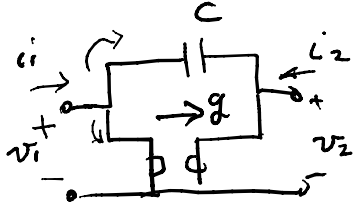

$$Y = Y_{cap} + Y_{gys} = \begin{bmatrix} c\alpha & -c\alpha \\ -c\alpha & c\alpha \end{bmatrix} + \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix}$$


$$= \begin{bmatrix} c\alpha & -g-c\alpha \\ g-c\alpha & c\alpha \end{bmatrix}; \det Y = (c\alpha)^2 - [-(g+c\alpha)(g-c\alpha)]$$

$$= (c\alpha)^2 + g^2 - (c\alpha)^2 = g^2$$


$$V = ZI, \quad Z = Y^{-1} = \frac{1}{g^2} \begin{bmatrix} c\alpha & (-1)(-g-c\alpha) \\ (-1)(g-c\alpha) & c\alpha \end{bmatrix} = \frac{1}{g^2} \begin{bmatrix} c\alpha & g+c\alpha \\ -g+c\alpha & c\alpha \end{bmatrix}$$

$$= \begin{bmatrix} \alpha(c/g^2) & \alpha(c/g^2) + 1/g \\ \alpha(c/g^2) - 1/g & \alpha(c/g^2) \end{bmatrix} = \alpha \left(\frac{c}{g^2} \right) \begin{bmatrix} 1 & 1 \\ -1 & 1 \end{bmatrix} + \begin{bmatrix} 0 & 1/g \\ -1/g & 0 \end{bmatrix}$$
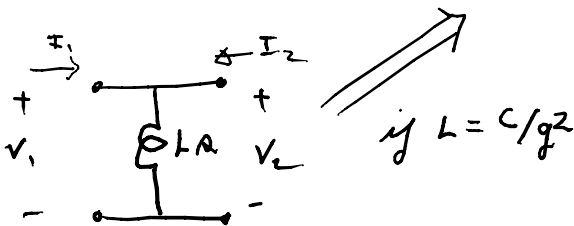
$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow Z(\alpha) = \begin{bmatrix} \alpha(c/g^2) & \alpha(c/g^2) \\ \alpha(c/g^2) & \alpha(c/g^2) \end{bmatrix}$$





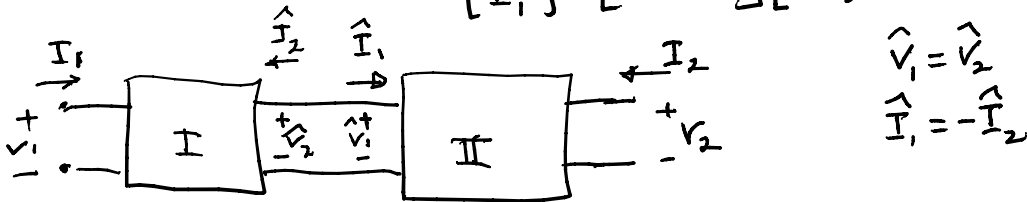Chain matrix: $Y \Rightarrow \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$



$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = Y_I \begin{bmatrix} \hat{v}_2 \\ -\hat{i}_2 \end{bmatrix} = \begin{bmatrix} \hat{v}_1 \\ \hat{i}_1 \end{bmatrix} = Y_{II} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} \Rightarrow \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = Y_I \cdot Y_{II} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

$$Y = Y_I \cdot Y_{II}$$

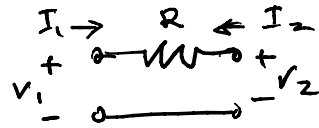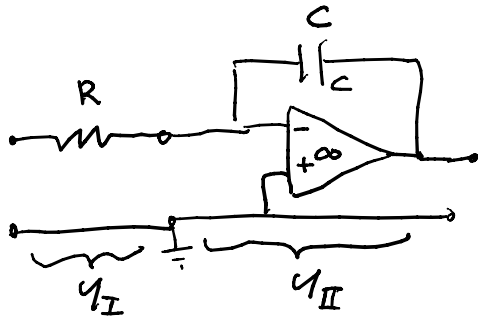

$$I_1 = -I_2$$

$$V_1 = V_2 - R I_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \mathcal{Y} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


$$\mathcal{Y} = \begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$

$$\mathcal{Y} = \mathcal{Y}_I \cdot \mathcal{Y}_{II}$$

$$= \begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ -AC & 0 \end{bmatrix}$$

$$= \begin{bmatrix} -ARC & 0 \\ -AC & 0 \end{bmatrix}$$
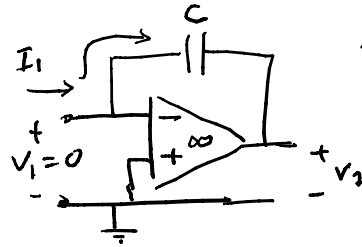
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} -ARC & 0 \\ -AC & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \Rightarrow V_2 = \frac{-1}{ARC} V_1 \Rightarrow \frac{V_2}{V_1} = \frac{-1}{ARC}$$




$$AC V_2 = -I_1$$

$$V_1 = 0$$

$$I_1 = -AC V_2$$
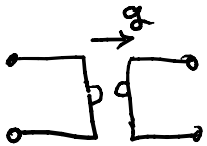
$$\mathcal{Y}_{II} = \begin{bmatrix} 0 & 0 \\ -AC & 0 \end{bmatrix}$$




$$I_1 = -g V_2$$

$$I_2 = g V_1$$

$$V_1 = \left(-\frac{1}{g}\right) (-I_2)$$

$$I_1 = -g V_2$$

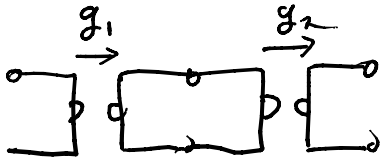
$$\mathcal{Y} = \begin{bmatrix} 0 & -1/g \\ -g & 0 \end{bmatrix}$$



$$\mathcal{Y} = \mathcal{Y}_I \cdot \mathcal{Y}_{II} = \begin{bmatrix} 0 & -1/g_1 \\ -g_1 & 0 \end{bmatrix} \begin{bmatrix} 0 & -1/g_2 \\ -g_2 & 0 \end{bmatrix}$$

$$V_1 = \frac{g_2}{g_1} V_2, I_1 = \frac{g_1}{g_2} (-I_2)$$

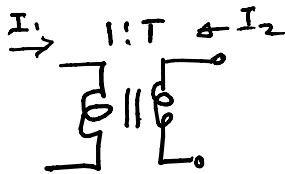
$$= \begin{bmatrix} g_2/g_1 & 0 \\ 0 & g_1/g_2 \end{bmatrix}$$



$$\sum \text{amp turns} = 0 \quad I_1(1) + I_2(T) = 0 \Rightarrow I_1 = -T \cdot I_2$$

$$V_2 = T \cdot V_1 = \frac{g_1}{g_2} V_1$$

$$\text{also gives } T = g_1/g_2$$

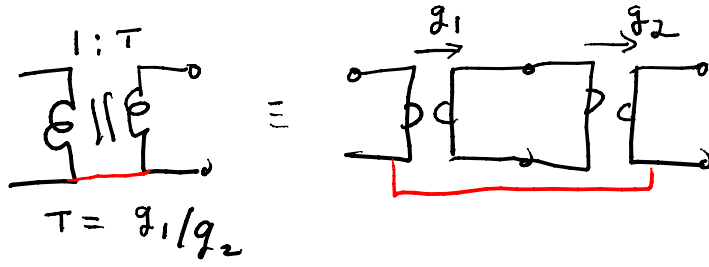

$$T = g_1/g_2$$

$$V_2 = TV_1$$

$$I_1 = -TI_2$$

no 2-port Z or Y for the ideal transformer