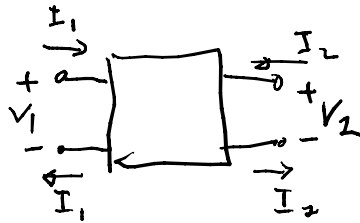


admittance = Y

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



EE 610
09/10/07

$Y = \text{chain}$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$I_2 = y_{21} V_1 + y_{22} V_2 \Rightarrow y_{21} V_1 = I_2 - y_{22} V_2 \Rightarrow V_1 = \frac{1}{y_{21}} (-I_2 - y_{22} V_2)$$

$$I_1 = y_{11} V_1 + y_{12} V_2 = y_{11} \left\{ \frac{1}{y_{21}} [-I_2 - y_{22} V_2] \right\} + y_{12} V_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} -\frac{y_{22}}{y_{21}} & -\frac{1}{y_{21}} \\ -\frac{\Delta y}{y_{21}} & \frac{y_{12}}{y_{21}} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \Leftarrow Y \text{ as a function of } Y$$


$\Delta y = y_{11} y_{22} - y_{12} y_{21}$

$$V_1 = A V_2 - B I_2 \Rightarrow +B I_2 = A V_2 - V_1 \Rightarrow I_2 = \frac{1}{B} (-V_1 + A V_2)$$

$$I_1 = C V_2 - D I_2 = C V_2 - D \left\{ \frac{-V_1 + A V_2}{B} \right\} = +\frac{D}{B} V_1 + \left(\frac{BC - AD}{B} \right) V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{D}{B} & -\frac{\Delta y}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \Leftarrow Y \text{ as a function of } Y$$

$\Delta y = AD - BC$

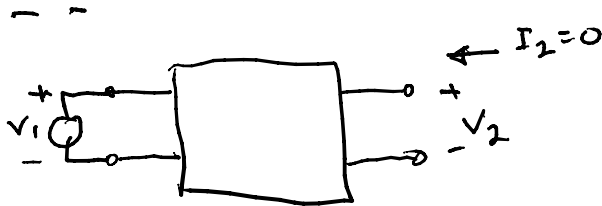


$$V_1 = A V_2 + B (-I_2) \Big|_{I_2=0} = A V_2$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{1}{A} \text{ when } I_2 = 0 \text{ (an open circuit load)}$$

in terms of Y

$$I_2 = 0 = y_{21} V_1 + y_{22} V_2 \Rightarrow \frac{V_2}{V_1} \Big|_{I_2=0} = -\frac{y_{21}}{y_{22}}$$

Now load

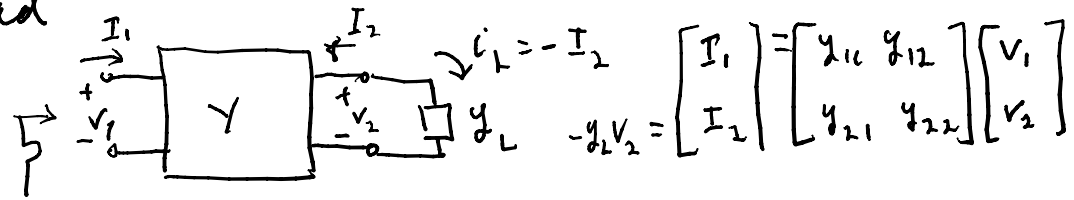

y_{in}


$$-y_L V_2 = y_{21} V_1 + y_{22} V_2 \Rightarrow (-y_L - y_{22}) V_2 = y_{21} V_1$$

$$\frac{V_2}{V_1} = -\frac{y_{21}}{y_{22} + y_L} \Rightarrow I_1 = y_{11} V_1 - y_{12} \frac{y_{21}}{y_{22} + y_L} V_1 = \left(\frac{y_{11} y_{22} + y_{11} y_L - y_{12} y_{21}}{y_{22} + y_L} \right) V_1$$

$$\frac{I_1}{V_1} = y_{in} = \frac{\Delta y + y_{11} y_L}{y_{22} + y_L}$$

next find y_L in terms of y_{in} : $y_{in}(y_{22} + y_L) = \Delta y + y_{11} y_L$
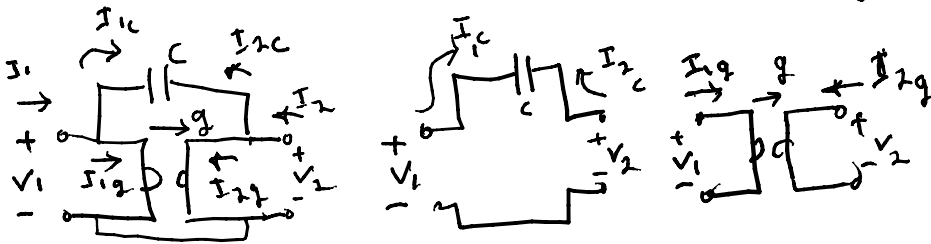
$$(y_{in} - y_{11}) y_L = \Delta y - y_{22} y_{in} \Rightarrow y_L = \frac{\Delta y - y_{22} y_{in}}{y_{in} - y_{11}}$$




$$I_1 = I_{1c} + I_{1g}$$

$$I_2 = I_{2c} + I_{2g}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_c = \begin{bmatrix} ca & -ca \\ -ca & ca \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_g = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_c + \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_g = \left\{ \begin{bmatrix} ca & -ca \\ -ca & ca \end{bmatrix} + \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \right\} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$
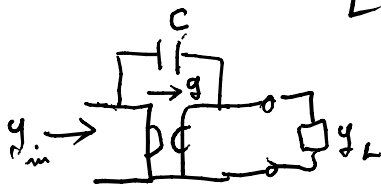
$$= \begin{bmatrix} ca & -ca - g \\ -ca + g & ca \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$




$$\Delta y = (ca)^2 - [-(ca + g)(-ca + g)]$$

$$(ca)^2 - [(ca)^2 - g^2] = g^2$$

$$y_{in} = \frac{\Delta y + y_{11} y_L}{y_{22} + y_L} = \frac{g^2 + CA \cdot y_L}{CA + y_L}$$

$$y_L = \frac{\Delta y - y_{22} y_{in}}{y_{in} - y_{11}} = \frac{g^2 - CA \cdot y_{in}}{y_{in} - CA} = \frac{g^2}{g^2} \left[\frac{1 - \left(\frac{CA}{g}\right) \cdot \frac{y_{in}}{g}}{\frac{1}{g} \left(\frac{y_{in}}{g} - \frac{CA}{g}\right)} \right]$$

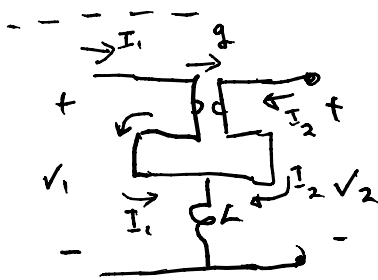
$$\frac{y_L}{g} = \frac{1 - \left(\frac{CA}{g}\right) \left(\frac{y_{in}}{g}\right)}{\left(\frac{y_{in}}{g}\right) - \left(\frac{CA}{g}\right)} \Rightarrow \text{leads to a Richards' function (P.I. Richards)}$$



here the Z matrices add $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = Z \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

$$Z = \frac{1}{g^2} \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} \Delta L & \Delta L \\ \Delta L & \Delta L \end{bmatrix}$$

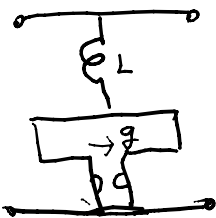
$$= \begin{bmatrix} \Delta L & \frac{1}{g} + \Delta L \\ -\frac{1}{g} + \Delta L & \Delta L \end{bmatrix}; \Delta Z = \frac{1}{g^2}$$



here Z no longer holds as $V_1 = V_2$ for the bottom g which destroys the law giving Z_{eq}

need the same law for the sub-circuits before and after connect.

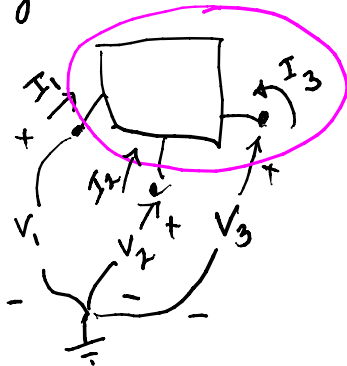Indefinite admittance; sum of entries in ^{any} row add to zero & the same for any column.



$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{ind} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

by KCL: $I_1 + I_2 + I_3 = 0$

