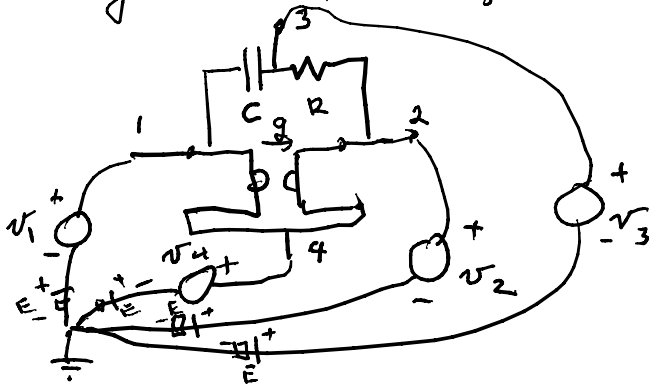



Indefinite Y , Y_{indef}

EE 610
09/17/07



$$i = Y_{indef} (v + E \begin{bmatrix} 1 \\ \vdots \\ 1 \end{bmatrix})$$

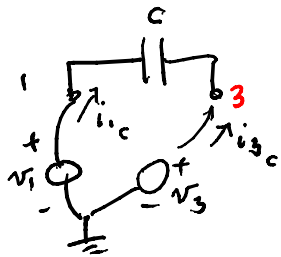
sum of entries in a row is zero & same for sum of entries in a column of Y_{indef} .



$$i_{1c} = AC(v_1 - v_3)$$

$$i_{3c} = AC(v_3 - v_1)$$

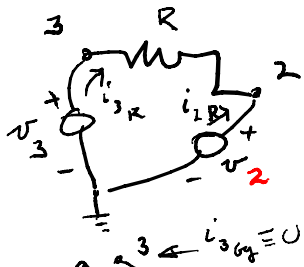
$$Y_{indef C} = \begin{bmatrix} AC & 0 & -AC & 0 \\ 0 & 0 & 0 & 0 \\ -AC & 0 & AC & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$



$$i_{2R} = G(v_2 - v_3) \quad G = 1/R$$

$$i_{3R} = G(v_3 - v_2)$$
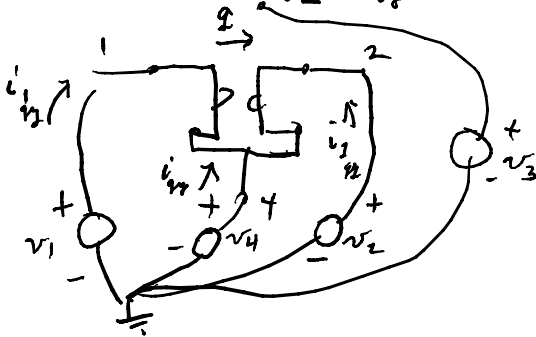
$$Y_{indef R} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & G & -G & 0 \\ 0 & -G & G & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$



$$i_{1R} = -g(v_2 - v_4)$$

$$i_{2R} = g(v_1 - v_4)$$

$$i_{3GR} = 0$$

$$i_{4R} = -i_{1R} - i_{2R} = -[-g(v_2 - v_4)] - g[v_1 - v_4]$$

$$= -g v_1 + g v_2$$


$$Y_{indef gR} = \begin{bmatrix} 0 & -g & 0 & g \\ g & 0 & 0 & -g \\ 0 & 0 & 0 & 0 \\ -g & g & 0 & 0 \end{bmatrix}$$

$$Y_{ind}^{(A)} = \begin{bmatrix} \alpha C & -g & -\alpha C & g \\ g & G & -G & -g \\ -\alpha C & -G & \alpha C + G & 0 \\ -g & g & 0 & 0 \end{bmatrix}$$


$$i = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = Y_{ind} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

move ground to node 4 $\Rightarrow v_4 = 0$ can scratch out last column as multiplies 0; ignore i_4 as $i_4 = -i_1 - i_2 - i_3$

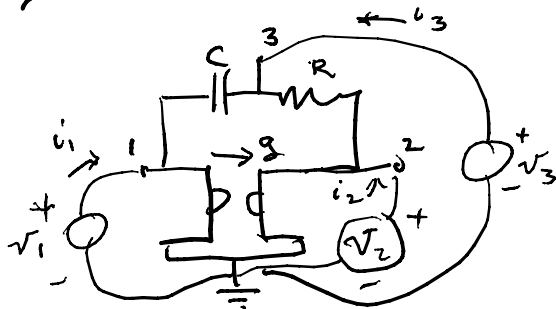gives the nodal admittance, $Y_{node} = \begin{bmatrix} \alpha C & -g & -\alpha C \\ g & G & -G \\ -\alpha C & -G & \alpha C + G \end{bmatrix}$


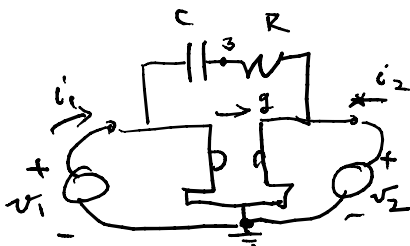
$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = Y_{node} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$



here $i_3 = 0$ but $v_3 \neq 0$; eliminate v_3 from

Y_{node} gives $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$

$$i_3 = 0 = -\alpha C v_1 - G v_2 + (\alpha C + G) v_3 \Rightarrow v_3 = \frac{\alpha C}{\alpha C + G} v_1 + \frac{G}{\alpha C + G} v_2$$


eliminate v_3 from 1st 2 rows:

$$i_1 = \alpha C v_1 - g v_2 - \alpha C \left[\frac{\alpha C}{\alpha C + G} v_1 + \frac{G}{\alpha C + G} v_2 \right] = \frac{\alpha C G}{\alpha C + G} v_1 - \left[g + \frac{\alpha C G}{\alpha C + G} \right] v_2$$

$$i_2 = g v_1 + G v_2 - G \left[\frac{\alpha C}{\alpha C + G} v_1 + \frac{G}{\alpha C + G} v_2 \right] = \left[g - \frac{\alpha C G}{\alpha C + G} \right] v_1 + \frac{\alpha C G}{\alpha C + G} v_2$$


$$Y = \begin{bmatrix} \frac{\alpha C G}{\alpha C + G} & -g - \frac{\alpha C G}{\alpha C + G} \\ g - \frac{\alpha C G}{\alpha C + G} & \frac{\alpha C G}{\alpha C + G} \end{bmatrix}$$

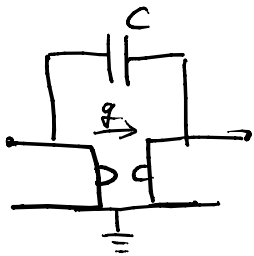if $G \rightarrow \infty$ $Y^{(A)} = \begin{bmatrix} \alpha C & -g - \alpha C \\ g - \alpha C & \alpha C \end{bmatrix}$



is the above with $R=0$

graph for original circuit

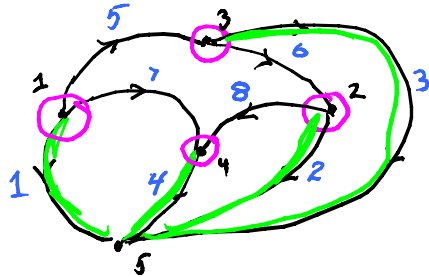

$$b = \# \text{ of branches} = 8$$

$$n = \# \text{ of nodes} = 5$$

$$t = \# \text{ of tree branches} = n - 1$$

(for a chosen tree)

= green branches

$$= 4 = 5 - 1$$

↑
one
"separate
part"

$$l = \# \text{ of cotree branches} = n - t \text{ if}$$

$$= \text{links} = b - t$$

$$= b - (n - 1)$$

↑
A separate
parts

↑
1 sep. part


$t = \# \text{ of independent current equations} = \text{KCL's}$

$l = \# \text{ of independent voltage law eqs} = \text{KVL's}$

$$\text{KCL} = 0 = C i_b$$

$i_b = \text{branch currents, a } b\text{-vector}$

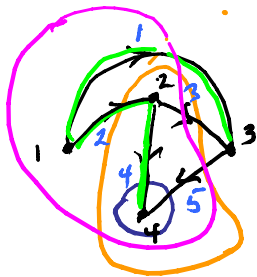$C = \text{cut set matrix, } t \times b \text{ matrix}$



$$C = \begin{bmatrix} 1 & 0 & 1 & 0 & -1 \\ 0 & 1 & -1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix} = 3 \times 5 \text{ matrix}$$

gives 3 linearly independent eqs

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = C \begin{bmatrix} i_{b1} \\ i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \end{bmatrix}$$