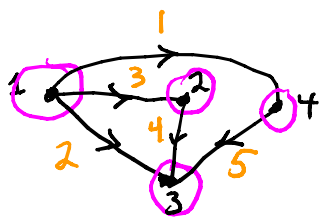


P. 124 3.12

$$n_T = \det(A A^T)$$

augmented incidence matrix A_a

EE610
09/19/07



$$A_a = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \left. \vphantom{\begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}} \right\} n$$


b

remove row 3 \Rightarrow node 3 = reference node


$$A = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$A A^T = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & -1 \\ 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 & -1 & -1 \\ -1 & 2 & 0 \\ -1 & 0 & 2 \end{bmatrix}$$


$$n_T = \det(A A^T) = 12 - 2 - 2 = 8$$

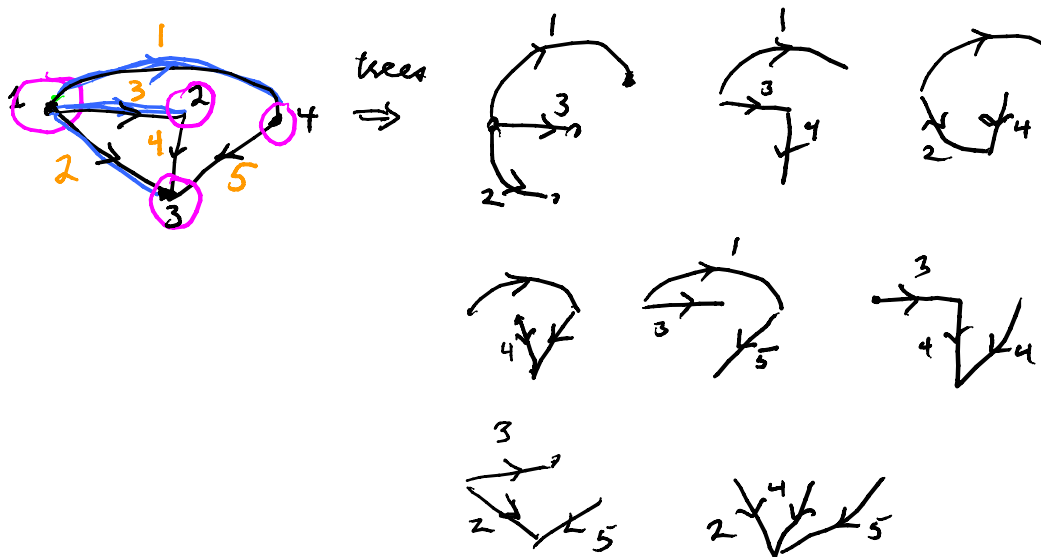

choose a tree, say branches 1, 3, 4

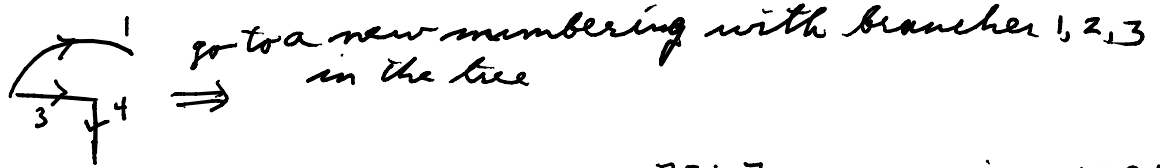


use

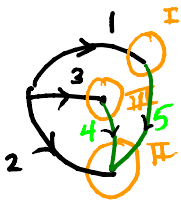

KCL $\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}_b \Rightarrow \underline{0}_t = \underline{e} \underline{i}_b$ KCL

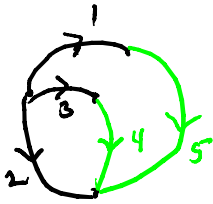$\underline{e} = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 & 0 \end{bmatrix}$, \underline{e} = cut-set matrix



KVL $\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} v_4 - v_2 + v_3 = 0 \\ v_5 - v_2 + v_1 = 0 \end{bmatrix} = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}_b$

$\underline{0}_l = \underline{\sigma} \cdot \underline{v}_b$ $\underline{\sigma}$ = tie-set matrix

$\underline{\sigma} = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix}$


$\underline{e} = \begin{bmatrix} 1_t & | & \underline{k}_r \\ \hline \underline{k}_t & | & 1_l \end{bmatrix}$
 $\underline{\sigma} = \begin{bmatrix} 1_t & | & \underline{k}_r \\ \hline \underline{k}_t & | & 1_l \end{bmatrix}$

$\underline{e} = \begin{bmatrix} 1_t & | & \underline{k}_r \\ \hline \underline{k}_t & | & 1_l \end{bmatrix} \} t$ n $\underline{k}_r = t \times l = \begin{bmatrix} 0 & -1 & 1 \\ 1 & -1 & 0 \end{bmatrix}$

$\underline{\sigma} = \begin{bmatrix} 1_t & | & \underline{k}_r \\ \hline \underline{k}_t & | & 1_l \end{bmatrix} \} l$, $\underline{k}_t = \begin{bmatrix} 0 & -1 & 1 \\ 1 & -1 & 0 \end{bmatrix} = l \times t$

note $\underline{k}_t = -\underline{k}_r^T \Rightarrow$ KCL \Rightarrow KVL or KVL \Rightarrow KCL

$\underline{e} \underline{\sigma}^T = \begin{bmatrix} 1_t & | & \underline{k}_r \\ \hline \underline{k}_t & | & 1_l \end{bmatrix} \begin{bmatrix} \underline{k}_t^T = -\underline{k}_r \\ \hline 1_l \end{bmatrix} = -\underline{k}_r + \underline{k}_r = \underline{0}_{t \times l}$

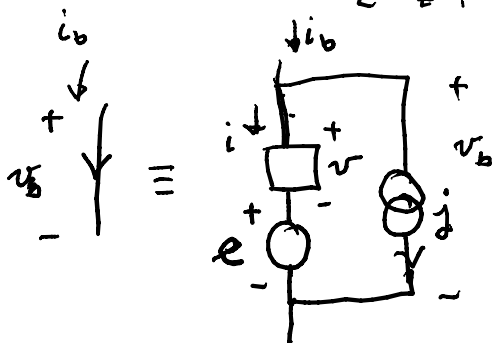

$i_b = i + j$
 $v_b = v + e$

assume an admittance law: $i = Y_b v$

but $v_b = e^T v_t$, $i_b = \mathcal{J}^T i_\ell$

$$0 = \mathcal{J} v_b = [k_t | 1_\ell] \begin{bmatrix} v_t \\ v_\ell \end{bmatrix} = \begin{matrix} 0 \\ -\ell \end{matrix} = k_t v_t + v_\ell \Rightarrow v_\ell = -k_t v_t = k_\ell^T v_t$$

$$v_t = 1_t v_t$$

$$v_b = \begin{bmatrix} v_t \\ v_\ell \end{bmatrix} = \begin{bmatrix} 1_t \\ k_\ell^T \end{bmatrix} v_t = e^T v_t = v_b$$



$$i_b = \mathcal{J}^T i_\ell = i + j = Y_b v_b + j = Y_b e^T v_t + j$$

but $e i_b = 0_t$; $\Rightarrow e i_b = 0 = e \mathcal{J}^T i_\ell = e Y_b e^T v_t + e j$

$$-e j = e Y_b e^T v_t \quad \text{gives } t \text{ eqs. in } t \text{ unknowns } v_t$$

gives current source j

Ex:

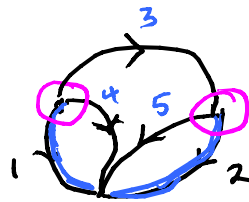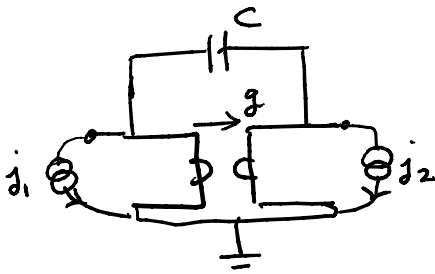

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & +1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$Y_b = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathcal{A}C & 0 & 0 \\ 0 & 0 & 0 & 0 & -g \\ 0 & 0 & 0 & +g & 0 \end{bmatrix}$$

$$= e \cdot i_b$$

$$e Y_b e^T = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathcal{A}C & 0 & 0 \\ 0 & 0 & 0 & 0 & -g \\ 0 & 0 & 0 & g & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & -1 \\ -1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ \mathcal{A}C - \mathcal{A}C \\ 0 & -g \\ g & 0 \end{bmatrix}$$

$$= \begin{bmatrix} \mathcal{A}C & -\mathcal{A}C - g \\ -\mathcal{A}C + g & \mathcal{A}C \end{bmatrix}, \quad -e j = \begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 0 & -1 & 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} j_1 \\ j_2 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -j_1 \\ -j_2 \end{bmatrix}$$

$$\begin{bmatrix} -j_1 \\ -j_2 \end{bmatrix} = \begin{bmatrix} sC & -sC-g \\ -sC+g & sC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \text{2-port admittance description}$$