

Homeworks now due on W

EE 610
10/01/07


minimal here means least number of components

passivity \equiv positive real function

(can not get more energy out than put in)

$Z(s) = -2s$ at $s=1$, $\text{Re} Z(s) = -2 < 0$ so not positive-real

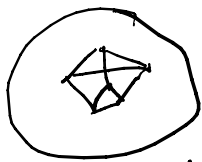For a graph; $v_b^T \cdot i_b = 0$ as = power into the "graph" from the outside



$v_b = e^T v_t$
 $i_b = \sigma^T i_r$ } into $v_b^T i_b = (v_t^T e)(\sigma^T i_r) = 0$ from

but can find a graph with v_t freely chosen & same for i_r here then can cancel v_t & i_r




$\Rightarrow e \sigma^T = 0_{t \times r}$

Now consider 2 circuits with the same graph; $N \subseteq \hat{N}$

$v_t^T e \sigma^T \hat{i}_r = 0$
" " " " " "
 $v_b^T \hat{i}_b$

v_b, i_b \hat{v}_b, \hat{i}_b
 $v_b = e v_t$ $\hat{i}_b = \sigma^T \hat{i}_r$


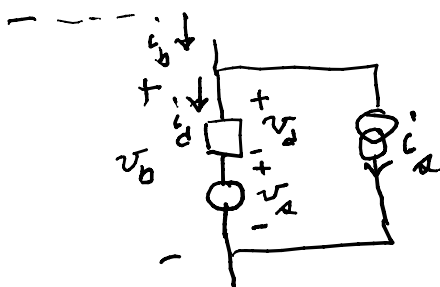
$\Rightarrow v_b^T \hat{i}_b = 0 \Rightarrow$ Tellegen's Theorem



$i_b = i_a + i_d$
 $v_b = v_a + v_d$

d = device
a = independent source

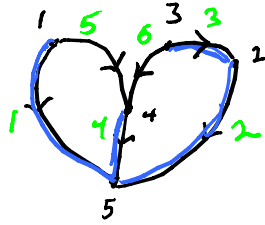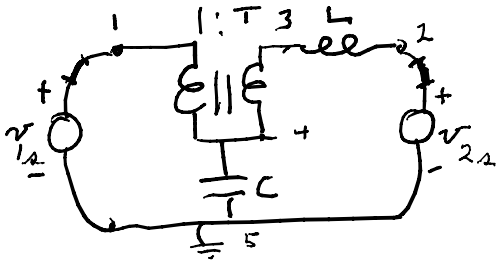$A v_d = B i_a$
 $v_b = e^T v_t, i_b = \sigma^T i_r$



— = tree

here $b=6, t=4, r=2$

laws of transforms

$$i_5 + T i_6 = 0$$

(Σ of Amp turns = 0)

$$v_5 = T v_6$$

$$\begin{matrix} \text{shorts} \rightarrow \\ \text{inductors} \rightarrow \\ \text{capacitors} \rightarrow \\ \Sigma AT = 0 \rightarrow \\ \text{Voltage amp} \rightarrow \end{matrix} \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & AC & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -T & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & At & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & T \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

$$v_a = \begin{bmatrix} v_{1a} \\ v_{2a} \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}; \quad i_a = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Now

$$v_d = v_b - v_a = e^T v_t - v_a$$

$$i_d = i_b - i_a = g^T i_r - i_a$$


$$A v_d = B i_d$$

$$A [e^T v_t - v_a] = B [g^T i_r - i_a]$$

$$A e^T v_t - B g^T i_r = A v_a - B i_a$$

$$= \underbrace{[A e^T \quad -B g^T]}_{b \times b} \underbrace{\begin{bmatrix} v_t \\ i_r \end{bmatrix}}_{b\text{-vector}} = A v_a - B i_a$$

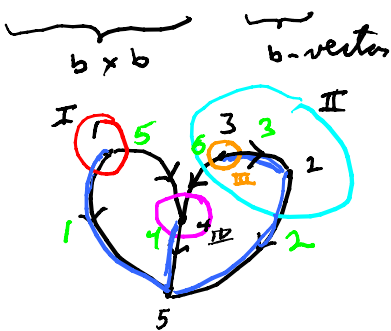let $x = \begin{bmatrix} v_t \\ i_r \end{bmatrix}$ (semi-state) vector



$$\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}_b$$

cut set eqs.

tie set eqs.

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 1 & 1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}_b$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 4C & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -T & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & -1 \\ 0 & 1 & 1 & -1 \end{bmatrix} = A e^T = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 4C \\ 0 & 0 & 0 & 0 \\ -T & 1 & 1 & T-1 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 4L & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & T \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 0 & -1 \\ 0 & -1 \\ -1 & -1 \\ -1 & 0 \\ 0 & -1 \end{bmatrix} = B e^T = \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & -4L \\ -1 & -1 \\ -1 & T \\ 0 & 0 \end{bmatrix}$$

$$[A e^T | -B e^T] = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 4L \\ 0 & 0 & 0 & 4C & -1 & -1 \\ 0 & 0 & 0 & 0 & -1 & -T \\ -T & 1 & 1 & T-1 & 0 & 0 \end{bmatrix}$$

multiplies $x = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$

$$A v_a = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_{1a} \\ v_{2a} \end{bmatrix}$$

The circuit equations are $[A e^T - B e^T] x = A v_a$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 4L \\ 0 & 0 & 0 & 4C & -1 & -1 \\ 0 & 0 & 0 & 0 & -1 & -T \\ -T & 1 & 1 & T-1 & 0 & 0 \end{bmatrix} x = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_{1a} \\ v_{2a} \end{bmatrix}$$

gives 6 eqs. & 6 unknown

Rewrite to put s multiplied terms on the left, $s = \frac{d}{dt}$

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \frac{dx}{dt} = \begin{bmatrix} -1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 & -1 \\ -1 & -1 & -1 & 0 & 0 \end{bmatrix} x + \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} u, \quad u = \text{input vector} = \begin{bmatrix} v_{12} \\ v_{24} \end{bmatrix}$$

in the form

$$\begin{cases} E \dot{x} = Ax + Bu \\ y = Cx \end{cases}$$

let $y = \text{output}$
 assume linear combinations
 of branch voltages & currents

generic form for circuit differential equations
 call these the semi-state equations