

P. J. Richards, "A special class of Functions with Positive Real part in Half Plane," *Duke Math<sup>emathical</sup> Journal*, Vol. 14, 1947, pp. 777-786. (on line via VMD library, e-journals)

(color of 10/12/07 corrections) EE 610  
10/10/07  
Homework extended until M 10/15/07


PR Test of p. 339 rational with real coefficients  $\Rightarrow y(s) = \frac{N(s)}{D(s)}$   
N & D polynomial in s

(a)  $D(s)$  has no zeros in  $\text{Re } s > 0$

(b) poles on  $j\omega$  axis are simple, residues  $> 0$

$$\frac{k}{s - j\omega_0} = \frac{|k| e^{j\Delta k}}{|s - j\omega_0|} e^{j\Delta k - j\omega_0 t}$$

$r = \text{radius}$

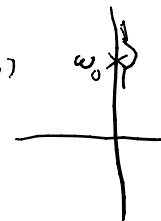

Ex:  $\frac{4s}{s^2+3} = \frac{k_1}{(s+j\sqrt{3})} + \frac{k_2}{(s-j\sqrt{3})}$


$$-\frac{\pi}{2} < \angle(s - j\omega) < \frac{\pi}{2} \text{ as } \sigma > 0$$

$$\Downarrow = \frac{2k_1 s}{s^2+3} \Rightarrow k_1 = 2$$

$\Rightarrow \Delta k = 0$  as otherwise  $\text{Re}(e^{j\Delta k - j\omega_0 t})$  would be negative  
 $\Downarrow$   $k$  real & positive

$$y(s) = \frac{4s}{s^2+3}$$
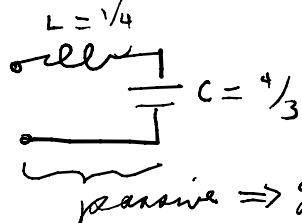
$$z(s) = \frac{1}{y(s)} = \frac{s^2+3}{4s} = \frac{1}{4}s + \frac{3}{4s}$$



residue  $\Rightarrow y(s)$  is PR

(c)  $\text{Re } y(j\omega) > 0$  for  $-\infty \leq \omega \leq \infty \equiv 0 \leq \omega \leq \infty$


$$\text{Ev } y(s) \Big|_{s=j\omega} = \text{Re } y(j\omega) = \frac{y(s) + y(-s)}{2} \Big|_{s=j\omega} = \frac{y(j\omega) + y(-j\omega)}{2} = \frac{y(j\omega) + y^*(j\omega)}{2} = \text{Re } y(j\omega)$$

gives a test for PR property

sensitivity of  $T(x)$  with respect to a parameter  $x$

$$S_x^{T(x)} = \frac{1}{\frac{T(x)}{x}} \frac{dT(x)}{dx}$$



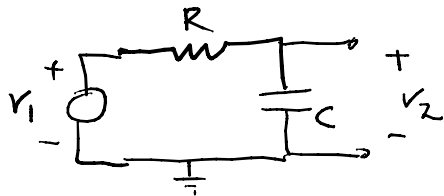
can use the adjoint circuit (p. 406 of Paikari)



$$T(x) = \frac{V_2}{V_1} = \frac{1/sC}{R + 1/sC} = \frac{1}{RCs + 1}$$

$$S_R^T = \frac{R}{\frac{1}{RCs+1}} \cdot \frac{d\left(\frac{1}{RCs+1}\right)}{dR} = \frac{-RCs}{RCs+1}$$
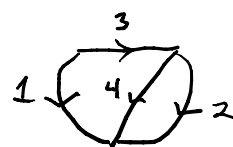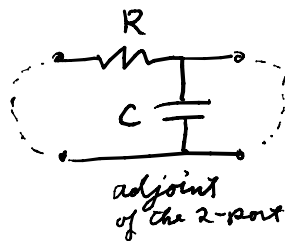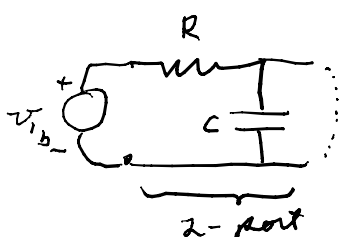
$$\frac{d}{dR} \left( \frac{1}{RCs+1} \right) = \frac{-1}{(RCs+1)^2} \times Cs = \frac{-Cs}{(RCs+1)^2}$$



$$v_d^a = \begin{bmatrix} v_3 \\ v_4 \end{bmatrix}, i_d^a = \begin{bmatrix} i_3 \\ i_4 \end{bmatrix}$$

$$i_b^T v_b^a = 0 \quad \text{we} \quad \Delta i_b^a, \Delta v_b^a$$

$$i_b^a, v_b^a$$

$$\Delta i_b^T v_b^a - i_b^{aT} \Delta v_b^a = 0 \Rightarrow \Delta i_{b_1}^a v_{b_1}^a + \Delta i_{b_2}^a v_{b_2}^a - i_{b_1}^a \Delta v_{b_1}^a - i_{b_2}^a \Delta v_{b_2}^a + \Delta i_d^T v_d^a - i_d^{aT} \Delta v_d^a = 0$$

fix  $v_{b_1}, C$ , and adjoint components,  $\Delta v_{b_2}^a$

and set  $v_{b_1} = 1$  so  $T(x) = V_2(x)$


as not interested in  $\Delta i_{b_1}^a$ , set  $v_{b_1}^a = 0 \Rightarrow$  short

set  $i_{b_2}^a = \pm 1 \Rightarrow$  current source

on original  $\Delta i_{b_2} = 0$  as an open circuit

when measure  $V_2$

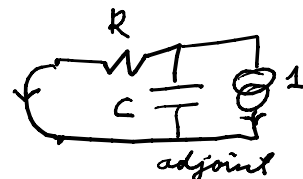$\Delta v_{b_1}^a = 0$  as  $v_{b_1} = 1 = v_{b_1}$



$$\begin{pmatrix} i_{b_2} \\ i_{b_1} \\ i_d \end{pmatrix}^T \begin{pmatrix} \Delta v_{b_2}^a \\ \Delta v_{b_1}^a \\ \Delta v_d^a \end{pmatrix} = \begin{pmatrix} + \\ - \\ + \end{pmatrix} \Delta v_{b_2}^a = \begin{pmatrix} + \\ - \\ + \end{pmatrix} \Delta T(x) = \Delta i_d^T v_d^a - i_d^{aT} \Delta v_d^a$$

$$\begin{aligned}
 & (\Delta [i_d = Y v_d])^T v_d^a - (i_d^a = Y^a v_d^a)^T \Delta v_d \\
 &= (\Delta Y \cdot v_d + Y \Delta v_d)^T v_d^a - v_d^{aT} Y^{aT} \Delta v_d \\
 &= v_d^T \Delta Y v_d^a + \underbrace{\Delta v_d^T Y^T v_d^a}_{\text{free}} - v_d^{aT} Y^{aT} \Delta v_d
 \end{aligned}$$


$b \times b =$  branch  $\times$  branch of the 2-port. ( $\neq$  2-port)

$$\begin{aligned}
 \pm \Delta T(\alpha) &= v_d^T (\Delta Y^T) v_d^a \\
 &= v_d^{aT} \Delta Y v_d
 \end{aligned}$$

$\Delta v_d^T (Y^T - Y^a) v_d^a$   
 $Y^a = Y^T$

here  $Y = \begin{bmatrix} G & -G \\ +G & G+AC \end{bmatrix}$
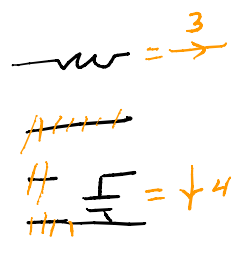
$$\begin{aligned}
 \Delta G &= \Delta \frac{1}{R} = -\frac{1}{R^2} \Delta R \\
 \Delta Y &= -\frac{1}{R^2} \Delta R \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}
 \end{aligned}$$



Need  $\begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = v_d, \begin{bmatrix} v_3^a \\ v_4^a \end{bmatrix} = v_d^a$


$$\pm \frac{\Delta T(\alpha)}{\Delta R} = \begin{bmatrix} v_3 & v_4 \end{bmatrix} \begin{bmatrix} -1/R^2 & 0 \\ 1/R^2 & 0 \end{bmatrix} \begin{bmatrix} v_3^a \\ v_4^a \end{bmatrix}$$



$$v_3 = \frac{R}{R+1/C}, \quad v_4 = \frac{1/C}{R+1/C}$$

analyze  $N^a + R v_3^a$

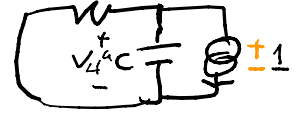here  $v_3^a = -v_4^a = \frac{1}{G+AC} \times (\pm 1)$   
 $= \frac{\pm 1}{G+AC} \times 1$



$$\pm \frac{\Delta T(\alpha)}{\Delta R} = \left(-\frac{1}{R^2}\right) v_3 v_3^a = -\frac{1}{R^2} \cdot \frac{R}{(R+1/C)} \cdot \frac{\pm 1}{G+AC} = \frac{\pm 1/C}{(ACR+1)^2}$$

shows either sign on  $L_{b_2}^a$  gives the same result