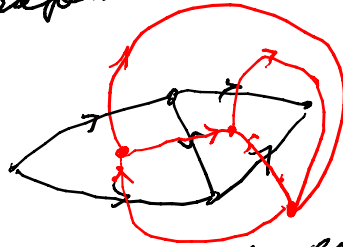



Ex of dual graph

EE610
10/22/07



red = dual graph

If non-planar can't do this construction

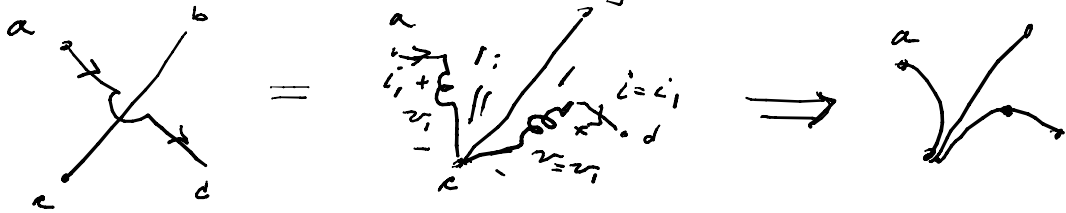

now no crossing wires and all currents & voltages are preserved

scattering matrix


incident $\Rightarrow 2v^i = v + \underbrace{Z_0 i}_i$; $Z_0 = R = \underline{1_n}$
 reflected $\Rightarrow 2v^r = v - \underbrace{Z_0 i}_i$

$$2v = 2v^i + 2v^r \Rightarrow v = v^i + v^r$$

$$e = v + Ri = v + i = 2v^i$$

$$i = \gamma_a \cdot e$$
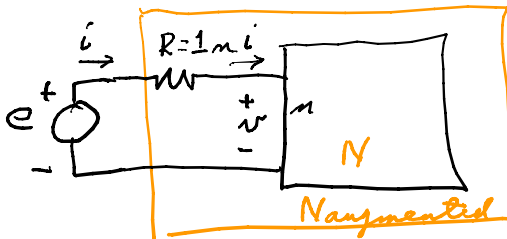
$$v = e - i = e - \gamma_a e = (1_n - \gamma_a) e$$



$$v^i = \frac{v+i}{2} = \frac{e}{2}$$

$$v^r = \frac{v-i}{2} = \frac{(1_n - 2\gamma_a)e}{2}$$

$$v-i = e - 2i = e - 2\gamma_a e = (1_n - 2\gamma_a)e$$

$$= (1_n - 2\gamma_a) v^i \Rightarrow v^r = S(\lambda) \cdot v^i$$

$$S(\lambda) = 1_n - 2\gamma_a(\lambda)$$

also if $i = \gamma v$; $e = v + \gamma v = 2v^i$

$$2v^r = v - i = v - \gamma v = v^r = \frac{(1_n - \gamma)v}{2}$$

$$v^i = \frac{(1_n + \gamma)v}{2}$$

$$\frac{v}{2} = (1_n + Y)^{-1} v^i \Rightarrow v^n = (1_n - Y) \frac{v}{2} = (1_n - Y)(1_n + Y)^{-1} \cdot v^i$$

$$S(s) = (1_n - Y(s))(1_n + Y(s))^{-1} ; \text{ if } N \text{ is passive}$$

$(1_n + Y(s))^{-1}$ exists
 in $\text{Re } s > 0$ if $Y(s)$
 exists

$$(1_n - Y)(1_n + Y)^{-1} = (1_n + Y)^{-1}(1_n - Y) \quad \times (1_n + Y) \text{ on right \& left}$$

$$(1_n + Y)(1_n - Y) = (1_n - Y)(1_n + Y)$$

$$= 1_n - Y^2 = 1_n - Y^2$$

$$P(s; \omega) = \text{Re}(v^{*T} I) = \frac{v^{*T} I + v^T I^*}{2} = \frac{v^{*T} I + I^T v}{2} \geq 0 \text{ if passive}$$

$$v = v^i + v^n$$

$$I = v^i - v^n$$

$$= \frac{(v^i + v^n)(v^i - v^n) + (v^i - v^n)^{*T} (v^i + v^n)}{2}$$

$$= v^{i*T} v^i - \underline{v^{i*T} v^n} + \underline{v^{n*T} v^i} - v^{n*T} v^n = v^{i*T} v^i - v^{n*T} v^n$$

* conjugates


$$P(s; \omega) = v^{i*T} v^i - v^{i*T} S^T(s) S(s) v^i = v^{i*T} [1_n - S^T(s) S(s)] v^i \geq 0 \text{ if passive}$$

\therefore for a passive circuit $S(s)$ is bounded-real

- 1) $S(s)$ is real for $s = \sigma > 0$
- 2) $S(s)$ is analytic in $\sigma > 0$
- 3) $1_n - S^T(s) S(s)$ is positive semi-definite in $\sigma > 0$

Can not have poles on $j\omega$ axis as $|S|^2 \leq 1$ for $s = j\omega$

For a 2-port

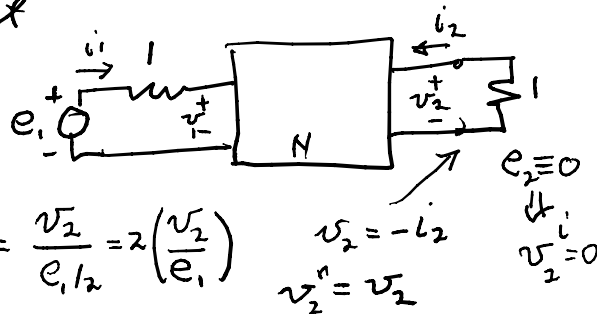

$$S_{21} = \frac{v_2^n}{v_1^i} = \frac{v_2}{e_{1/2}} = 2 \left(\frac{v_2}{e_1} \right)$$

$$v^i = \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} = \begin{bmatrix} e_1/2 \\ 0 \end{bmatrix}$$

$$v^n = \begin{bmatrix} v_1^n \\ v_2^n \end{bmatrix} = \begin{bmatrix} (v_1 - i_1)/2 \\ v_2 - i_2/2 \end{bmatrix}$$

$$= \begin{bmatrix} v_1^n \\ 2v_{2/2} \end{bmatrix}$$

$$S_{11} = \frac{v_1^n}{v_1^i} = \left. \frac{(v_1 - v_1^i)/2}{(v_1 + v_1^i)/2} \right|_{v_2^i = 0} = \text{reflection coefficient if } S_{11} = 0$$

input to N when loaded looks like a unit resistor \equiv match

If N is lossless $P(j\omega) = 0 \Rightarrow \mathbf{1}_m - S^T(j\omega)S(j\omega) = \mathbf{0}_n$

$$= \mathbf{1}_m - S^T(-j\omega)S(j\omega)$$


$$= \mathbf{1}_m - S^T(-s)S(s) \Big|_{s=j\omega} = \mathbf{0}_n$$

if $S(s)$ is rational this is for every ω , $-\infty < \omega < \infty$

if $S(s)$ is rational and N is lossless & passive then $\mathbf{1}_m - S^T(-s)S(s) = \mathbf{0}_n$ for all s

$$\Rightarrow \mathbf{1}_m = S^T(-s)S(s) \text{ or } S^{-1}(s) \text{ exists \& } S^{-1}(s) = S^T(-s)$$

Ex:

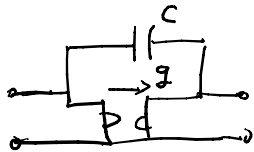

$$Y(s) = \begin{bmatrix} sC & -sC - g \\ -sC + g & sC \end{bmatrix}$$

$$S(s) = (\mathbf{1}_2 - Y)(\mathbf{1}_2 + Y)^{-1}$$

$$\mathbf{1}_2 + Y = \begin{bmatrix} 1 + sC & -sC - g \\ -sC + g & 1 + sC \end{bmatrix}; \quad (1 + sC)^2 - (-sC + g)(-sC - g) = \Delta Y$$

$$= 1 + 2sC + (sC)^2 - (sC)^2 + g^2 = 1 + 2sC + g^2$$

$$= (1 + g^2) + 2sC$$

$$S(s) = \frac{1}{(1 + g^2) + 2sC} \begin{bmatrix} 1 - sC & sC + g \\ sC - g & 1 + sC \end{bmatrix} \begin{bmatrix} 1 + sC & sC + g \\ sC - g & 1 + sC \end{bmatrix}$$

poles at $s = -\frac{(1 + g^2)}{2C}$

in LHP

$$m_{11} = (1 - sC)(1 + sC) + (sC + g)(sC - g) = 1 - (sC)^2 + (sC)^2 - g^2$$

$$m_{12} = (1 - sC)(sC + g) + (sC + g)(1 + sC) = 2(sC + g)$$

$$m_{21} = (sC - g)(1 + sC) + (1 - sC)(sC - g) = 2(sC - g)$$

$$m_{22} = (sC - g)(sC + g) + (1 + sC)(1 - sC) = m_{11}$$

$$S(\alpha) = \frac{1}{2c + (1+g^2)} \begin{bmatrix} 1-g^2 & 2(\alpha+g) \\ 2(\alpha-g) & 1-g^2 \end{bmatrix}$$

check $S^T(-\alpha) S(\alpha)$ should = $\frac{1}{2} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

$$\frac{1}{-2\alpha + (1+g^2)} \begin{bmatrix} 1-g^2 & 2(-\alpha-g) \\ 2(-\alpha+g) & 1-g^2 \end{bmatrix} \frac{1}{2(\alpha) + (1+g^2)} \begin{bmatrix} 1-g^2 & 2(\alpha+g) \\ 2(\alpha-g) & 1-g^2 \end{bmatrix}$$

$$= \frac{1}{(1+g^2)^2 - 4(\alpha)^2} \begin{bmatrix} (1-g^2)^2 - 4(\alpha^2 - g^2) & (1-g^2)2(\alpha+g) - 2(\alpha+g)(1-g^2) \\ 2(-\alpha+g)(1-g^2) + (1-g^2)2(\alpha-g) & 4(-\alpha+g)(\alpha+g) + (1-g^2)^2 \end{bmatrix}$$

$\begin{matrix} = 0 & = 0 \\ = 0 & \end{matrix}$

$$= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

check $(1-g^2)^2 - 4(\alpha)^2 + 4g^2$

$$= -4(\alpha)^2 + 1 - 2g^2 + g^4 + 4g^2$$

$$= -4(\alpha)^2 + (1+g^2)^2$$